


Switched Mode One-Quadrant Power Converters

R. Petrocelli


Summary

- Power Electronics. Basics definitions and rules
- Basic DC-DC Power Converters
- Control of DC-DC Power Converters
- Derived Topologies
- Other Issues


Power converter Definition

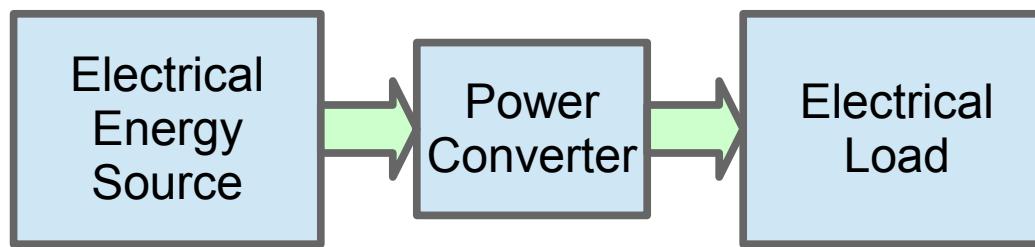



Classification of Power converters

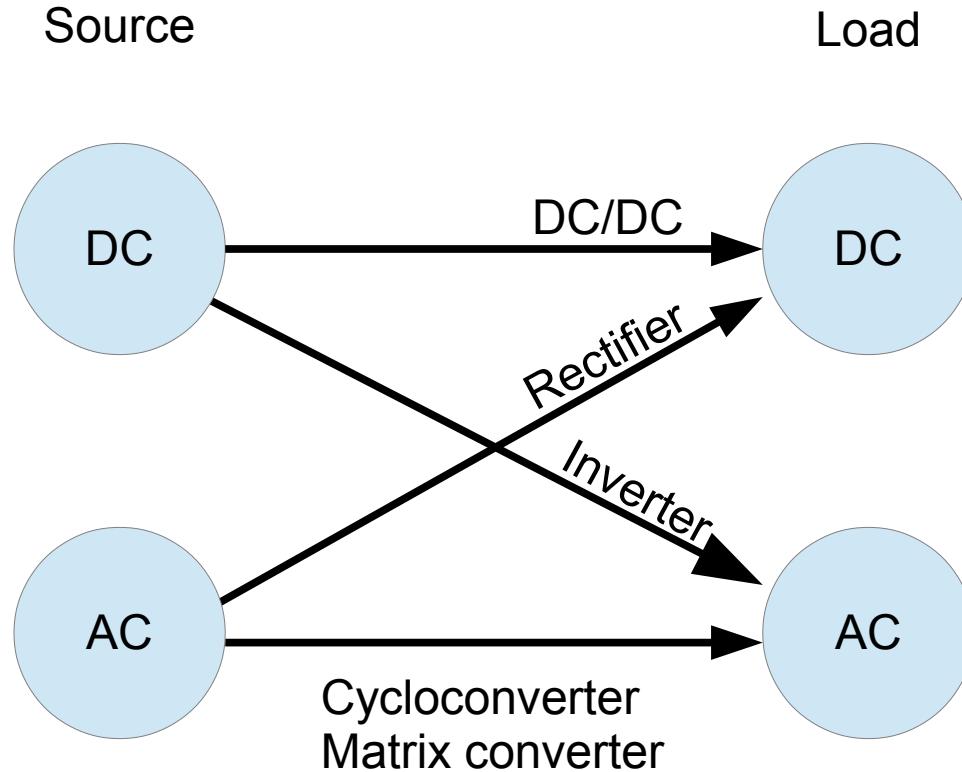

One-Quadrant Definition

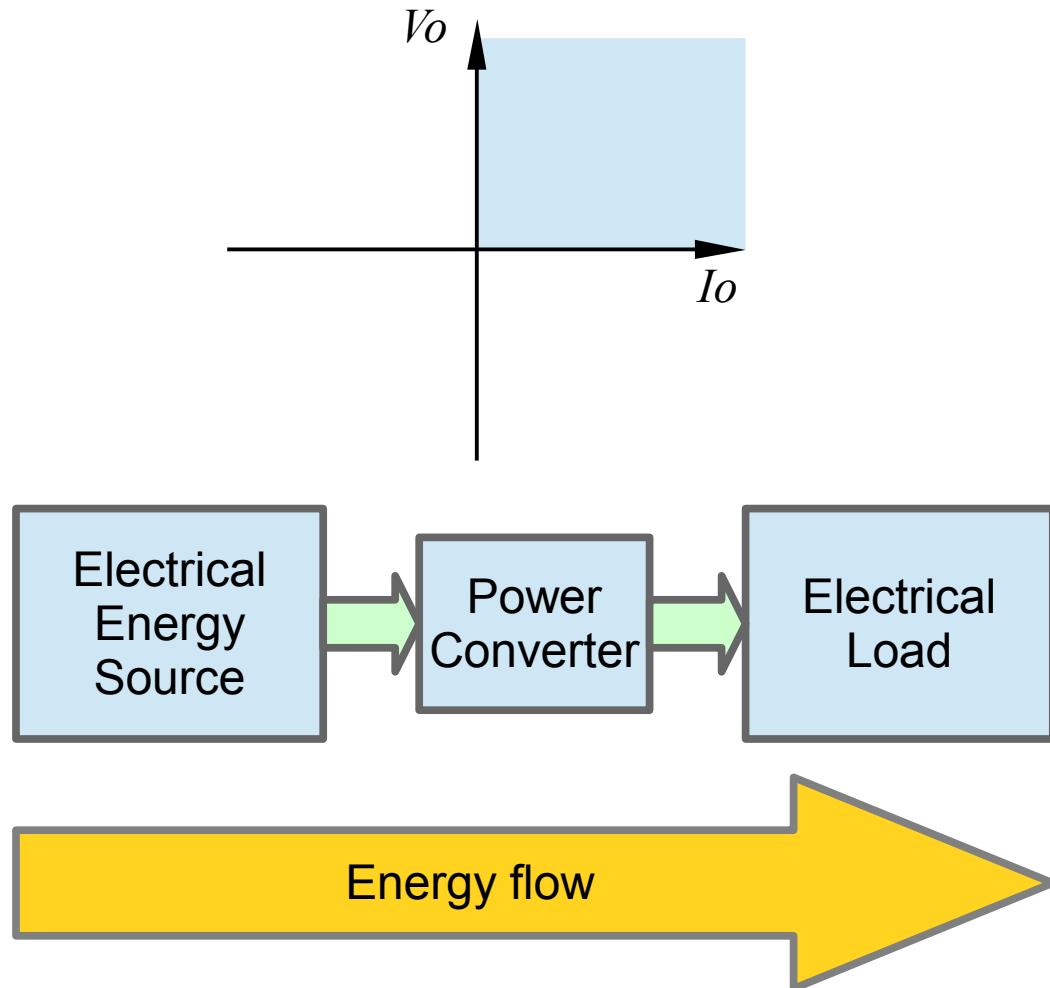


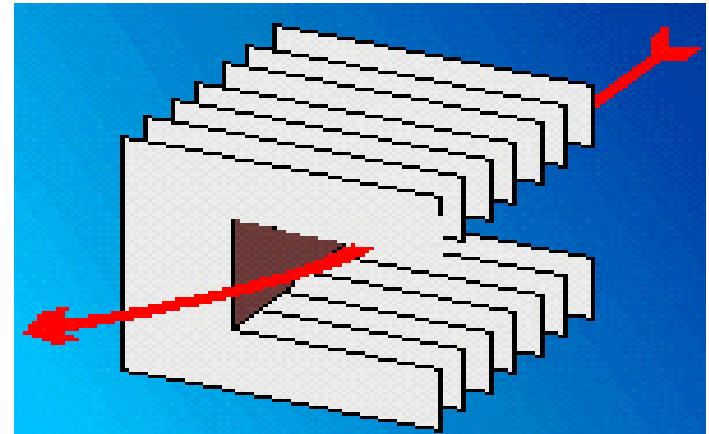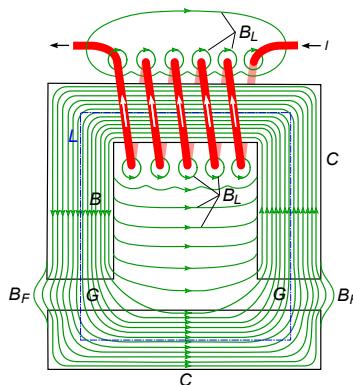One-Quadrant Power Converter in Particle Accelerators




■ 2n-pole:


dipole

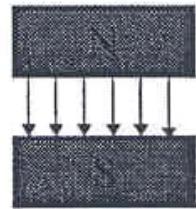


quadrupole

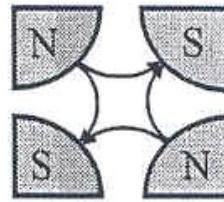

sextupole

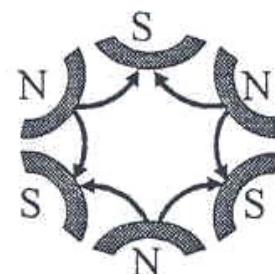

octupole ...

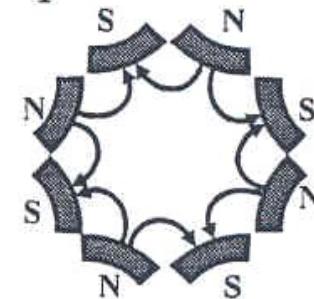

n:

1

2

3

4

...

Power Electronics



Basic Definition and Rules

- Sources Definition
- Basic Rules
- Interconnection Rules

Type of Sources

Voltage Source

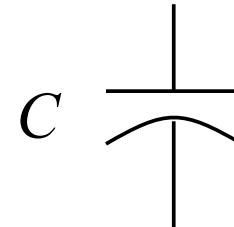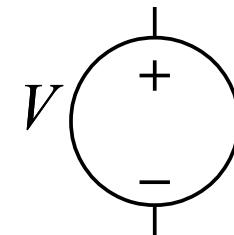
- A voltage source is able to impose a voltage regardless of the current flowing through it.
- In a more open sense, if the voltage across an element can not have discontinuities in time due to the current flowing through it



Source Type

Current Sources

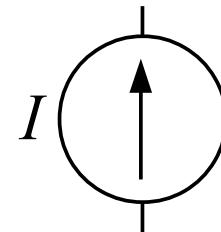A current source are able to impose current regardless the voltage across its terminals.




Similar to the voltage sources this can be extended to elements which current can not have discontinuities.




Basic Rules

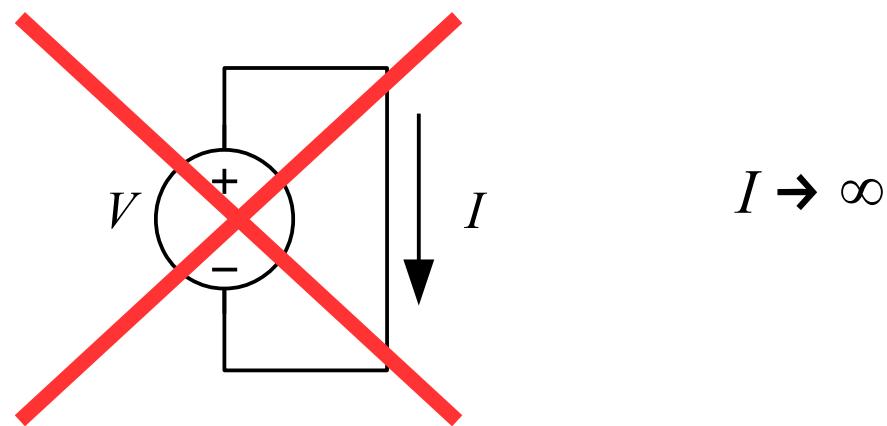- Rule 1: A voltage source must never be short-circuited




Basic Rules

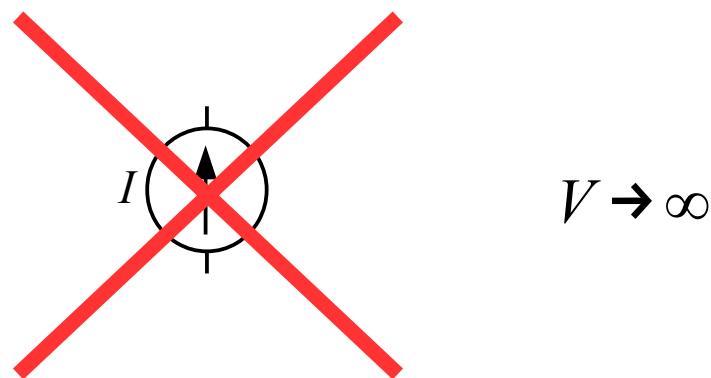- Rule 2: A current source must never be open-circuited



Basic Rules


- Interconnection Rules

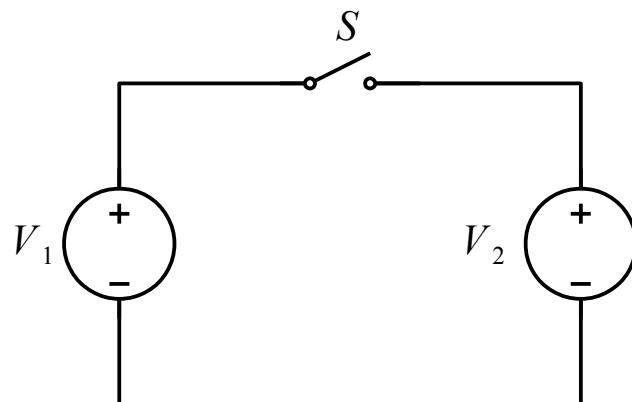

S must not be closed

Unless

$$V_1 = V_2$$

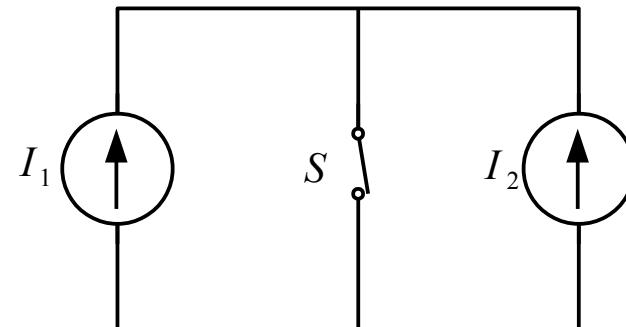


S must not be open

Unless

$$I_1 = -I_2$$

Interconnection Rules

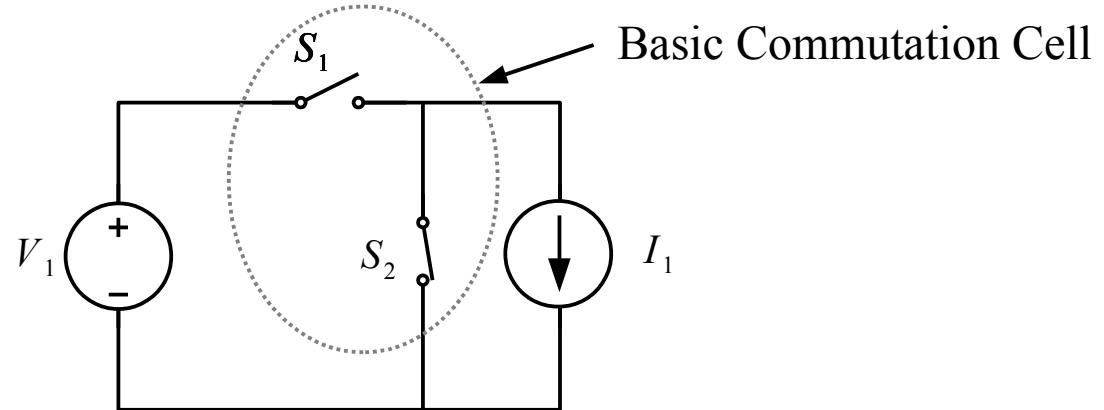



S_1	S_2	
<i>open</i>	<i>open</i>	Not allowed
<i>open</i>	<i>closed</i>	Allowed
<i>closed</i>	<i>open</i>	Allowed
<i>closed</i>	<i>closed</i>	Not allowed

Basic DC-DC Converter

- Chopper
- Buck Converter
- Boost Converter
- Buck-Boost Converter


DC Chopper

- Resistive Load

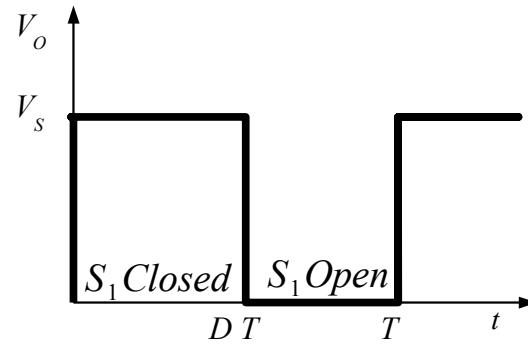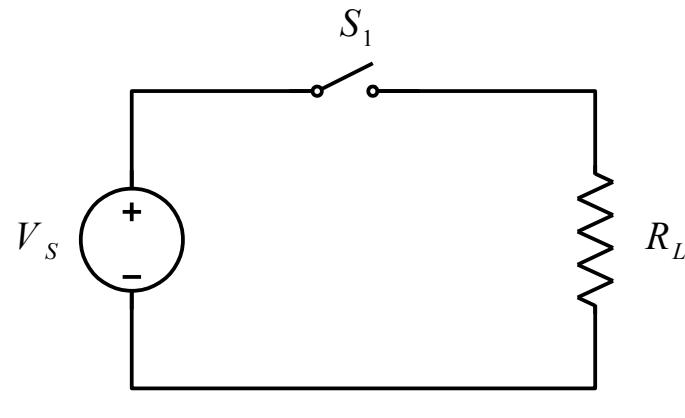


DC Chopper

- Inductive Load

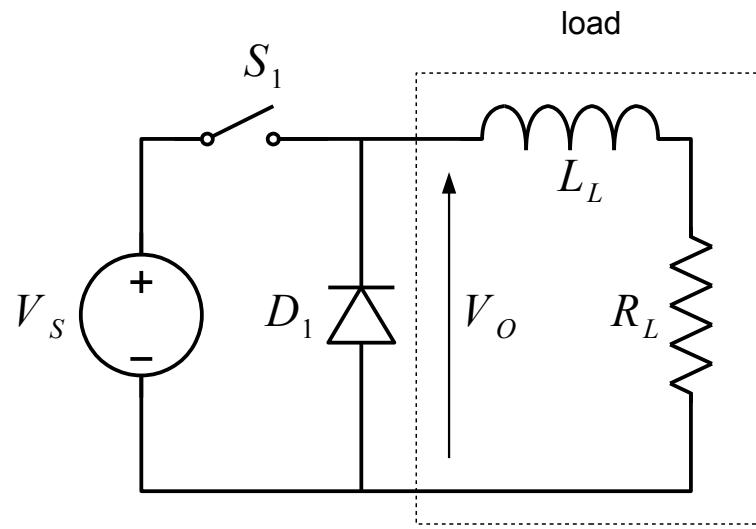


- Application: Motor control


Chopper Waveforms

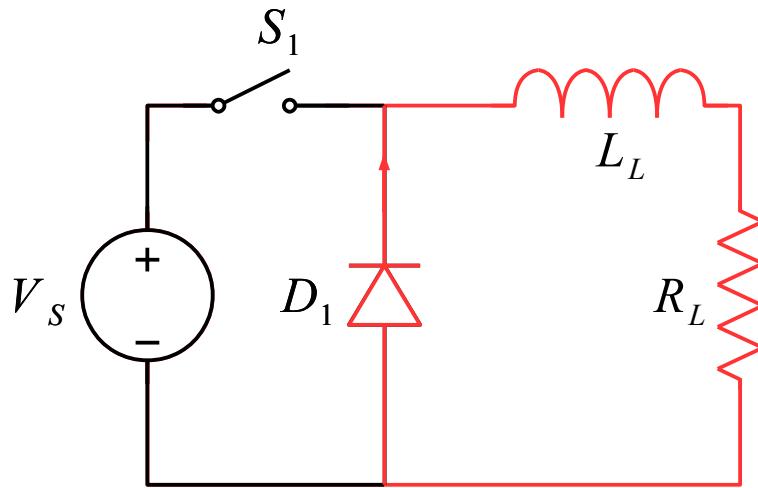


$$\bar{I}_L = \frac{V_S D}{R_L}$$

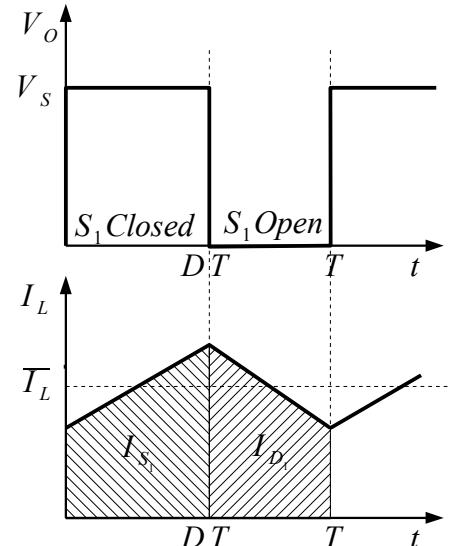

Buck Converter

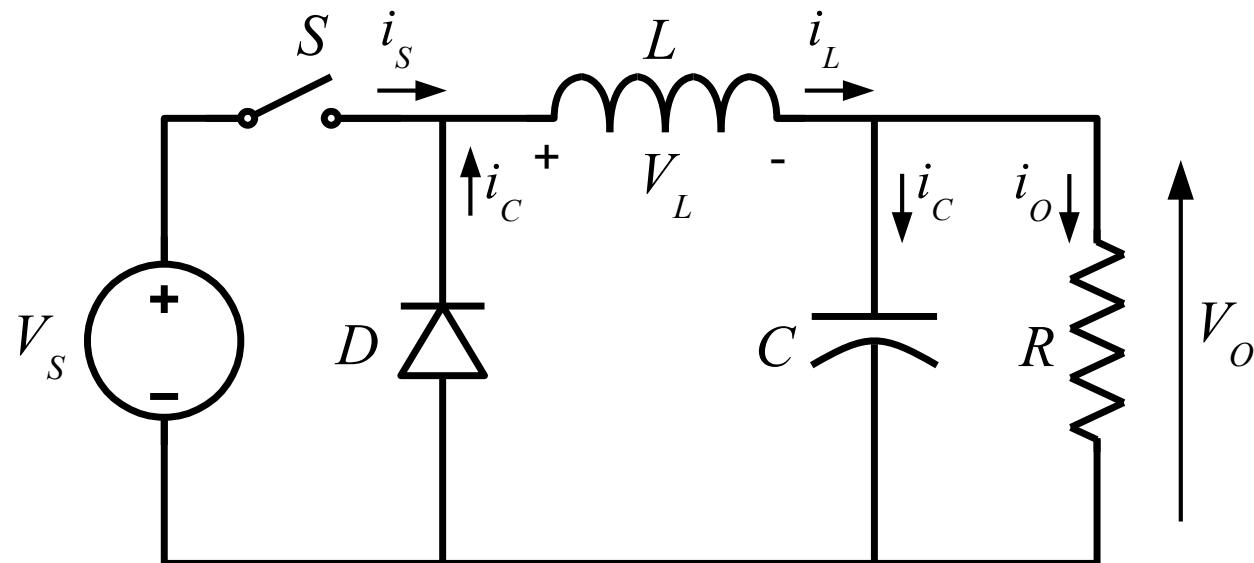


Buck Converter

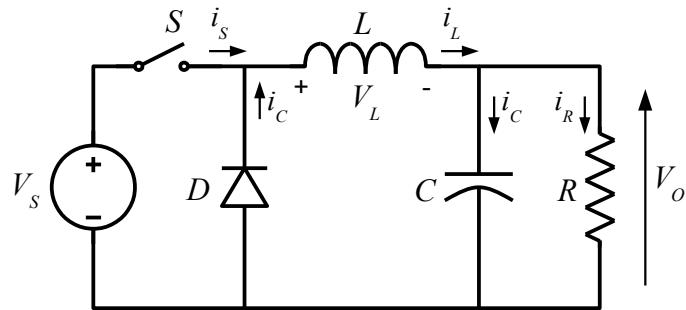


Faraday Law :
volt-second product of the inductor
voltage should be zero for steady-
state operation

$$(V_s - V_o)DT = V_o(1 - D)T$$

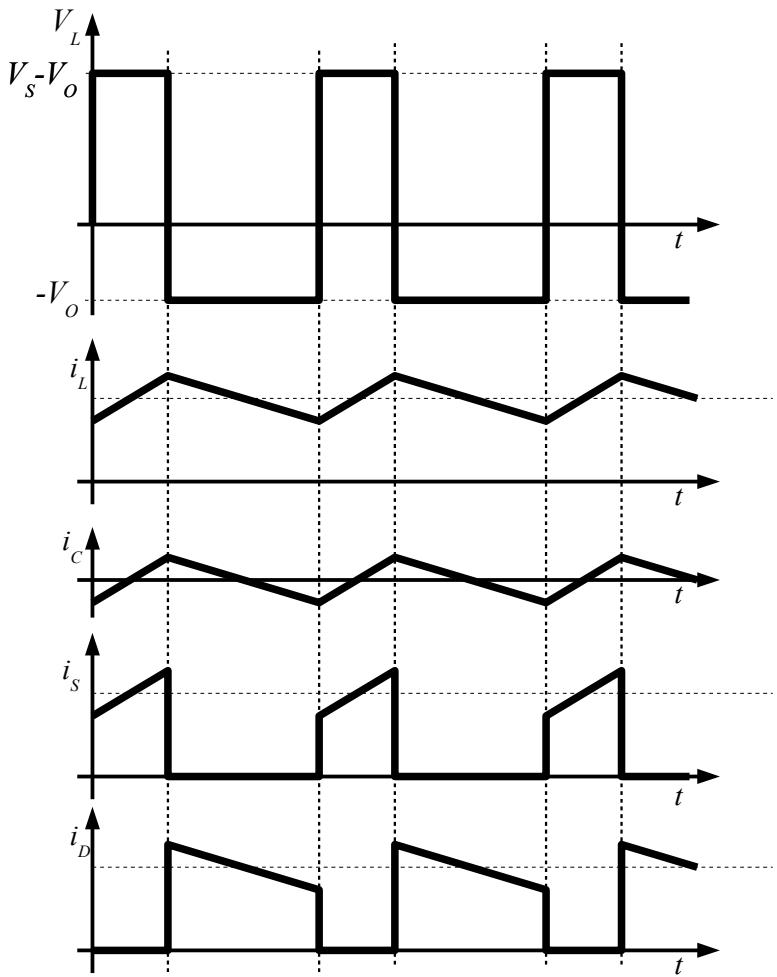

Output-Input Voltage Ratio

$$M_V \equiv \frac{V_o}{V_s} = D$$

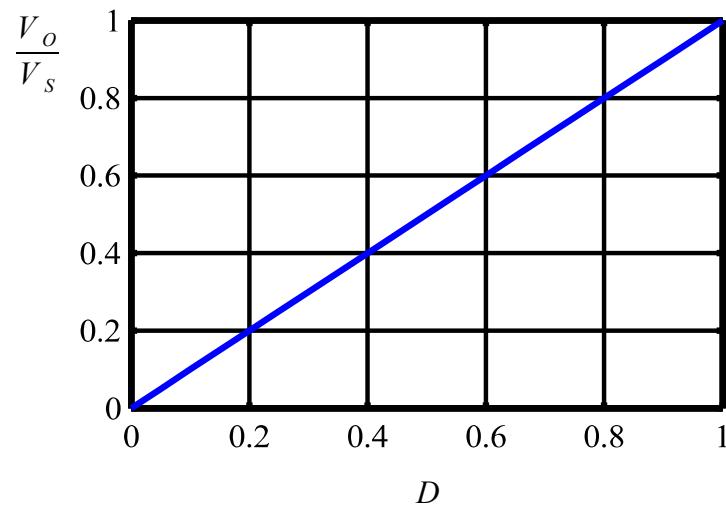



$$L_b = \frac{(1-D)R}{2f}$$

Inductance for boundary between CCM and DCM

$$C_{min} = \frac{(1-D)V_o}{8V_r L f^2}$$

Minimum capacitance for an output voltage ripple V_r


Continuous and Dis-Continuous Mode

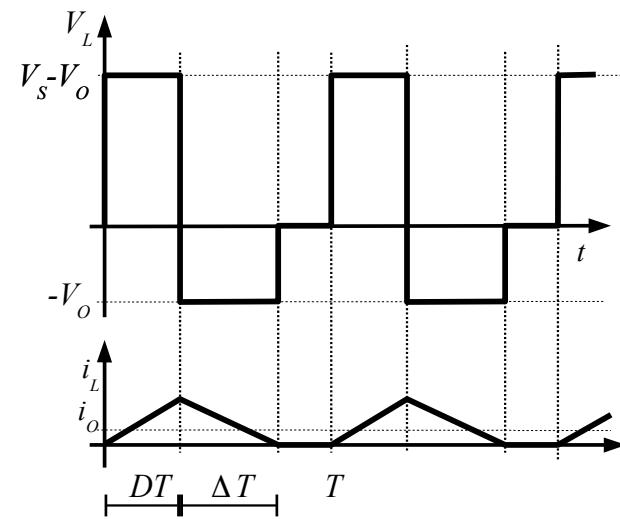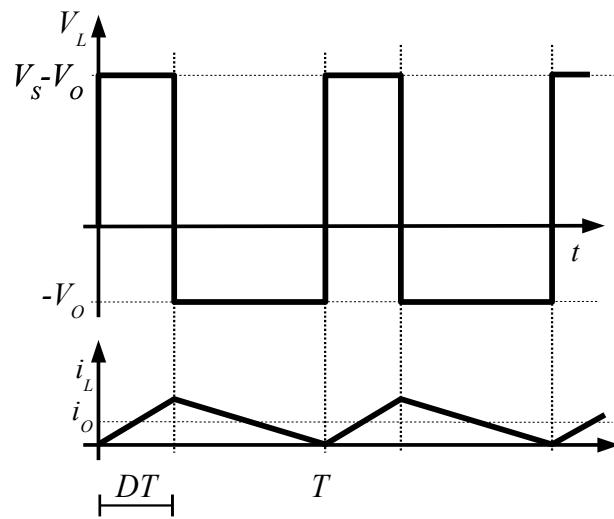


CCM and DCM Boundary

$$i_{OB} = \frac{DT}{2L}(V_s - V_o) = \frac{TV_s}{2L}(D - D^2)$$

$$I_{OB_{MAX}} = \frac{TV_s}{8L}$$

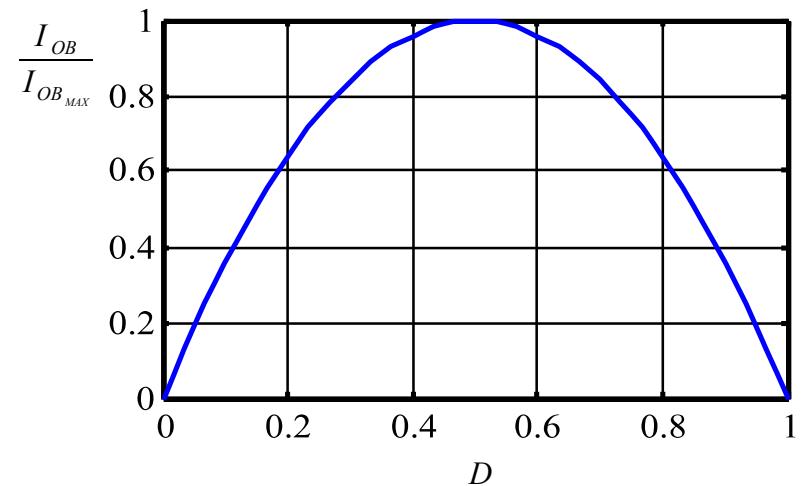

$$(V_s - V_o) D T = V_o \Delta T$$

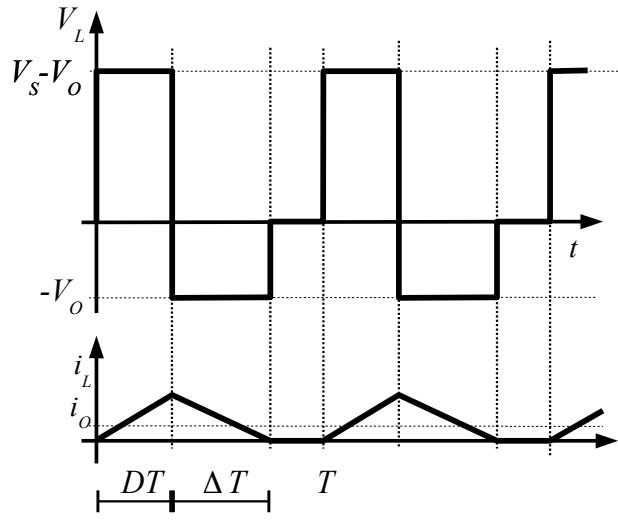

$$\frac{V_o}{V_s} = \frac{D}{(D + \Delta)}$$


$$I_o = \frac{I_{L_{peak}} (D + \Delta) T}{2 T}$$

$$I_{L_{peak}} = \frac{V_o \Delta T}{L}$$

$$I_o = 4 I_{OB_{MAX}} D \Delta$$

Output-Input Voltage Ratio in DCM

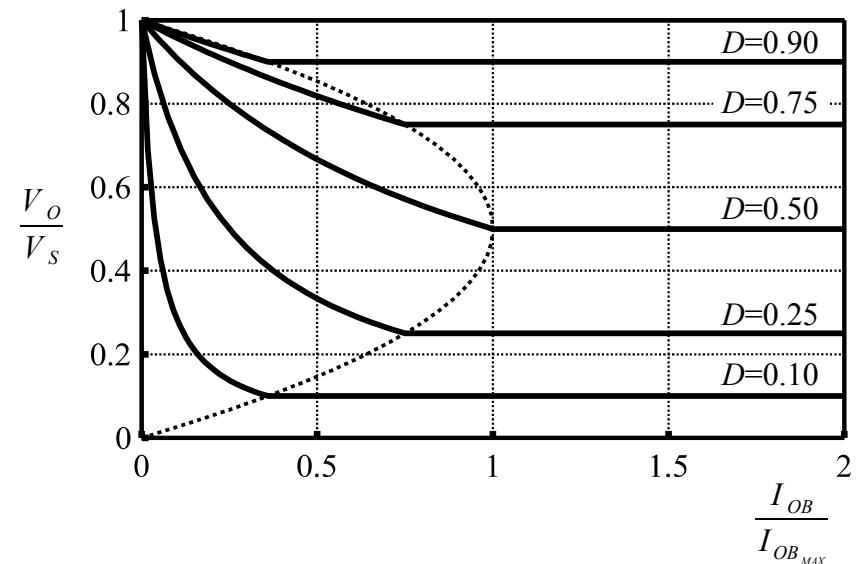
$$\frac{V_o}{V_s} = \frac{D^2}{D^2 + \frac{1}{4} \frac{I_o}{I_{OB_{MAX}}}}$$




Buck Converter

- Widely used. Even for high power converters
- Advantages:
 - Simple
 - Linear output-input voltage ratio. It makes easier the control.
 - Smooth output current.
- Disadvantages:
 - Discontinuous input current
 - No isolation.

Boost Converter

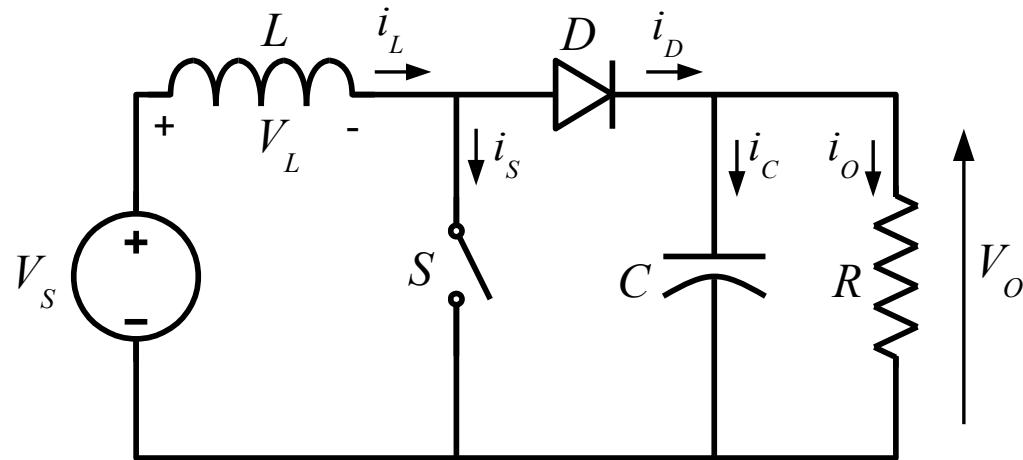

Boost Converter

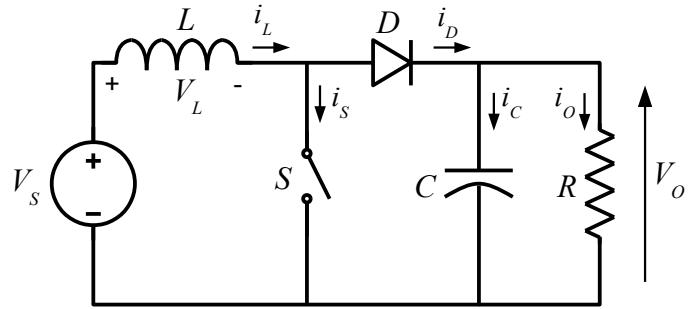


Faraday Law :

$$V_s D T = (V_o - V_s)(1 - D)T$$

$$M_V \equiv \frac{V_o}{V_s} = \frac{1}{(1 - D)}$$


$$L_b = \frac{(1 - D)^2 D R}{2 f}$$

$$C_{min} = \frac{D V_o}{V_r R f}$$

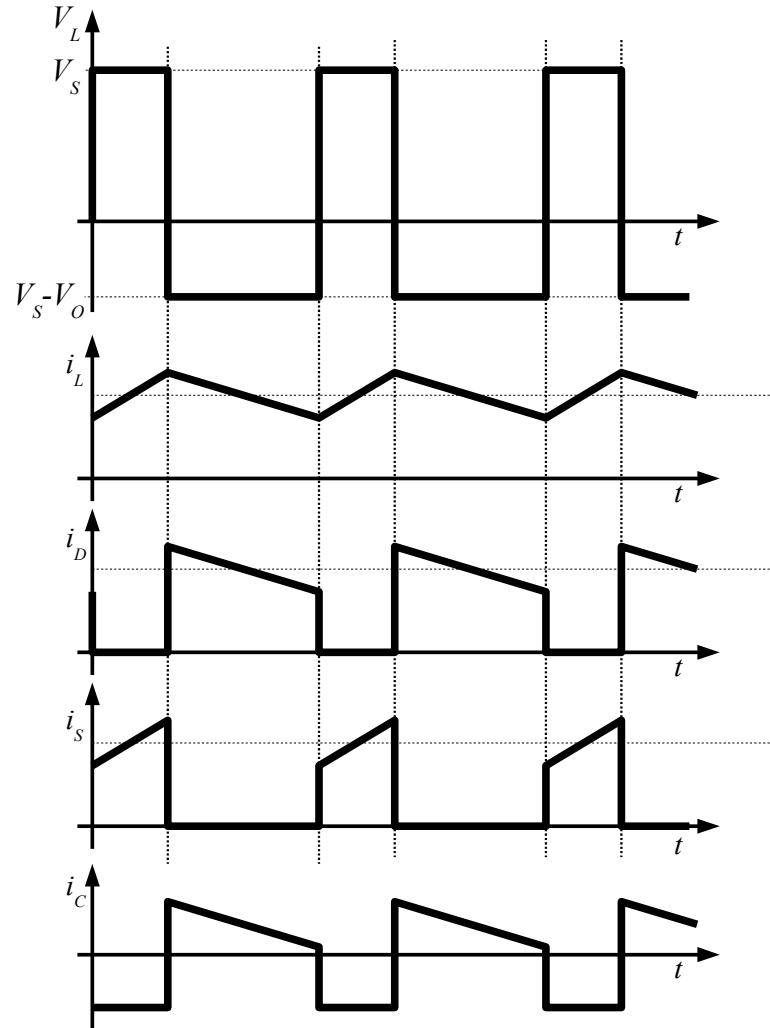

Boost Converter: Output-Input Voltage Ratio

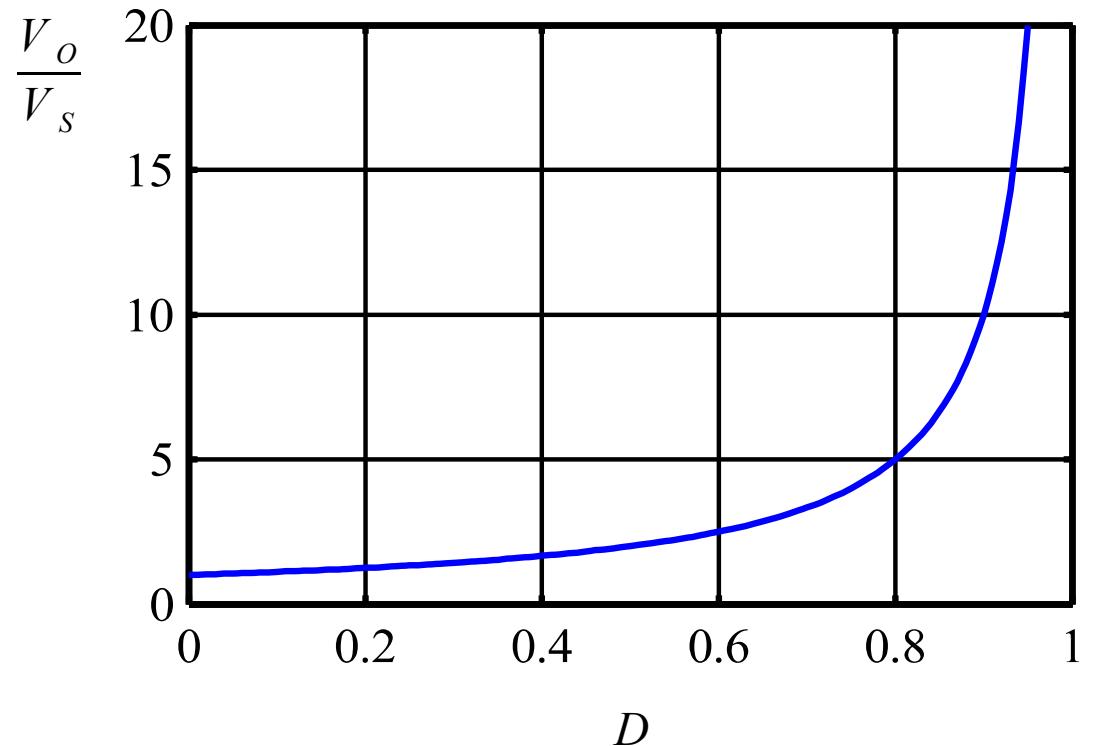
$$M_V \equiv \frac{V_O}{V_S} = \frac{1}{(1-D)}$$




Boost Converter

- Output voltage higher than input voltage
 - Advantages:
 - Simple
 - Smooth input current.
 - Disadvantages:
 - Discontinuous output current. Stress the output capacitor
 - No isolation.
-

Buck-Boost Power Converter

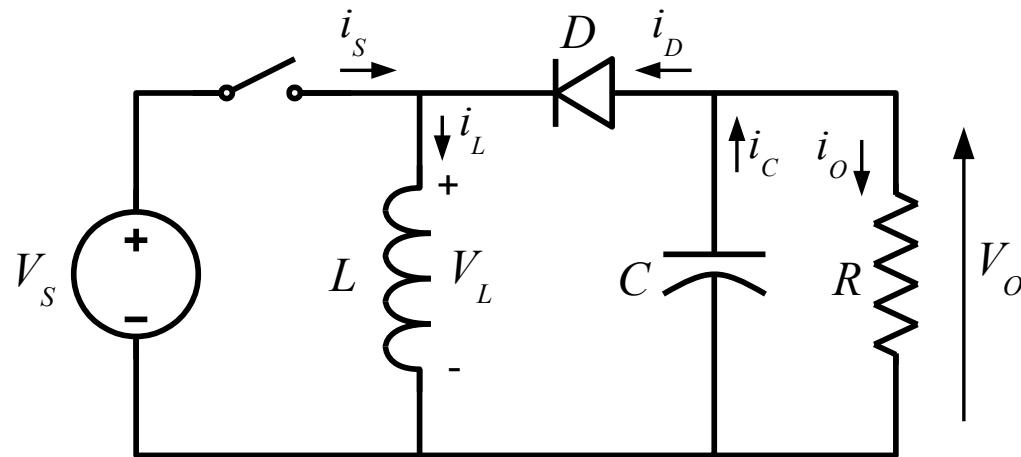


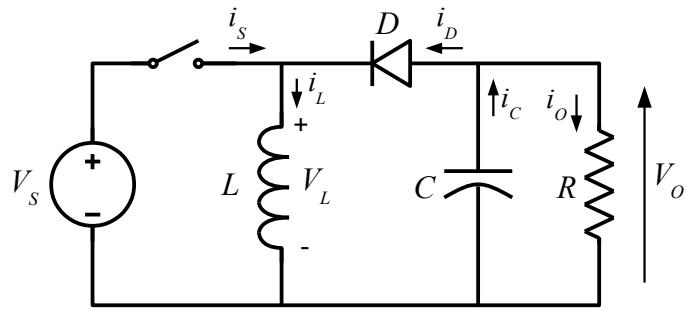

$$V_s T D = -V_o (1-D) T$$


$$M_V \equiv \frac{V_o}{V_s} = -\frac{D}{(1-D)}$$

$$L_b = \frac{(1-D)^2 D R}{2 f}$$

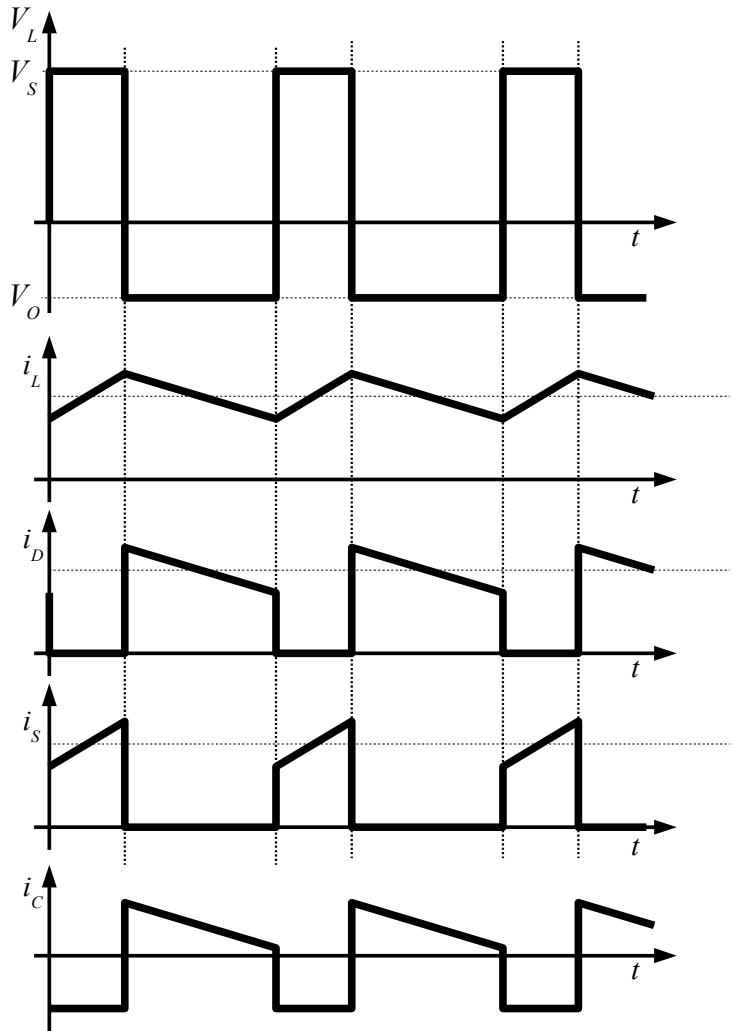

Buck-Boost Converter: Output-Input Voltage Ratio
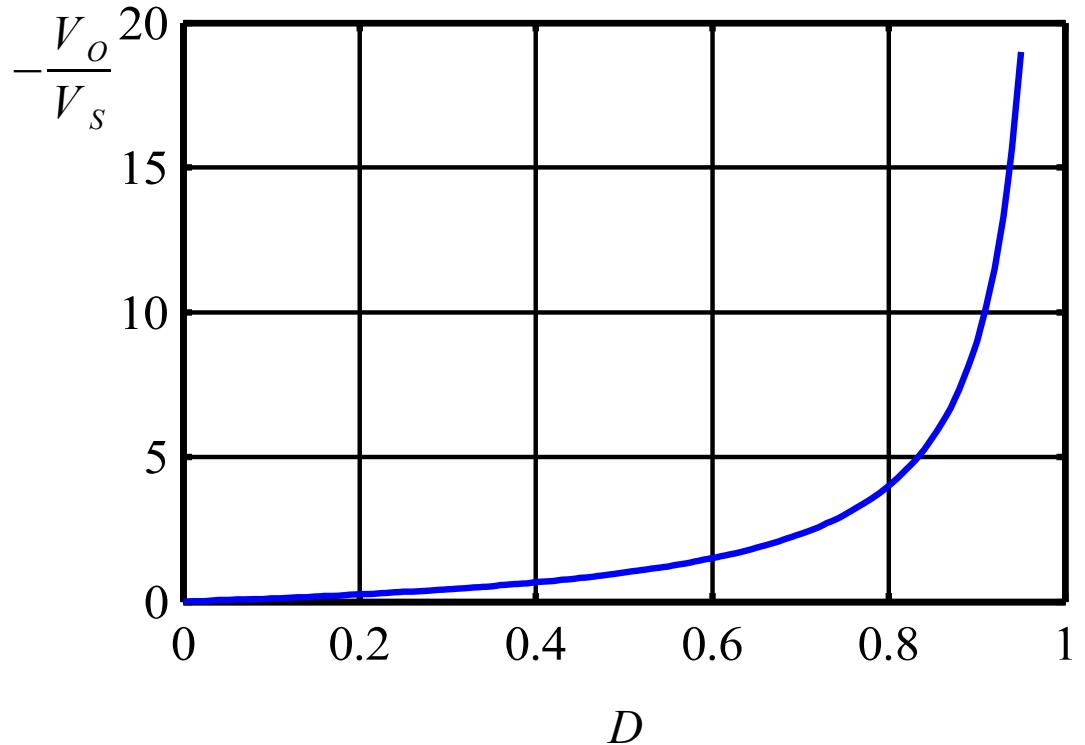
$$M_V \equiv \frac{V_O}{V_S} = -\frac{D}{(1-D)}$$



Buck-Boost Converter

Reverse voltage polarity

- Advantages:
 - Simple
 - Step-down and step-up
 - Disadvantages:
 - Discontinuous input and output current.
 - No isolation.
-

Control of DC-DC Power Converters

- Regulation
- Pulse-Width Modulation. (PWM)
- Current Mode
- Variable Structure Control

Control of Switched Mode DC-DC Power Converter

Switching function.


Definition:

The switching function, $S(t)$, has a value of 1 when the corresponding physical switch is *on* and 0 when it is *off*.


Switching functions are discrete-valued functions of time, and control of switching devices can be represented with them.

$$s(t) = \begin{cases} 1 & \text{when the switch is on} \\ 0 & \text{when the switch is off} \end{cases}$$

Power Converter Block Diagram

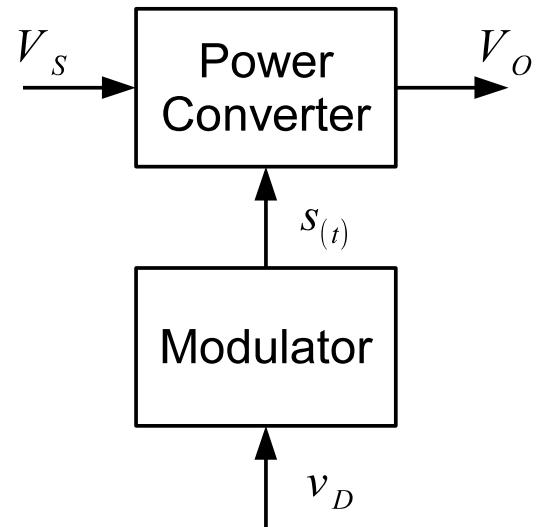


Regulation – Feedback

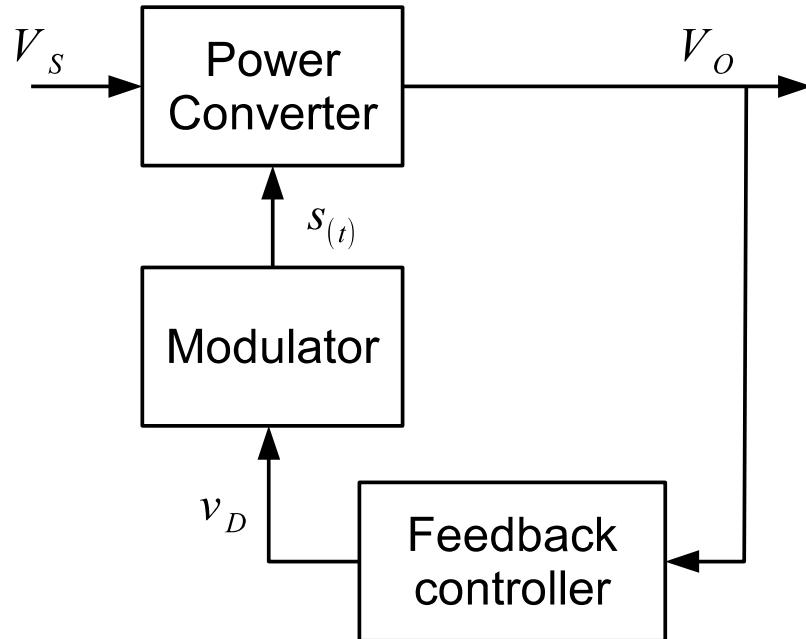



- Close loop, the output voltage is sensed and the feedback controller acts to get the wished value.
- Stability issues

Regulation – Feed-Forward

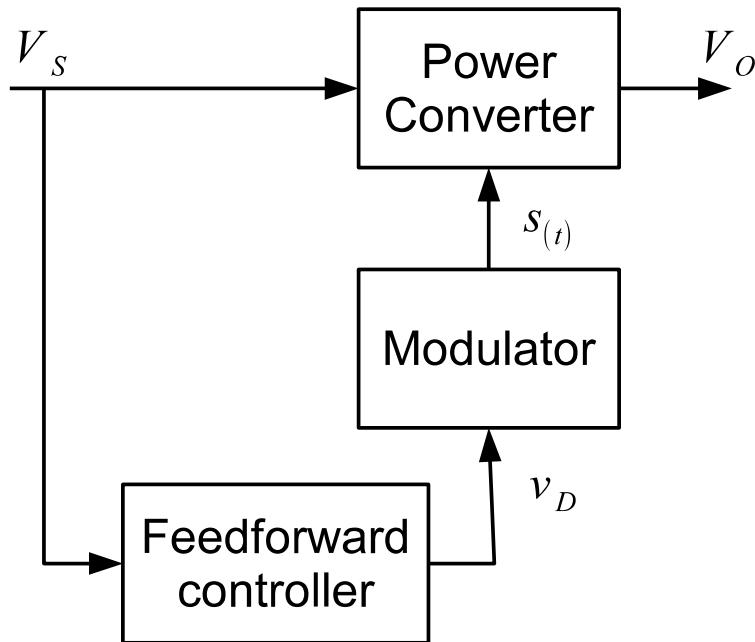


- It is very fast. Perturbations do not have to reach the output in order to be compensated.
- It need a good model of the converter in order to design the controller.
- Usually is used together with a feedback loop.

Constant Frequency PWM

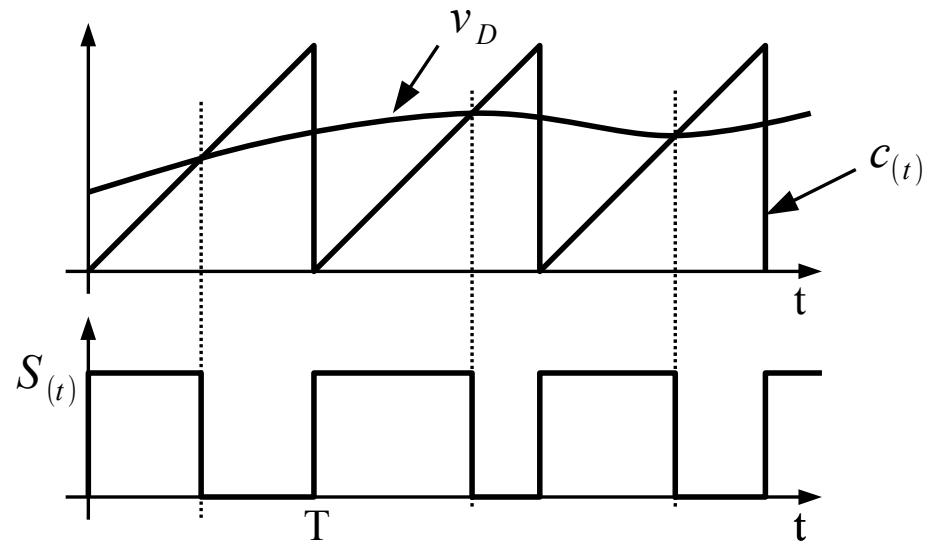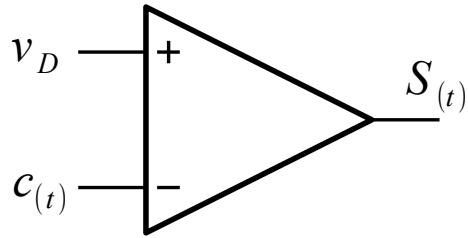



Variable Frequency PWM

constant off-time, variable on-time

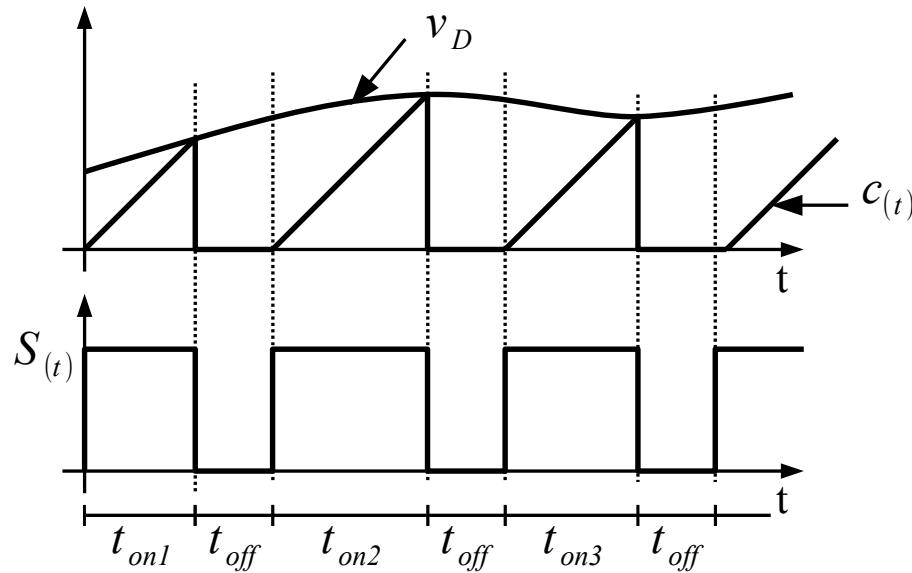

constant on-time, variable off-time

Current Mode Control (CMC)

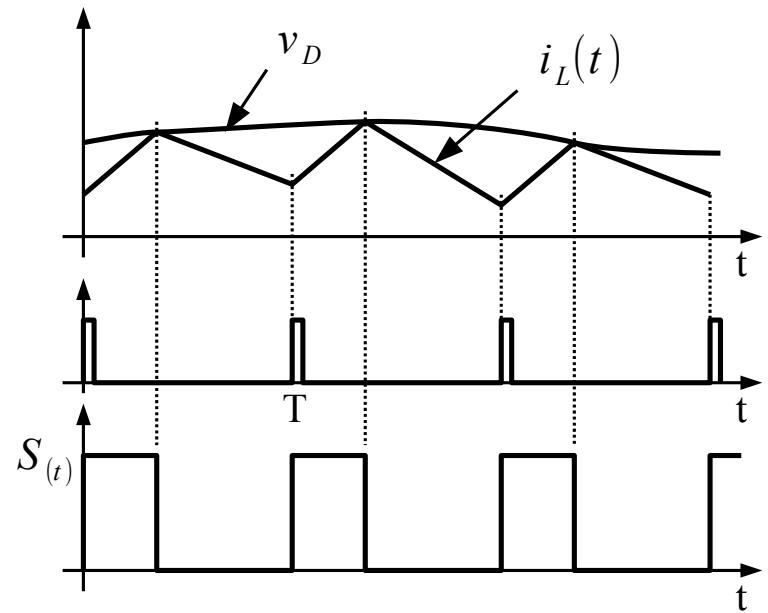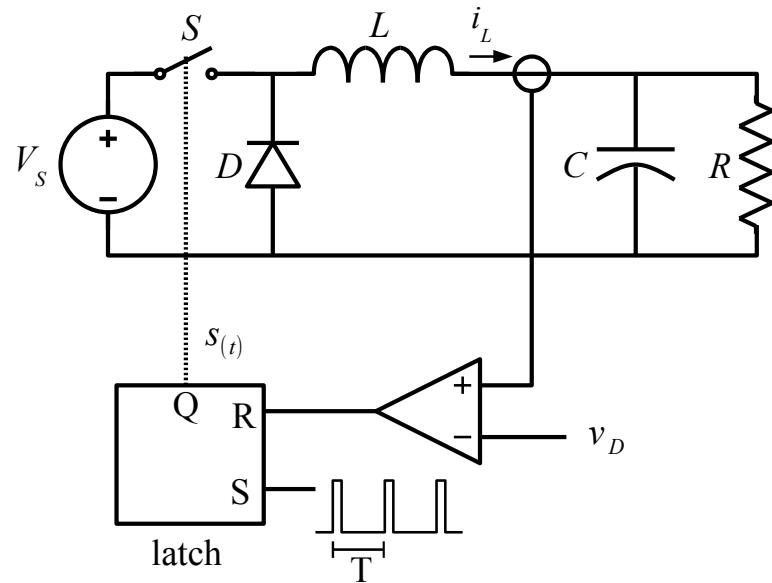

Current Mode Control

The CMC controls the inductor current. An outer control loop is needed for output voltage regulation.

Advantages:

- Simple
- Low cost
- Easy input voltage feed-forward

Disadvantages

- Sub-harmonic oscillation for $D>0.5$. An slope compensation solves this problem.

Variable Structure Control

It is a nonlinear control which generates the switching function according to the state-space variables of the system.

Advantages:



- Low sensitivity to plant parameter uncertainty
- Robustness

Disadvantages

- Chattering
- Variable frequency

Variable Structure Control

Hysteresis control

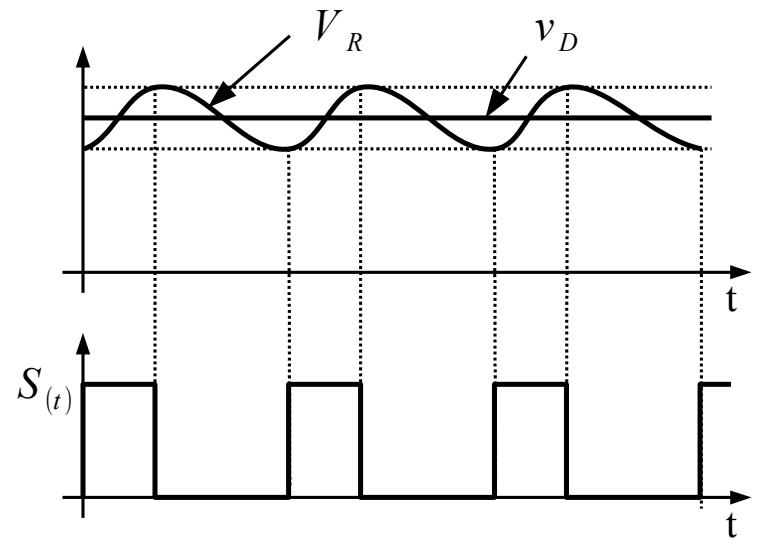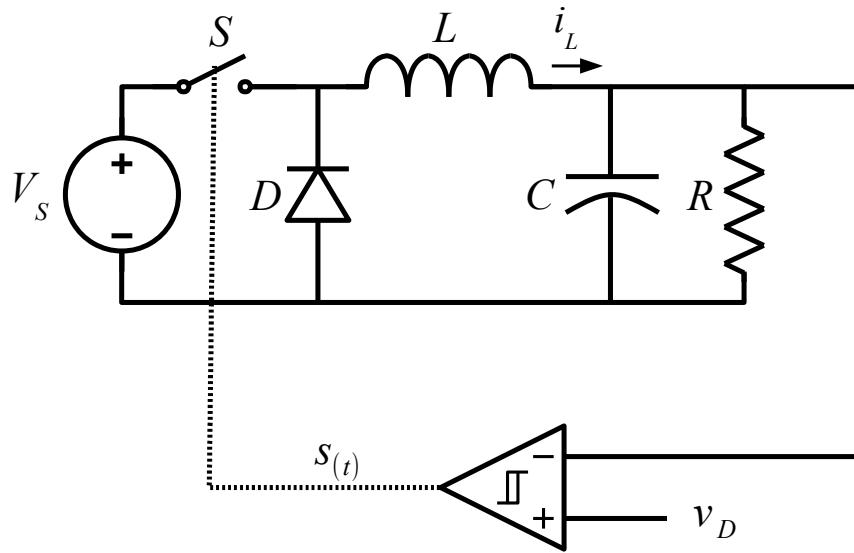


Derived Topologies

- Half Bridge Converter
- Push-Pull Converter
- Full Bridge Converter
- Forward Converter
- Flyback Converter
- Ćuk Converter


Derived Topologies

Half Bridge Converter

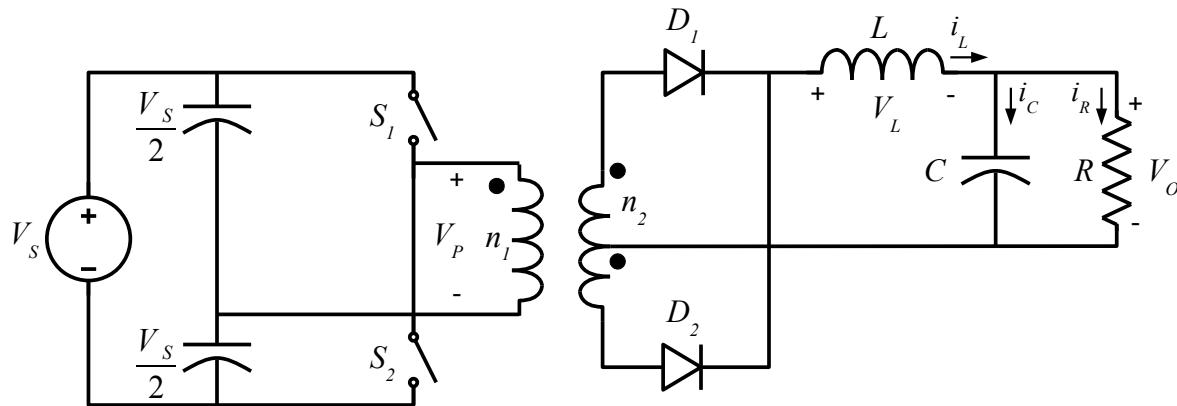


Transformer Input Waveform

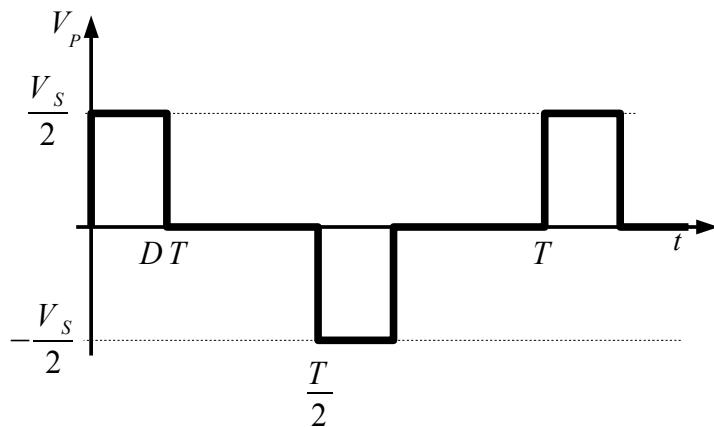- Volt-second product over a period must be zero to avoid transformer saturation



Derived Topologies


Push-Pull Converter

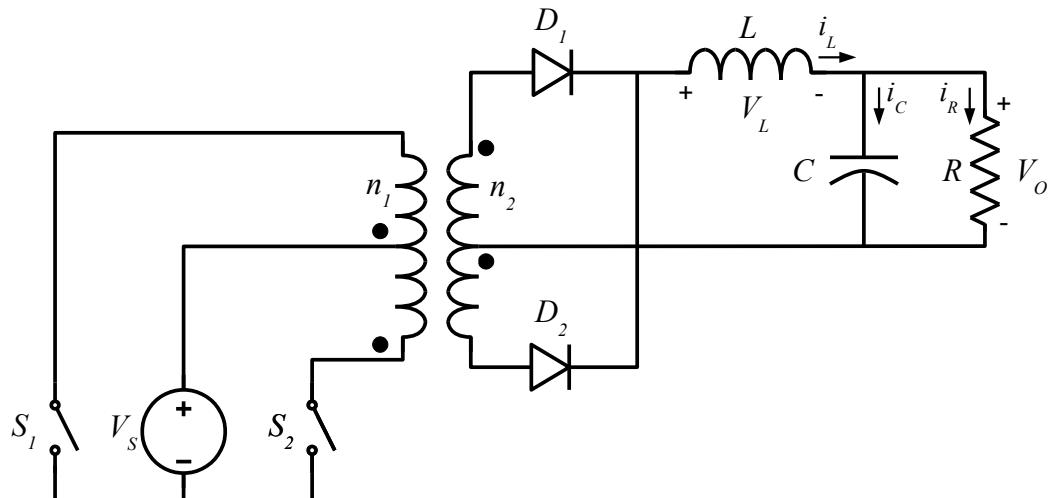

$$M_V \equiv \frac{V_o}{V_s} = 2 D \frac{n_2}{n_1}$$

Derived Topologies


Full Bridge Converter

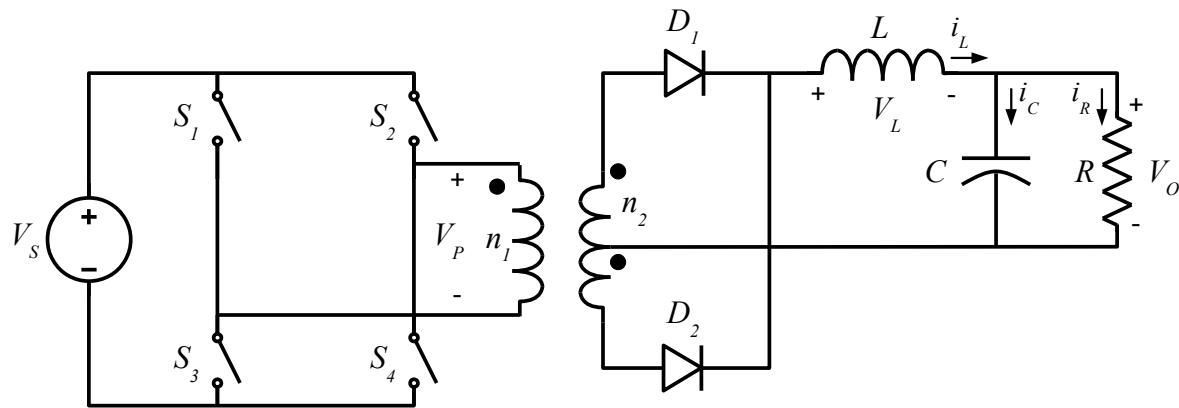

$$M_V \equiv \frac{V_o}{V_s} = 2D \frac{n_2}{n_1}$$

Derived Topologies

Forward Converter

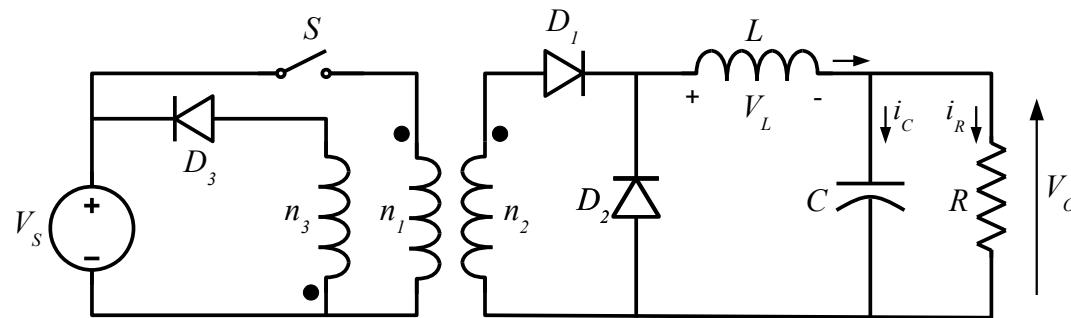


$$M_V \equiv \frac{V_o}{V_s} = D \frac{n_2}{n_1}$$

$$n_1 D \leq n_3 (1 - D)$$

Derived Topologies


Flyback Converter

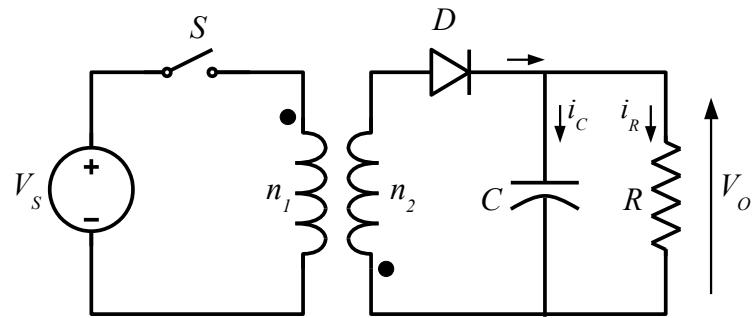

$$M_V \equiv \frac{V_o}{V_s} = \frac{n_2}{n_1} \frac{D}{1-D}$$

Derived Topologies

Ćuk Converter

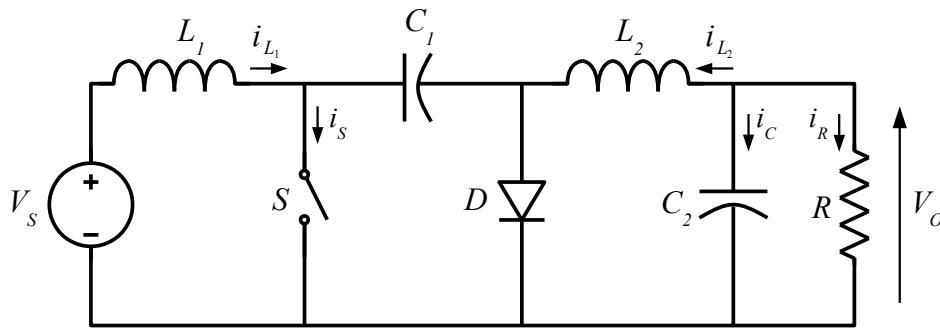

$$I_{L_2}DT = I_{L_1}(1-D)T$$

$$P_{IN} = V_s I_{L_1} = -V_o I_{L_2} = P_{OUT}$$

$$M_V \equiv \frac{V_o}{V_s} = \frac{D}{(1-D)}$$

Derived Topologies

Ćuk Converter

There is also an isolated version.

The inductors can be integrated using only one magnetic core

Advantage:

- Smooth input and output current

Disadvantage:

- More components

Other Issues

- Synchronous Rectification
- Interleaved Converters
- Hard Switching, Snubbers and Soft Switching
- DC-DC Resonant Converters
- References and Further Readings


Synchronous Rectification

Conduction losses


$$P_D = V_F I_O (1 - D) \quad V_F = \text{diode forward voltage drop}$$

$$\eta = \frac{V_o I_o}{V_o I_o + V_F I_o (1 - D)} = \frac{V_o}{V_o + V_F (1 - D)}$$

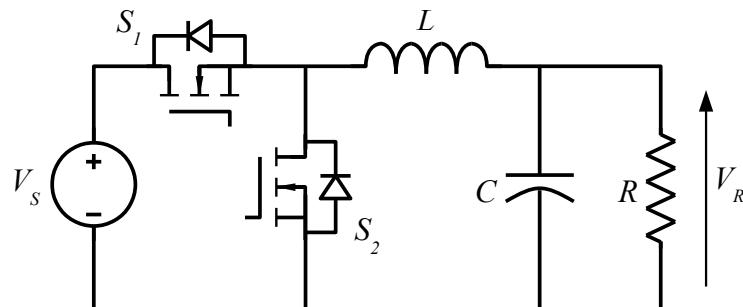
Efficiency is low for low output voltage power converters




Power Losses in Diode and MOSFET

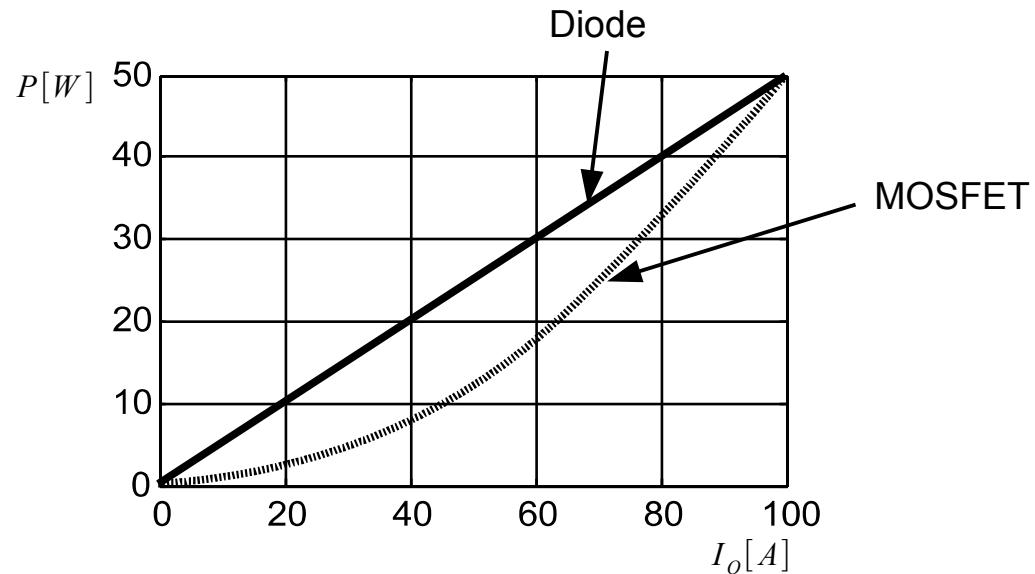


Interleaved Converters

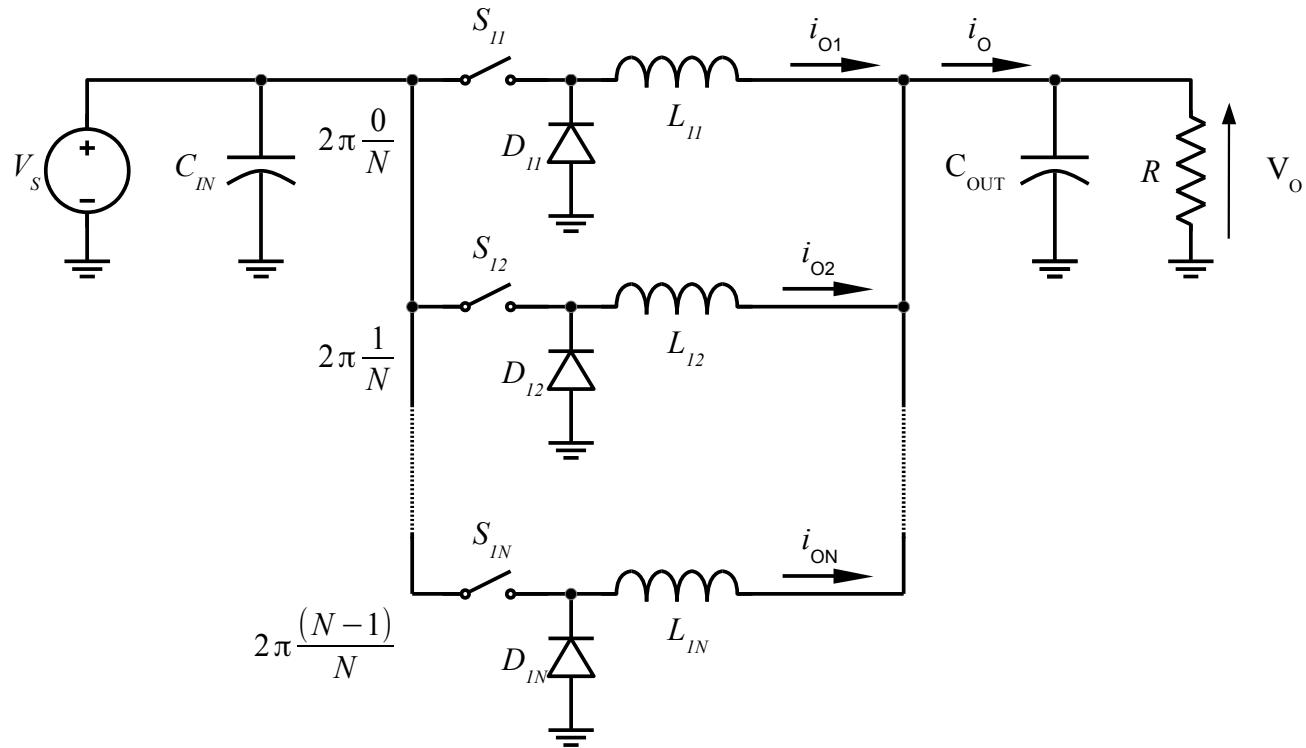


Interleaved Converters: Output Current

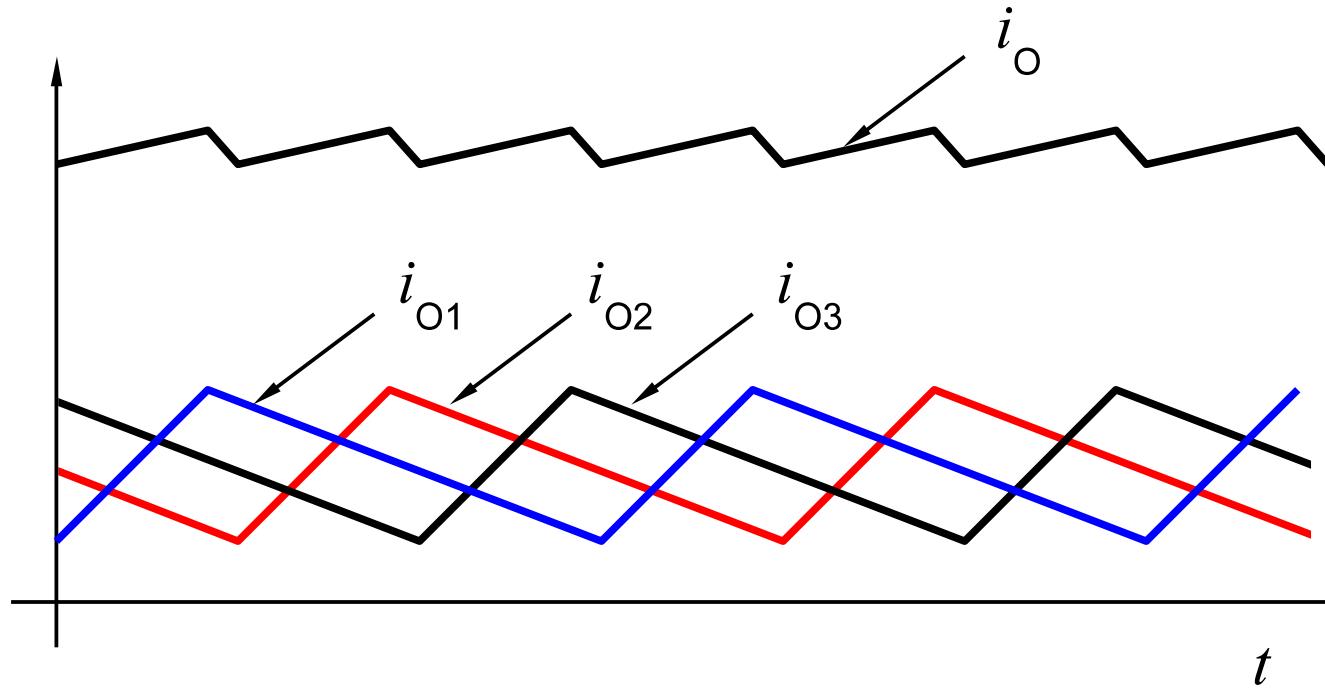

Normalized Output Current Ripple

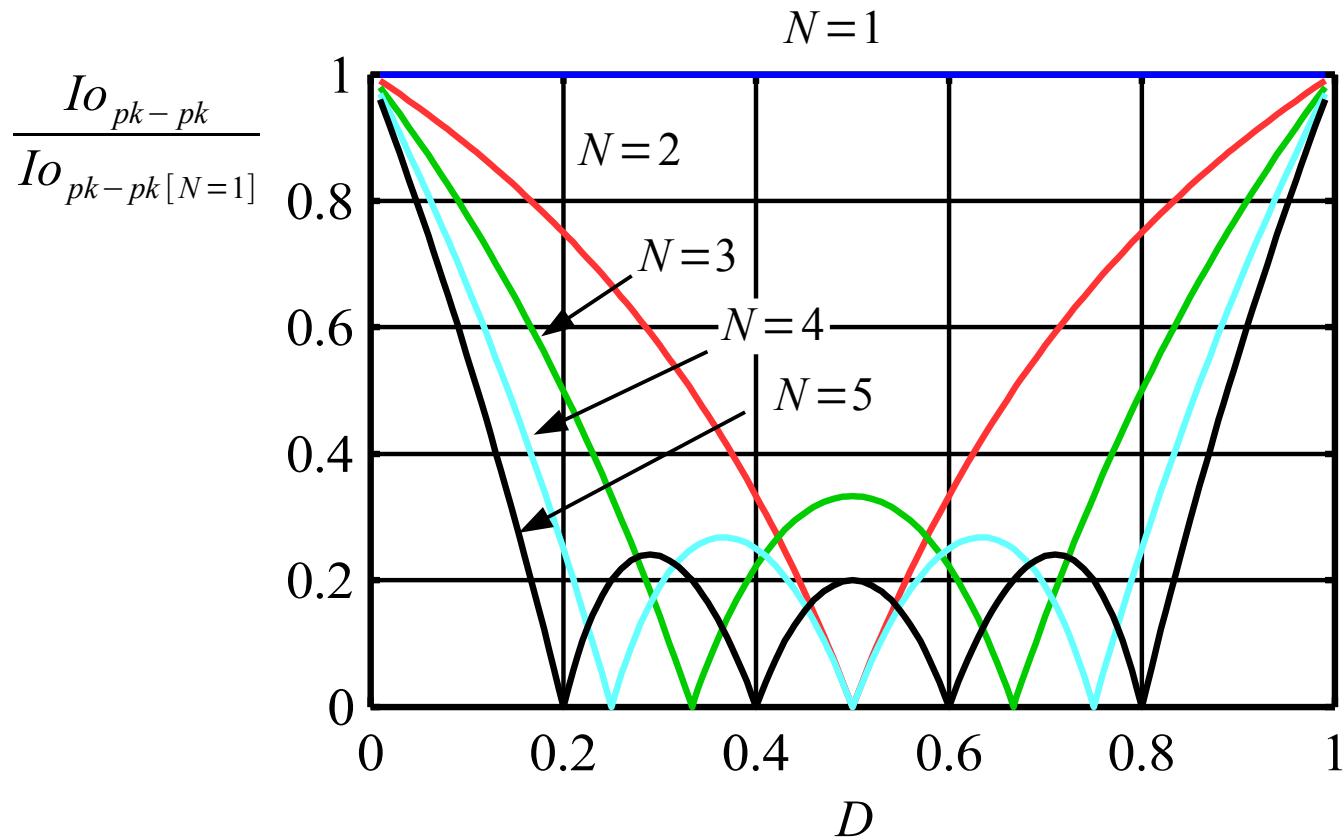


Normalized Input Capacitor RMS Current

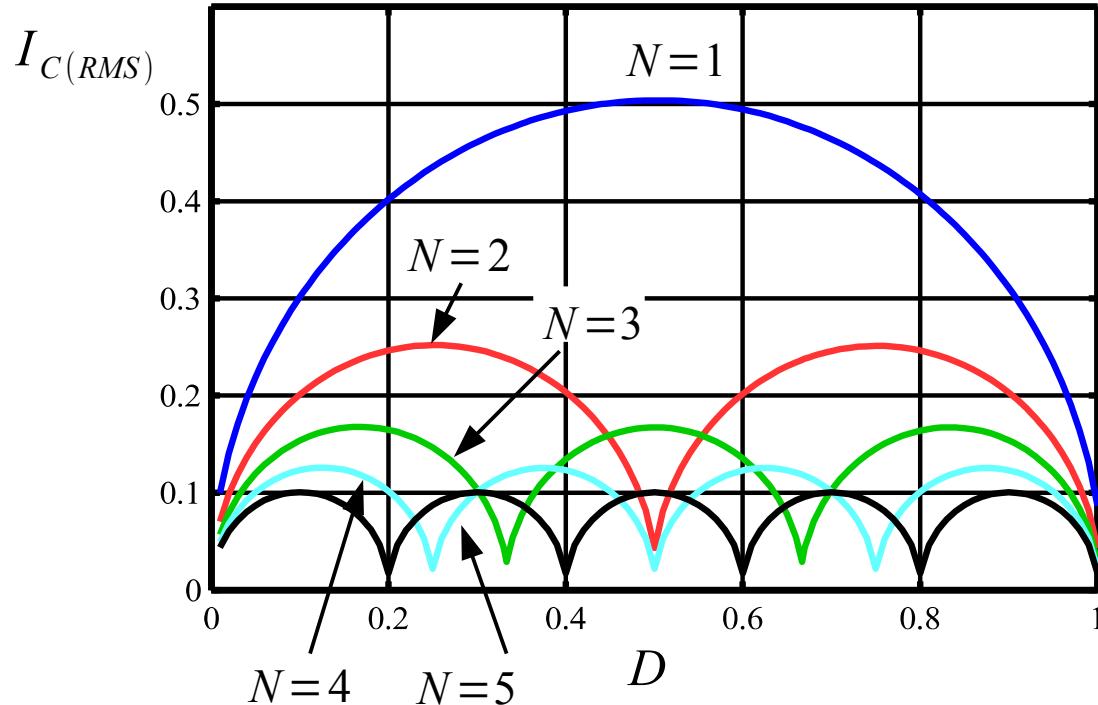



$$I_O = 1 A.$$

$$\Delta I_{ON} = 0.30 I_{ON}.$$



Hard Switching

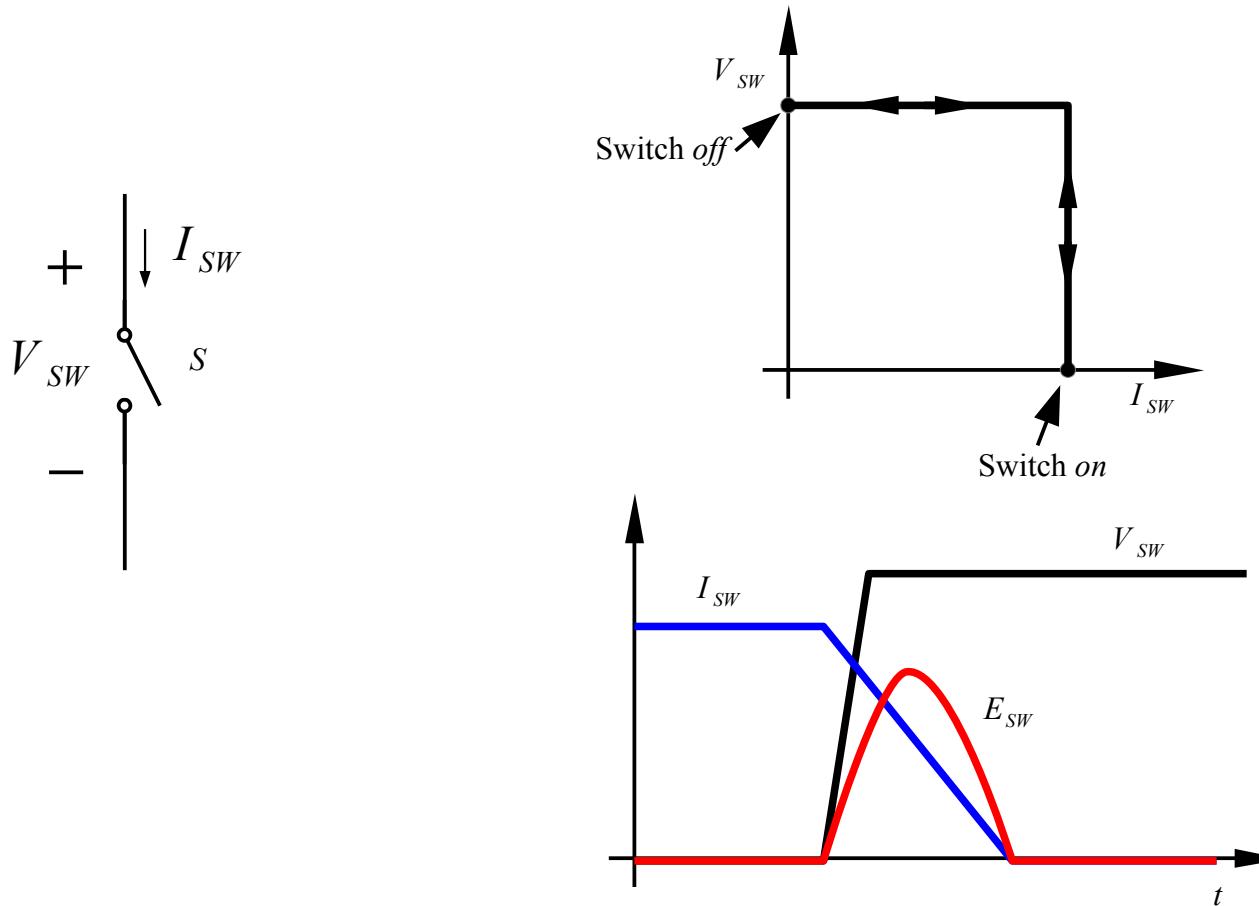



Snubbers

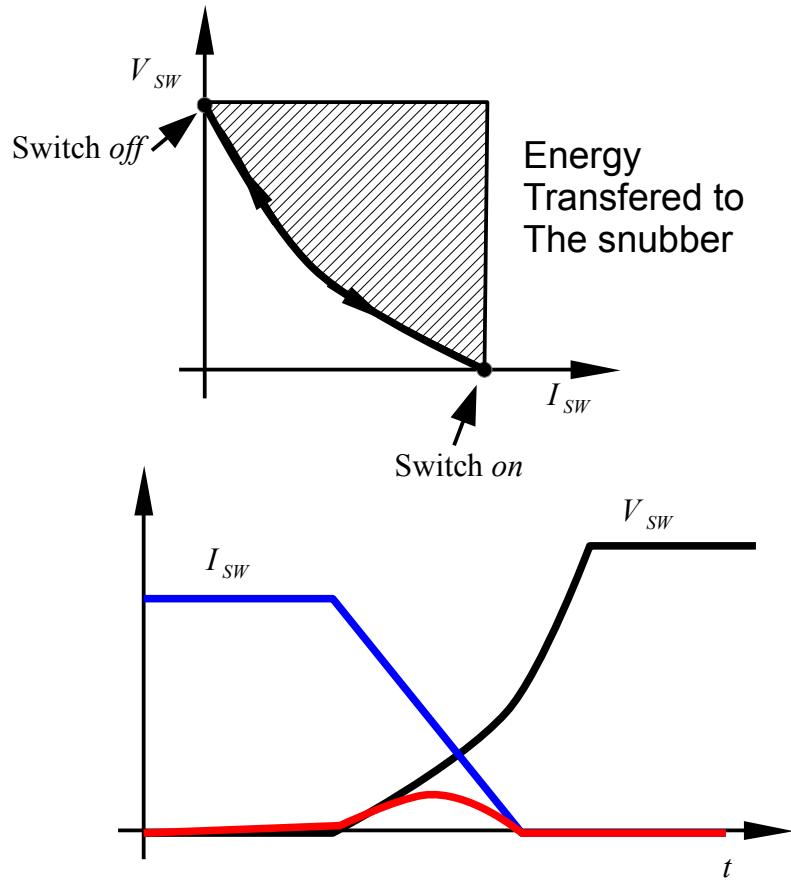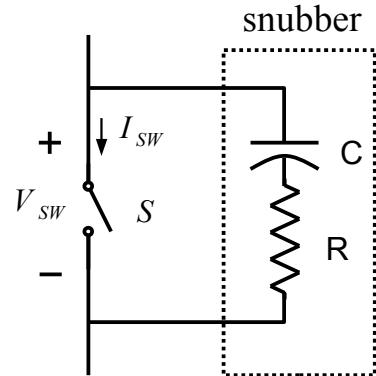

Soft Switching

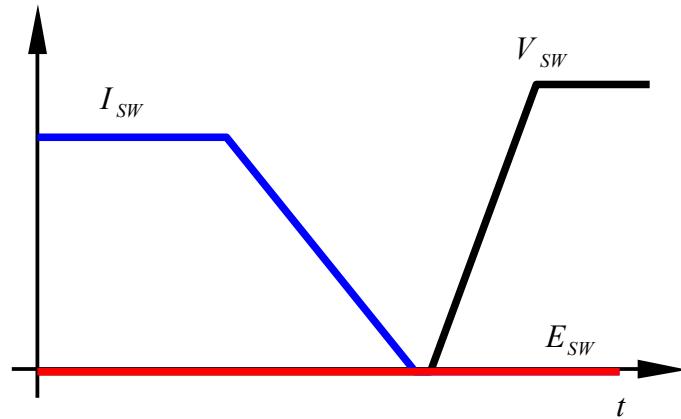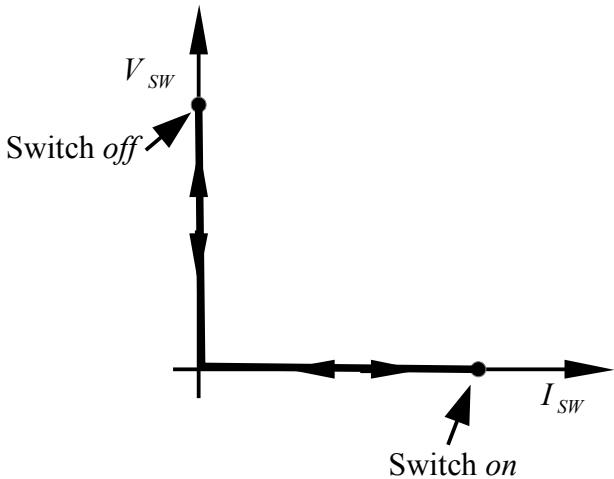


Soft Switching

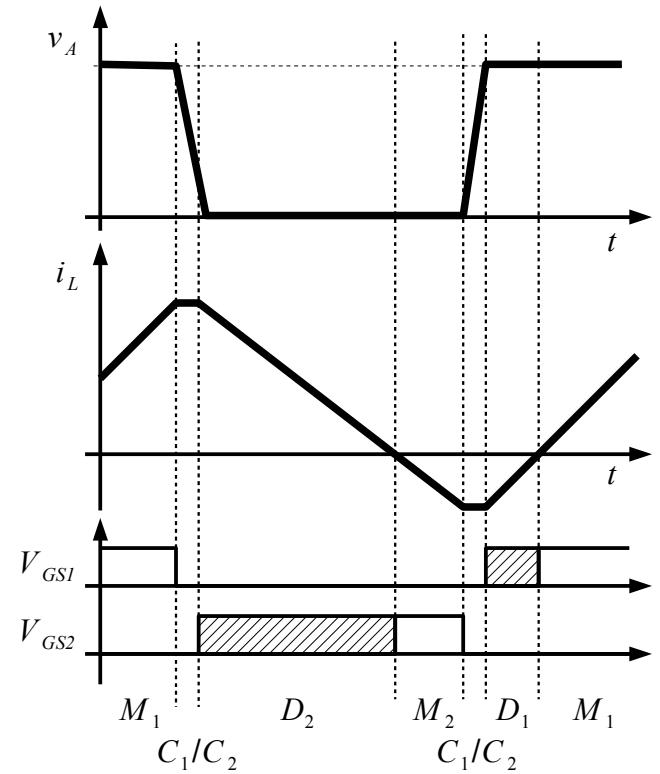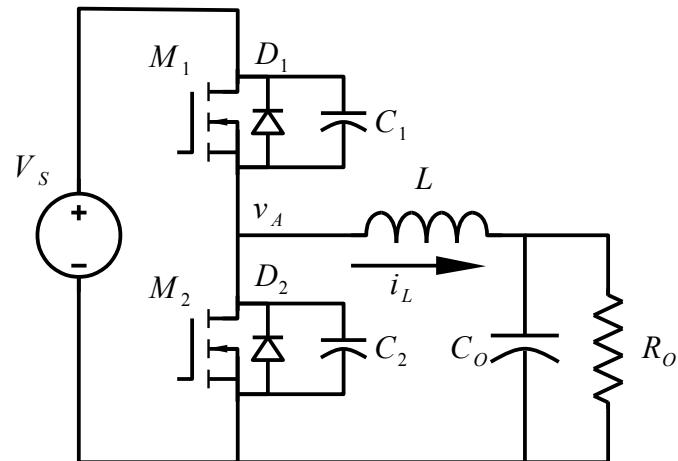


DC-DC Resonant Converters

Resonant Converters operates by applying a square voltage or current generated by switches to a resonant circuit.

- Series resonant converter

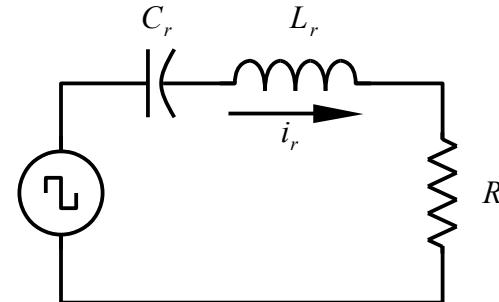

- Parallel resonant converter

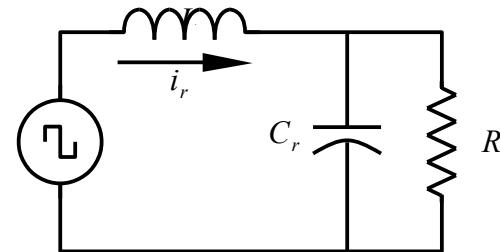


The converters operate at frequencies close to the resonant frequency.


The energy transferred to the load is controlled by changing the operating frequency.

LCC and LLC Resonant Converters

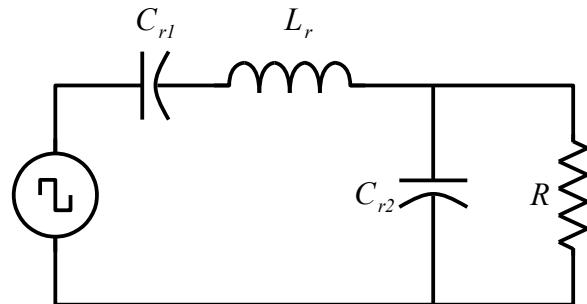
- LCC resonant converter
 - Disadvantages: two capacitors



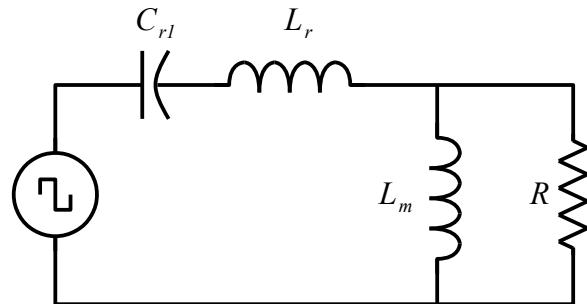
- LLC resonant converter
 - Advantage: the two inductances can be integrated into one magnetic component



LLC Resonant Converters

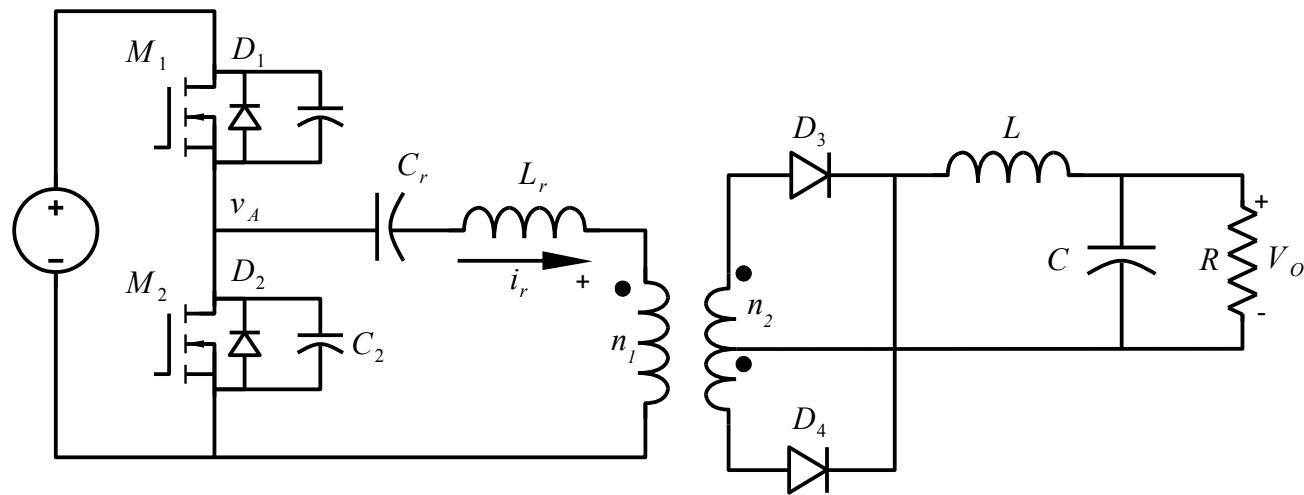

LLC Converter Waveforms. ZVS

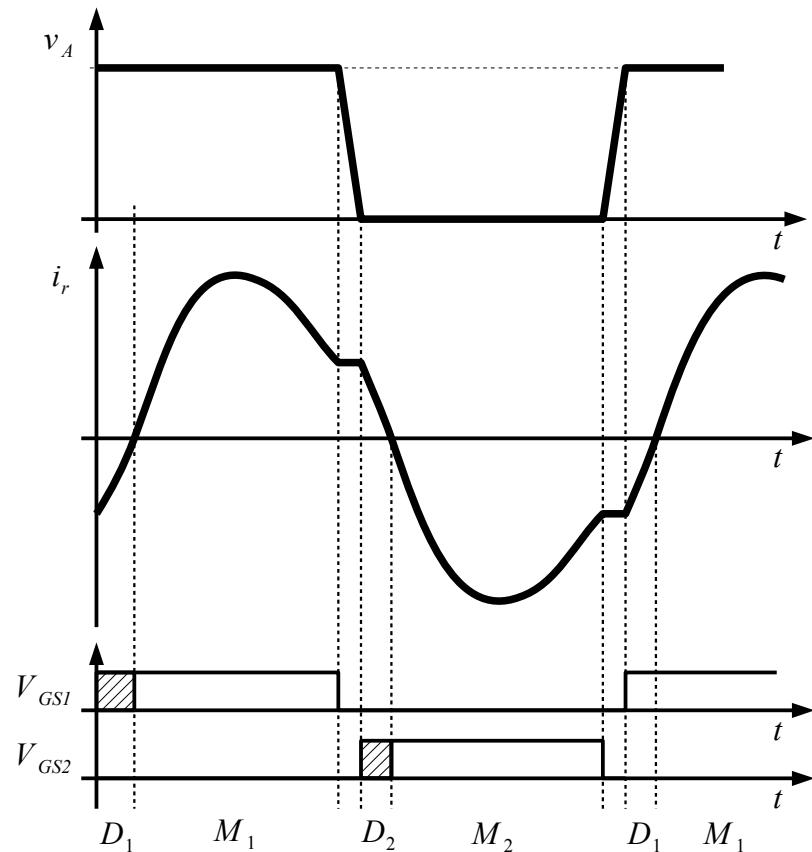

DC-DC Resonant Converters

- High Efficiency – Soft switching operation
- High operating frequency – small reactive components
- High power density
- More complex control
- Stress in semiconductors (large voltages and currents)

References and Further Reading

- MOHAN, Ned; UNDELAND, TORE M.; ROBBINS, W. P. Power electronics: converters, applications and design, 1995. 1997. ISBN: 978-0471226932
- RASHID, Muhammad H. (ed.). Power electronics handbook. Academic Pr, 2001.. ISBN: 978-0123820365
- BORDRY, F. Power converters: definitions, classification and converter topologies. CAS CERN Accelerator School and CLRC Daresbury Laboratory. 2004.
- SHEEHAN, Robert; ANATOLE, Hilton. Understanding and Applying Current-Mode Control Theory. En Power Electronics Technology Exhibition and Conference, Dallas. 2007. p. 1-26.
- HUNG, John Y.; GAO, Weibing; HUNG, James C. Variable structure control: a survey. Industrial Electronics, IEEE Transactions on, 1993, vol. 40, no 1, p. 2-22.
- MAPPUS, Steve. Synchronous rectification for Forward Converters. Fairchild Semiconductor Power Seminar 2010-2011.
- HEGARTY, T. Benefits of multi-phasing buck converters. EE Times–India, 2007, p. 1-4.
- HUANG, Hong. Designing an LLC resonant half-bridge power converter. En TI Power Supply Design Seminar SEM1900. 2010.

Thank You !