



CERN

European Organization for Nuclear Research  
Organisation Européenne pour la Recherche Nucléaire

# Power converters

*Definitions and classifications*  
*Converter topologies*

*Frédéric BORDRY*  
*CERN*

"Introduction to Accelerator Physics"  
28 October - 9 November, 2012  
GRANADA - SPAIN



# Menu

- Power converter definition and classification
- Power converter topologies:  
*line commutated and switch mode based*  
Sources, power switches (semiconductors),  
commutation rules,...
- Special case for magnet powering  
(Voltage source - Current source)
- Pulsed power converters
- Control and precision
- *Conclusions*

In 1 hour ????





# High energy physics and power converters

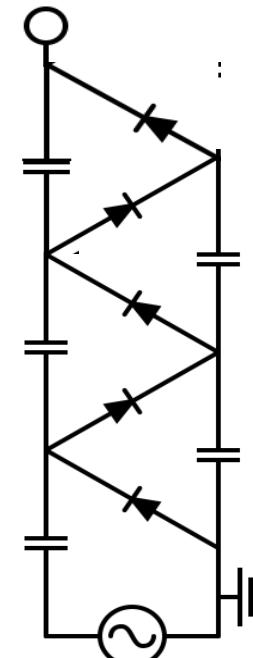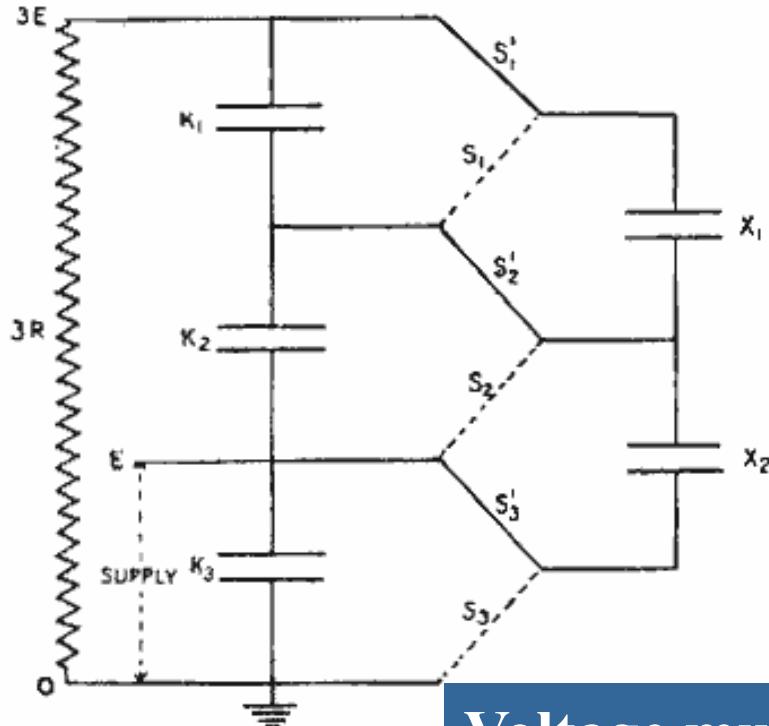
## The « Nobel prize » power converter :

[Cockcroft & Walton] who in 1932 used this **voltage multiplier** to power their **particle accelerator**, performing the first artificial nuclear disintegration in history. They used this cascade circuit for most of their research, which in 1951 won them the **Nobel Prize in Physics** for "Transmutation of atomic nuclei by artificially accelerated atomic particles".

Schematic of Cockcroft and Walton's voltage multiplier. Opening and closing the switches S, S' transfers charge from capacitor K3 through the capacitors X up to K1.



Voltage multiplier : switches...

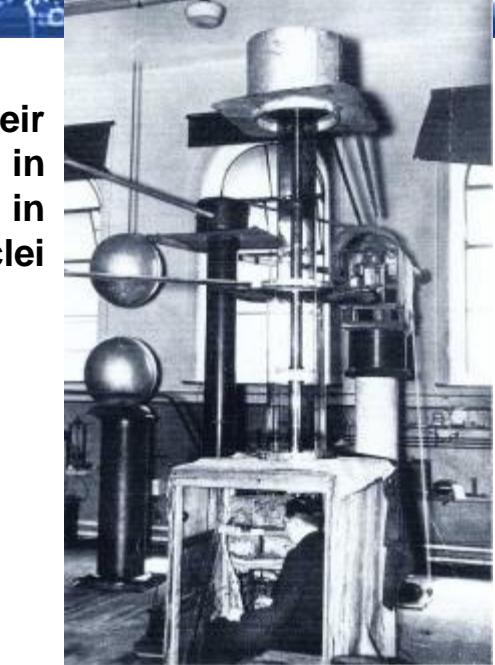

# “On a new principle for the production of higher voltages.”


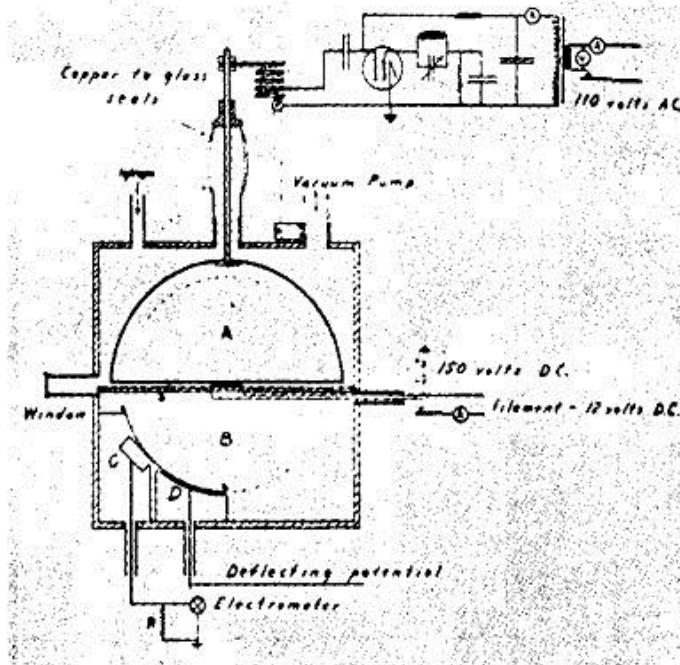


Diagram of the first successful cyclotron constructed by Lawrence and M. S. Livingston. The single dee is five inches in diameter.

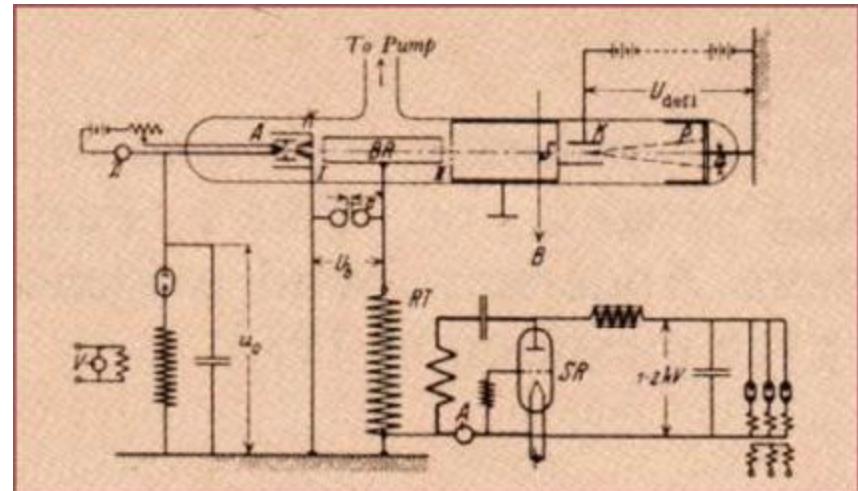

The difficulties of maintaining high voltages led several physicists to propose accelerating particles by using a lower voltage more than once. **Lawrence** learned of one such scheme in the spring of 1929, while browsing through an issue of *Archiv für Elektrotechnik*, a German journal for **electrical engineers**. Lawrence read German only with great difficulty, but he was rewarded for his diligence: he found an article by a Norwegian engineer, **Rolf Wideröe**, the title of which he could translate as “On a new principle for **the production of higher voltages**.” The diagrams explained the principle and Lawrence skipped the text.

# Power converters : Definitions

The source of the beam blow-up when we could not prove it was the RF  
(Control room operator)

A powerful (small) black box able to convert MAD files into currents  
(Accelerator Physics group member)

An equipment with three states, ON, OFF and FAULT  
(Another operator)

Is it the same thing as a power supply?  
(Person from another physics lab)

A big box with wires and pipes everywhere and blinking lamps. Occasionally it goes BANGG!  
(Former CERN Power Converter Group secretary view)

# Power converters : Definitions (cont'd)

**That which feeds the magnets**

**(a visitor)**

**A stupid installation taking a non-sinusoidal current  
at poor power factor (Power distribution engineer)**

**A standard piece of equipment available from  
industry off-the-shelf**


**(a higher management person, not in in this room !)**
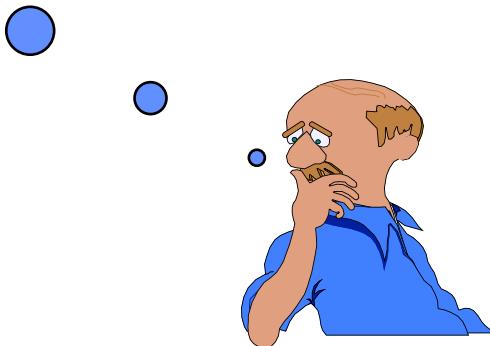
# Power converters specifications

"Do you have one or two power converters for the test of magnet prototypes? 40 A will be enough ?  
Precision is not important for time being.  
Don't worry it's not urgent. Next month is OK "  
(Email received 05.12.08)




40A power converter:  
Size? Weight ? Cost?



# [40A, 100 kV,] klystron power converter

DC Power: 4 MW

November 2012

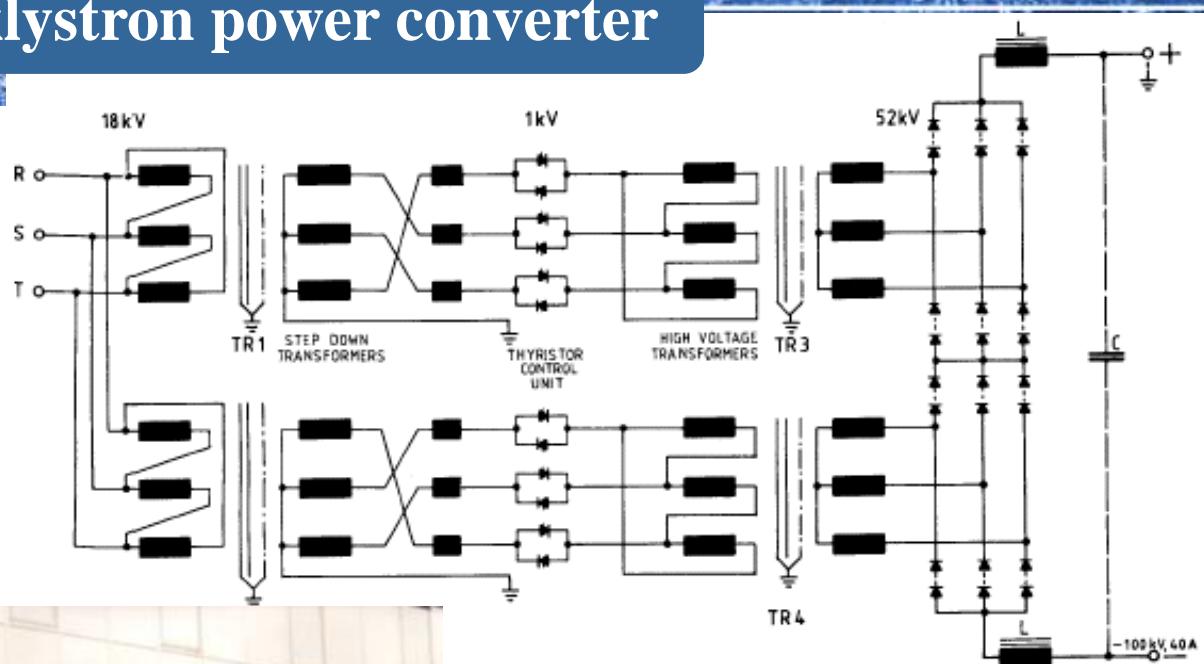


DC operation



# Pulsed klystron modulators for LINAC 4

Specification	symbol	Value	unit
Output voltage	$V_{kn}$	110	kV
Output current	$I_{out}$	50	A
Pulse length	$t_{rise} + t_{set} + t_{flat} + t_{fall}$	1.8	ms
Flat-Top stability	FTS	<1	%
Repetition rate	$1/T_{rep}$	2	Hz

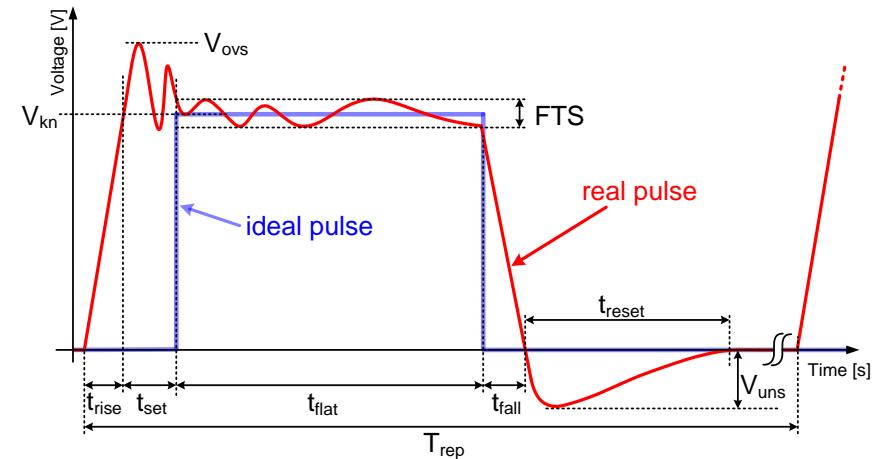

**Peak power : 5.5MW**  
**Average power: 20kW**



# LHC orbit corrector : [ $\pm 60\text{A}$ , $\pm 8\text{V}$ ]

Magnet :  $L=7\text{ H}$  ;  $R = 30\text{ m}\Omega$  (60m of  $35\text{ mm}^2$ )  
 $T = L/R = 300\text{ s} \Rightarrow f^{OL}_B \approx 0.5\text{ mHz}$

$$U_{\text{static}} = R \cdot I = 1.8\text{V}$$



**6 V for the  $dI/dt$  with  $L= 7\text{ H}$**

**( $dI/dt_{\text{max}} \approx 1\text{A/s}$ ) OK**

**Small signal :  $f^{CL}_B \approx 1\text{ Hz} : \Delta I = 0.1\text{ A} = 0.15\% \text{ I}_{\text{max}}$**

“The power converters involved in feedback of the local orbit may need to deal with correction rates between 10 and 500 Hz”;

$$f^{CL}_B \approx 50\text{Hz} (\Delta I = 1\% : U_{\text{max}} = 2400\text{ V ?????...})$$

**( $U_{\text{max}} = 8\text{V} \Rightarrow \Delta I = 30\text{ ppm I}_{\text{max}} \text{ at } 50\text{ Hz}$ )**



# Power converters specifications

"Do you have one or two power converters for the test of magnet prototypes? 40 A will be enough ?  
Precision is not important for time being.  
Don't worry it's not urgent. Next month is OK "  
(Email received 05.12.08)

## Need of more specification data:


- Output Voltage
- DC or Pulsed (pulse length and duty cycle)
- Output voltage and current reversibility
- Precision (short and long term)
- Ripple (load definition)

Environment conditions: grid, volume, water ,....

# Energy source




# Applications

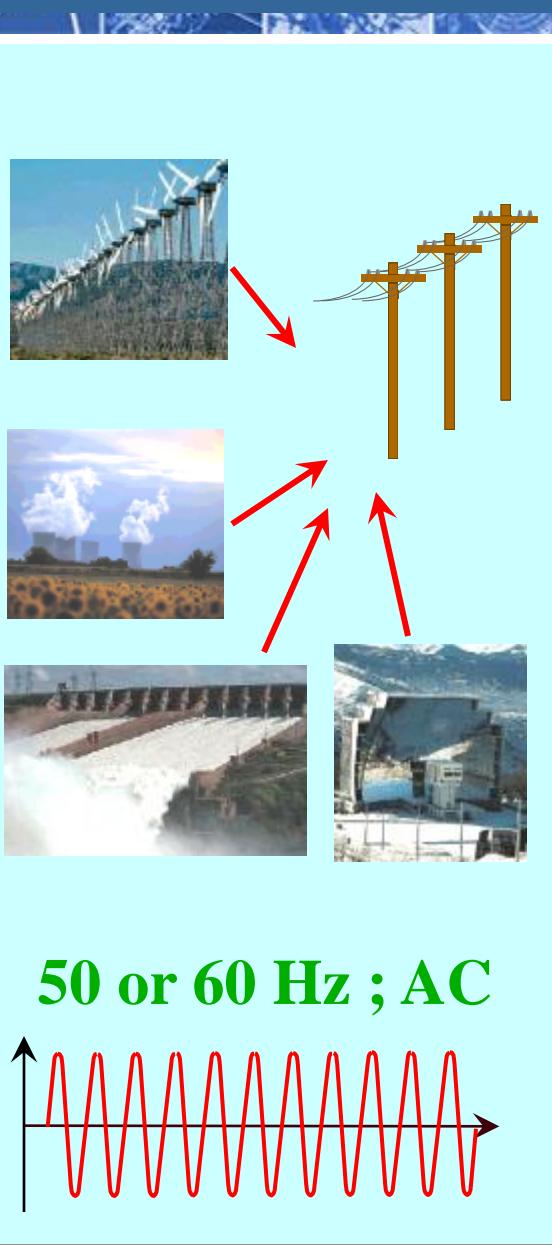
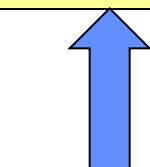
## Power converter

The task of a power converter is to process and control the flow of electric energy by supplying voltages and currents in a form that is optimally suited for user loads.



Control



Traction  
and auxiliary





Domestic Appliance



Medical applications

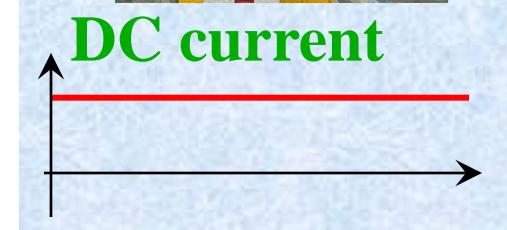Industrial applications,  
Welding, Induction Heating, ....



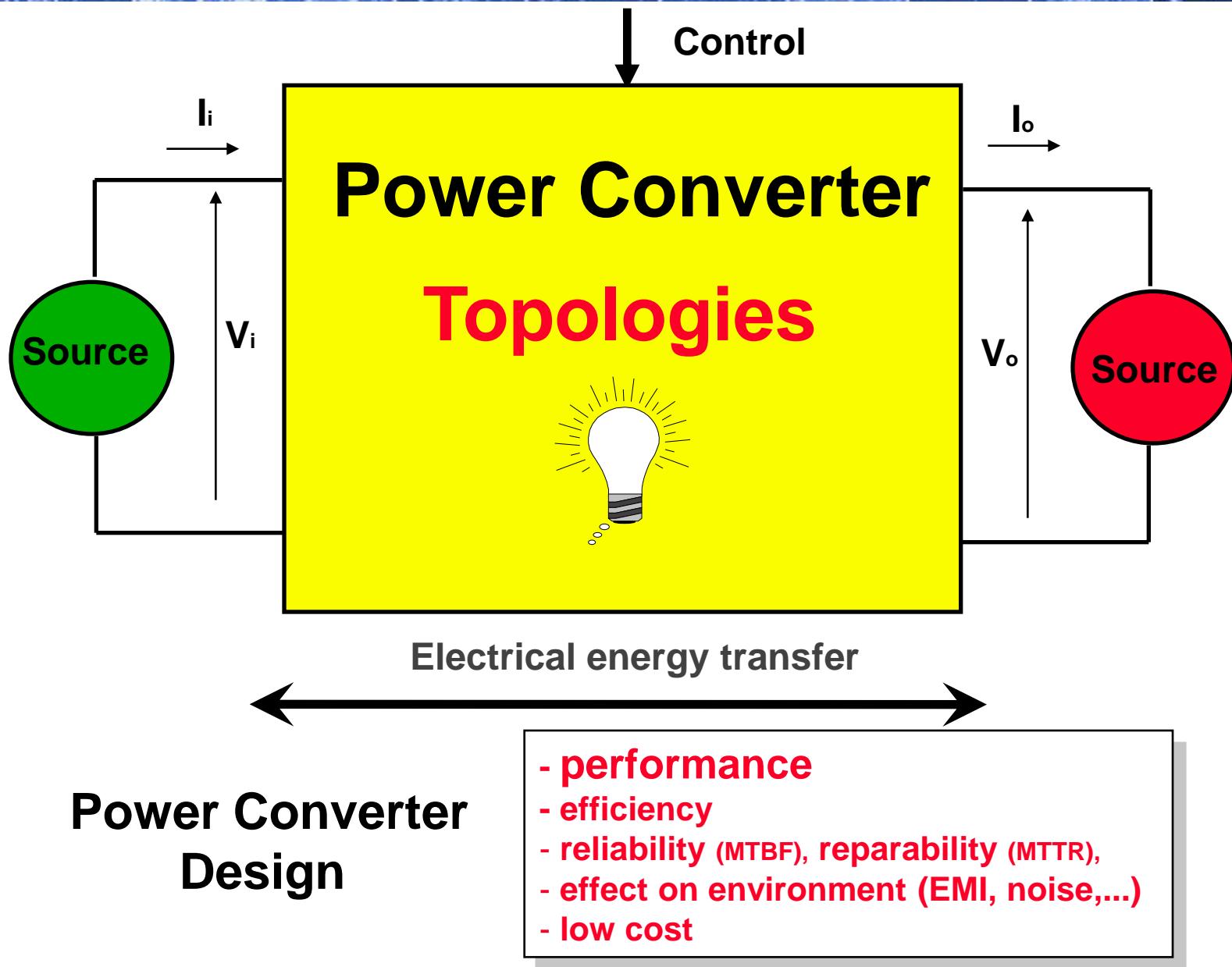

# Source definition

**Source definition:** any element able to impose a voltage or a current, independently of, respectively, the current flowing through, or the voltage imposed at its terminals.

**A source could be a generator or a receptor.**

Two types of sources:


## Voltage source

which imposes a voltage independently of the current flowing through it. This implies that the series impedance of the source is zero (or negligible in comparison with the load impedance)
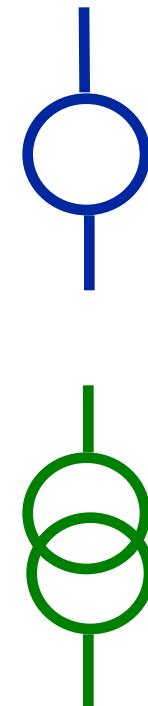
## Current source

which imposes a current independently of the voltage at its terminals.

This implies that the series impedance of the source is infinite (or very large in comparison with the load impedance)




# Source characteristics


Voltage source




Turn On impossible

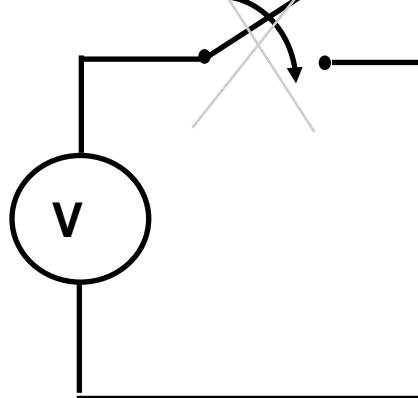

Current source

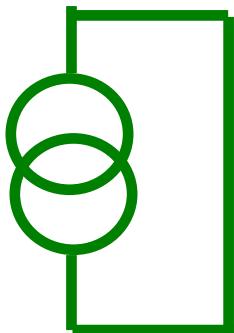


Turn Off impossible


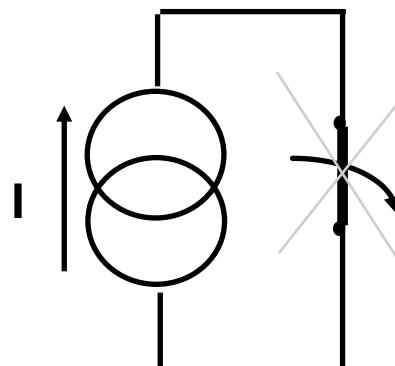

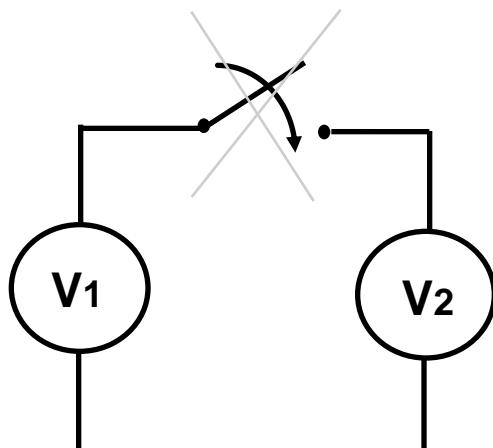
# Commutation rules

- *electronic switches modify the interconnection of impeding circuits*
- *any commutation leading instantaneous variations of a state variable is prohibited*



Turn On impossible

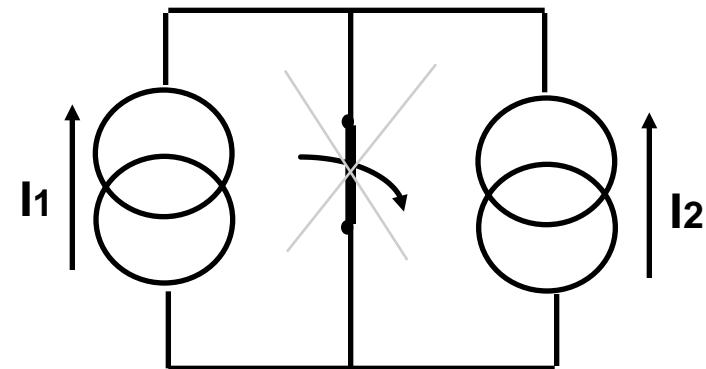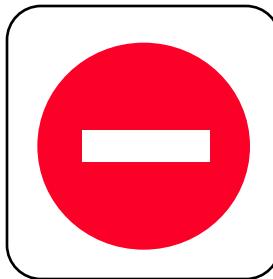


Turn Off impossible

Interconnection between two impeding networks can be modified only if :


- the two networks are sources of different natures (voltage and current)
- the commutation is achieved by TWO switches. The states of the two switches must be different.

# Commutation

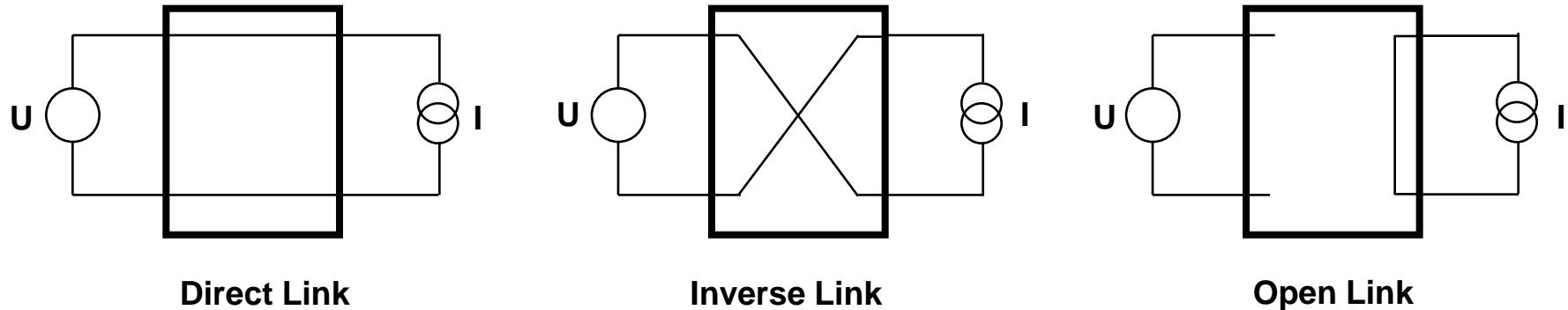


**Active components used as switches to create a succession of link and no link between sources to assure an energy transfer between these sources with high efficiency.**
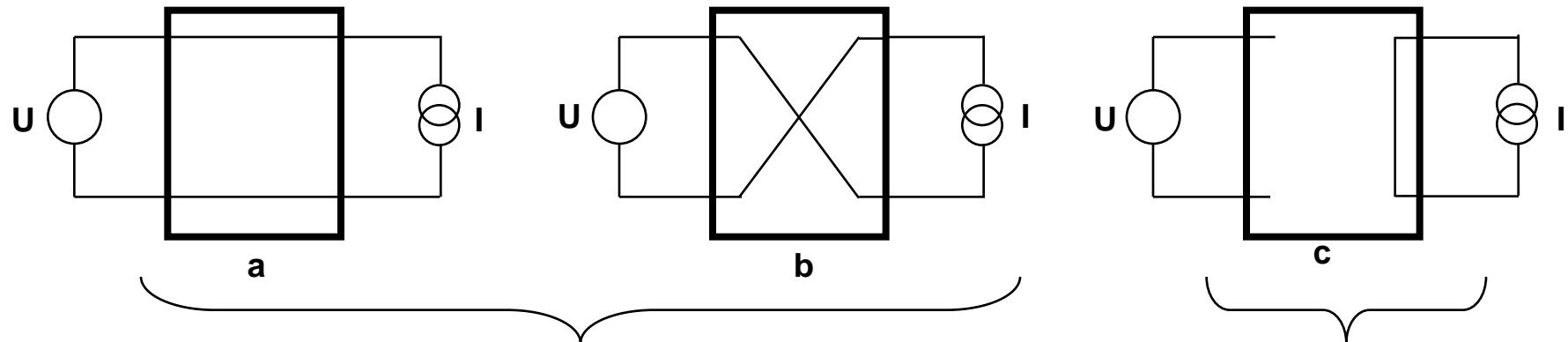
# Direct link configuration : Direct voltage-current converters



**Connexion**  
(energy flow between sources)

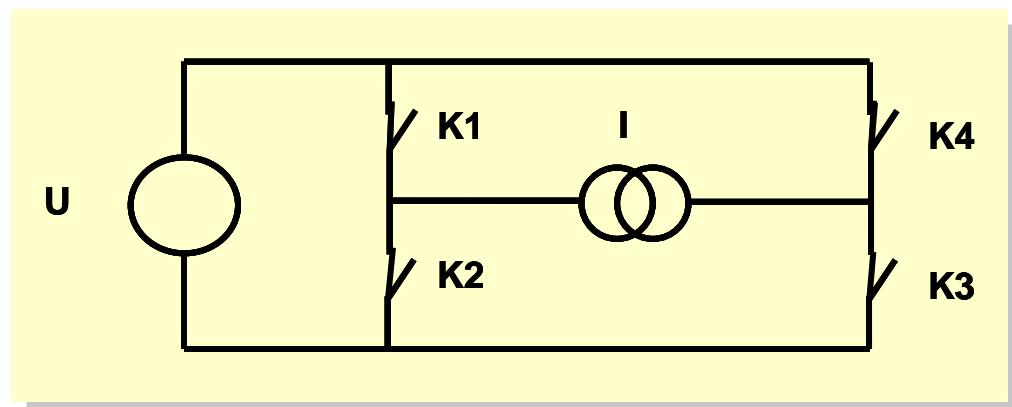**Disconnexion**  
(current source short-circuited,  
voltage source open circuited)





- K1 and K3 closed => a
- K2 and K4 closed => b
- K1 and K4 (or K2 and K3) closed => c

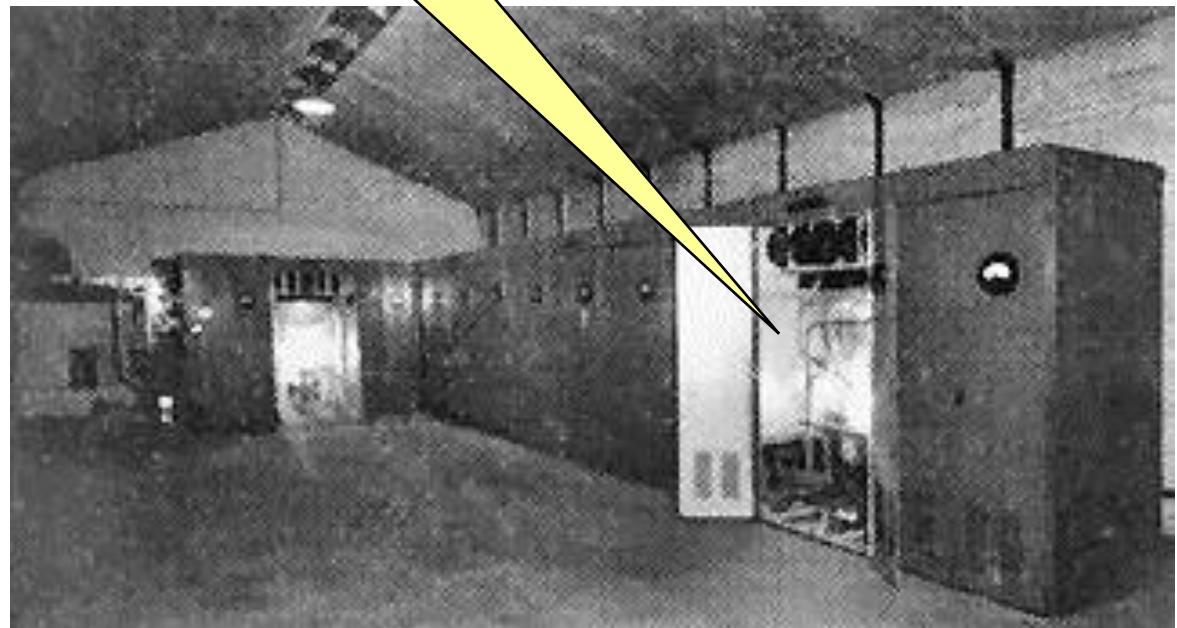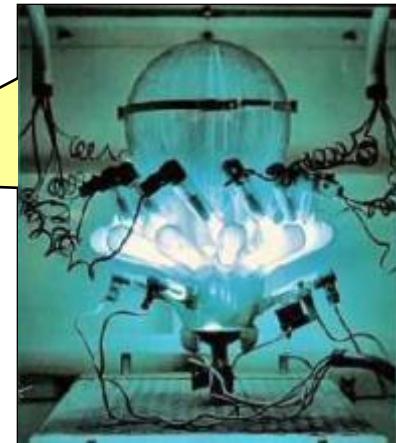
# Once upon a time.... not so far



This is a 6-phase device,  
150A rating with grid  
control.  
It measures 600mm high  
by 530mm diameter.



# Power Semiconductors

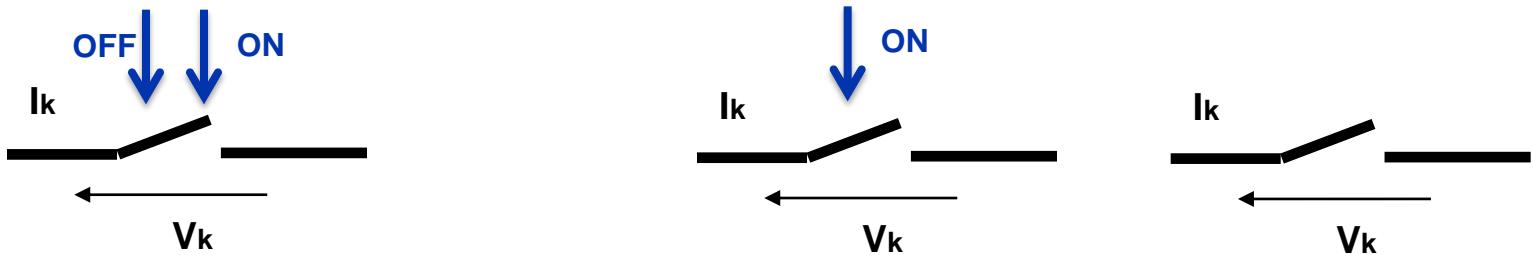


## Power Semiconductors

### Turn-off Devices


#### Transistors

- MOSFETs
- Darlings
- IGBTs

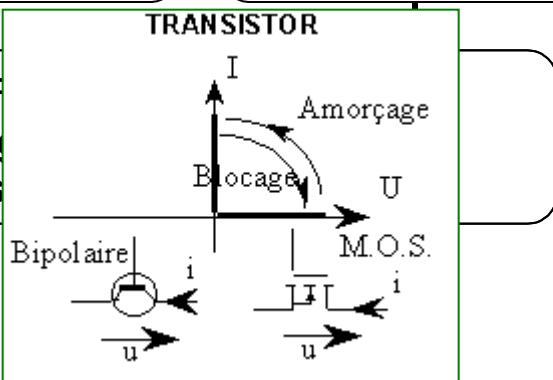

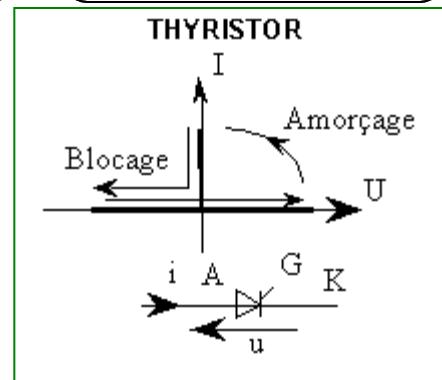
### Thyristors

- Line commutated
- Fast
- Bi-directional
- Pulse




### Diodes

- Fast
- Line commutated
- Avalanche

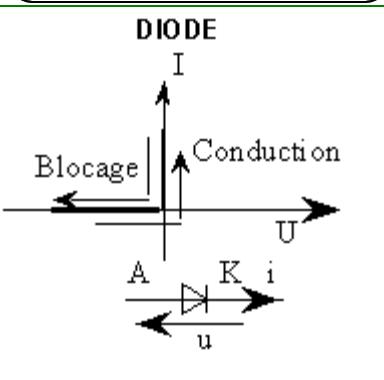
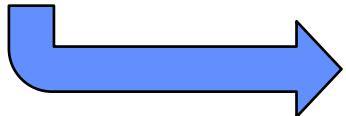
# Evolution of Power Switches

From mercury arc rectifier,  
grid-controlled vacuum-tube  
rectifier, inignitron ,....



...to solid state electronics (semiconductors)

**From 1960**

Power Diode and Thyristor

or SCR (Silicon-Controlled Rectifier )



L<sub>1</sub> Frequency of the  
electrical network  
50 Hz (60 Hz)

**From 1985**

New Power Electronics Topologies

High freq power semiconductors :  
MosFet, IGBTs , GTOs, IGCTs,....




High frequency => high  
performances (ripple,  
bandwidth, perturbation  
rejection,...)  
small magnetic  
(volume, weight)



# Power semiconductor switches capabilities


*Effective(\*) switching capabilities*

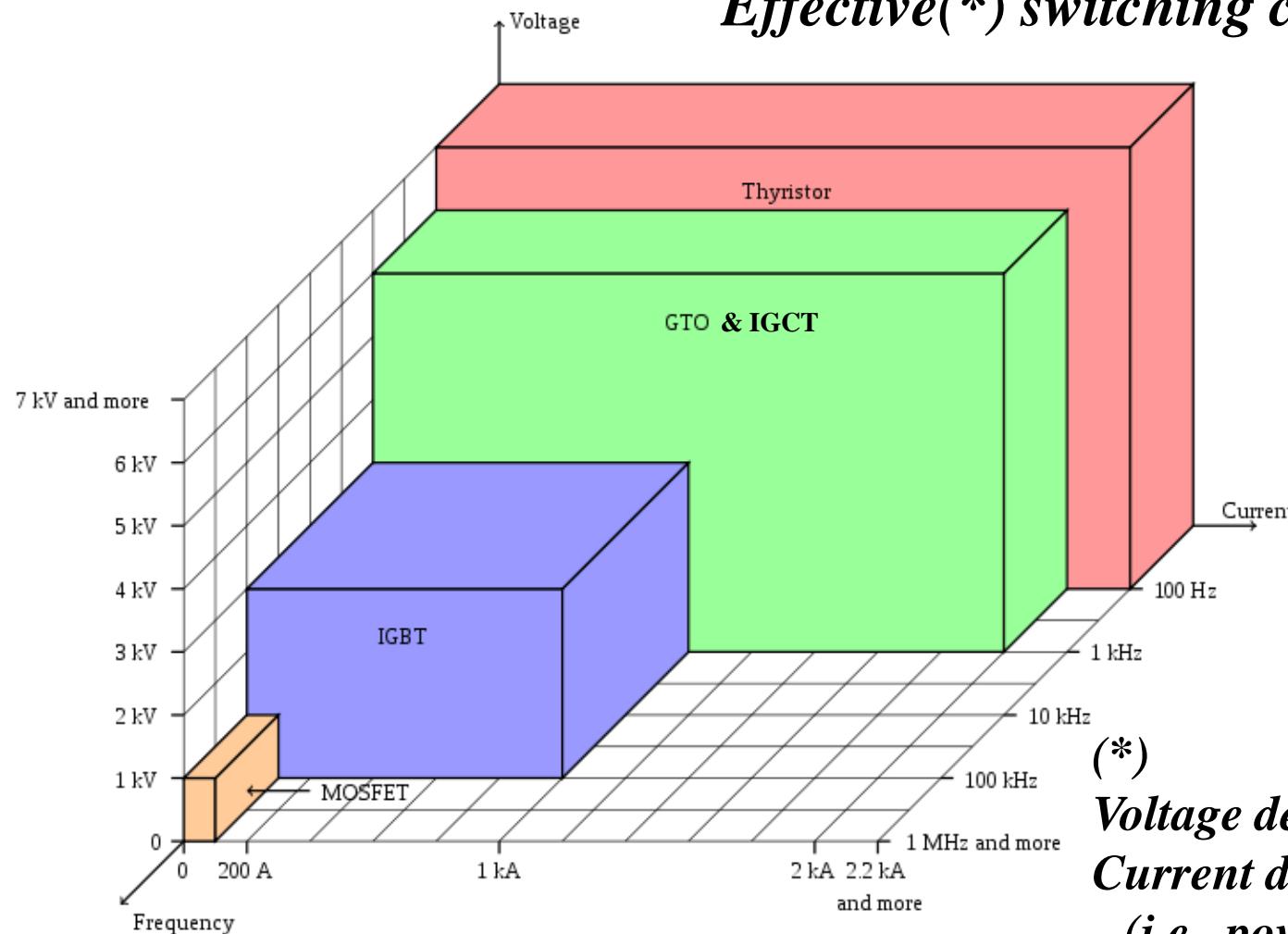

(\*)

*Voltage de-rating: 1.6;  
Current de-rating: ~1.3;  
(i.e., power de-rating:  $1.6 \times 1.3 \approx 2$ )*

# Power Converter for magnets

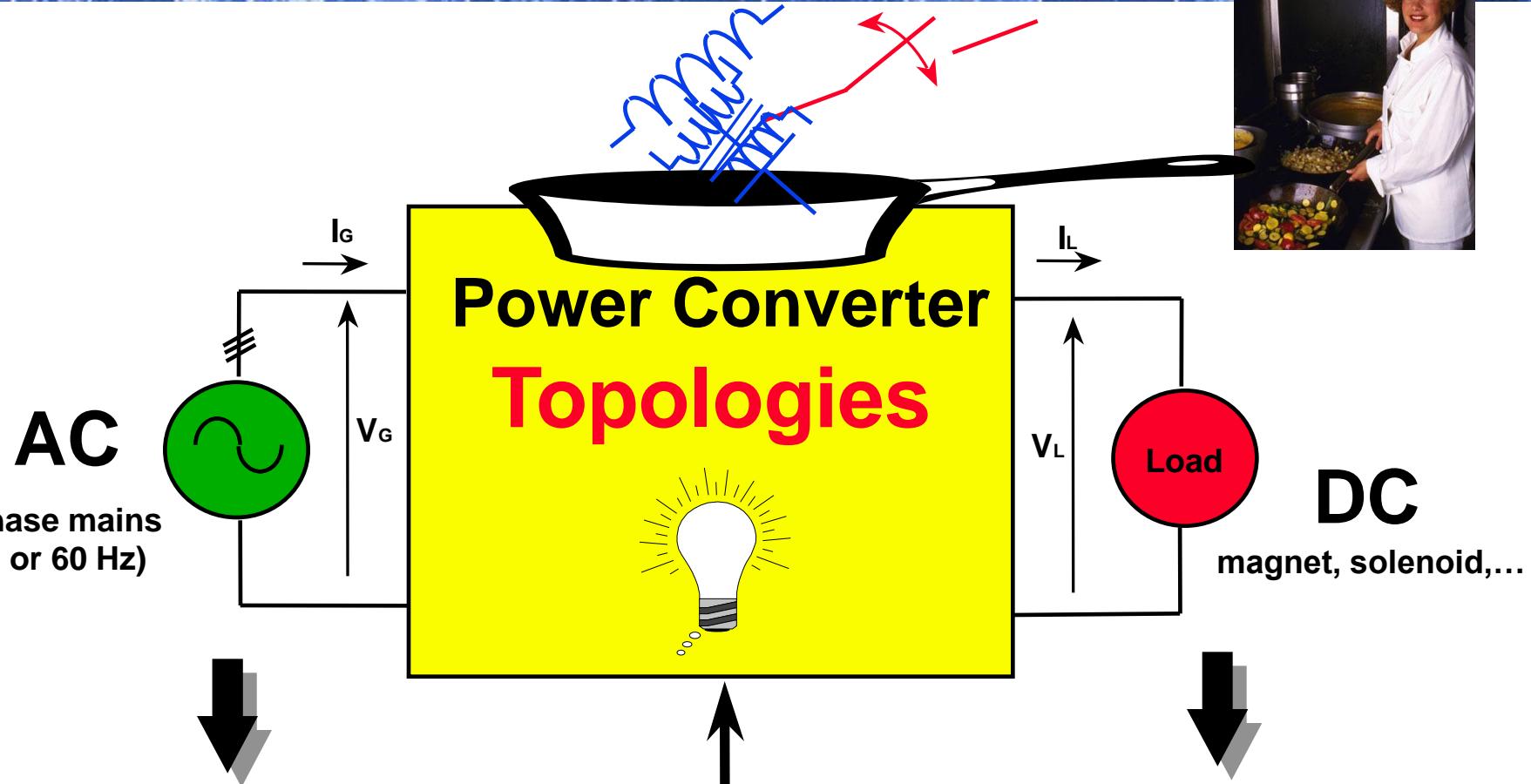


Achieving high performance : **COMPROMISE**





# Operating Modes



1 Quadrant mode

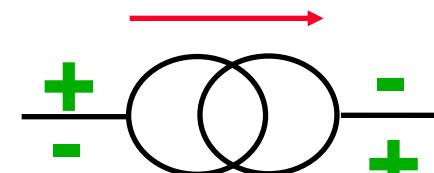


2 Quadrants mode

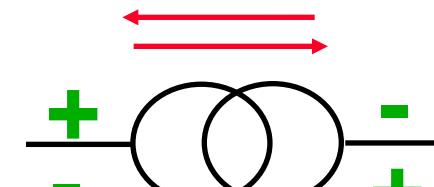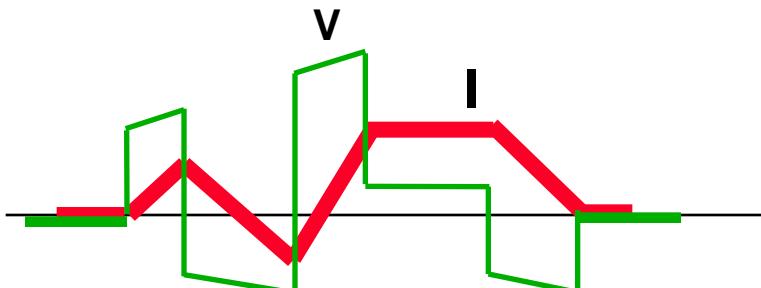


4 Quadrants mode

Output  
Source



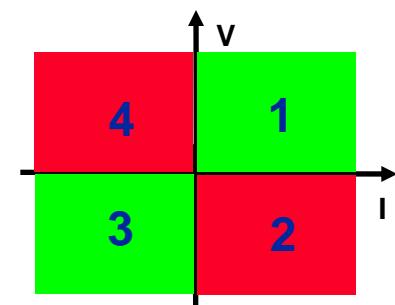


# General power converter topologies



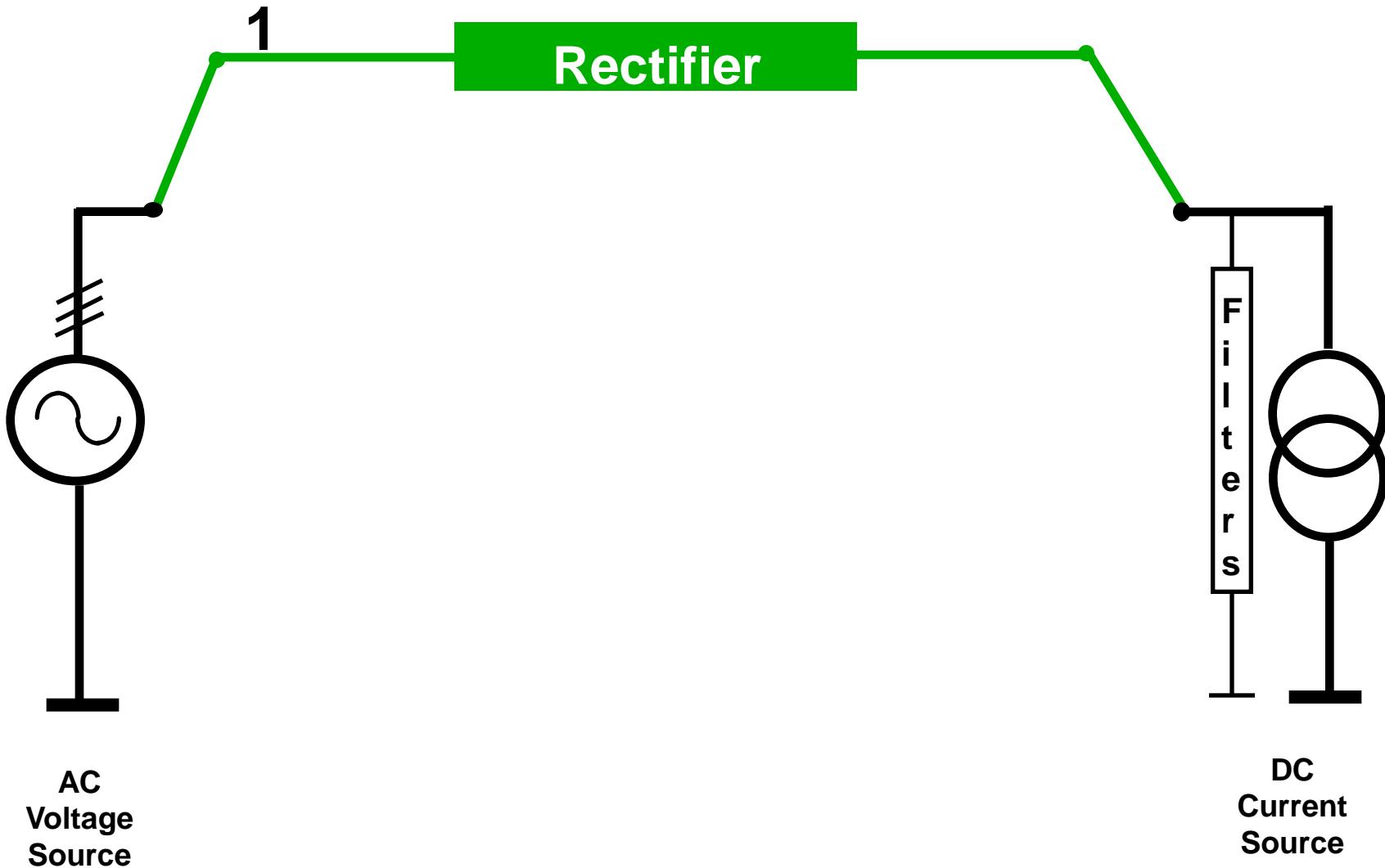


# Direct Converters : Rectifiers

5<sup>th</sup> November 2012

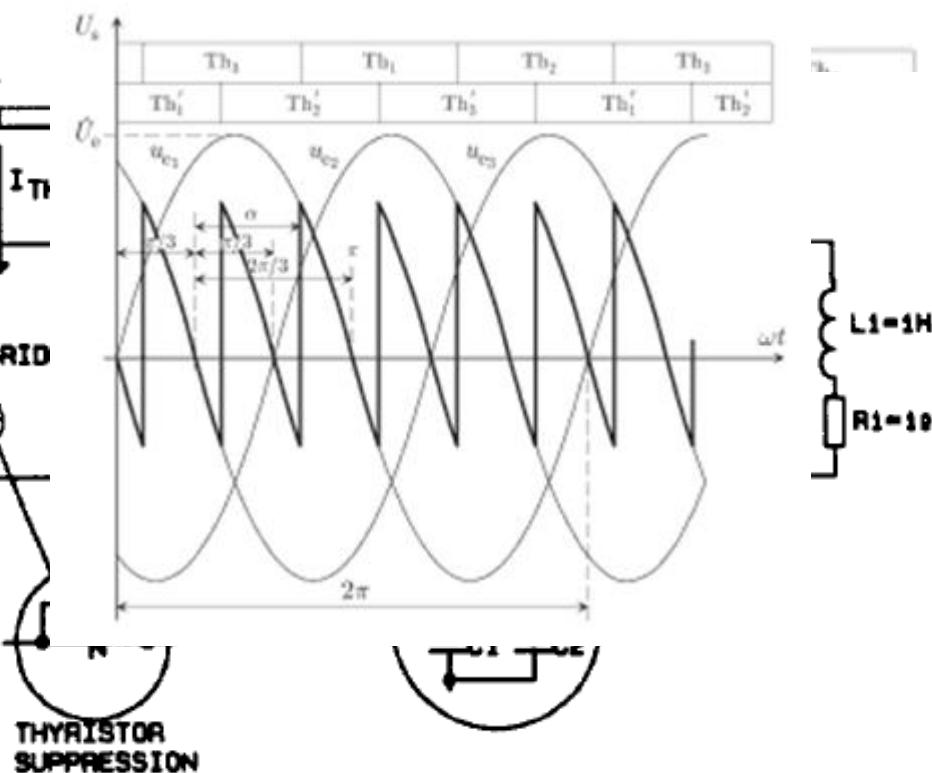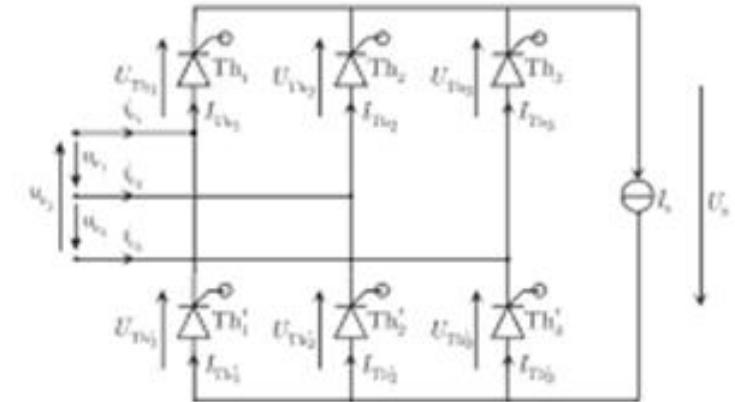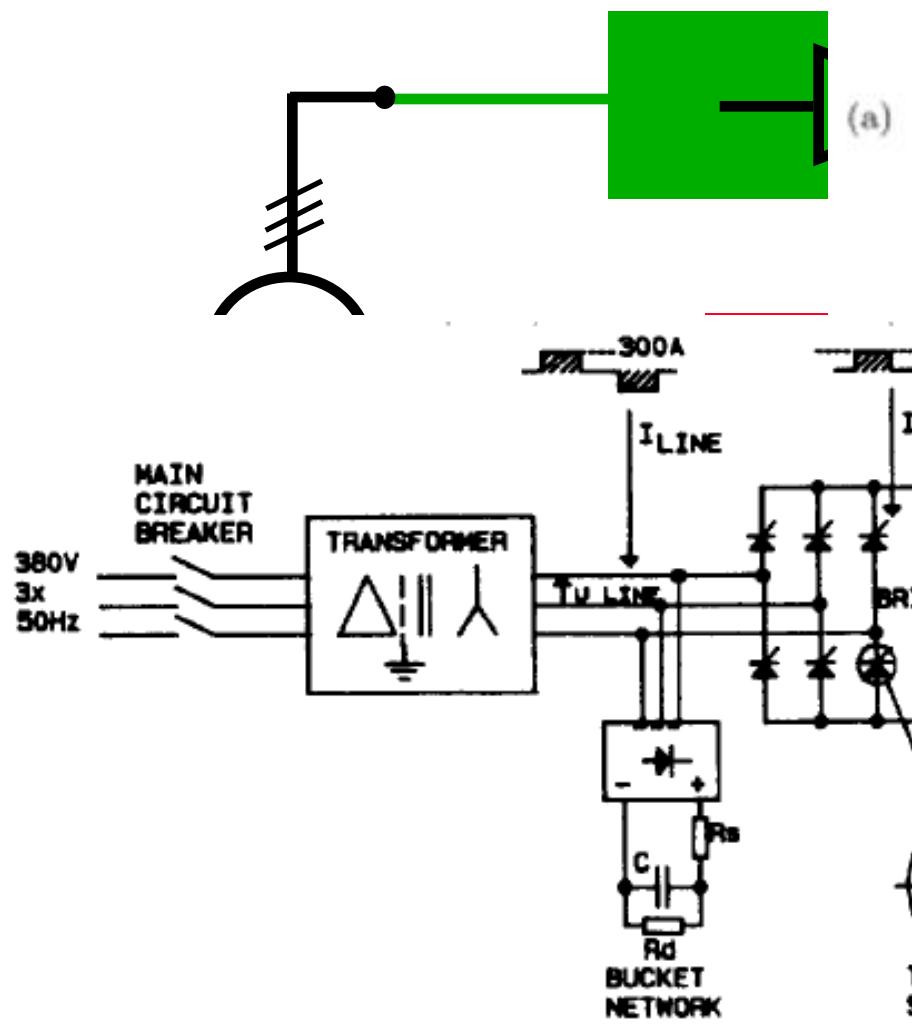


# SPS Main power converters

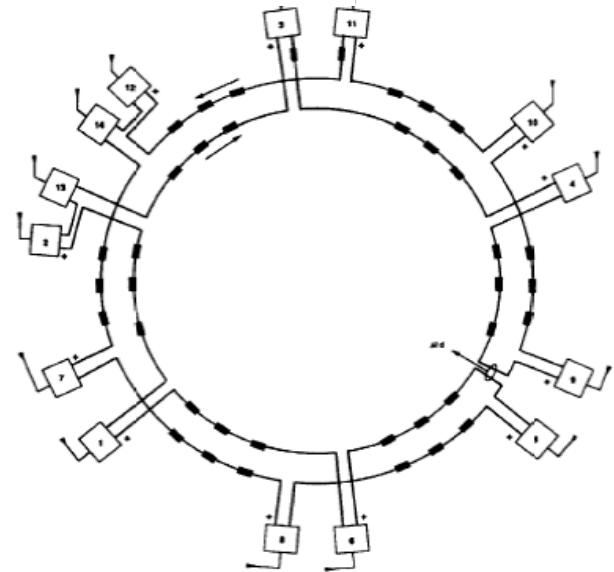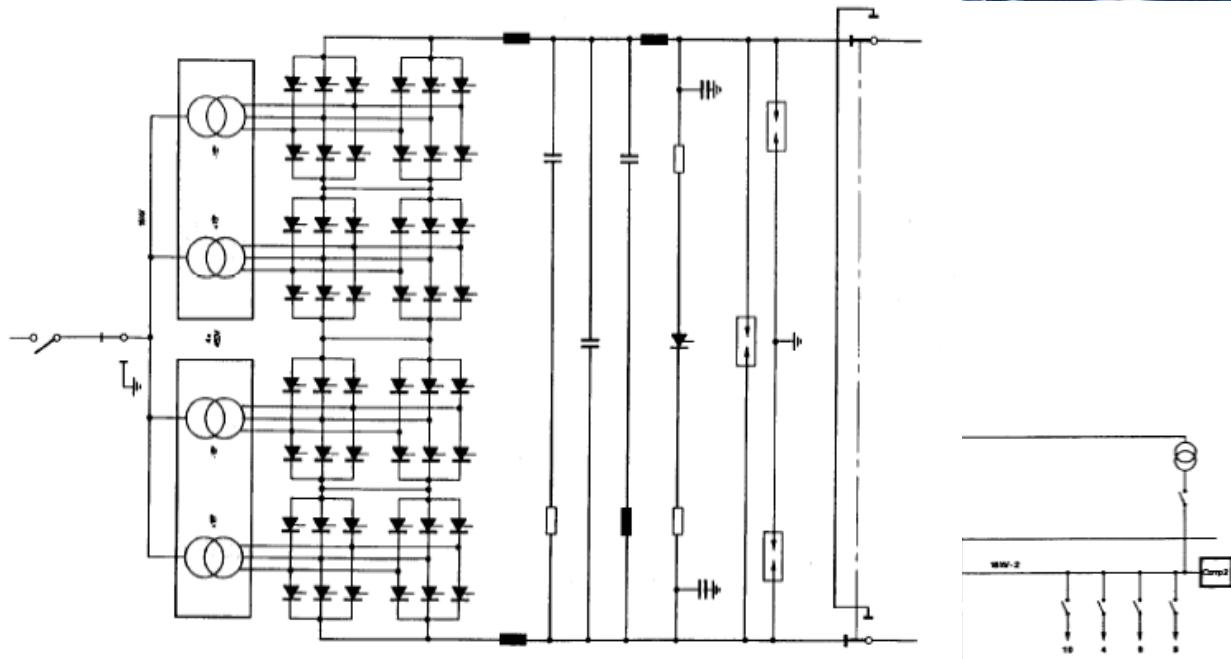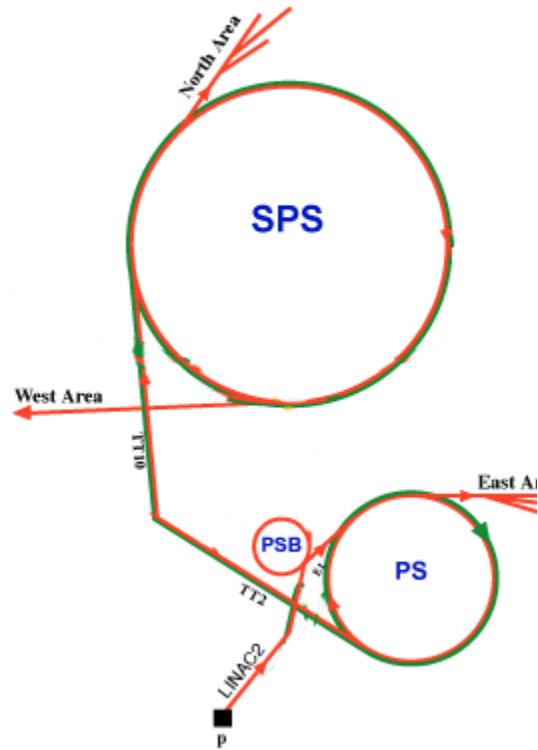


Main power converters  
12 x [6kA, 2 kV]

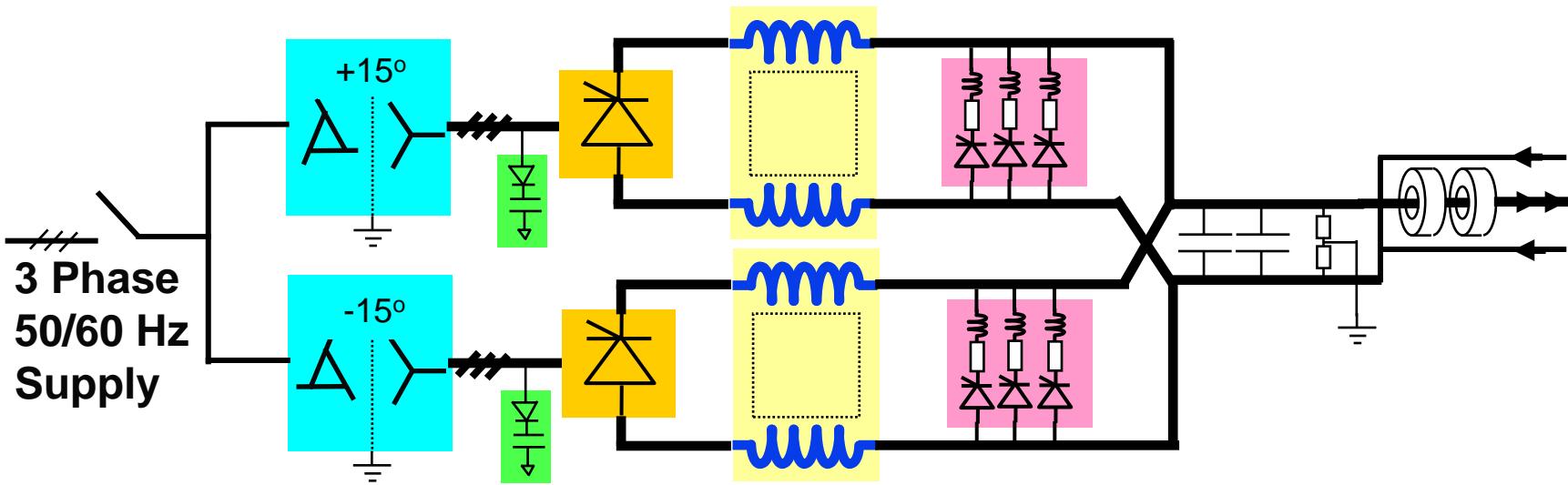
## Two Quadrant Phase Controlled Rectifiers for high current SC magnets



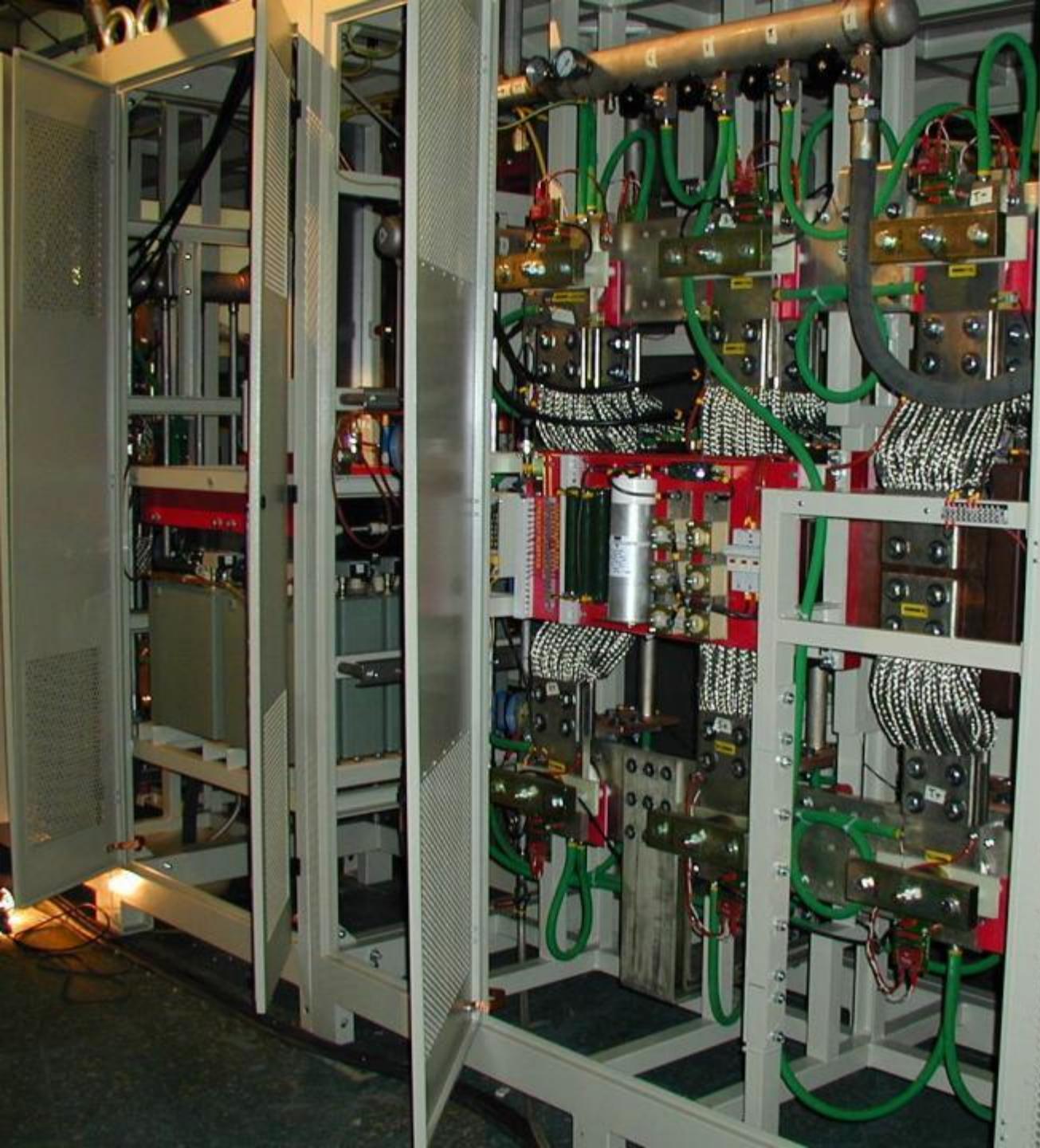**LHC main bending power  
converters  
[13 kA, 190 V]**



# Direct Converters : Rectifiers

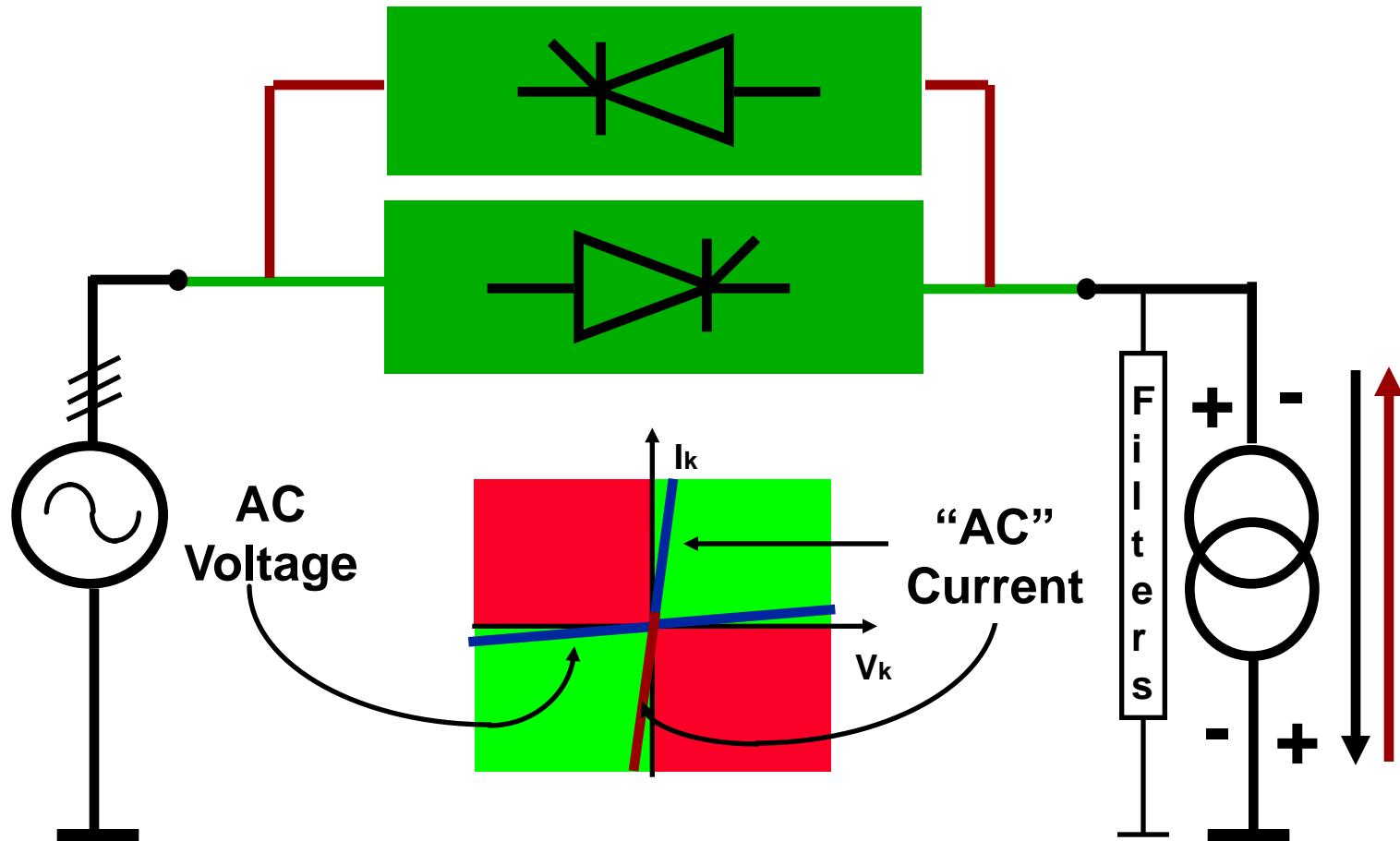

# Direct Converters : Phase Controlled Rectifiers


- ☺ very high power capability
- ☺ moderate prices and competitive market
- ☺ simple structure, well understood (but care needed with high currents)
  
- ☹ three phase transformer operates at low frequency (50 or 60 Hz)
- ☹ variable power factor from 0 to 0.8
- ☹ harmonic content on input current
- ☹ response time is large (ms)
- ☹ current ripple is large (passive or active filters)



**passive (active) filters operating at  
low frequency**


Increase of pulse number (3,6,12,24,48) but  
complexity (cost, control,...)

# General power converter topologies

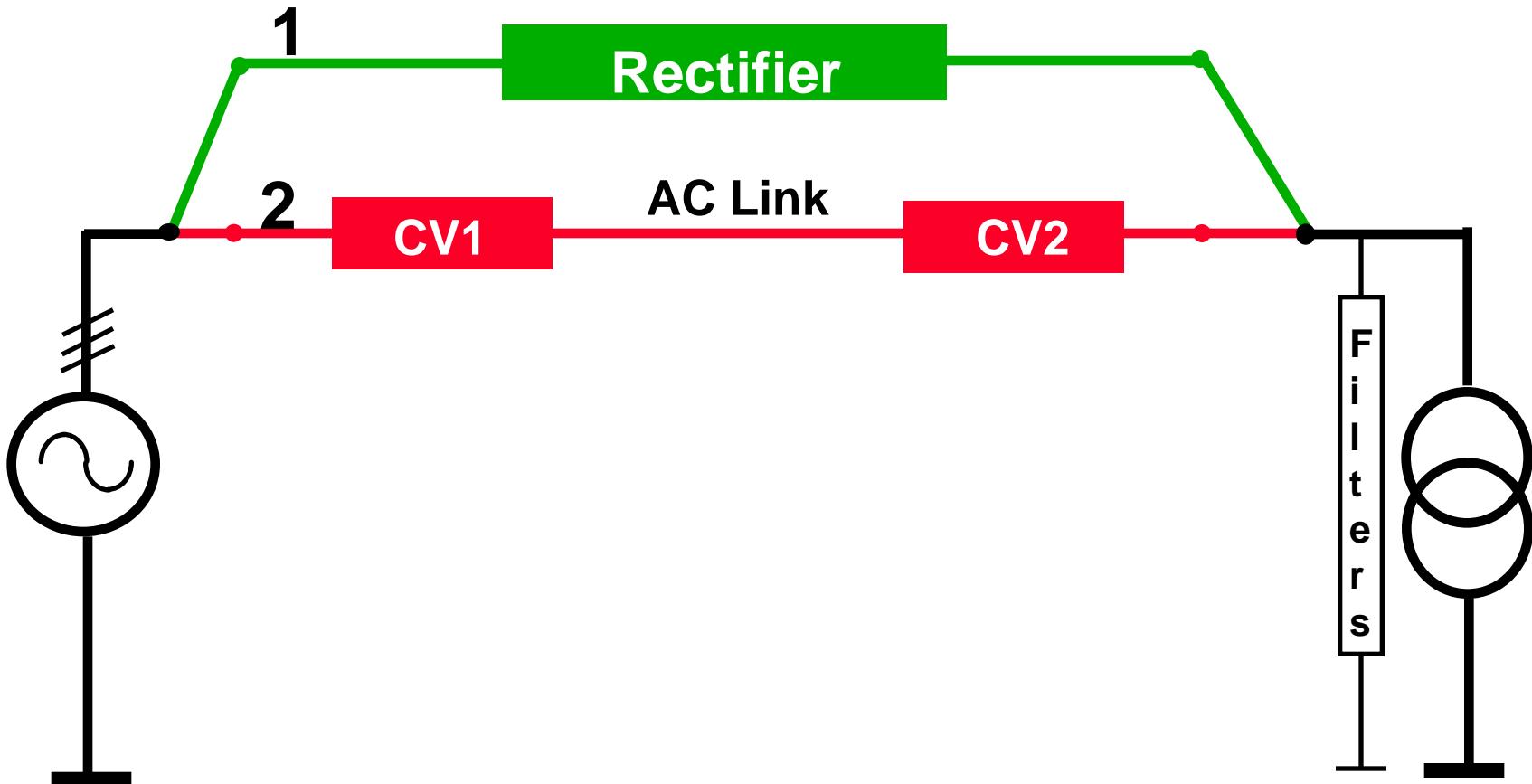


**Application :- very high currents with low voltages  
- (very high voltages with low currents)**
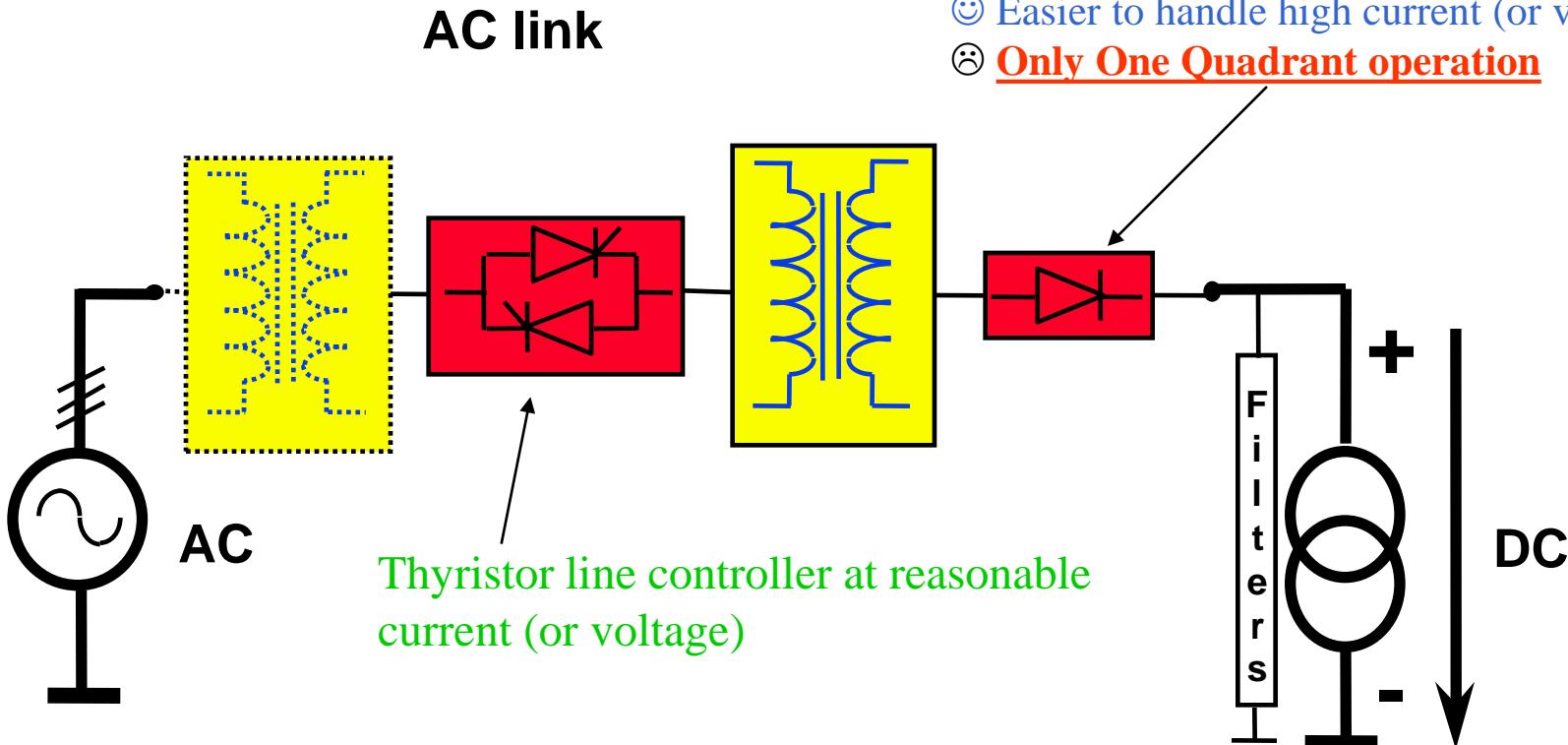
# Direct Converters : AC link (AC line controller)



# [100 kV, 40A] klystron power converter


November 2012

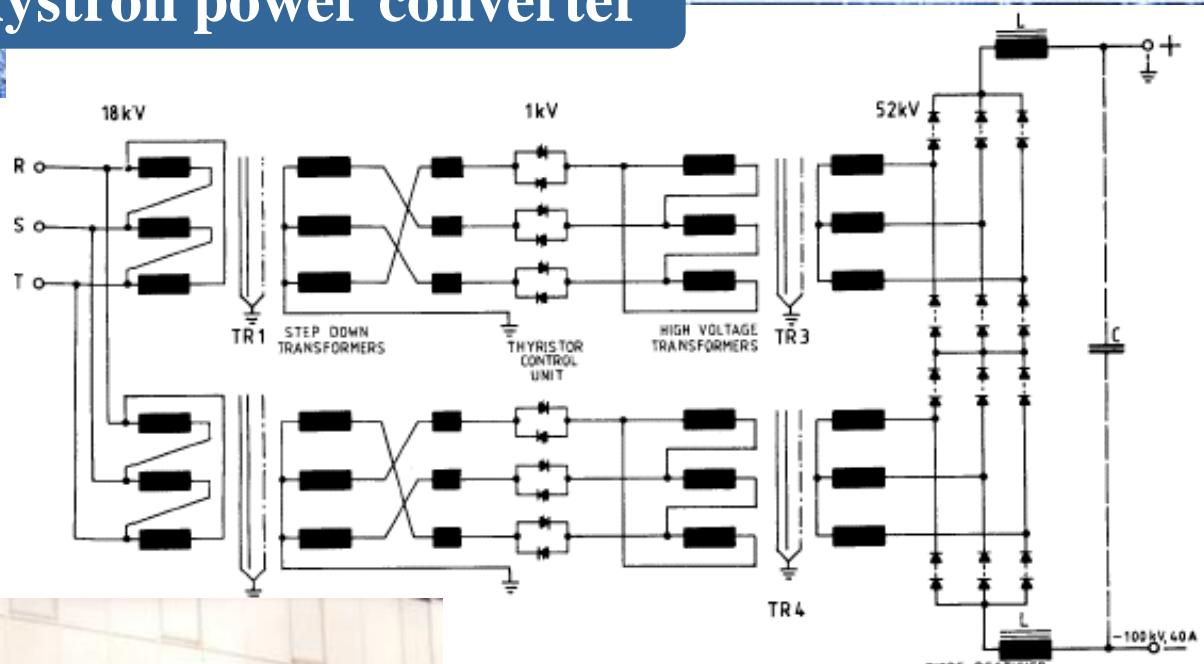


**DC operation**



# General power converter topologies

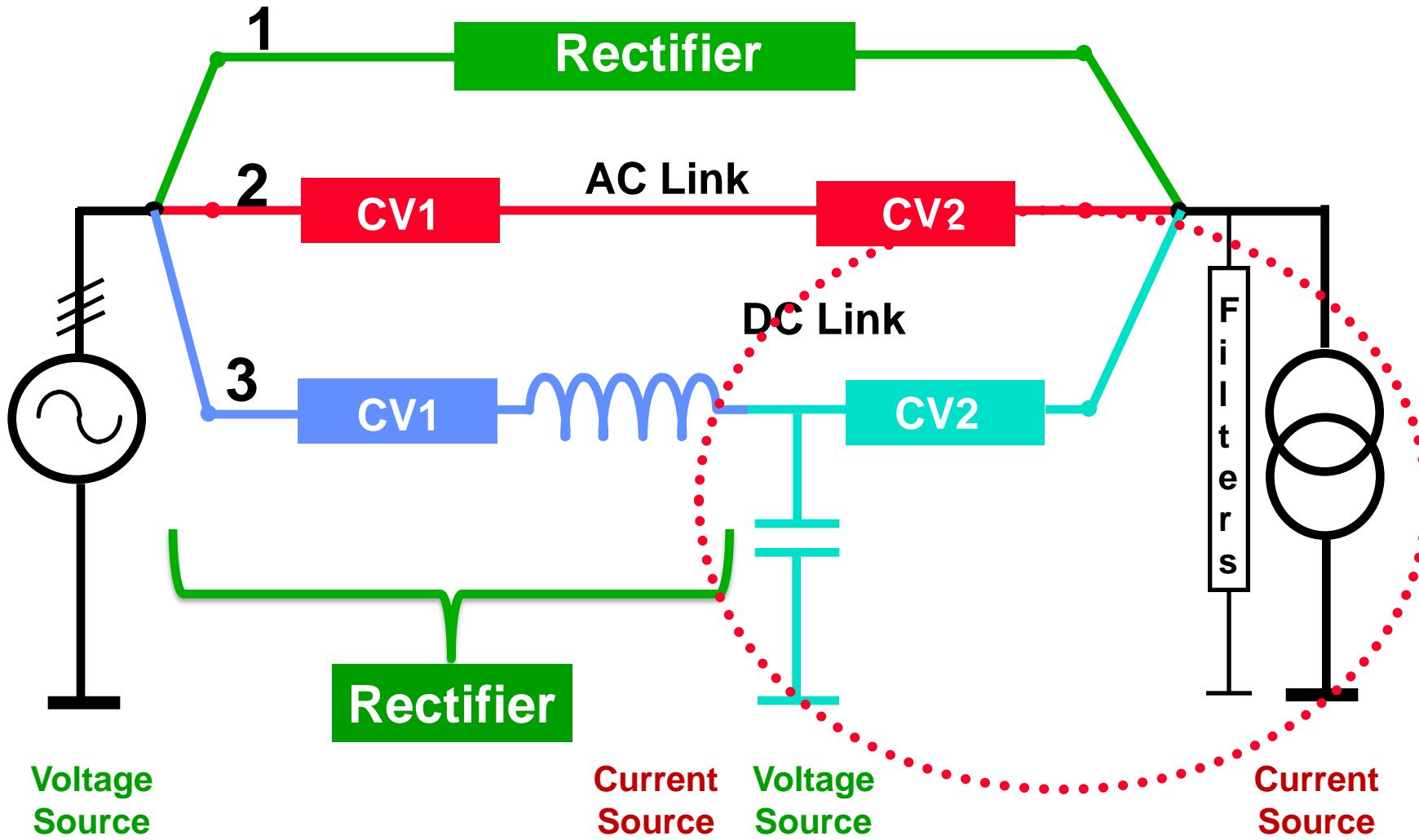

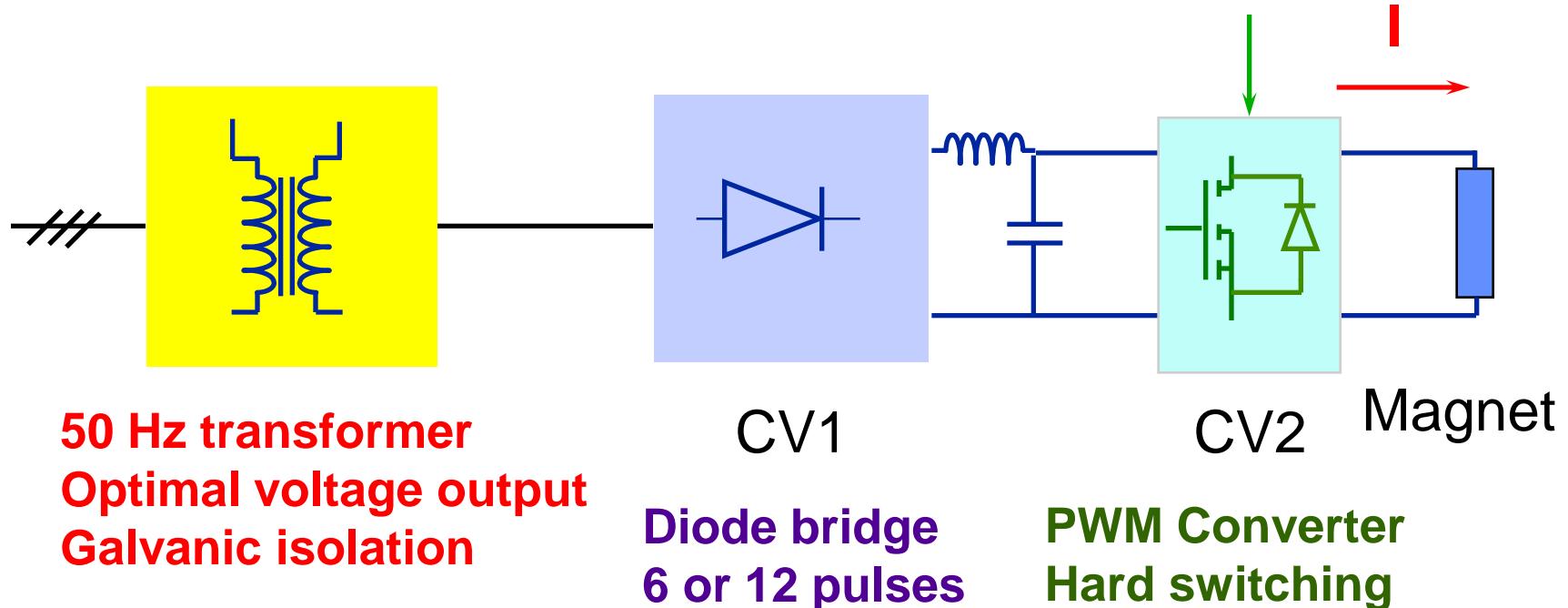
# Galvanic isolation at AC input source (50Hz transformer)



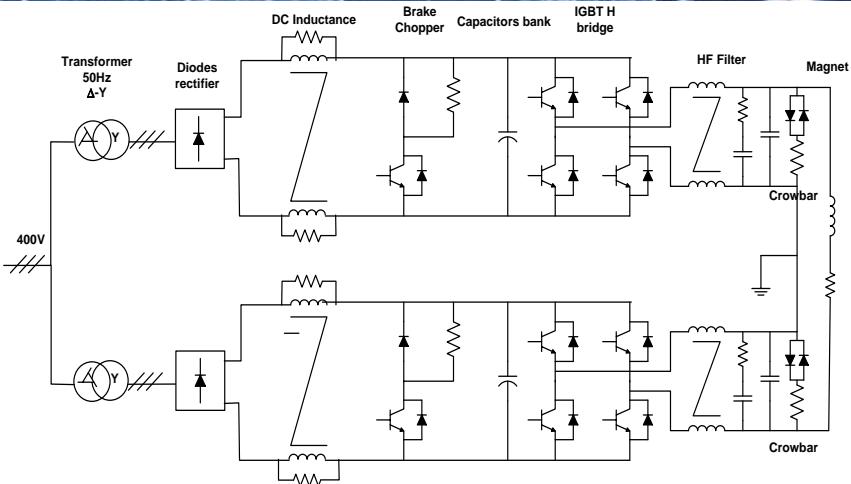
# New PS Auxiliary Power Converters

**Peak Power:** 405 kW  
**Voltage:**  $\pm 900V$   
**Max Current:**  $\pm 450A$



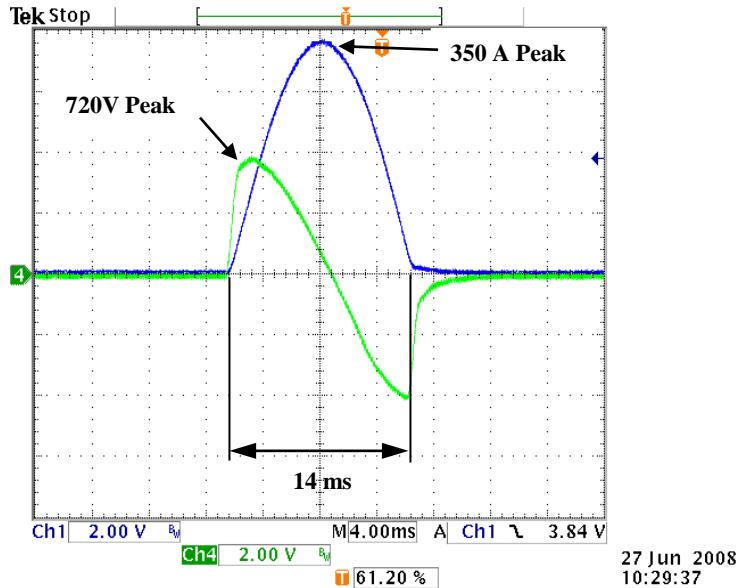Multi-Turn Extraction: Current/Voltage waveforms




Current Loop Bandwidth  $\approx 1\text{kHz}$

# Indirect AC-DC-AC-DC converter


Three cascade power conversion stages:

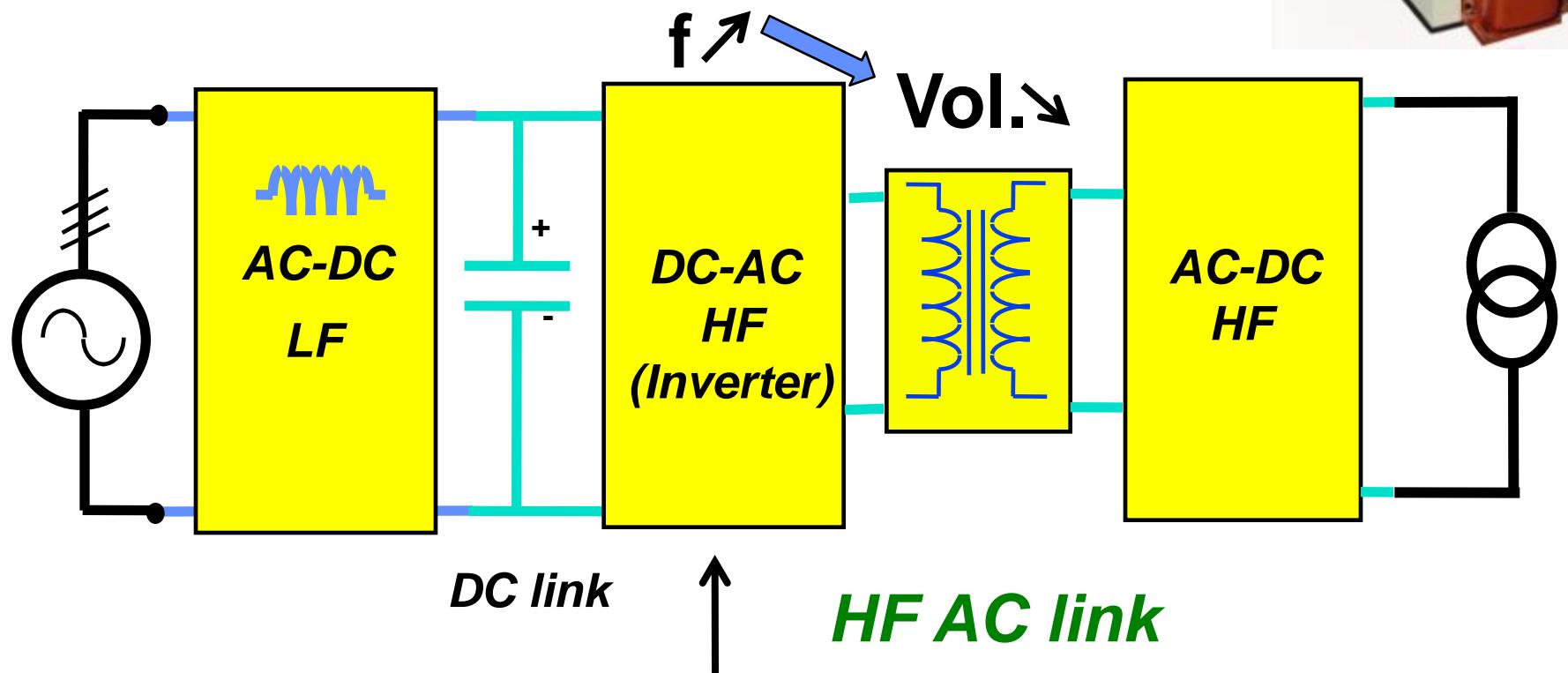- 1) Simple DC source (Diode (thyristor) rectifiers)
- 2) HF DC-AC converter (Inverter)
- 3) HF AC-DC converter (Rectifier) (often diode rectifier)

HF transformer to provide the galvanic isolation



# LHC Switch-Mode Power Converters

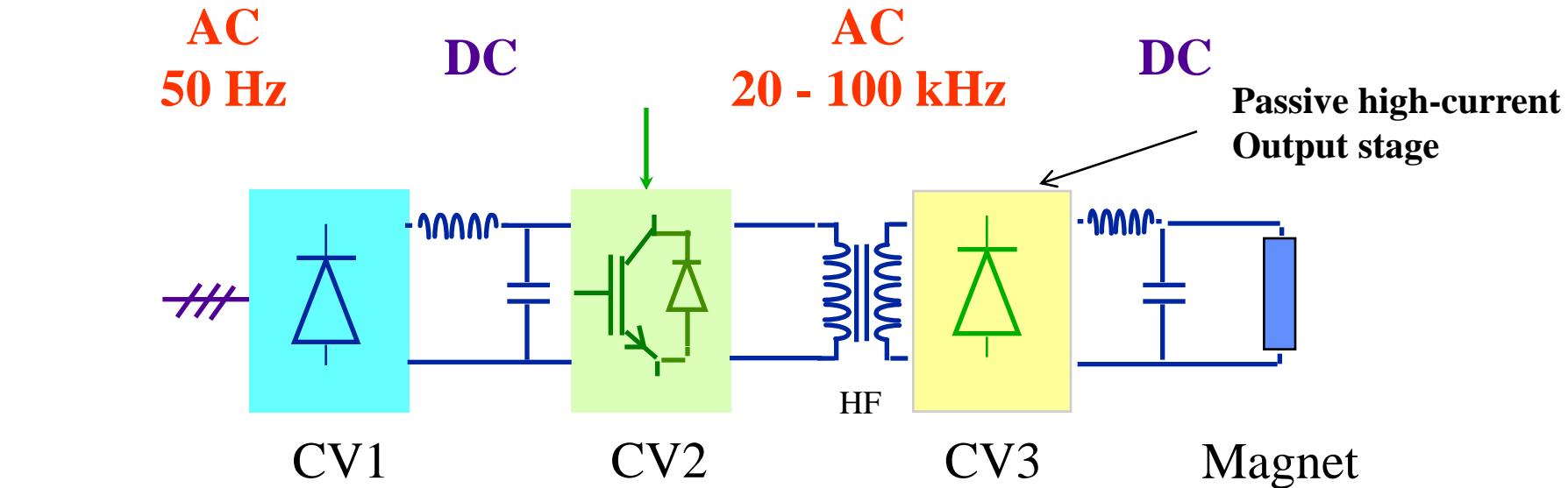

- light weight, reduced volume (HF transformers and filters)
- good power factor (0.95)
- high bandwidth and good response time
- Soft commutation gives low losses and low electrical noise
- small residual current ripple at output
- More complex structure, less well understood, limited number of manufacturers

# LHC:1-quadrant converter: modular approach



## 1-quadrant converters:

- [13kA,18V] : 5\*[3.25kA,18V]
- [8kA,8V] : 5\*[2kA,8V]
- [6kA,8V] : 4\*[2kA,8V]
- [4kA,8V] : 3\*[2kA,8V]




**MTBF and MTTR optimization**



**[2kA, 8V]**

# DC and slow pulsed converters

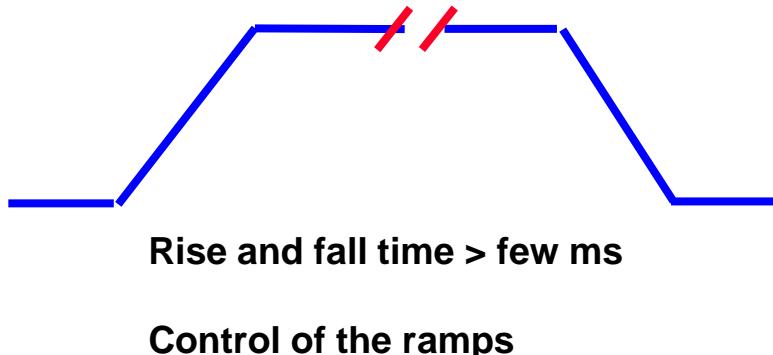

## High and medium power

### Phase Controlled Rectifiers

- Diodes and thyristors rectifiers
- 50Hz transformers and magnetic component (filters)
- 1-quadrant and 2-quadrants (but unipolar in current) : energy back to the mains
- 4-quadrant: back-to-back converters

## Low and Medium power


### Switch-mode power converters

- Mosfets , IGBTs, IGCTs,... turn-off semiconductors
- HF transformers and passive filters
- excellent for 1-quadrant converter
- 4-quadrant converters but with energy dissipation (very complex structure if energy has to be re-injected to mains)

# Pulsed converters

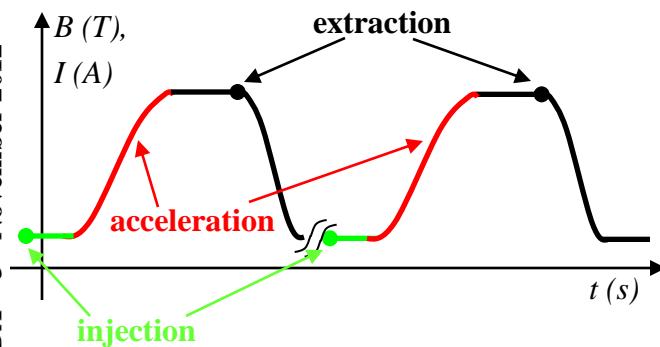
## Synchrotrons

- Beam is injected, accelerated and extracted in several turns;


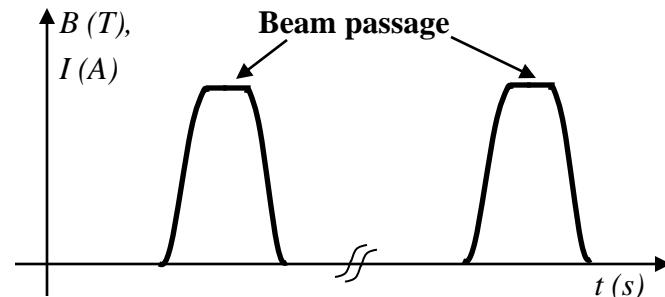
## Linac's and transfer lines

- Beam is passing through in one shot, with a given time period;




Rise and fall time < few ms

Direct Energy transfer  
from mains is not possible:

Intermediate storage of energy


Peak power : could be > MW ( average power kW)
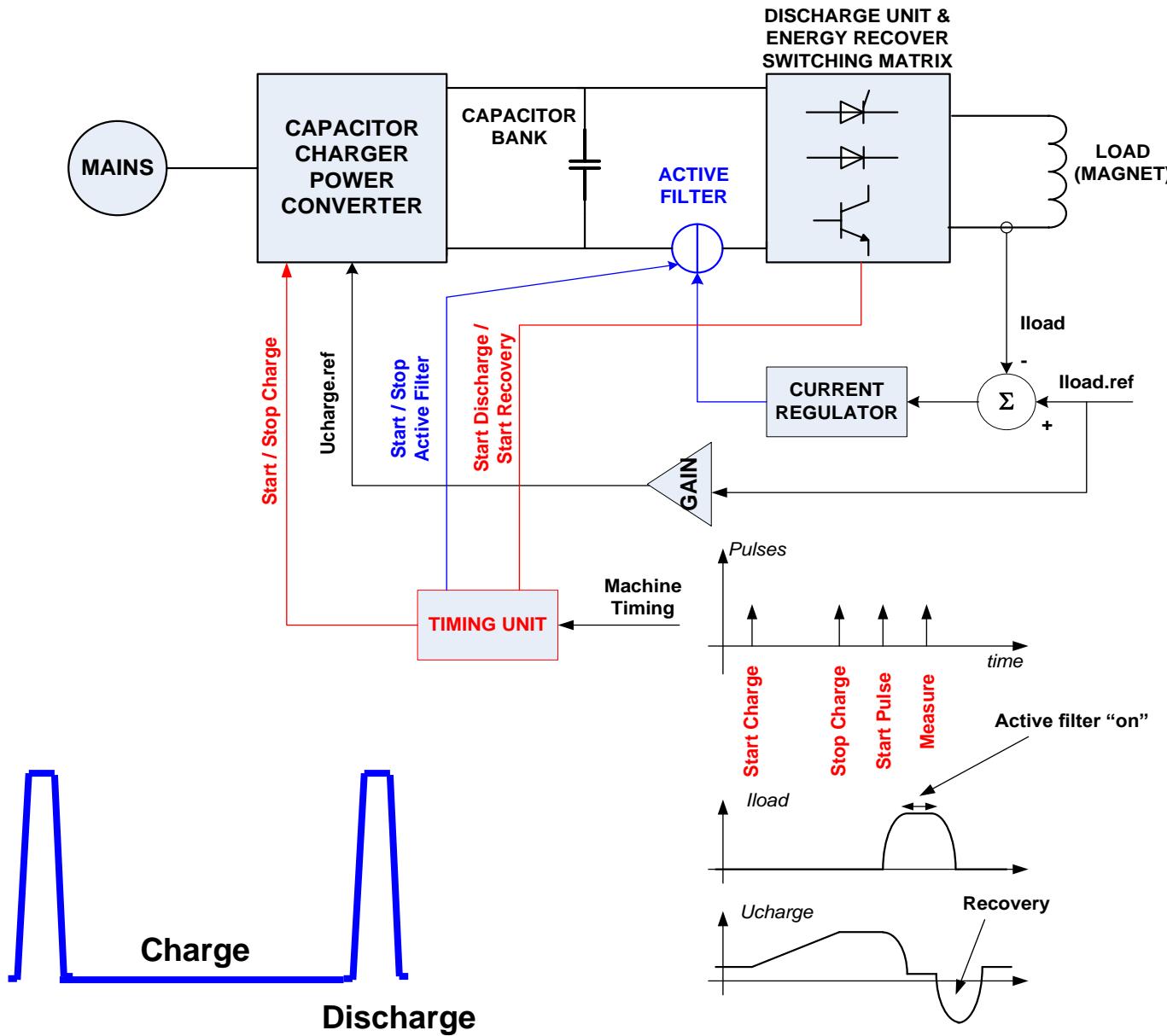
# Block schematic of a fast pulsed converter




# High current, high voltage discharge capacitor power converters
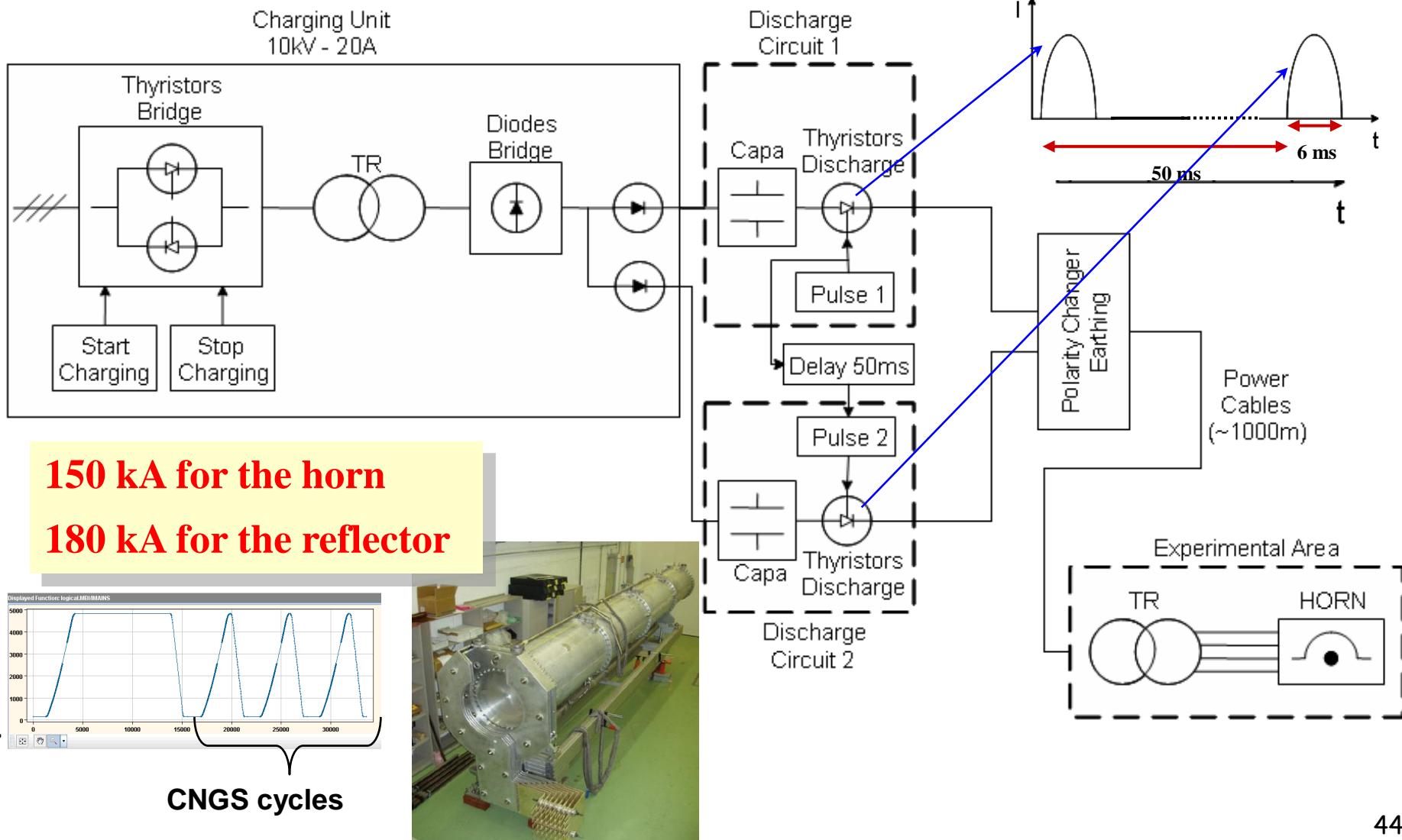
## CNGS horn and reflector power converters




# Pulsed klystron modulators for LINAC 4

Specification	symbol	Value	unit
Output voltage	$V_{kn}$	110	kV
Output current	$I_{out}$	50	A
Pulse length	$t_{rise} + t_{set} + t_{flat} + t_{fall}$	1.8	ms
Flat-Top stability	FTS	<1	5
Repetition rate	$1/T_{rep}$	2	Hz

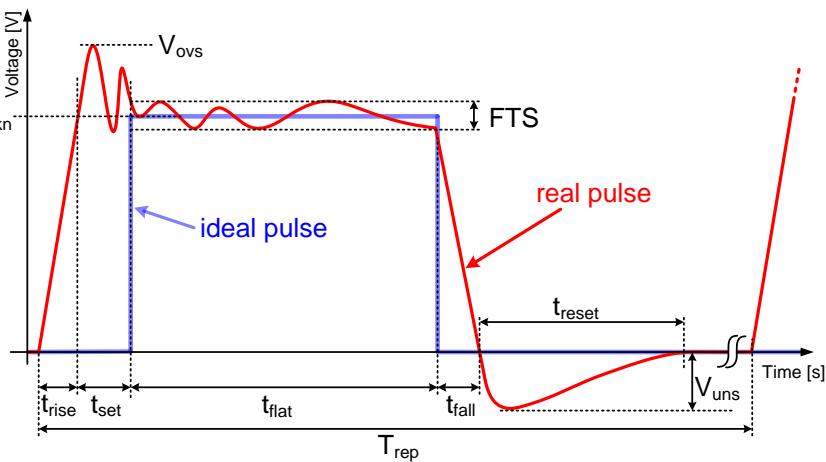


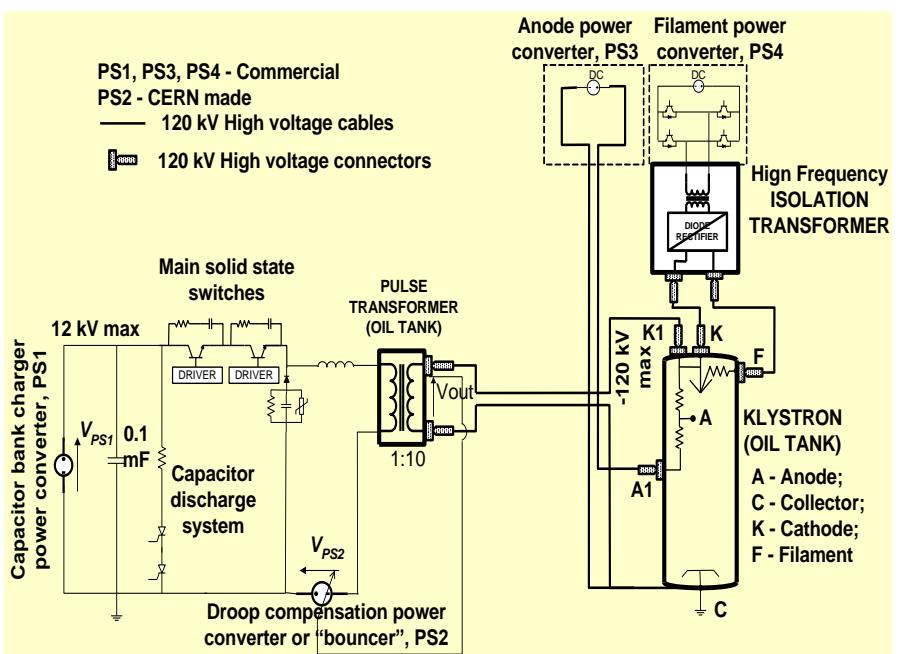**Peak power : 5.5MW**  
**Average power: 20kW**




# Pulsed klystron modulators for LINAC 4


Specification	symbol	Value	unit
Output voltage	$V_{kn}$	110	kV
Output current	$I_{out}$	50	A
Pulse length	$t_{rise} + t_{set} + t_{flat} + t_{fall}$	1.8	ms
Flat-Top stability	FTS	<1	5
Repetition rate	$1/T_{rep}$	2	Hz

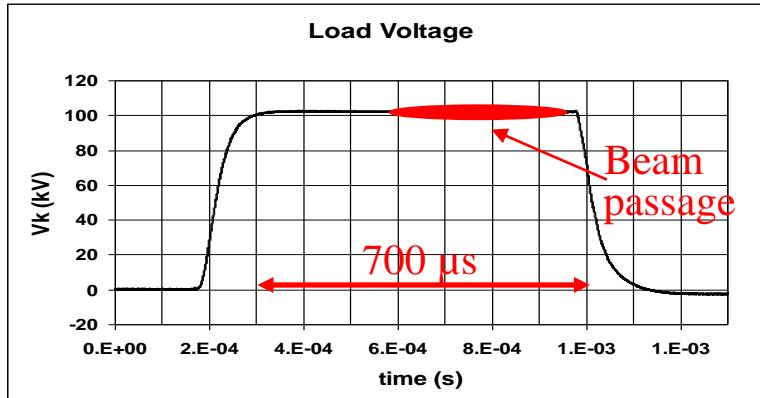

# Power Converter % Load


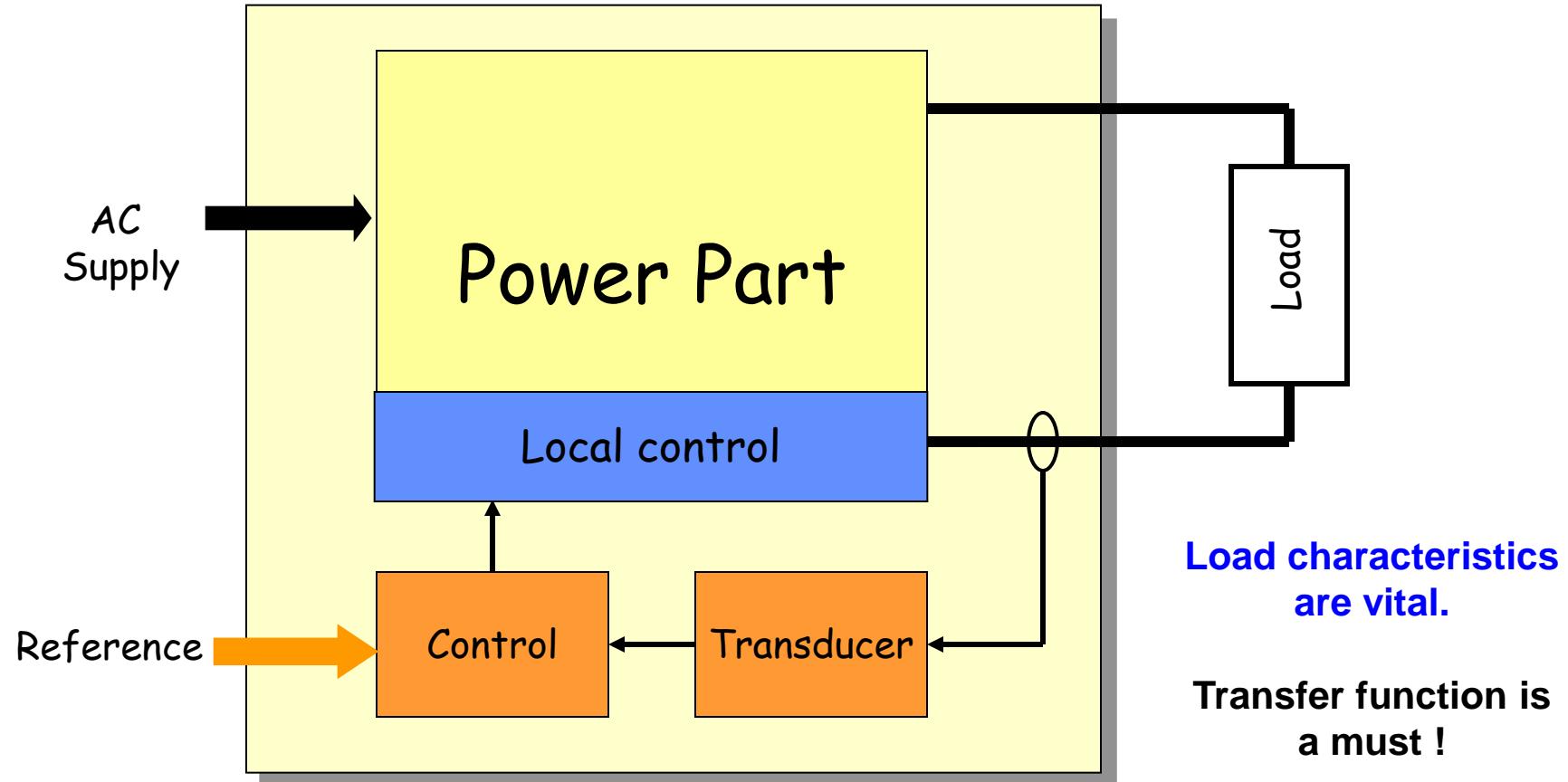


# Example :LHC power converter control

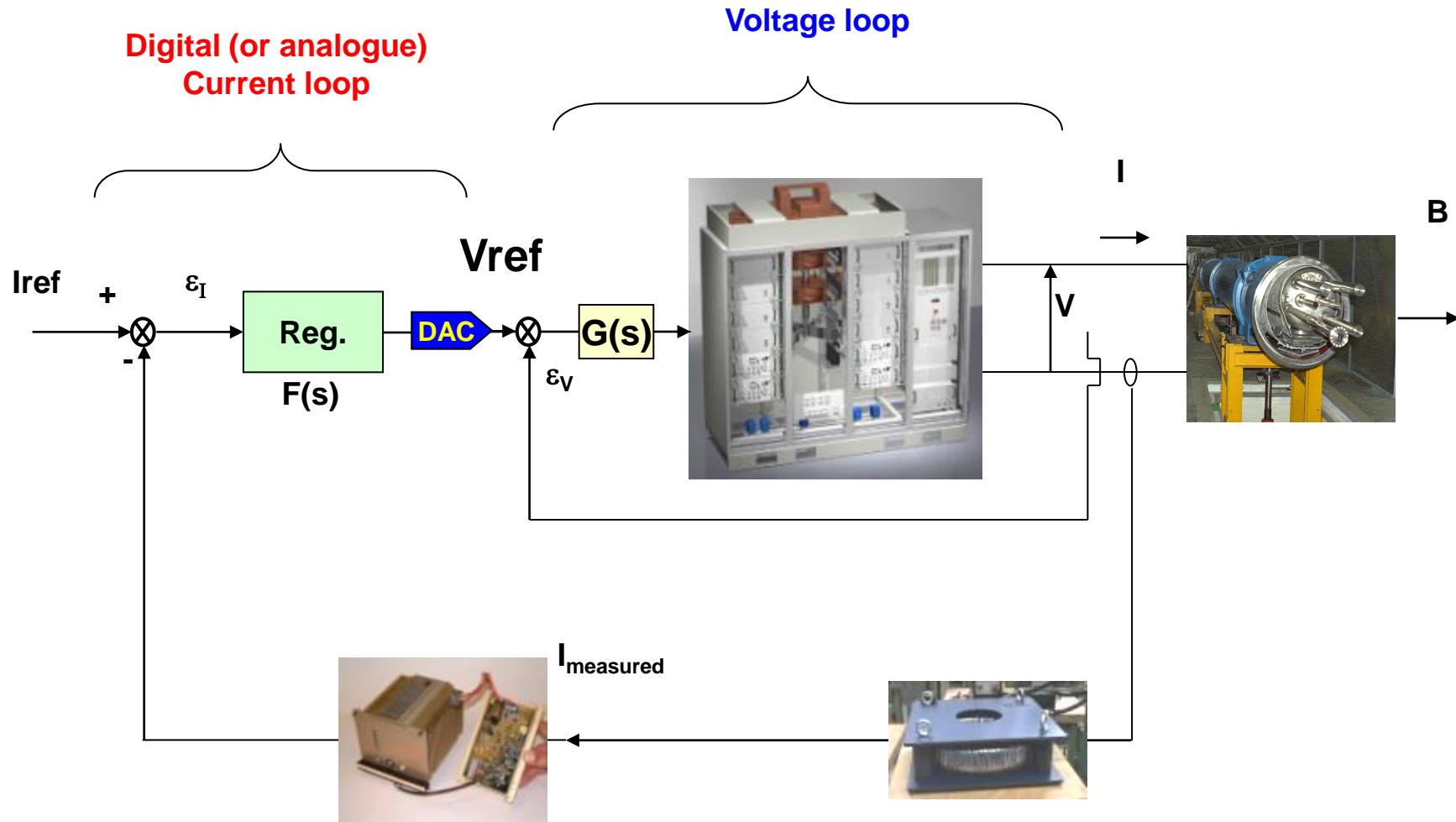

# Power converter :Performance requirements

Overshoot  
Bandwidth

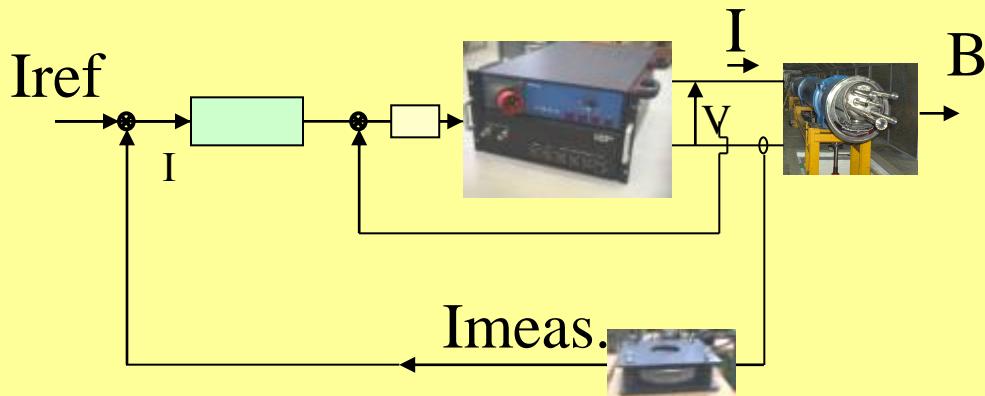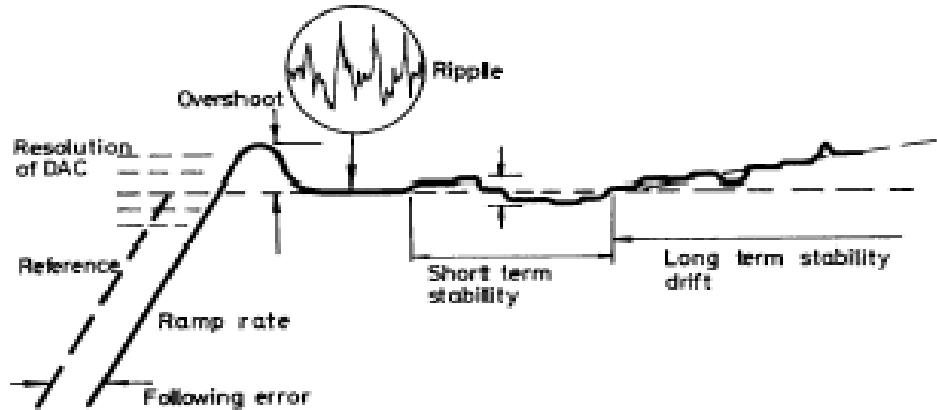

Accuracy   Reproducibility   Stability   Resolution ?




# Glossary

## - Accuracy

Long term setting or measuring uncertainty taking into consideration the full range of permissible changes\* of operating and environmental conditions.

\* requires definition

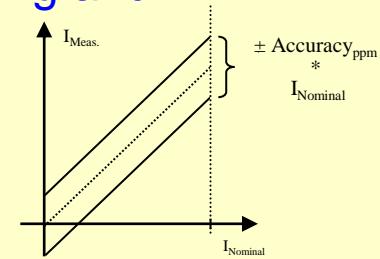


## - Reproducibility

Uncertainty in returning to a set of previous working values from cycle to cycle of the machine.
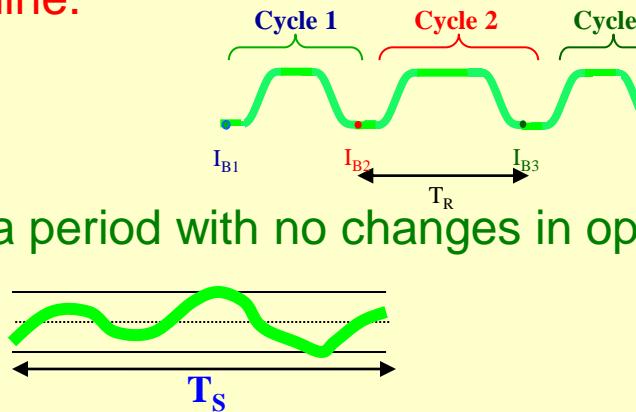
## - Stability

Maximum deviation over a period with no changes in operating conditions.




Accuracy, reproducibility and stability are defined for a given period

Precision is qualitative . Accuracy, reproducibility, stability are quantitative.

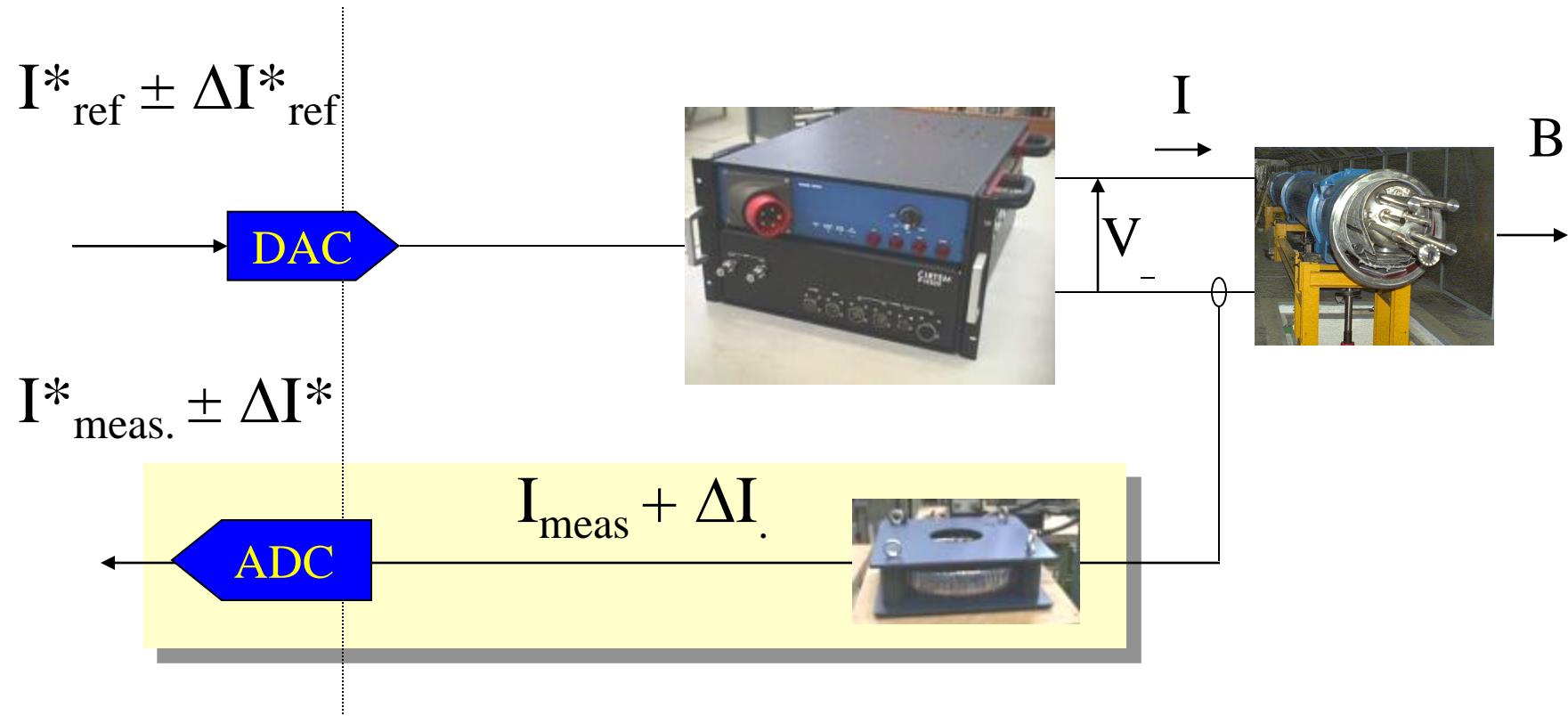
# Resolution

Smallest increment that can be induced or discerned.


The resolution is expressed in ppm of  $I_{\text{Nominal}}$ .  
Resolution is directly linked to A/D system


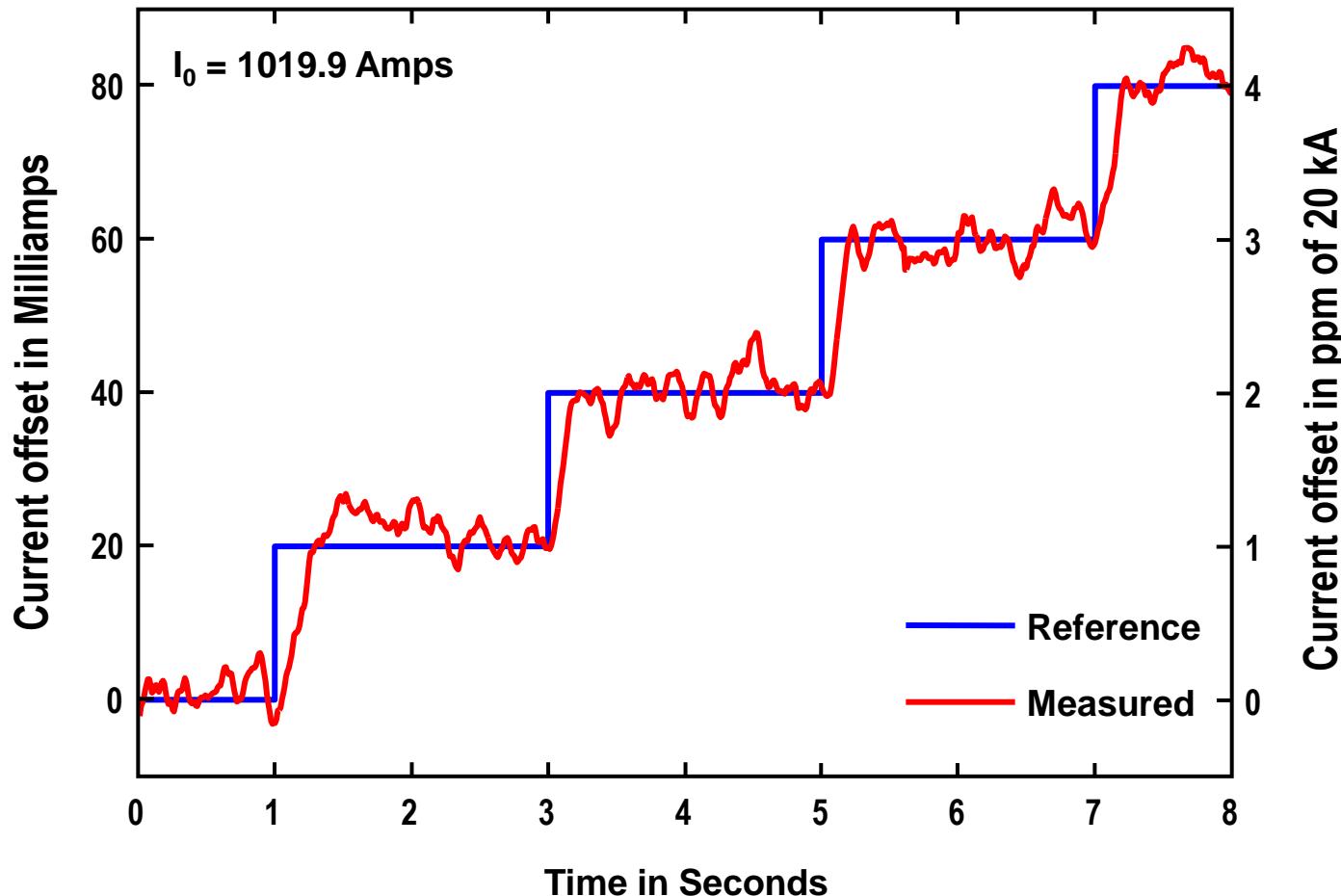
# Results of Resolution Test with the LHC Prototype Digital Controller



# RIPPLE

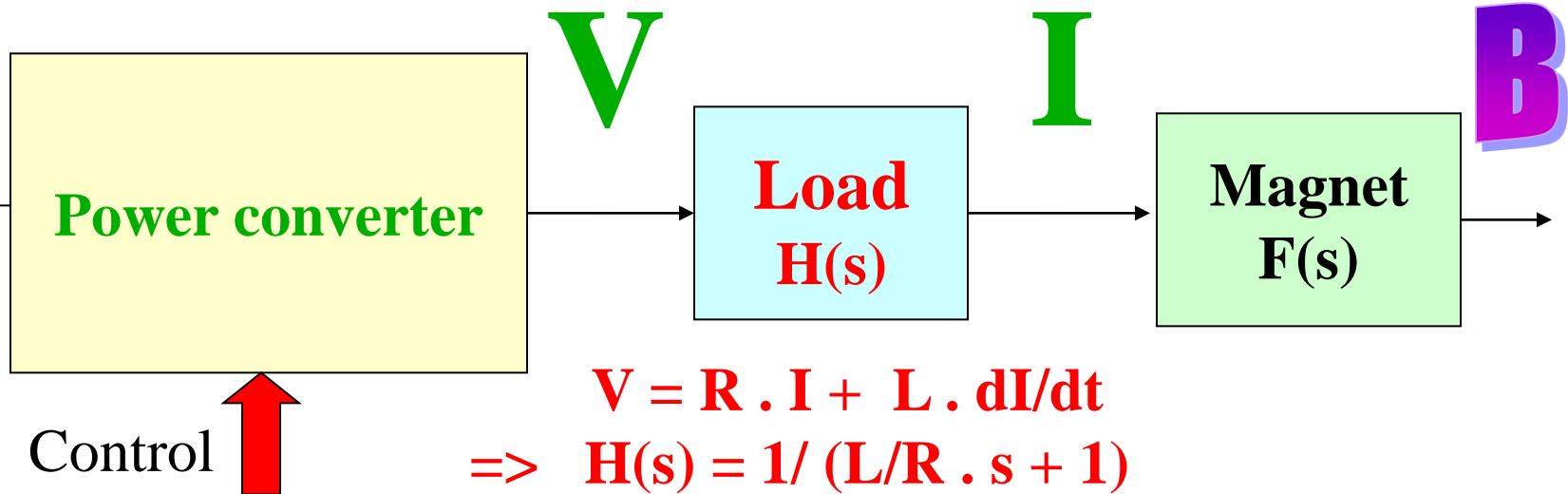

**Voltage ripple is defined by the power converter**

**Current ripple : load transfer function**

**(cables, magnet inductance,...)**

**(good identification is required if the load is a long string of magnets )**

**Field ripple : magnet transfer function (vacuum chamber,...)**

# Power converters specifications

"Do you have one or two power converters for the test of magnet prototypes? 40 A will be enough ?  
Precision is not important for time being.  
Don't worry it's not urgent. Next month is OK "  
(Email received 05.12.08)

Load characteristics : I and V reversibility ( 1 , 2 or 4-quadrants ?) ;  
Transfer function (at least R, L, C) => will define V and then power

Range : Imax (and Imin)

Rise and fall time (dl/dt max; voltage constraint on the load); is the precision an issue during the ramps (beam or no beam) => Pulsed converters with intermediate storage ?  
=> bandwidth (topology and control strategy)

Precision: accuracy, reproducibility, stability - Resolution

Ripple:  $\Delta V(f)$  => passive (or active) filters ; control strategy (SMPC)

Is the volume a constraint ? Is water cooling possible ?

Environment: temperature and humidity; EMI conditions, radiation,...

Hardware design and production take time.....

# Power Converter Design: Typical R&D procedure



**Utility grid specs**  
(Voltage, power quality,...)

**Efficiency, cost, volume,  
EMI,..., specs**

**Specs analysis for  
topology selection**  
(1,2,4 quadrants,  
active/passive  
converter – closed/open  
loop regulation,  
switches technology,  
...)

**Numerical  
verification of  
selected topology**  
(dedicated numerical  
simulations for general  
converter functionality)

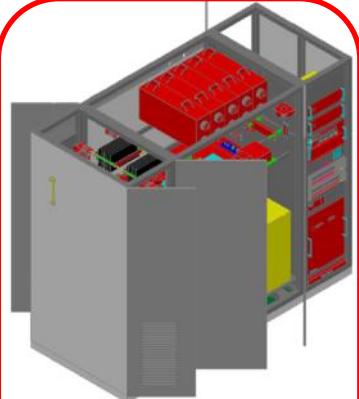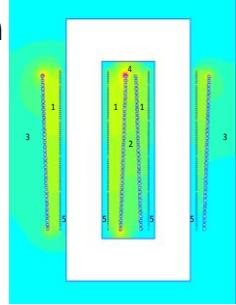
**Components design  
and/or  
specifications**  
(analytical or  
numerical  
approaches)



**3D Mechanical  
integration &  
construction**



**Laboratory tests**

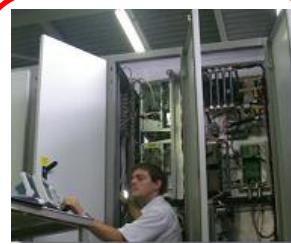

**On site  
commissioning**

**Load specs**  
(L, R, C values,  
precision, ...)

**Load examples:**

- Magnet (high current)
- Klystron (High Voltage)
- Particles source (HV)
- RF equipment (HV)



# The end


**CAS - CERN Accelerator School :  
Power converters for particle accelerators**  
26 - 30 Mar 1990, Switzerland

**CAS - CERN Accelerator School :  
Specialised CAS Course on  
Power Converters for particle accelerators**  
12 - 18 May 2004 - Warrington, UK

**2014: Next Specialised CAS Course on  
Power Converters for particle accelerators**

CERN Accelerator School &  
the University of Granada  
will organise a course on  
**Introduction to  
Accelerator Physics**  
28 October - 9 November 2012  
Granada, Spain

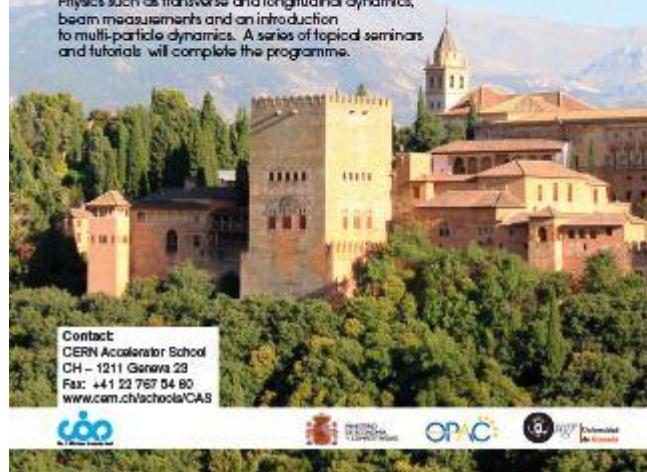This basic introductory course will be of interest to young staff from laboratories, universities and companies manufacturing accelerator equipment. The course will focus on the basics of Accelerator Physics such as transverse and longitudinal dynamics, beam measurements and an introduction to multi-particle dynamics. A series of topical seminars and tutorials will complete the programme.



Contact:  
CERN Accelerator School  
CH - 1211 Geneva 23  
Fax: +41 22 767 84 80  
[www.cern.ch/schools/CAS](http://www.cern.ch/schools/CAS)







# Reserved slides

# Energy conversion : transfer of energy between two sources

## Introductive example

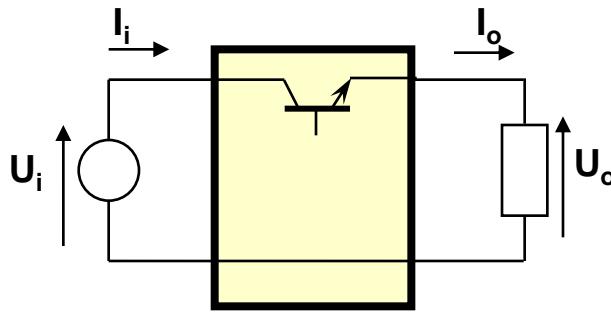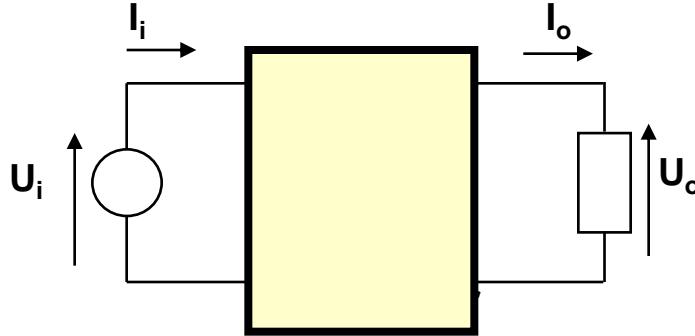

Linear solution


## Transfer of energy between

- DC voltage source  $U_i$
- DC source (nature is not defined) :  $U_o$ ,  $I_o$
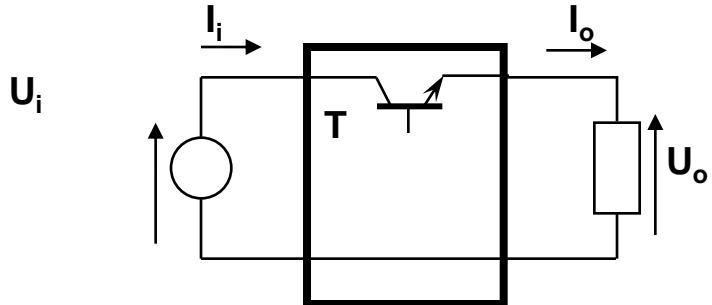
# Linear solution

$$U_i = 24V ; U_o = 10 V \text{ and } I_o = 600A$$

$$P_o = U_o \cdot I_o = 10 \cdot 600 = 6'000 W$$



$$P_T (\text{power dissipated by the switch}) = U_T \cdot I_T = (U_i - U_o) \cdot I_o = (24 - 10) \cdot 600 = 8'400 W$$

$$\text{Converter efficiency} = P_o / (P_T + P_o) = 42 \% !!!!!$$


Furthermore, it'll be difficult to find a component (semiconductor) able to dissipate 8'400 W .

**Then impossible for medium and high power conversion**

## Commutation

$$\left. \begin{array}{l} - U_T \approx 0 \text{ if } I_T \neq 0 \\ - I_T = 0 \text{ if } U_T \neq 0 \end{array} \right\} P_T \approx 0 \text{ (if power switches are ideal)}$$

~~Linear mode~~

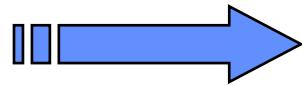

**switch mode**  
(power switches either saturated or blocked)



# Power Converter topology synthesis: the problem

the interconnection of sources by switches

Fundamental rules  
and  
source natures

Power converter topologies

switch characteristics

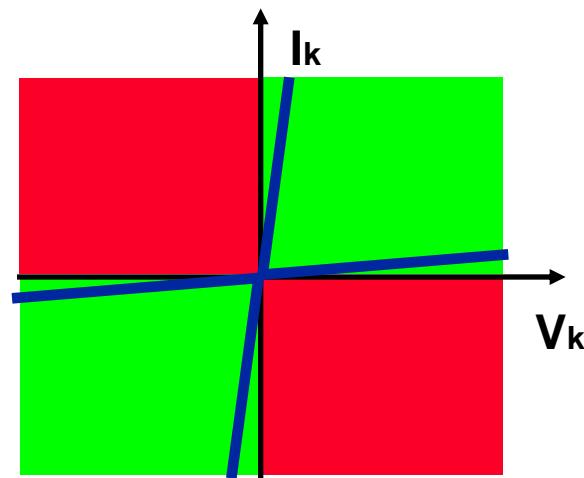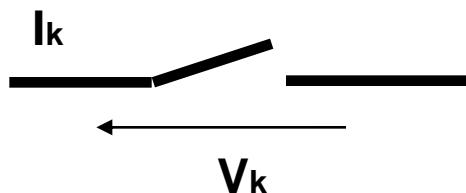


# Switch characteristics

**Switch : semiconductor device functioning in commutation**

*The losses in the switch have to be minimized*


*Zon very low*

*Zoff very high*

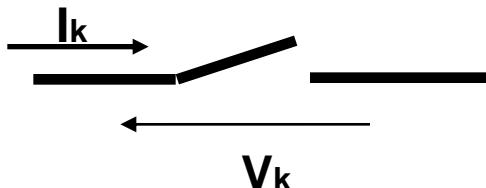

**Switch : at least two orthogonal segments**

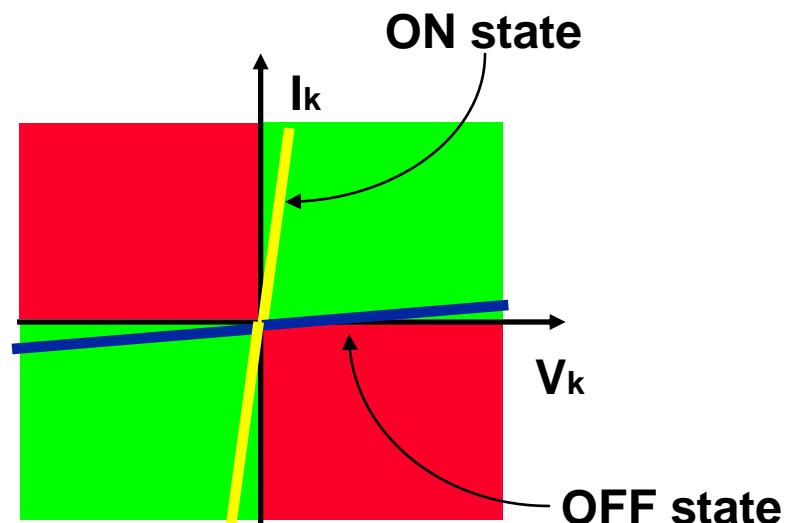**(short and open circuit are not switches)**



# Classification of switches

- According to the degree of controllability:
- Diodes: On and Off states controlled by the power circuit (uncontrolled).
- Thyristors: Turned On by a control signal but turned off by the power circuit (semi-controlled).
- Transistors: Controllable switches. Can be turned On and Off by a control signal.
- For analysis purposes power switches are usually considered ideal: Instantaneous, lossless, and infinite current and voltage handling capability.

# Diodes


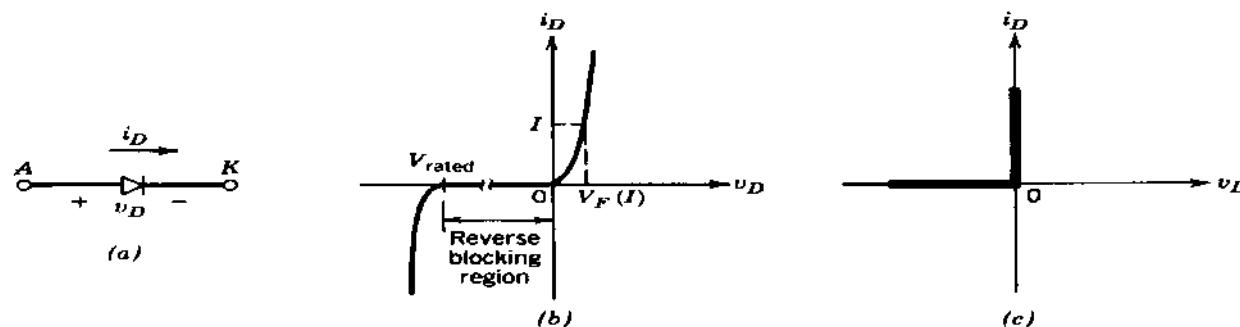


Figure 2-1 Diode: (a) symbol, (b)  $i$ - $v$  characteristic, (c) idealized characteristic.

- 2 terminals device.
- An **ideal diode** turns On when forward biased and Off when its forward current goes to zero.



## press-pack case (high power)

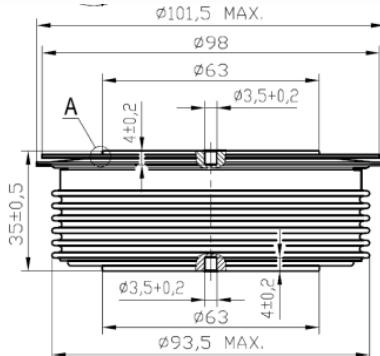

Ex: 6 kV<sub>pk</sub>, 3 kA<sub>av</sub>

## modules case (medium power)

**SEMIKRON**  
innovation + service

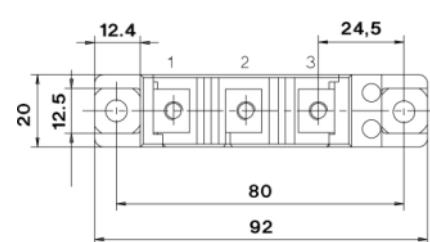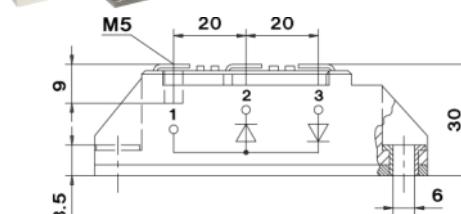

Ex: 1.8 kV<sub>pk</sub>, 80 A<sub>av</sub>

## Other cases (low power)

**IXYS**

**SOT-227**  
**Minibloc**  
case

Ex: 1000V<sub>pk</sub>, 2x30A<sub>av</sub>



**DO-203 Stud case**

Ex: 800V<sub>pk</sub>, 110A<sub>av</sub>



**TO-220 case**

Ex: 600V<sub>pk</sub>, 30A<sub>av</sub>




# **Thyristor (Silicon Controlled Rectifier - SCR)**

## 3 terminals device.

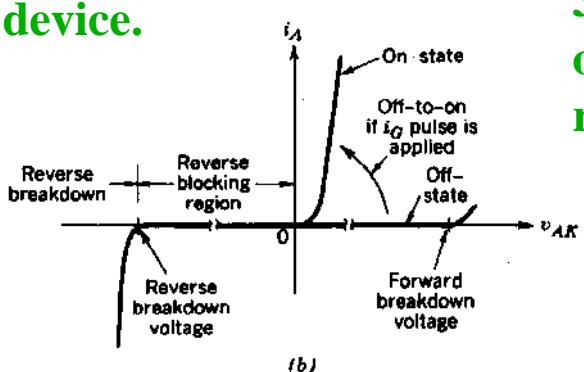
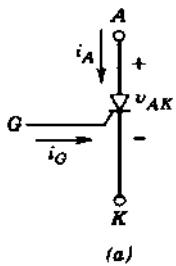


**3 main operating regions.**

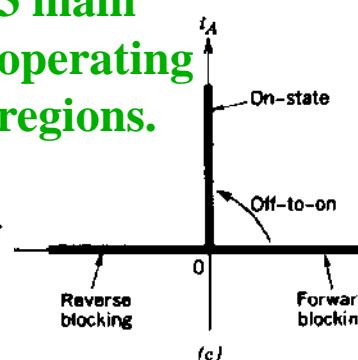


- Latches On by a gate current pulse when forward biased and turns Off as a diode.
  - Requires low power gate drives and is very rugged.

## press-pack case *(high power)*

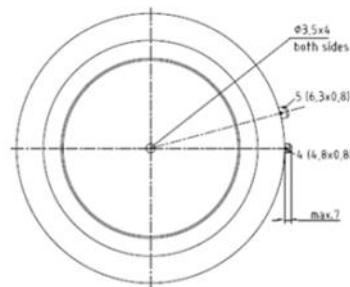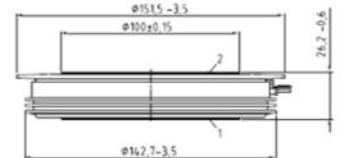

Ex: 4.8kV<sub>pk</sub>, 3.2 kA<sub>av</sub>

## modules case (medium power)

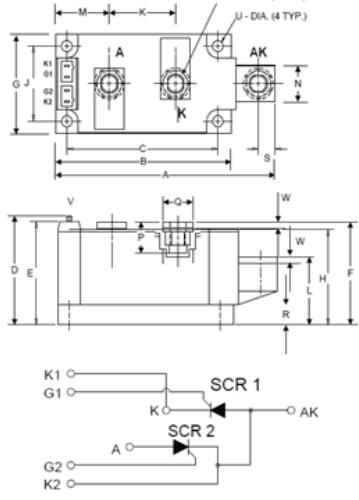

**Ex:** 1.8 kV<sub>pk</sub>, 500A<sub>av</sub>

## Other cases *(low power)*



## **TO-93 case**



TO-208AA  
(TO-48)



**Ex: 1200V<sub>pk</sub>, 325A<sub>av</sub>**

*TO-220 case*


TO-208 Stud case

**Ex: 800V<sub>pk</sub>, 30A<sub>av</sub>**

**Ex: 800V<sub>pk</sub><sup>64</sup>, 20A<sub>av</sub>**

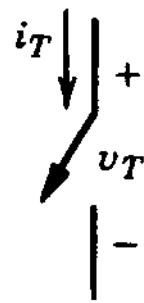
# Controllable switches

- Used in forced-commutated converters ( $f_{sw} > 60$  Hz )
- Different types: MOSFET, IGBT, GTO, IGCT.
- Gate requirements and performance are quite different.
- Generic switch: Current flows in the direction of the arrow when the device is On.



Generic controllable switch

# MOSFET

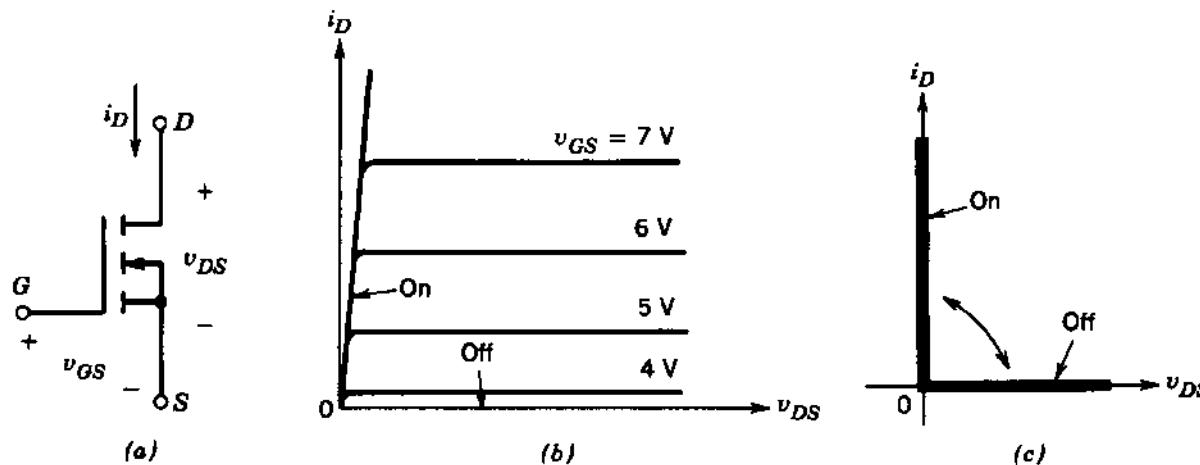


**Figure 2-9** N-channel MOSFET: (a) symbol, (b)  $i$ - $v$  characteristics, (c) idealized characteristics.

International  
**IR** Rectifier



SMD-220 case

Ex: 200V, 70A

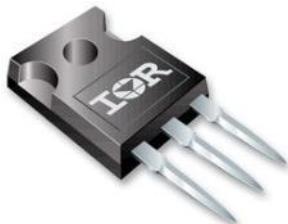

TO-247 case

Ex: 200V, 130A

- High input impedance on the gate (voltage controlled) device.
- Fast commutation times (tens to hundreds of ns). Low switching losses;
- Low On state resistance ( $R_{DS\_On}$ ).
- Easy paralleling
- Limited in voltage and power handling capabilities. Great for low voltage ( $V_{DS} < 250V$ ) and low current ( $I_{DS} < 150A$ ) applications.

# Insulated Gate Bipolar Transistor (IGBT)


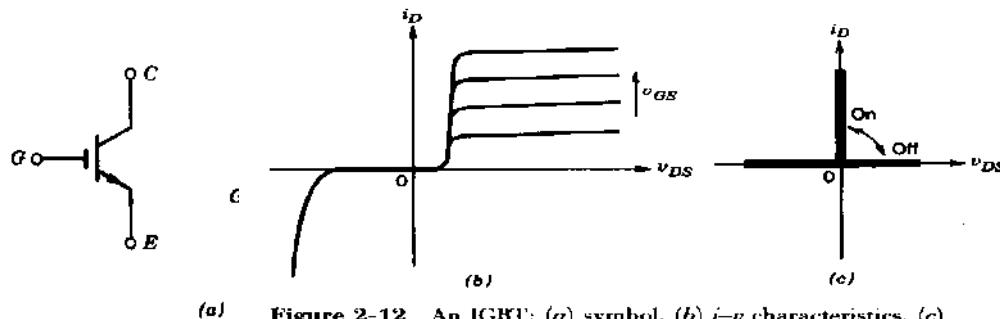


Figure 2-12 An IGBT: (a) symbol, (b)  $i$ - $v$  characteristics, (c) idealized characteristics.

press-pack case  
(high power)


**WESTCODE**

An IXYS Company

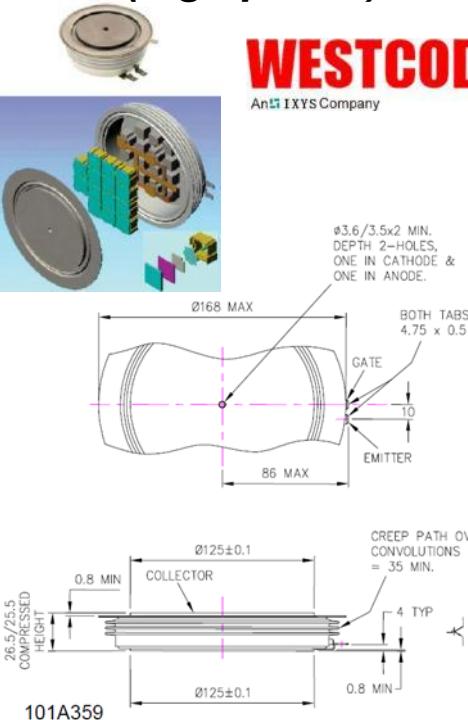

Ex: 4.5kV, 2.4 kA

modules case  
(medium power)

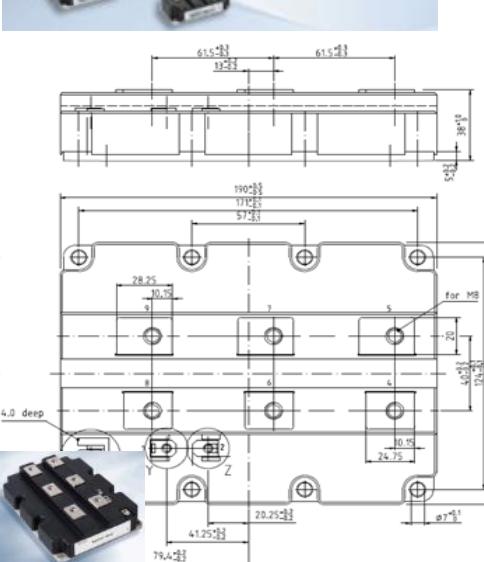

# Gate-Turn-Off (GTO) thyristor

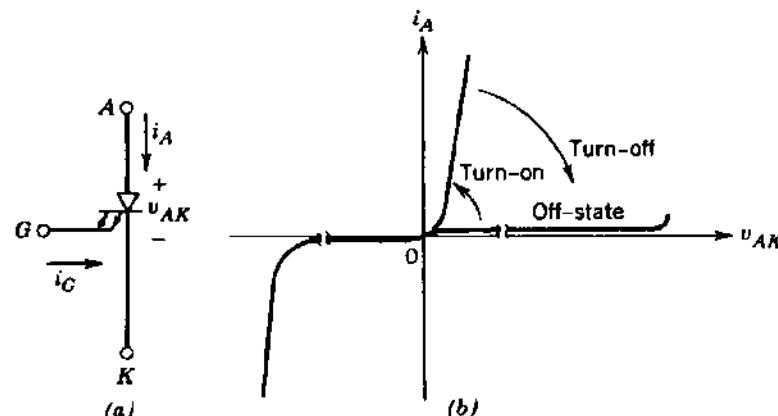



Figure 2-10 A GTO: (a) symbol, (b)  $i$ - $v$  characteristics, (c) idealized characteristics.

- Turns on and latches as an SCR but requires a large ( $I_{AK}/3$ ) negative gate current to turn-off (elaborated gate control circuit);
- Blocks negative voltages but has low switching speeds;
- Still used in ultra high power applications.

**press-pack case**  
**(ultra high power)**



**WESTCODE**  
An IXYS Company

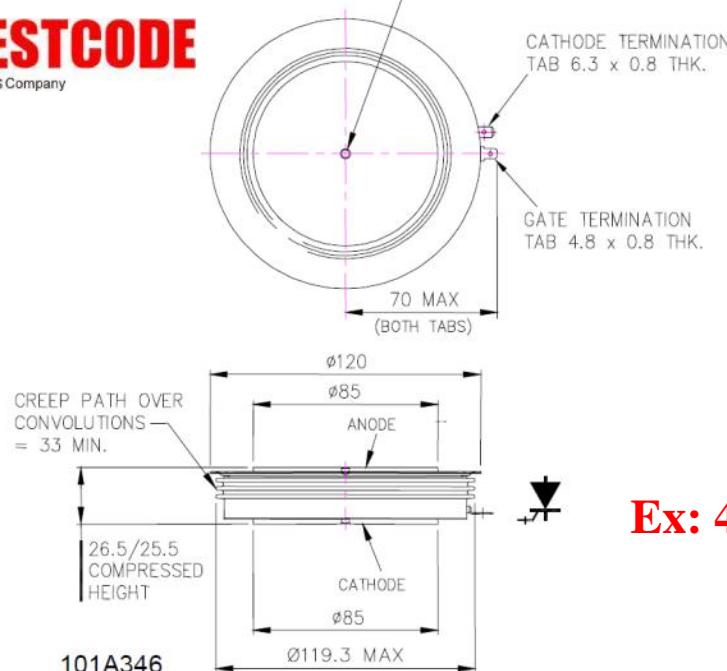

**Ex: 4.5kV, 4 kA**

# Comparison of controllable switches

obsolete  
Most popular  
(low power)  
Most popular  
(high power)



**Table 2-1** Relative Properties of Controllable Switches

		<i>Effective(*) switching</i>	
	<i>Device</i>	<i>Power Capability</i>	<i>Switching Speed</i>
obsolete	BJT/MD	Medium	Medium
Most popular (low power)	MOSFET	Low ( $< \sim 15$ kW)	Fast (~0.1μs)
	GTO	High ( $< \sim 10$ MW)	Slow (~5μs)
Most popular (high power)	IGBT	Medium ( $< \sim 3$ MW)	Medium (~0.5μs)

(\*)

*Voltage de-rating: 1.6; Current de-rating: ~1.3  
(i.e., power de-rating:  $1.6 \times 1.3 \approx 2$ )*

# Reactive Components of Power Converters



## Inductors & Capacitors Functionalities in Power Converters

- Electrical Energy storage  
(POPS, SMES, indirect-link converters)
- Adaptation of converter I/O sources  
(DC or AC current & voltage filters, Bouncers ...)
- Phase control of power flow through HF resonant LC stage
- Implementation of non dissipative commutation  
(ZCS or ZVS snubbers)

## Transformer Functionalities in Power Converters

- Galvanic Isolation
- High Voltage or Low Voltage converters  
(Klystrons or Magnets)




## Reactive Components can degrade:

- Converter Efficiency
- Converter Power Density:  $\text{W/m}^3$  &  $\text{W/kg}$
- Converter Control Bandwidth: Filter Time constants

# Reactive Components of Power Converters

## Basic Dimensional Analysis of Reactive Components

### Transformer Apparent Power (VA)

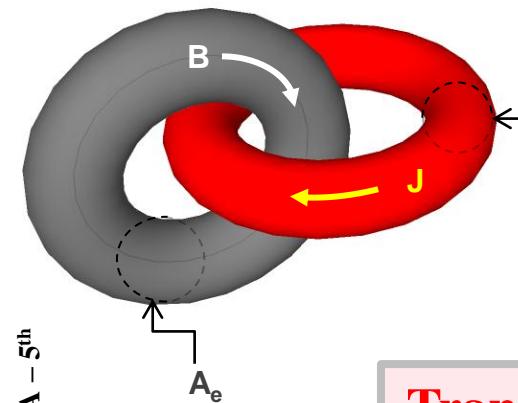

$$S = \sum VI = f \cdot K_u \cdot K_v \cdot B \cdot J \cdot A_e \cdot S_{Cu} \propto f \cdot B \cdot J \cdot [L]^4$$

### Transformer Losses (W)

$$MagLosses \propto B^{\approx 2} \cdot [L]^3$$

$$CopperLosses \propto J^2 \cdot [L]^3$$

### Transformer Temperature Rise

$$TempRise = \frac{Losses}{h \cdot S_{ext}} \propto [L]$$

### Transformer Apparent Power at Constant Temp Rise ( $B \cdot J \propto [L]^{-1}$ )

$$S(VA) \propto f \cdot [L]^3 \propto f \cdot Volume$$

### Inductor Stored Magnetic Energy (J)

$$W_{mag} = \frac{1}{2} L I^2 = K_u \cdot B \cdot J \cdot A_e \cdot S_{Cu} \propto B \cdot J \cdot [L]^4$$


### Inductor Stored Magnetic Energy at Constant Temp Rise

$$(B \cdot J \propto [L]^{-1})$$

$$W_{mag}(J) \propto [L]^3 \propto Volume$$

# Reactive Components of Power Converters
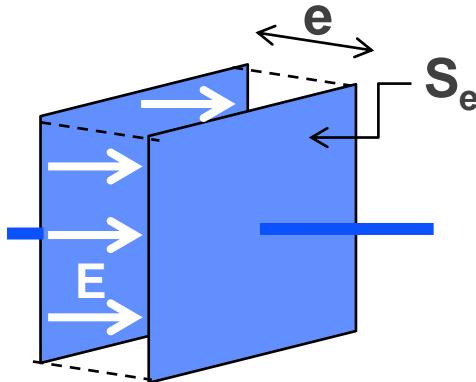
## Basic Dimensional Analysis of Reactive Components



### Capacitor Stored Magnetic Energy (J)

$$W_{el} = \frac{1}{2} CV^2 = K \cdot \epsilon \cdot E^2 \cdot S_e \cdot e \propto \epsilon \cdot E^2 \cdot [L]^3$$

$$W_{el}(J) \propto [L]^3 \propto Volume$$



## Basic Dimensional Analysis of Converter I/O Filters

### Inductor Current Filter L

$$V = L \cdot \frac{\Delta I}{\Delta t} \propto \frac{Volume}{I_o^2} \Delta I_{ppm} \cdot I_o \cdot f$$


$$\Delta I_{ppm} = \frac{\Delta I}{I_o} \quad \Delta t \propto \frac{1}{f}$$

$$Volume \propto \frac{V \cdot I_o}{f \cdot \Delta I_{ppm}}$$
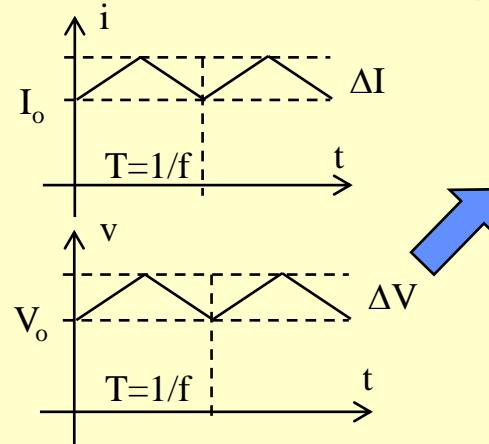
### Capacitor Voltage Filter C

$$I = C \cdot \frac{\Delta V}{\Delta t} \propto \frac{Volume}{V_o^2} \Delta V_{ppm} \cdot V_o \cdot f$$

$$\Delta V_{ppm} = \frac{\Delta V}{V_o} \quad \Delta t \propto \frac{1}{f}$$



$$Volume \propto \frac{V_o \cdot I}{f \cdot \Delta V_{ppm}}$$

# Reactive Components of Power Converters

Trade-off on dynamic performance

Main Time Constant of LC Filter

$$\tau = \sqrt{L \cdot C} \propto \frac{1}{f \cdot \sqrt{V_{ppm} \cdot I_{ppm}}}$$

Main Design Trade off

Frequency

Volume  
Mass

Ripple ppm

Dynamics  $\tau$  (s)




# EMC : ELECTROMAGNETIC COMPATIBILITY

## COMPATIBILITY : Emission - Immunity

Norms for the power converters :
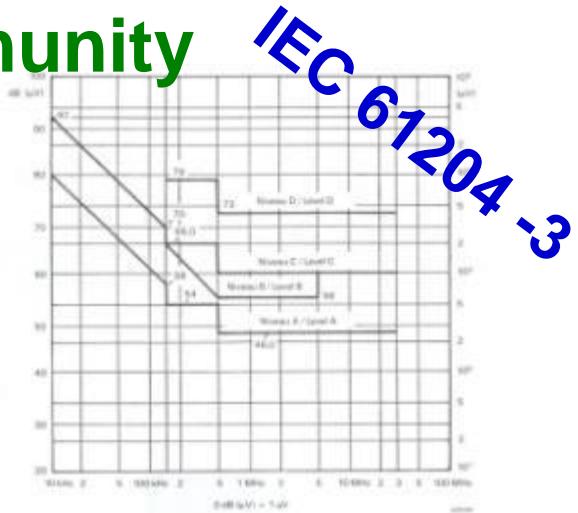
### Emission :


IEC 61204-3 ( replaced IEC-60478-3)  
(CISPR 11 ; EN 55011)



### Immunity :

IEC 61000 - 4 :  
Burst 61000 - 4 - 4  
Surge 61000- 4 - 5

IEC 61000-4-4

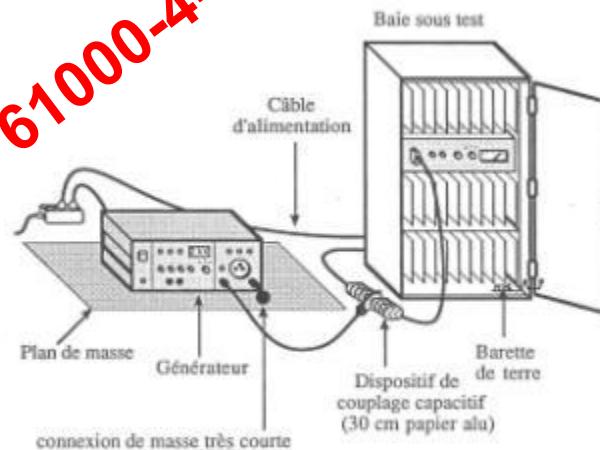

# Interdisciplinary nature of power converters

