

Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# Different power supplies for different machines

Hans-Jörg Eckoldt DESY Warrington, UK 17.05.04



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# Congratulation

for having chosen

# POWER ELECTRONICS



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# Power electronics needs the knowledge of

- Power electronic devices
- Mains behavior
- Regulation theory
- High precision measurement
- Mechanical capabilities
- Analog circuit technology
- Digital circuit technology
- Control system
- Statistics for large number of systems
- Databases
- Cooling technology
- Programming e.g. Internet, FPGAs, DSPs, PLCs
- Simulation tools
  - Missing RF, but with switched mode power supplies we are working on this



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# Sorry!

- Please be not disappointed, if your very interesting power supply is not mentioned here
- Due to the large number it is not possible



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

## Structure of the seminar

- Cycling machines
- Fast ramping machines
- Slow ramping machines
- Pulsed machines
  - Magnet Power Supply
  - Constant power power supply



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# **Cycling Machines**

- DESY II, Hamburg
- ESRF, Grenoble
- BESSY II; Berlin
- SLS, Villingen

- Operation at frequencies between 0.3 and some 10 Hz
- Special care has to be taken for the flicker frequencies



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### Disturbances to the mains

The amount of allowed disturbances is defined in the German standard VDE 0838, IEC 38 or the equivalent European standard EN 61000.

No energy consumer is allowed to produce more distortions than 3% of the voltage variation of the mains. For low frequencies in the visual spectrum this value is even more restricted. The low frequencies are called flicker frequencies. The human eye is very sensitive to changes in light intensities in this frequency domain.



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# Allowed disturbancies to the grid according to IEC 38/VDE 0838



Bild 5-2: Verträglichkeitspegel für regelmäßige rechteckförmige Spannungsänderungen



Hans-Jörg Eckoldt

#### THE CERN ACCELERATOR SCHOOL

### White circuit





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# Calculated Power with and without White circuit for BESSY II





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### DESY II 4.5 GeV, 7 GeV, 10 GeV max.

	Dipole	QP	SP
l <sub>max</sub>	1170 A	1530 A	530 A
I rms magnet	873 A	940 A	324 A
U rms Choke/magnet	4.3 kV * 12 51.6 kV	3.34 kV	273 V
I <sub>DC PS</sub>	585 A	765 A	255 A
U <sub>DC PS</sub>	27.7 V	122.4 V	32 V
I <sub>AC PS</sub>	665 A	540 A	187 A
U <sub>AC PS</sub>	990 V	3.22 kV	273 V



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

## **DESY II Overview (artist view)**





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### DESY II with compound inductor (White choke)





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### DESY II dipole power supply with Steinmetz circuit





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# DESY QP, SP circuit





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

## ESRF 6 GeV

	Dipole	QPF	QPDF
l <sub>max</sub>	1500 A	500 A	500 A
U rms Choke/magnet	11 kV	2 kV	2 V
I <sub>DC PS</sub>	800 A	200 A	180 A
U <sub>DC PS</sub>	600 V	200 V	200 V
I <sub>AC PS</sub>	800 A	200 A	180 A
U <sub>AC PS</sub>	V	V	V



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

## Power supply of ESRF





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# BESSY II 1.9 GeV

	Dipole	QPF	QPDF
I <sub>max</sub>	2277 A	492 A	395 A
U rms Choke/magnet	3112 kV	527 V	423V
I <sub>DC PS</sub>	800 A	200 A	180 A
U <sub>DC PS</sub>	120 V	70 V	70 V
I <sub>AC PS</sub>	778 A	200 A	200 A
U <sub>AC PS</sub>	311V	184 V	184 V



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

## Schematic of the BESSY II Power supply





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### Power supply at SLS





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# Fast ramping machines

- DESY III
- Tevatron
- Fermilab Main Injector
- Cern Antiproton
   Decelerator
- PETRA

- Ramping times from a second to a minute
- U=R\*i + L\*di/dt
   Due to the inductance the
   term demands for a
   significant higher voltage
   than for steady state
- Negative voltage has to be applied for down ramping
- Precautions for the mains have to be taken



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# DESY III

	Dipole
I flat top	1160 A
U <sub>flat top</sub>	1 kV
I flat bottom	50 A
U flat bottom	42 V
di/dt	665 A/s
Ramping time	4 sec



Hans-Jörg Eckoldt

#### THE CERN ACCELERATOR SCHOOL

### DESY III Power supply with dynamic reactive power compensation





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# Signals for the DESY III ramp





Hans-Jörg Eckoldt

#### THE CERN ACCELERATOR SCHOOL

### DESY III Power supply with dynamic reactive power compensation





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

## Tevatron

	Dipole
I flat top	4400 A
U <sub>flat top</sub>	1 kV
I flat bottom	400 A
U flat bottom	42 V
di/dt	67 A/s
Ramping time	60 sec



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

## Tevatron distribution of power supplies





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

#### UUU MAGNETS uw 11 POWER LEAD 4.8mF SERIES SHUNT SCR SCR ٩ł DC BREAKER PASSIVE FILTER CHOKE DUMP 1 KV P.S. + DUMP RESISTOR

### Power supply of Tevatron

TEVATRON POWER SUPPLY SYSTEM POWER CIRCUIT



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### Fermilab Main Injector





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

## Fermilab main injector data

Requirement	
Dipole and quadrupole power, peak	120 MVA
Dipole and quadrupole power, average	60 MVA
RF, beamline power supplies, peak	30 MVA
RF, beamline power supplies, average	20 MVA
Backfeed capability, peak	40 MVA
Backfeed capability, average	30 MVA
Accelerator cycling time	1.5 sec



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# **CERN** Antiproton Decelerator Cycle





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### Antiproton decelerator power supply







Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### Power supply for the PS-Booster beam transport line with polarity switcher and regenerative circuit





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### **PETRA-Dipole ring** NW NO PETRA - DIPOLKREIS W 0 untere Spulenlage obere Spulenlage SW SO S



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# Voltage changes due to the ramping of the PETRA-machine





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# Slow ramping machines

- HERA
- LEP
- LHC
- Here nearly every lab can be named
- Ramping lasts several minutes or
- Working at steady state
- The variety of power supplies is large and shows in general the state of the art of the power electronics of that time



#### Hans-Jörg Eckoldt

#### THE CERN ACCELERATOR SCHOOL





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### HERA Proton Dipole Power Supply



8000 A, +500V,-300V Optical current 5600A



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# SCR Power supplies

- Power larger than 50 kW
- Currents larger than 800 A
- Voltages higher than 130 V
- Good prices
- Simple design
- Different Solutions according to the specs
  - LC filter
  - Praeg Filter
  - Active filter



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

## SCR supply with LC filter







Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

## SCR Power supply with Praeg filter

400 V





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### HERA Buck converter





Hans-Jörg Eckoldt

#### THE CERN ACCELERATOR SCHOOL

# Schematic of the LEP double resonant power supply



125 V, 300 A or 188 V, 200 A or 250 A, 150 V



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### LHC 600A/10V, 40V Power supply





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

## LHC 600A/10V, 40V Power supply





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

## LHC 600A/10V, 40V Power supply





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### SCR unit for LHC transport line with active filter





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# Pulsed machines

- Linear Collider, sometimes, somewhere
- XFEL, Hamburg
- VUV-FEL, Hamburg

- Machines are working with short pulses between a few µsec up to ms
- Repetition rates between 1 and 50 Hz
- High demands on power supplies
- Suppress the repetition rate toward the grid



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### New XFEL power supply for sc QP +/- 100 A/10V





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

Ζı

t

## **XFEL Power supply**





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### Web Access to the power supply





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### Voltage at XFEL Modulator





Hans-Jörg Eckoldt

#### THE CERN ACCELERATOR SCHOOL

# Switched mode power supply for constant power



G	Rectifier
i <sub>B</sub>	supply current
i <sub>L</sub>	primary current of the transformer
u <sub>C</sub>	voltage of the resonance capacitor
U <sub>Cload</sub>	output voltage to the switch of the
	klystron
i <sub>Bt1</sub>	current $i_B$ at the time t1
L	primary stray inductivity of the
	transformer
f	resonance frequency of the resonant
	circuit of L and C
n	gear ratio of the transformer and
	rectifier
Т	period time of the switching frequency
	of S1 and S2
С	resonance capacitor
UB	supply voltage
U <sub>N</sub>	line voltage
$C_{\rm f}$	filter capacitor

L<sub>f</sub> filter inductance



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# Derivation of the equivalent circuit to the switch mode power supply





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### Series connection of buck converters





Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

# Conclusion

- There are a lot of very interesting power supplies in the machines
- This was only a very short overview of what is installed into machines over the world
- It shall give an idea what kind and where solutions and help are to find when someone encounters a new problem
- A very good source of information is:
  - Joint Accelerator Conferences Website
  - http://accelconf.web.cern.ch/AccelConf/



Hans-Jörg Eckoldt

THE CERN ACCELERATOR SCHOOL

### Thanks for your attention