

Basics of Accelerator Science and Technology at CERN

Magnet powering scheme

Jean-Paul Burnet

- Definition
- What is special for magnet powering?
- Power electronics
- Converter topologies
- Converter association
- Nested circuits
- Energy management
- Discharged converter
- Power supply control
- What should specify an accelerator physicist?


Definition

Wikipedia: A power supply is a device that supplies electric power to an electrical load.

Power supplies are everywhere:
Computer, electronics, motor drives,...

Here, the presentation covers only the very special ones for particles accelerators : **Magnet power supplies**

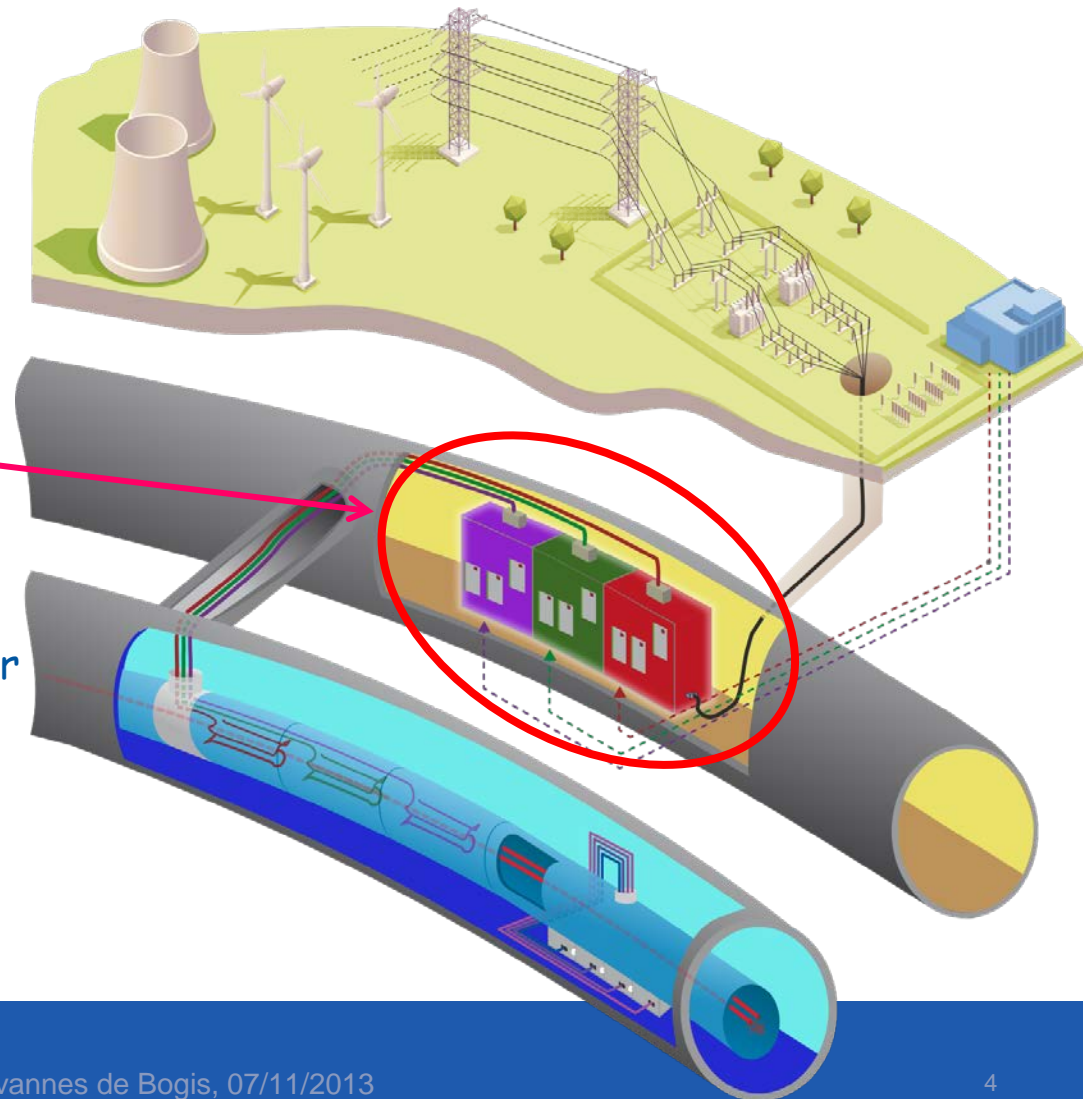
Power supply \neq power converter
US labs uses magnet power supplies
CERN accelerator uses power converter
CERN experiment uses power supply



What is special for magnet powering ?


In a synchrotron, the beam energy is proportional to the magnetic field.

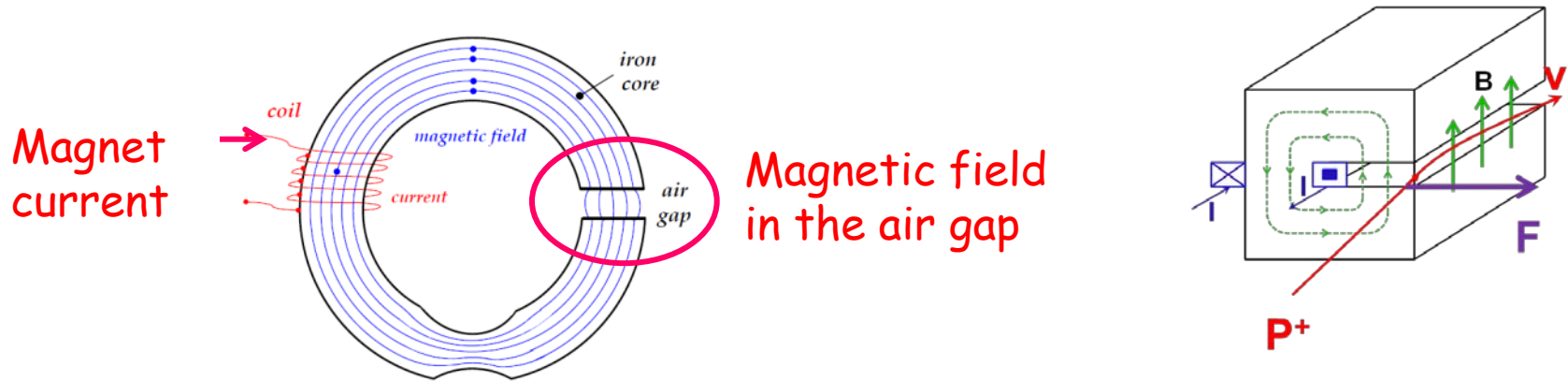The magnet field is generated by the current circulating in the magnet coils.



$$NI = \mathcal{R} \times \Phi$$

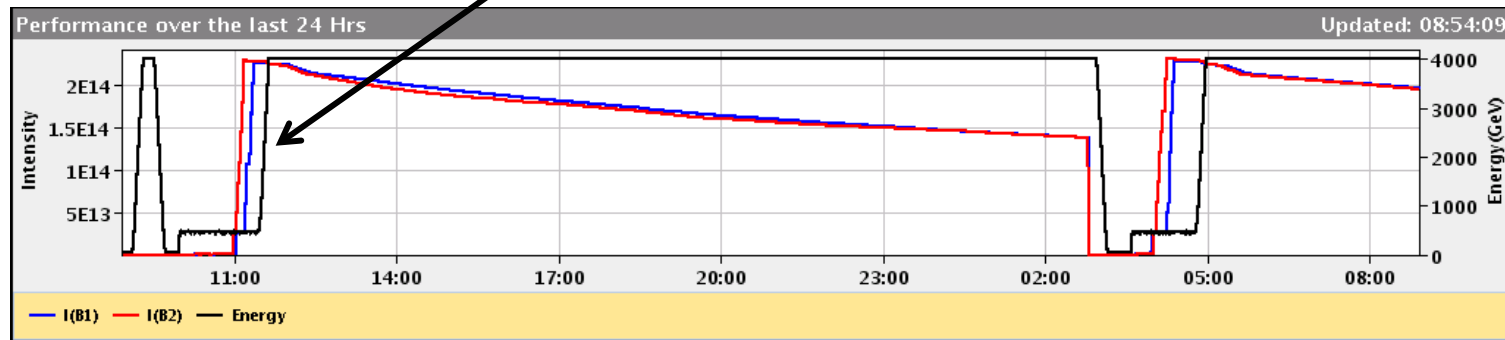LHC vistar : Beam Energy = Dipole Current




What is special for magnet powering ?

The relation between the current and B-field isn't linear due to magnetic hysteresis and eddy currents.

In reality, $\text{Beam Energy} = k_f \times \text{Dipole field} \neq k_i \times \text{Dipole Current}$

Classical iron yoke

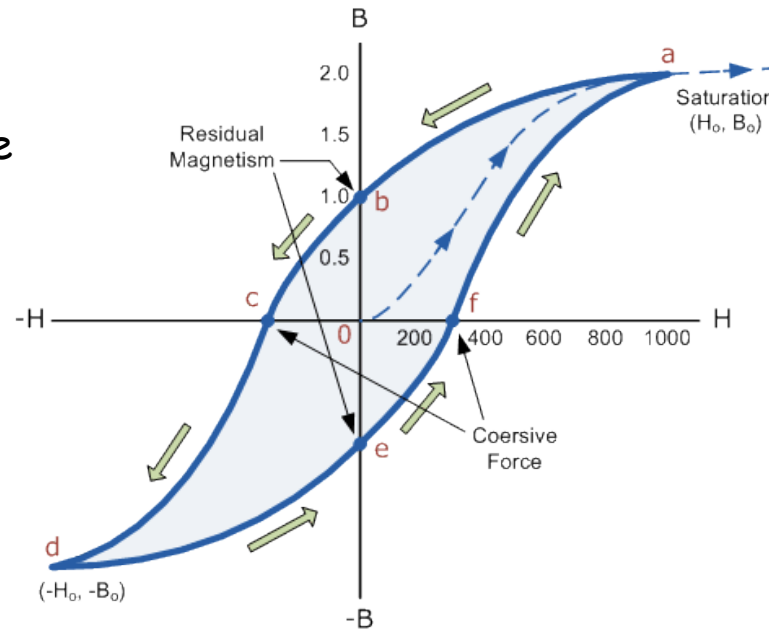

Magnet current



What is special for magnet powering ?

For superconducting magnet, the field errors (due to eddy currents) can have dynamic effects.

$$\vec{B}_y + i\vec{B}_x = \sum_{n=1}^{\infty} C_n \left(\frac{z}{R_{ref}} \right)^{n-1} = B_1 \sum_{n=1}^{\infty} \frac{(b_n + ia_n)}{10^4} \left(\frac{z}{R_{ref}} \right)^{n-1}$$

Decay is characterised by a significant drift of the multipole errors when the current in a magnet is held constant, for example during the injection plateau. When the current in a magnet is increased again (for example, at the start of the energy ramp), the multipole errors bounce back ("snap back") to their pre-decay level following an increase of the operating current by approximately 20 A.

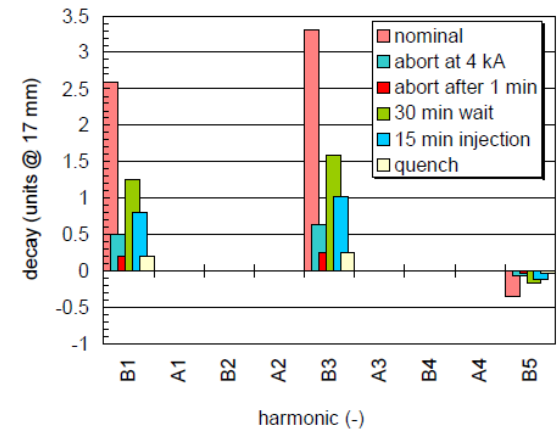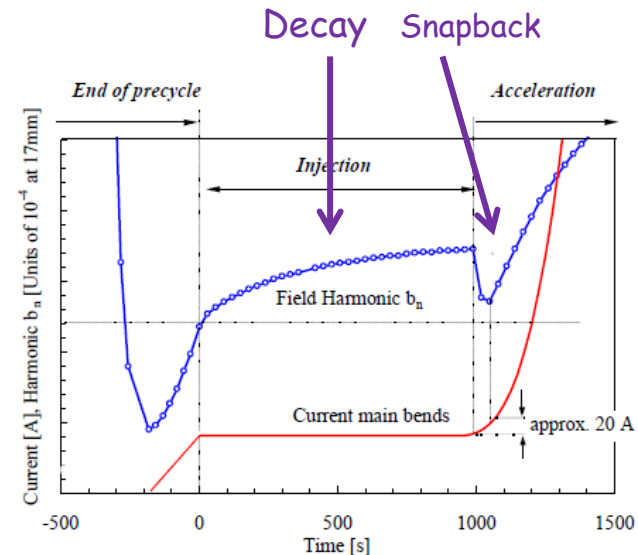For the energy ramp such as described in [3], the snapback takes 50-80 seconds but this can vary if, for example, the rate of change of current in the magnet is changed.






<http://accelconf.web.cern.ch/accelconf/e00/PAPERS/MOP7B03.pdf>

What is special for magnet powering ?

To solve this problem of hysteresis, the classical degauss technique is used.

For a machine working always at the same beam energy, few cycles at beam energy will degauss the magnets. Example LHC precycle.

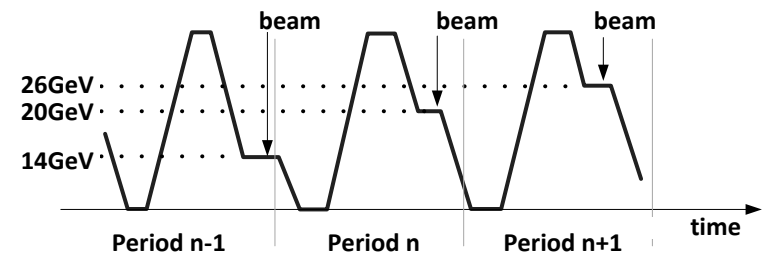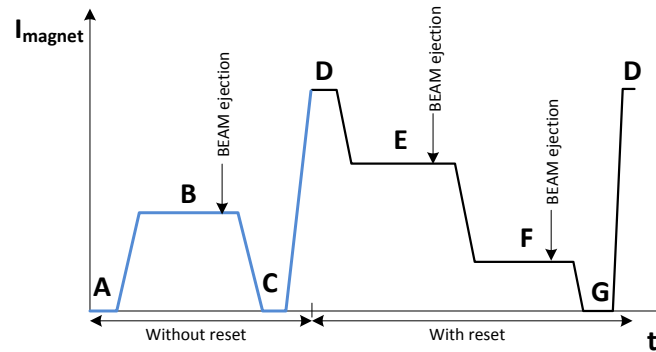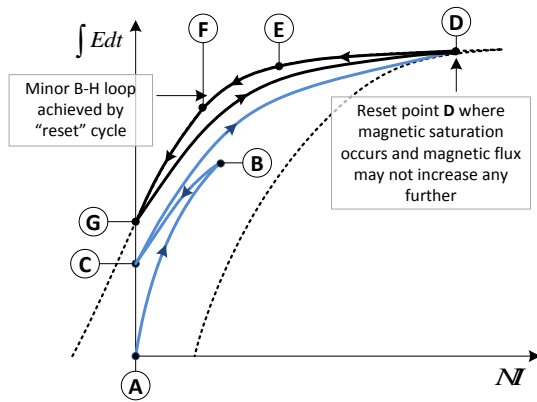For machine or transfer line with different beam energies, the degauss has to take place at each cycle. Solution, always go at full saturation in each cycle.



What is special for magnet powering ?

Measuring the magnetic field is very difficult and need a magnet outside the tunnel.

In most of the synchrotrons, all the magnets (quadrupole, sextupole, orbit correctors,...) are current control and the beam energy is controlled by the dipole magnet current.

For higher performance, the solutions are :

- Get a high-precision magnetic field model (10^{-4})
- Real time orbit feedback system
- Real time tune feedback
- Real time chromaticity feedback
- Or
- Real-time magnetic field measurement and control (10^{-4})

How an operator change the beam energy with a synchrotron?

To ramp up, the operator increases the dipole magnetic field.

The radiofrequency is giving the energy to the beam, but the RF is automatically adjusted to follow the magnetic field increase (Bdot control).

Magnet powering scheme


To get the same B-field in all the magnets, the classical solution is to put all the magnets in series.

Generally done with dipole and quadrupole.

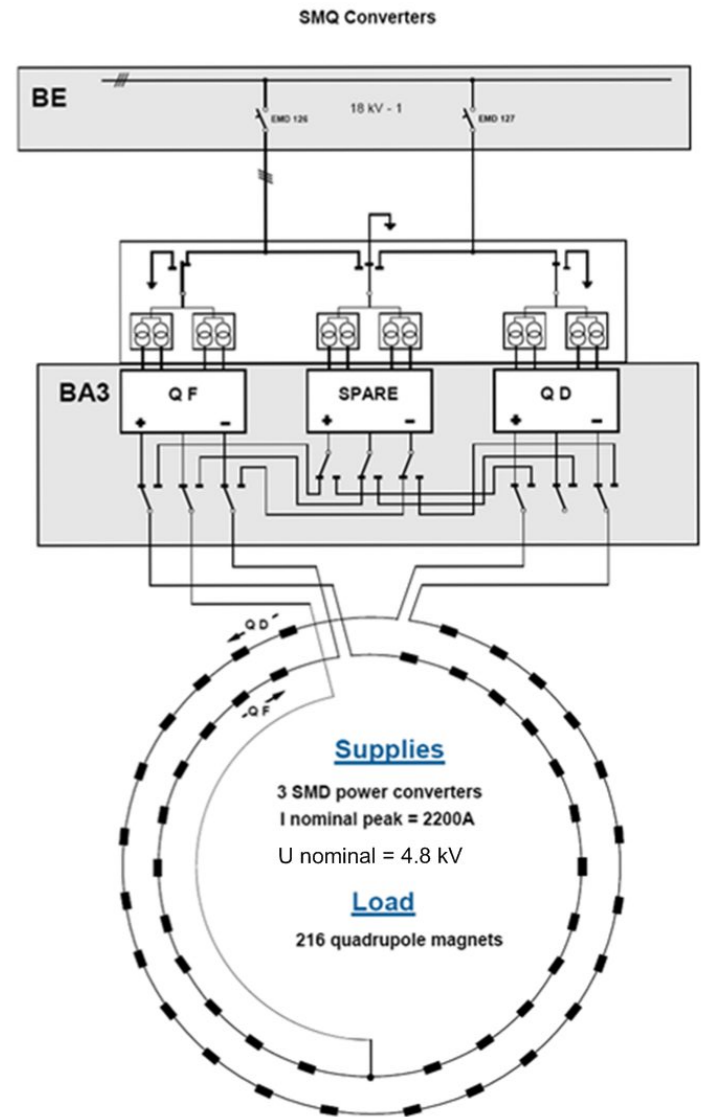Example of SPS quadrupole




Lead to high power system for Dipole and quadrupole.



Magnet powering scheme

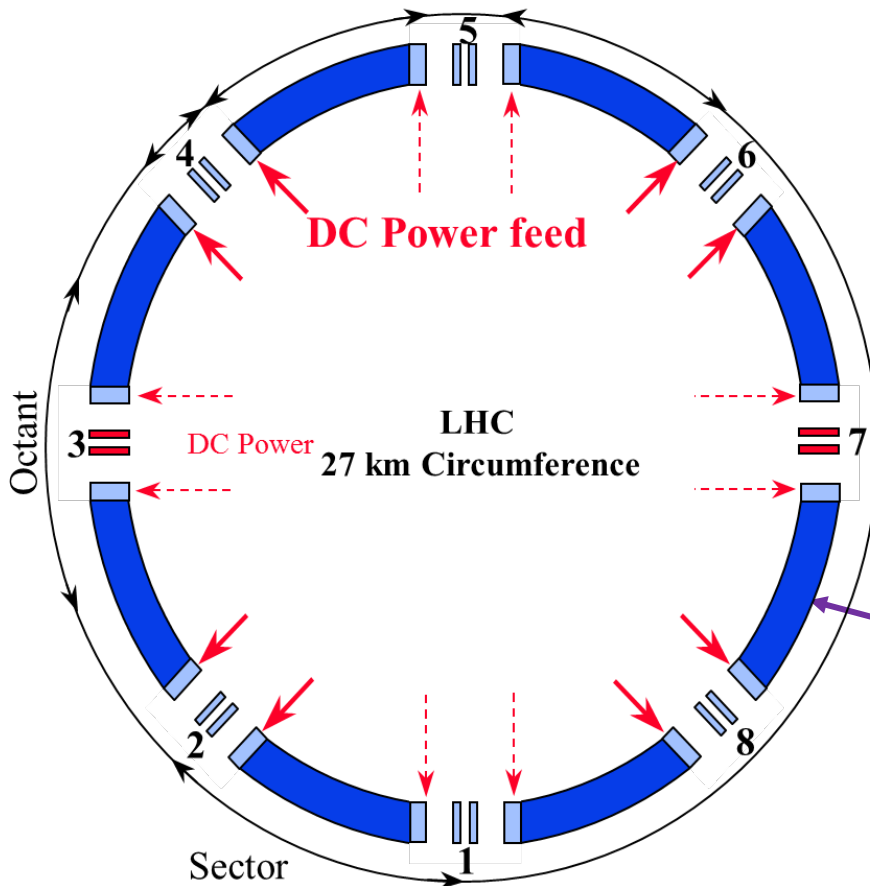
But when the power is becoming too high, the circuit can be split.
First time with LHC in 8 sectors.



Tracking between sector !

Powering Sector:
154 dipole magnets
total length of 2.9 km


Magnet powering scheme

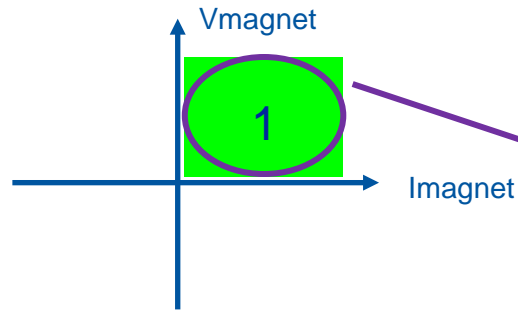




Magnet current operation






Power supply type

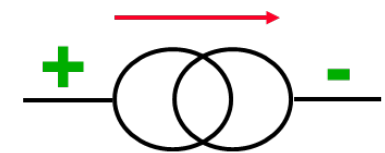

1 Quadrant mode

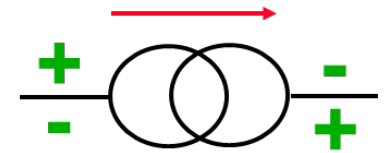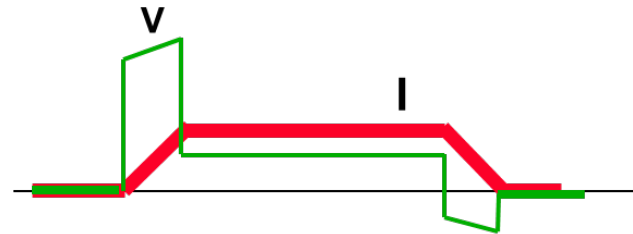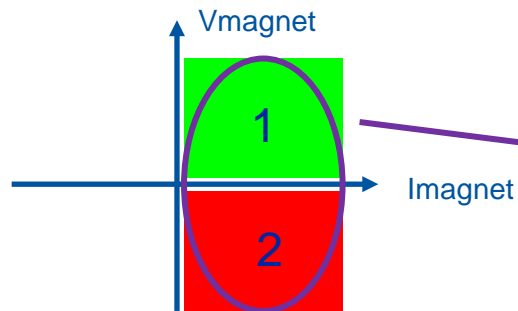

2 Quadrants mode

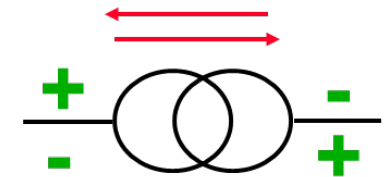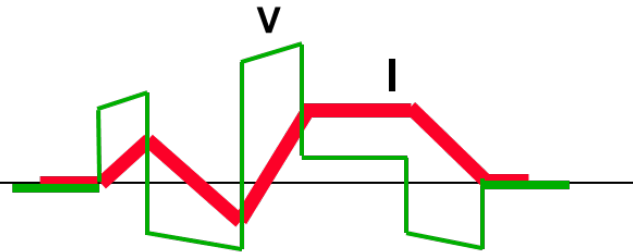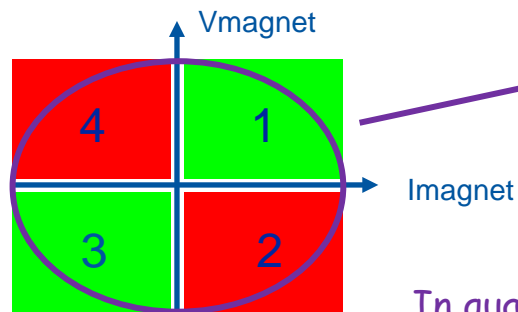

4 Quadrants mode

In quadrant 2 and 4, the magnet stored energy is returning to the power supply.

$$E_{magnet} = 0.5 * L_{magnet} * I^2$$

What is special for magnet powering ?

The magnet power supplies are high-precision current control.

To build it, the technical solutions are out the industrial standard:

- Need very low ripple
 - Need current and voltage control over large range
 - Operation in 1-2-4 quadrant
- } Special topologies
- Need high-precision measurement
 - Need high-performance electronics
 - Need sophisticated control and algorithm
- } Special electronics and control


Powering a magnet isn't classical, and few one the shelf product can be used
always custom power supplies

What is power electronics?

Power electronics

Power electronics is the application of solid-state electronics for the control and conversion of electric power.

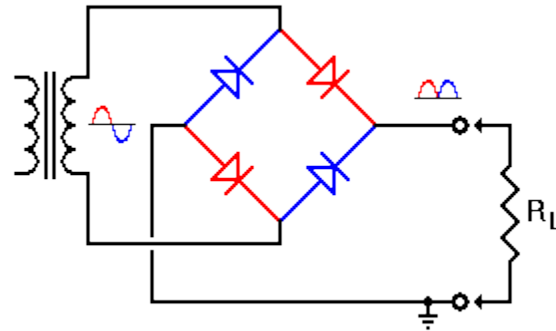Power electronics started with the development of mercury arc rectifier. Invented by Peter Cooper Hewitt in 1902, the mercury arc rectifier was used to convert alternating current (AC) into direct current (DC).



The power conversion systems can be classified according to the type of the input and output power


- AC to DC (rectifier)
- DC to AC (inverter)
- DC to DC (DC-to-DC converter)
- AC to AC (AC-to-AC converter)

Switching devices

Nowadays, the main power semiconductors are:



- Diode
- MOSFET
- IGBT
- Thyristor

The most popular is the IGBT

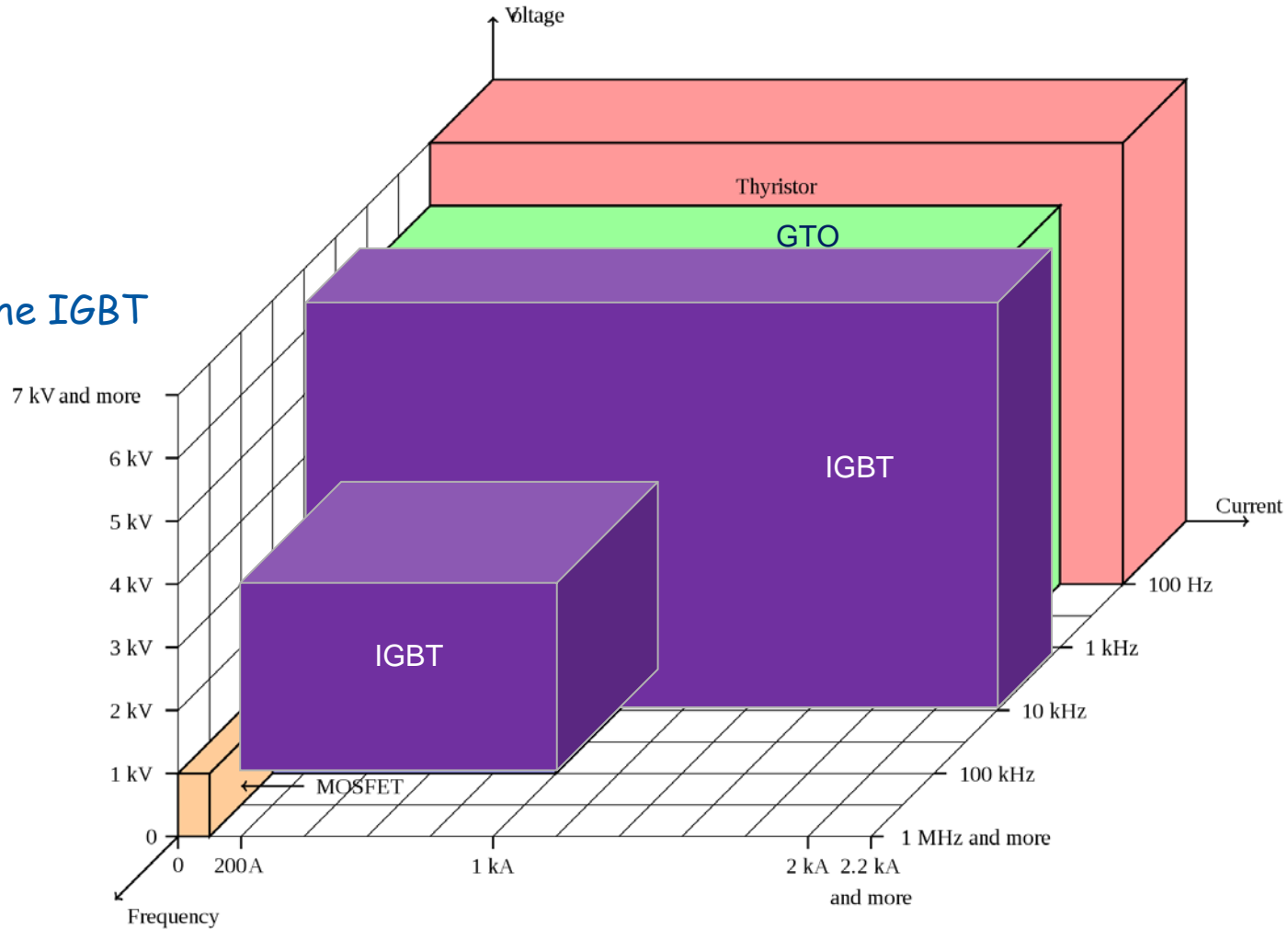

Thyristor principle

Thyristor (1956): once it has been switched on by the gate terminal, the device remains latched in the on-state (*i.e.* does not need a continuous supply of gate current to remain in the on state), providing the anode current has exceeded the latching current (I_L). As long as the anode remains positively biased, it cannot be switched off until the anode current falls below the holding current (I_H).

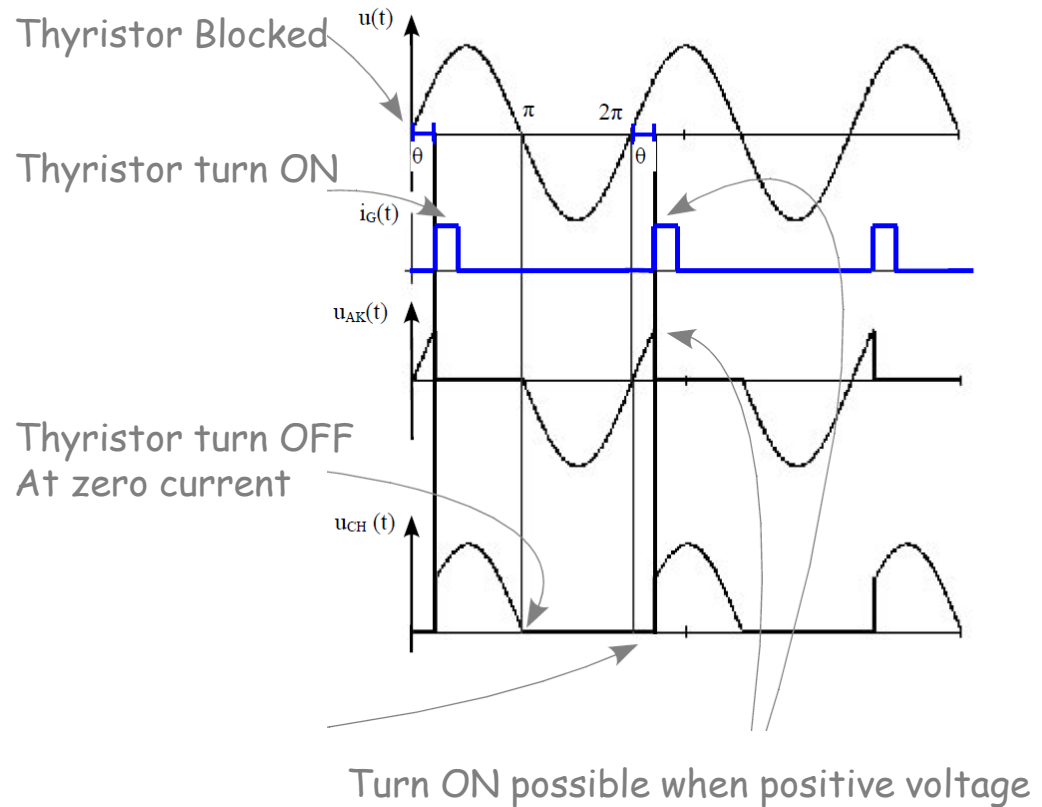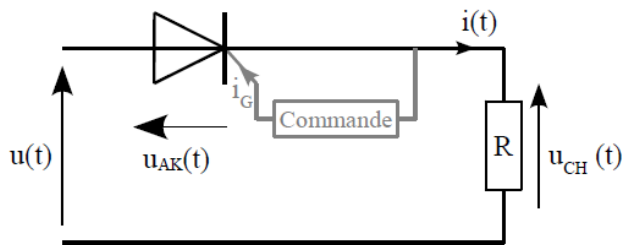

Topologies based on thyristor


The magnets need DC current.

The magnet power supplies are AC/DC.


The magnets need a galvanic isolation from the mains: 50Hz transformer



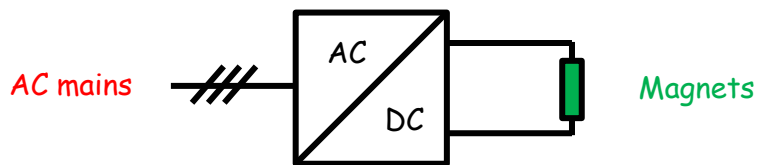The thyristor bridge rectifier is well adapted to power magnets.



Magnets

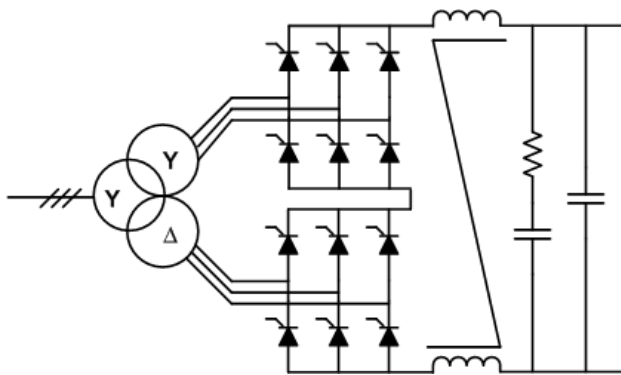

Thyristor advantages



- Very robust
- Cheap
- Low losses

Thyristor drawbacks

- Sensible to mains transients
- Low losses
- Low power density

Diode bridge rectifier



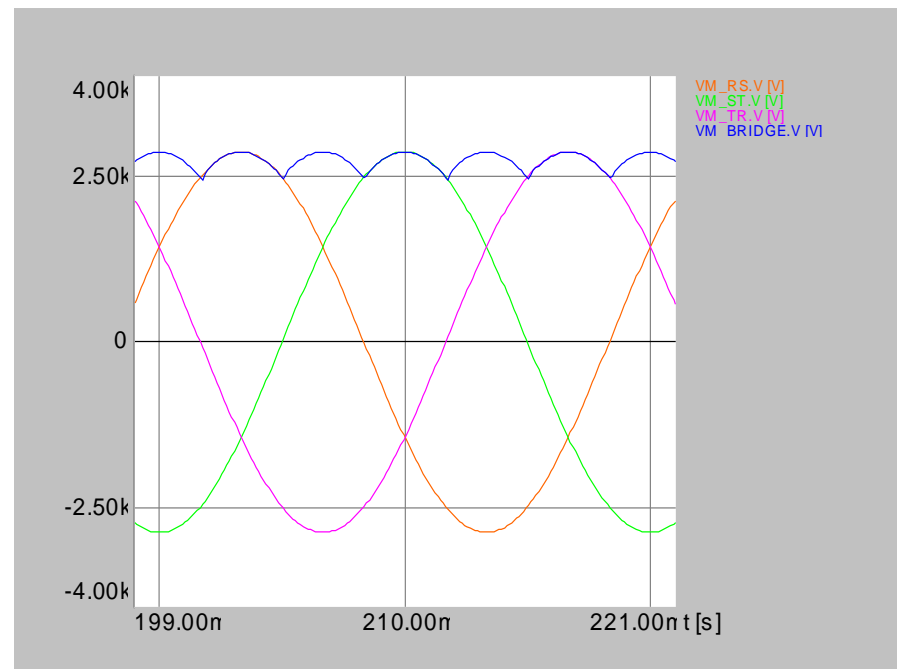
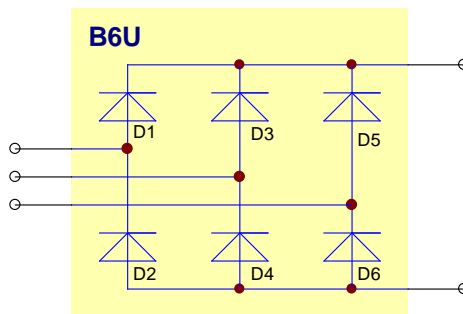
- 3 phases diode bridge voltage rectification
 - Bridge output voltage is fixed, $1.35 * U_{\text{line to line}}$



Thyristor bridge rectifier



- 3 phases Thyristor bridge voltage rectification
 - Can control the bridge output voltage by changing the firing angle α
 - $V_{out} = U_{max} * \cos \alpha$

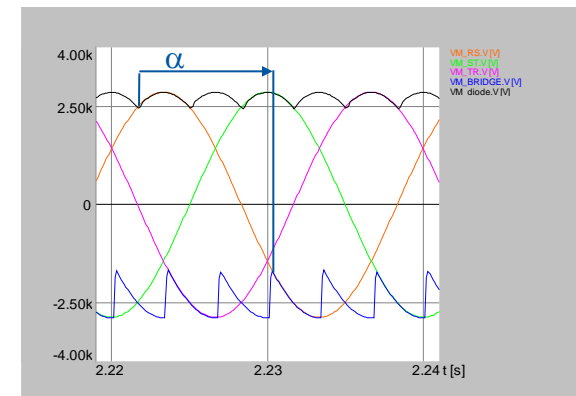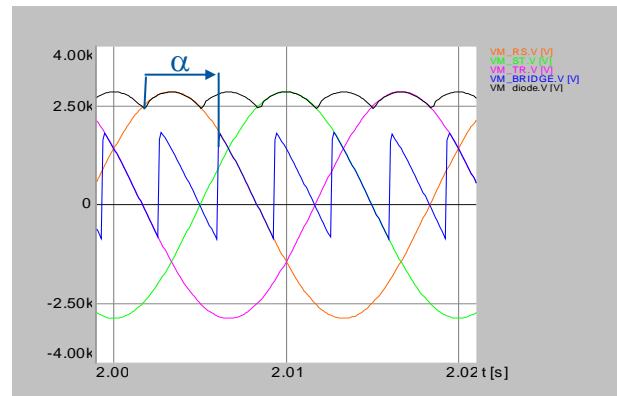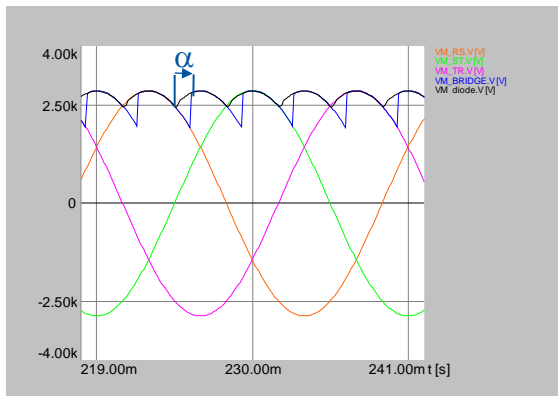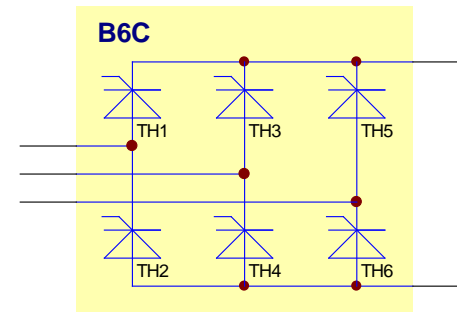- $\alpha = 15^\circ$, $V_{out} = 0.96 * U_{max}$
- $\alpha = 70^\circ$, $V_{out} = 0.34 * U_{max}$
- $\alpha = 150^\circ$, $V_{out} = -0.86 * U_{max}$





Thyristor bridge rectifier

- Maximum voltage, $\alpha = 15^\circ$

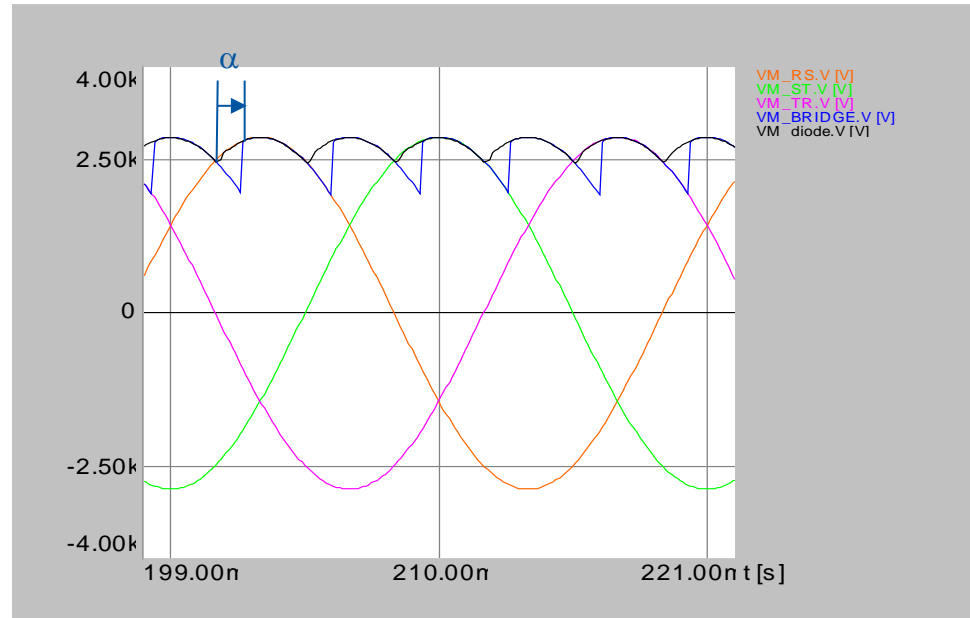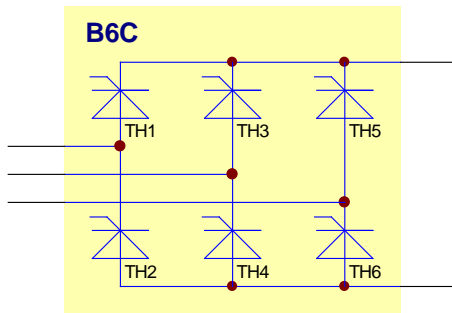

Thyristor bridge rectifier

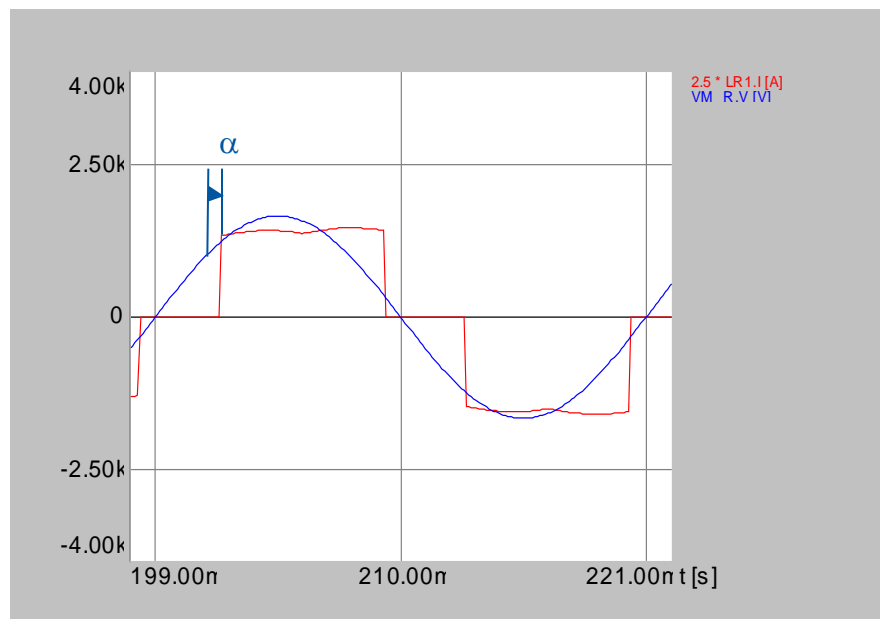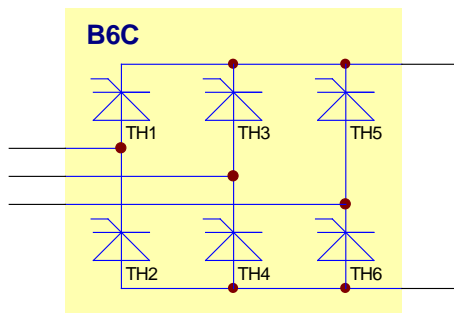- Transformer line current at maximum voltage, $\alpha = 15^\circ$
 - The diode bridge current is in phase with the voltage
 - For the thyristor rectifier, the AC line current is shifted with the angle α





Thyristor bridge rectifier

- Power analysis

- Power: $P(t) = V_r(t) * I_r(t) + V_s(t) * I_s(t) + V_T(t) * I_T(t)$
- Active power: $P = 3 * V_r * I_{Line\ rms} * \cos \alpha$
- Reactive power: $Q = 3 * V_r * I_{Line\ rms} * \sin \alpha$
- Apparent power: $S = \sqrt{P^2 + Q^2}$
- Power factor: $P/S = \cos \alpha$

- $\alpha = 15^\circ$



- Active power high
- Reactive power low

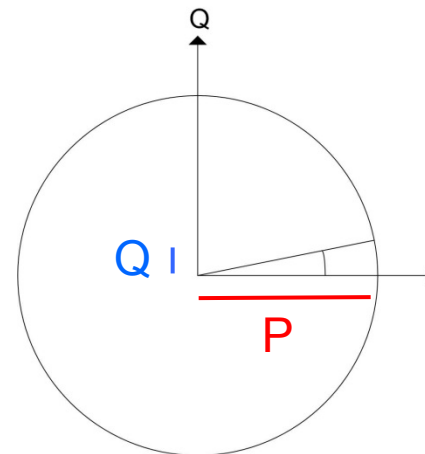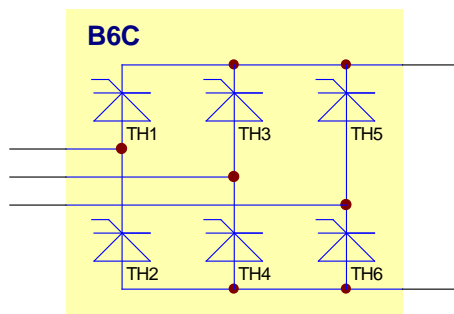

Thyristor bridge rectifier



- At flat top, $\alpha = 70^\circ$

Full current / low DC voltage

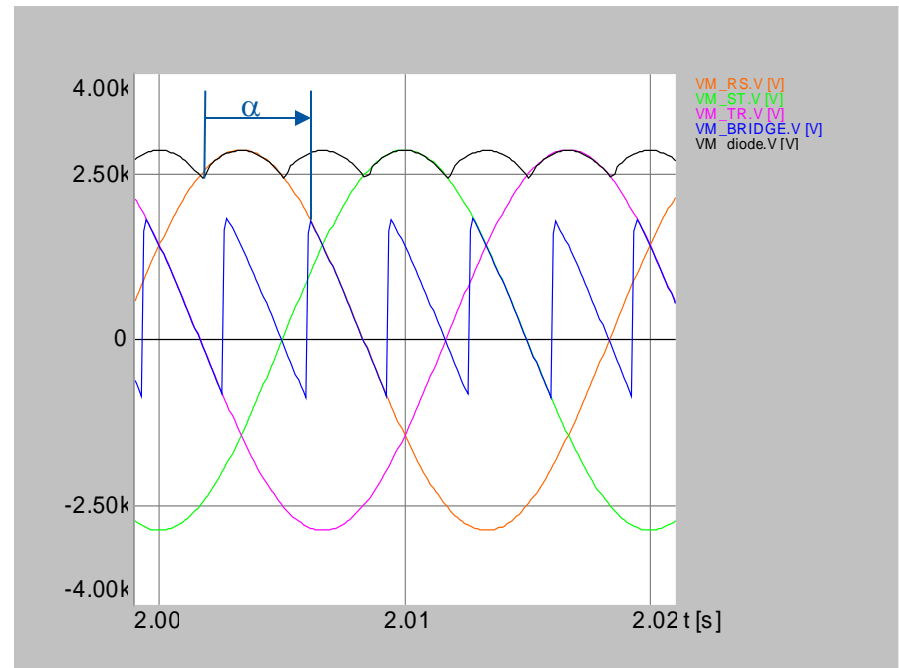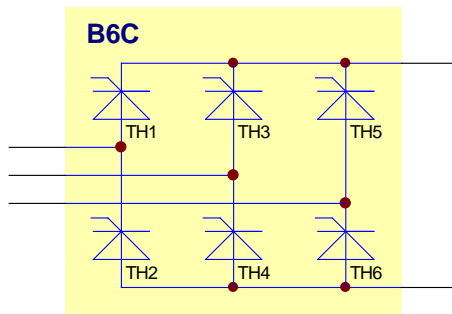

Thyristor bridge rectifier

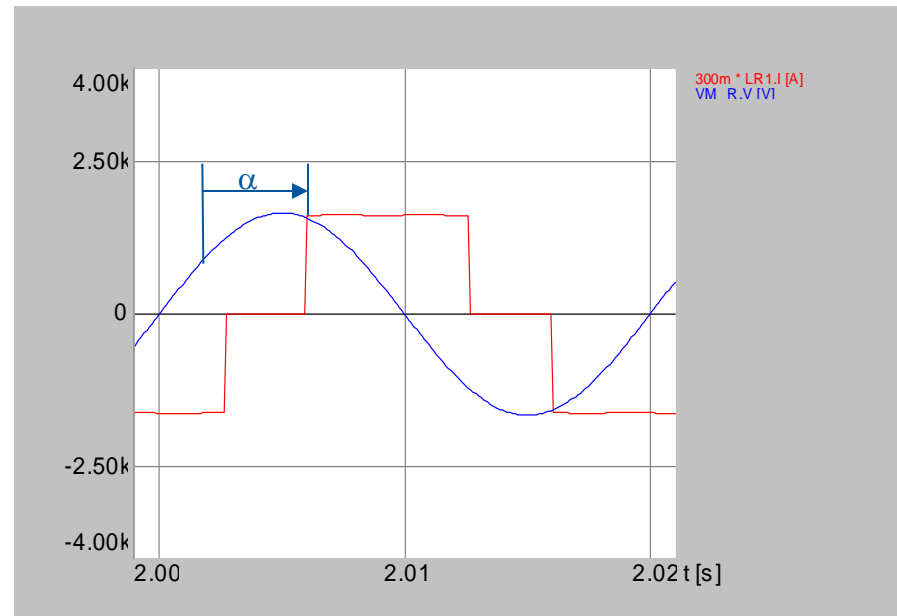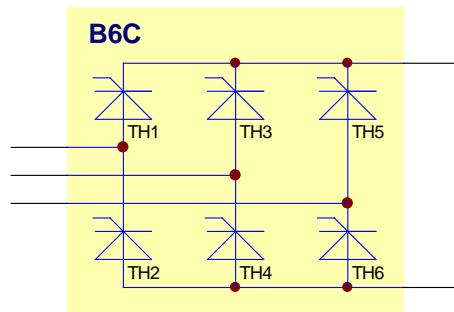- Transformer line current at flat top (at $\alpha = 70^\circ$)



Thyristor bridge rectifier

- Power analysis

- Active power:

$$P = 3 * V_r * I_{Line\ rms} * \cos \alpha$$

- Reactive power:

$$Q = 3 * V_r * I_{Line\ rms} * \sin \alpha$$



- Apparent power:

$$S = \sqrt{P^2 + Q^2}$$

- $\alpha = 70^\circ$

- Active power low

- Reactive power high

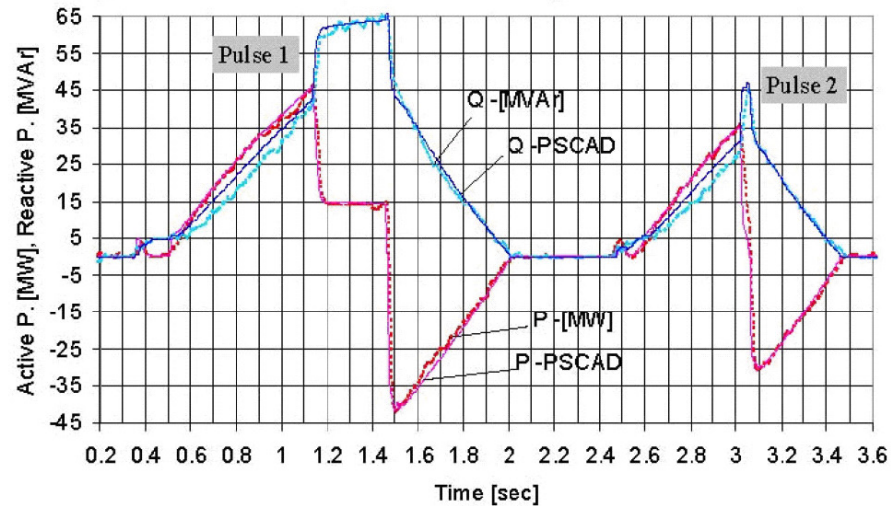
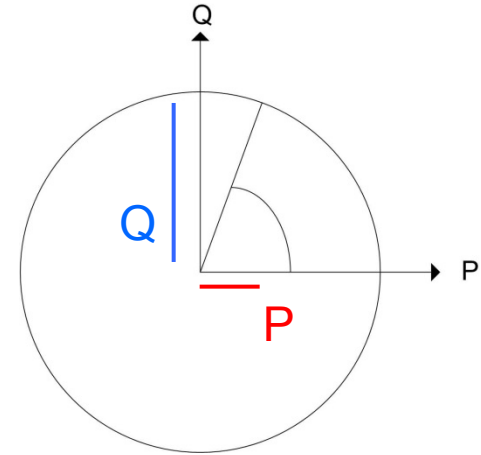


Reactive power compensation

Reactive power must be compensated.
Power factor > 0.93 for EDF.
Affect the mains voltage stability.



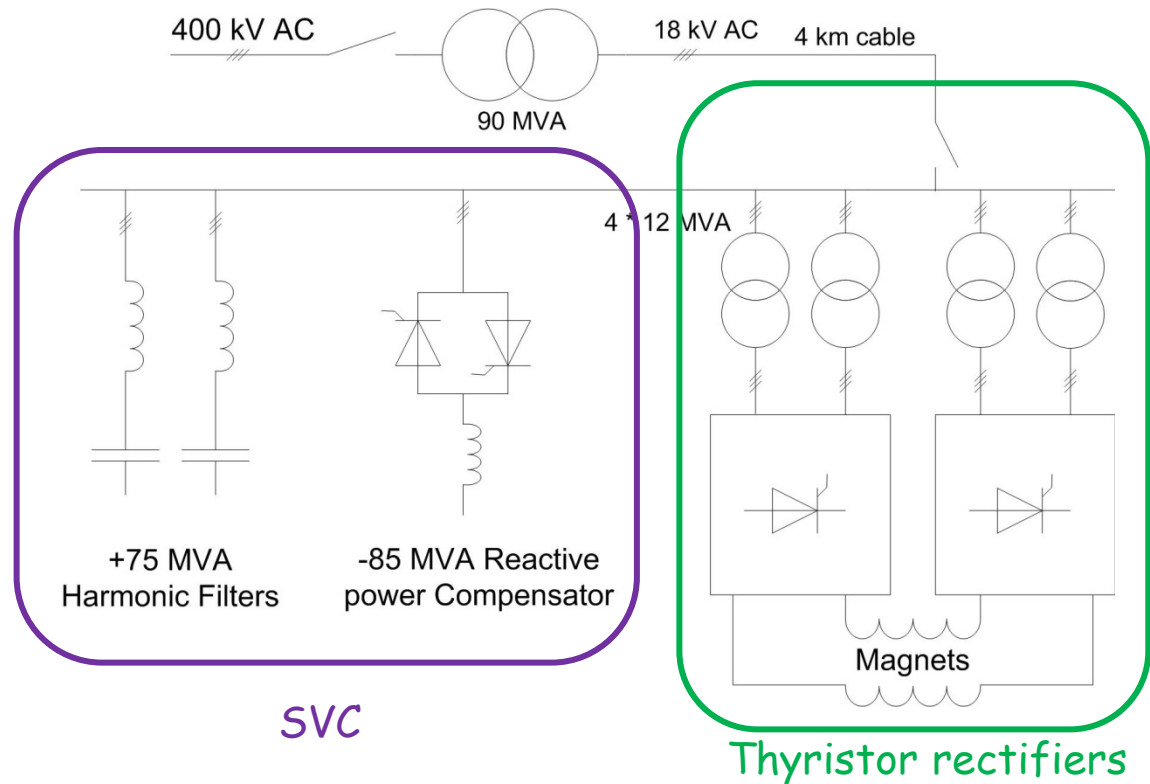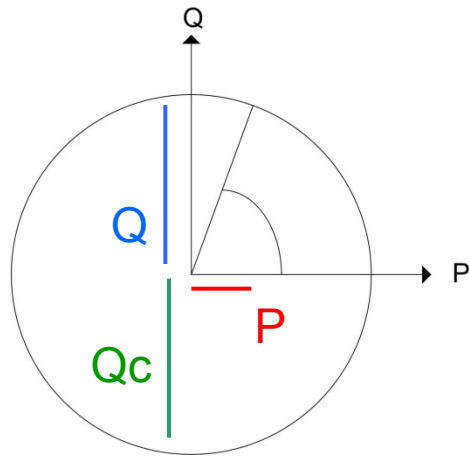Solution :SVC: Static VAR Compensator, Q_c



Reactive power compensation

SVC role on the 18kV

- Compensate reactive power (Thyristor Controlled Reactor)
- Clean the network (harmonic filters)
- Stabilize the 18kV network ($>\pm 1\%$)




Thyristor rectifier example

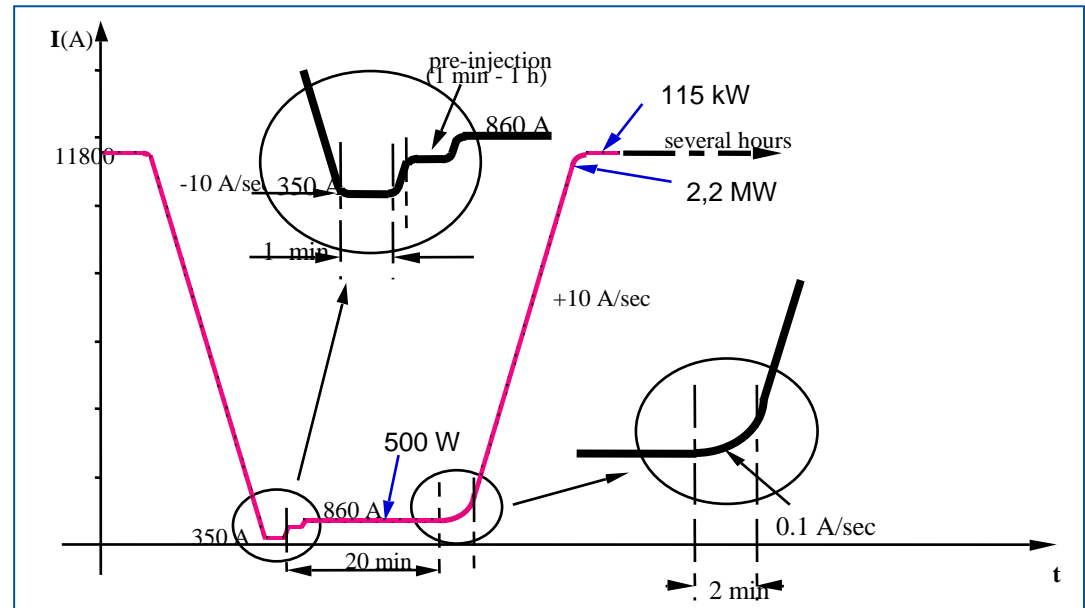Example: LHC dipole converter 13kA/180V



Magnet: $L = 15.7H$
 $R = 0.001\Omega$
Ultimate = 13kA

Magnet operation:
 $I_{injection} = 860A$
 $dI/dt = \pm 10A/s$
 $I_{4TeV} = 6.9kA$
 $I_{7TeV} = 11.8kA$
Magnet protected by
external dump resistor




Thyristor rectifier example

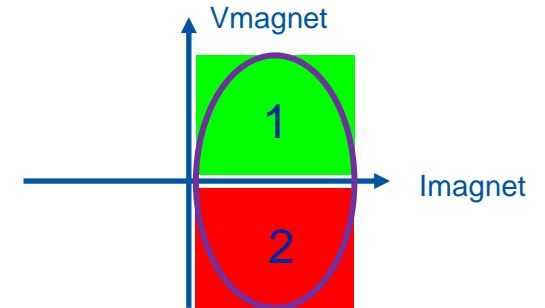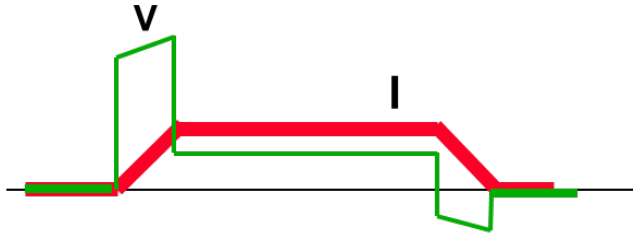Example: LHC dipole converter 13kA / 180V



18kV AC

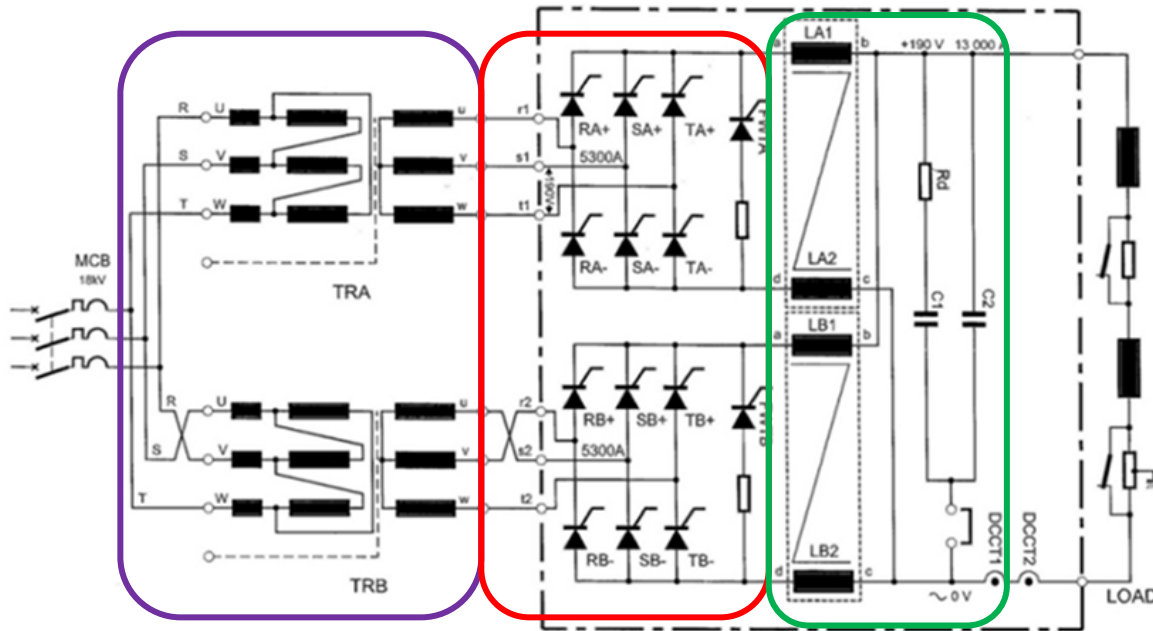






50Hz transformer

Output filter

Thyristor rectifier


Magnets

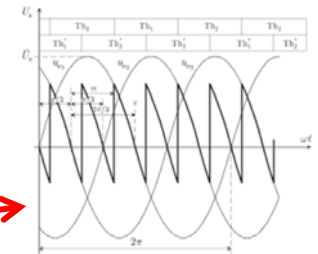

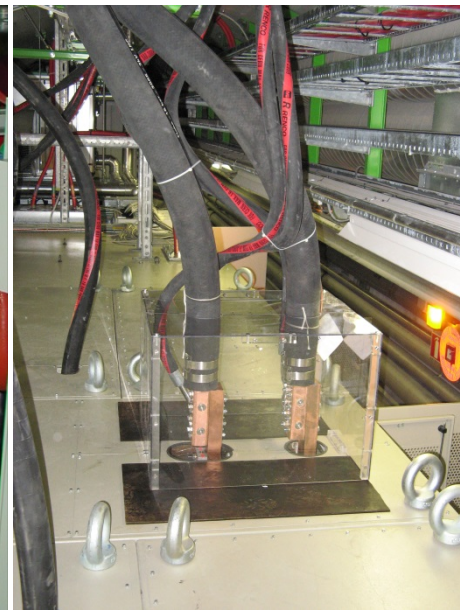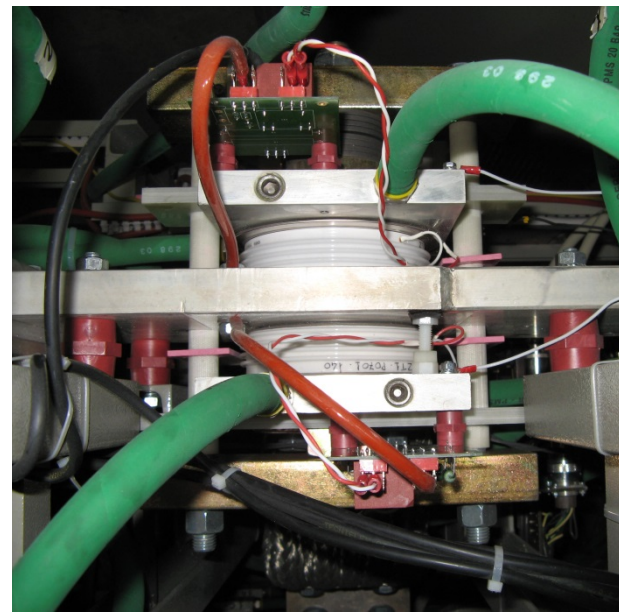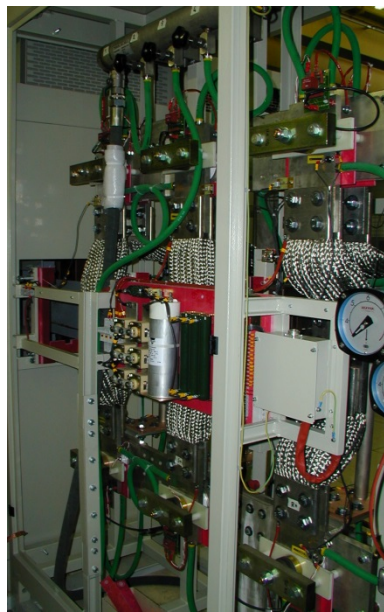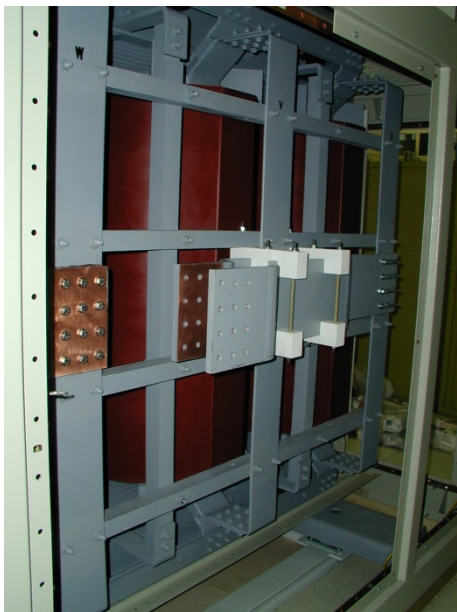


Thyristor rectifier

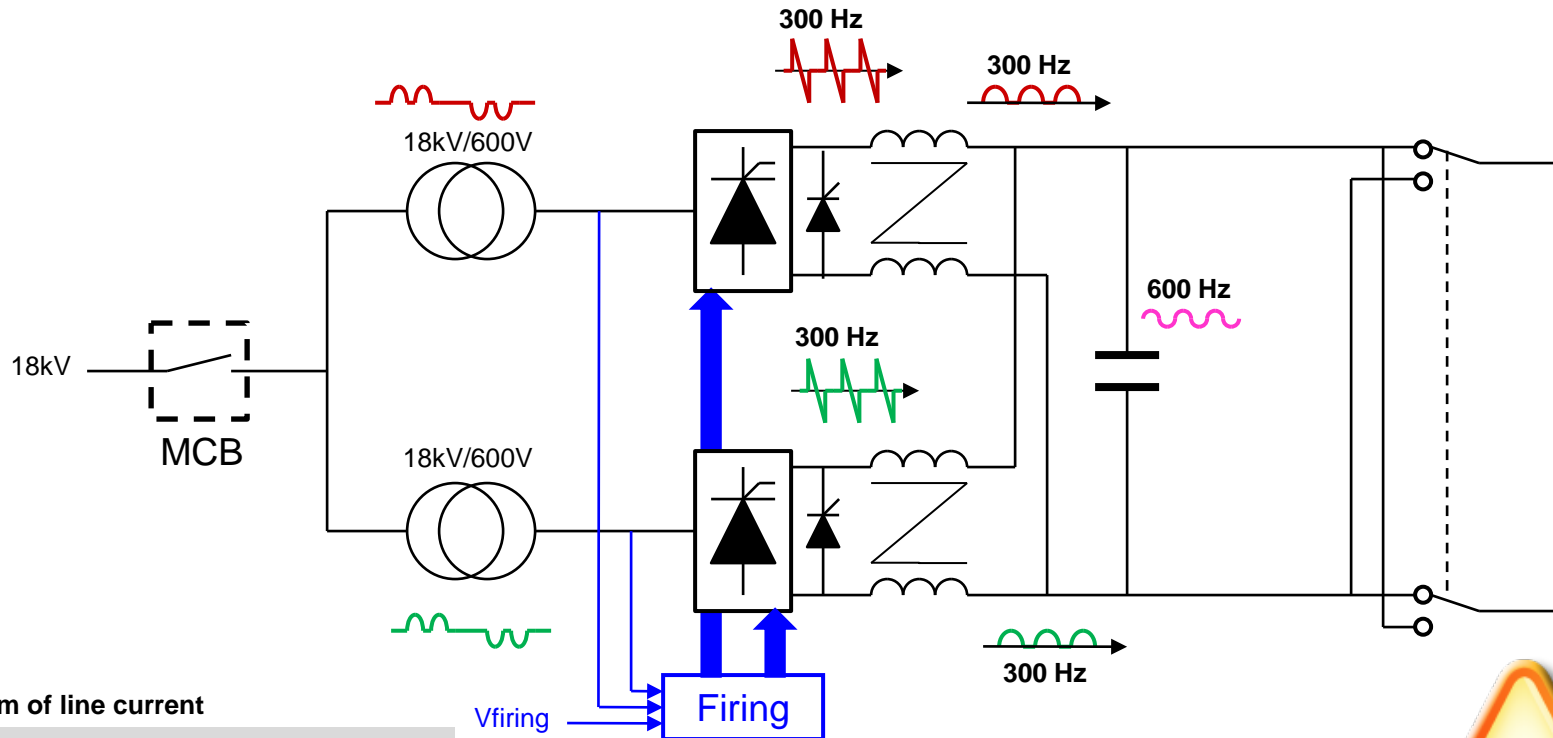
Limitation a low current due to discontinuity of current



Sum of line current

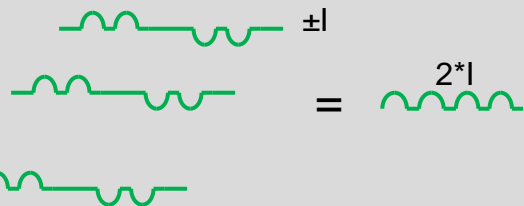

Sum of bridge voltages

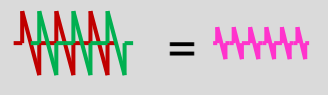

Minimum current



Topologies based on IGBT

What is an IGBT ?

The IGBT combines the simple gate-drive characteristics of the MOSFETs with the high-current and low-saturation-voltage capability of bipolar transistors.

The main different with thyristor is the ability to control its turn ON and turn OFF.

Many topologies can be built using IGBT.

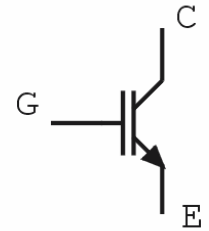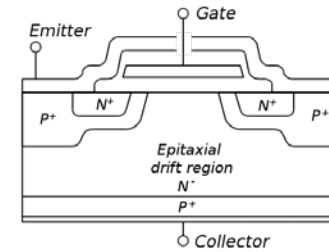

200A




1kA



3kA

10A



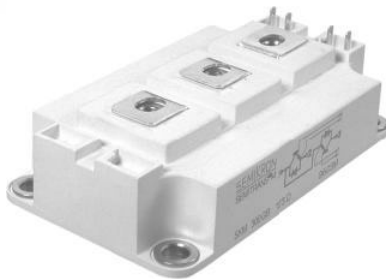


IGBT

Real IGBT turn-on and turn-off:

Very fast di/dt , $dv/dt \Rightarrow$ EMC

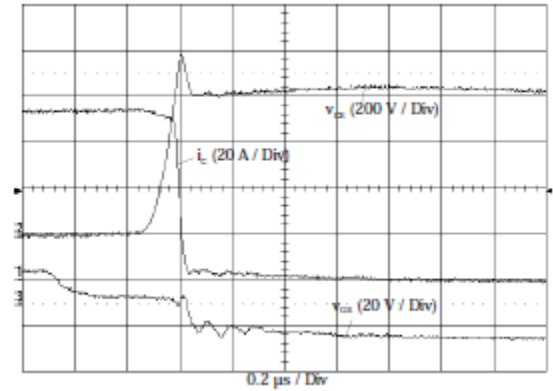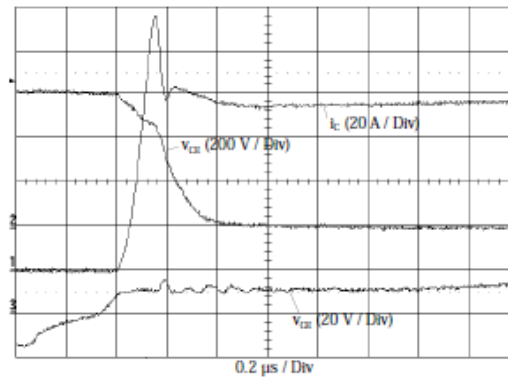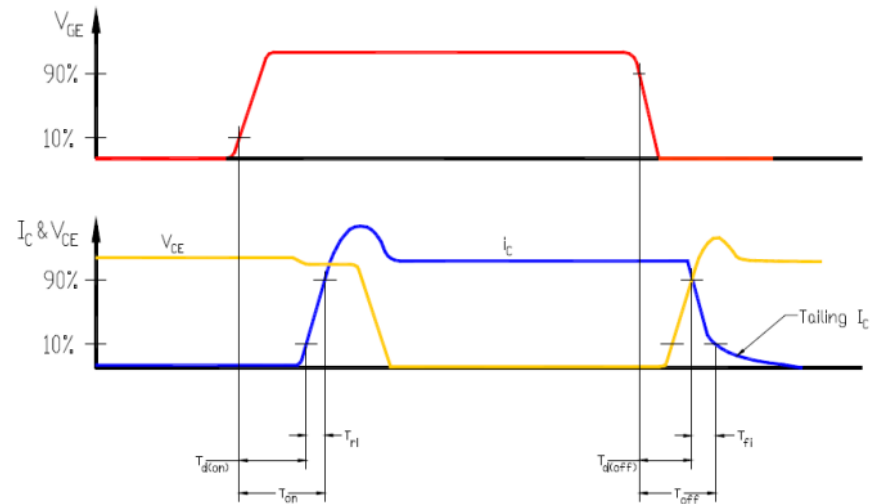Switching losses \Rightarrow thermal limitation





IGBT




Number of cycles

Thermal cycling of the IGBT

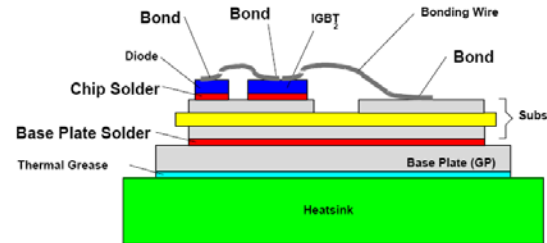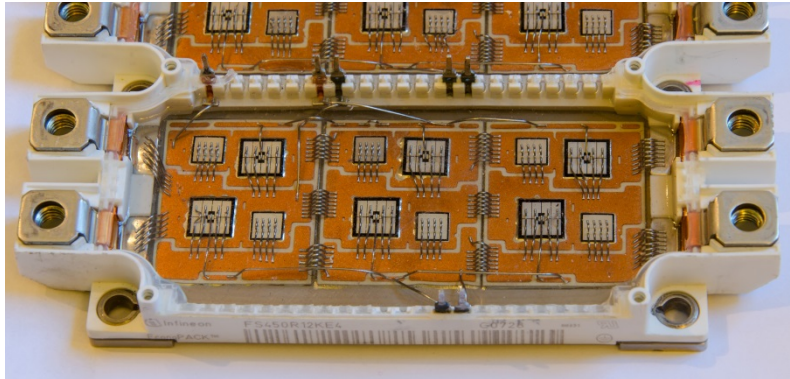


IGBT bonding can break after few thousand of thermal cycles

Evolution de $T_J - T_c - T_h$

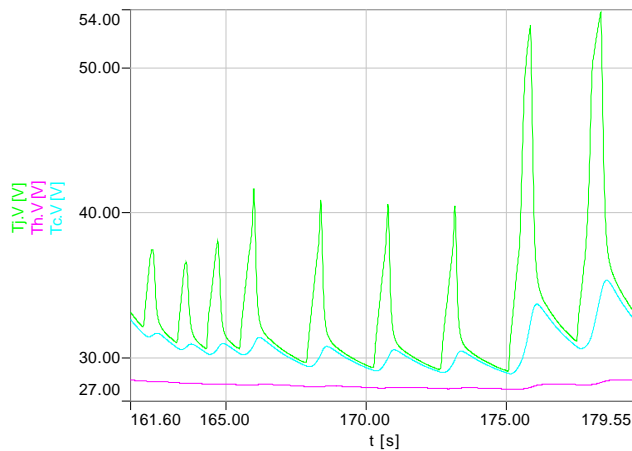

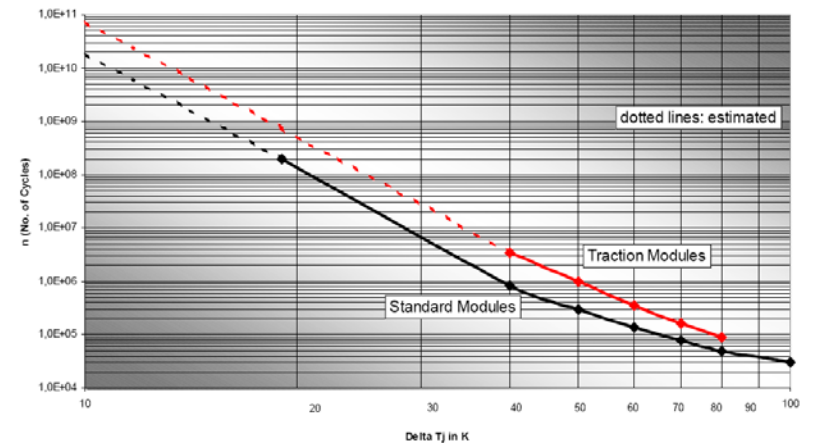
Power Cycling: Medium & High Power Modules
($T_{Jmax} = 125^\circ\text{C}$)



Power electronics basic concept


The basic principle is to command a switch to control the energy transfer to a load.

Example of a BUCK converter:

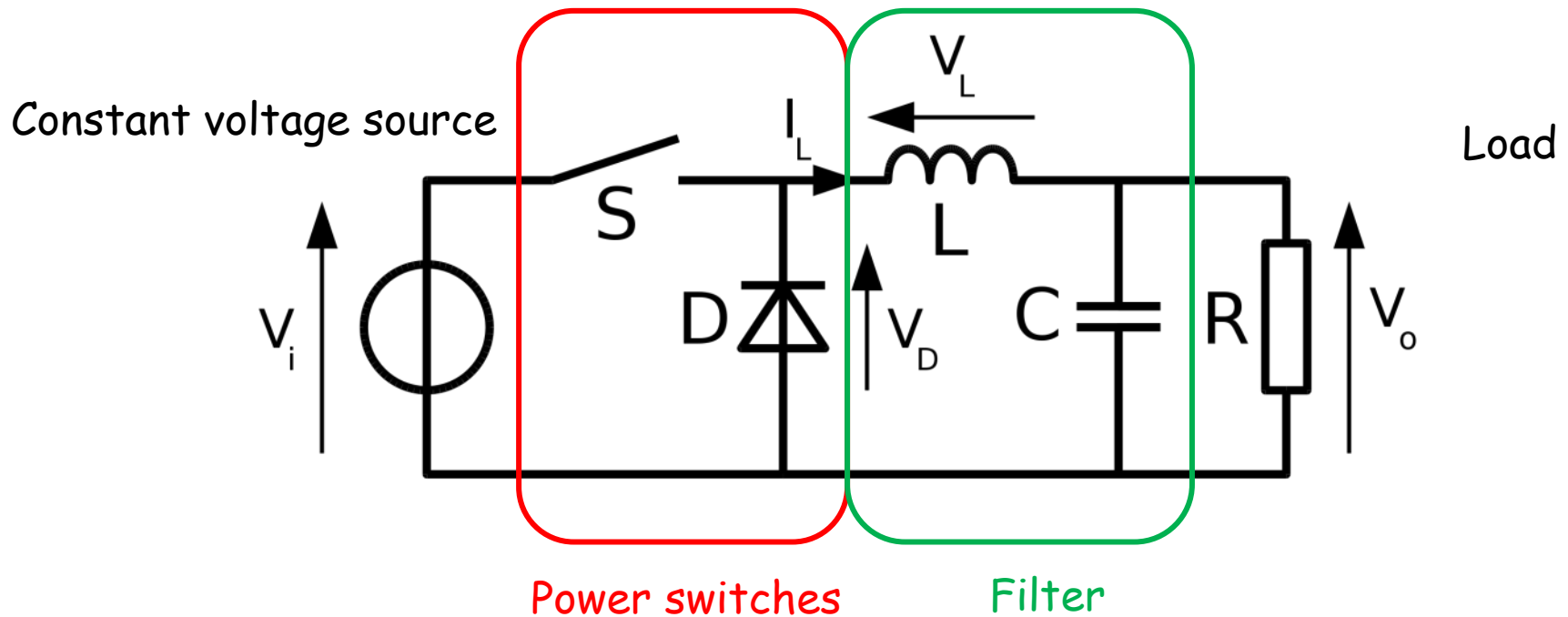


Power electronics basic concept

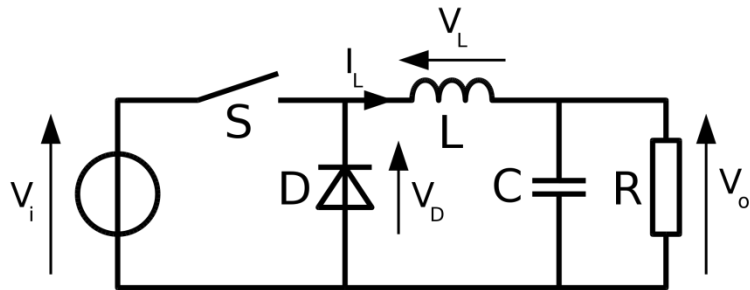The switch S is switched ON during a short period which is repeated periodically.




$$\langle V_o \rangle = T_{on}/T \times V_i$$

$$V_{out} = a \times V_i$$



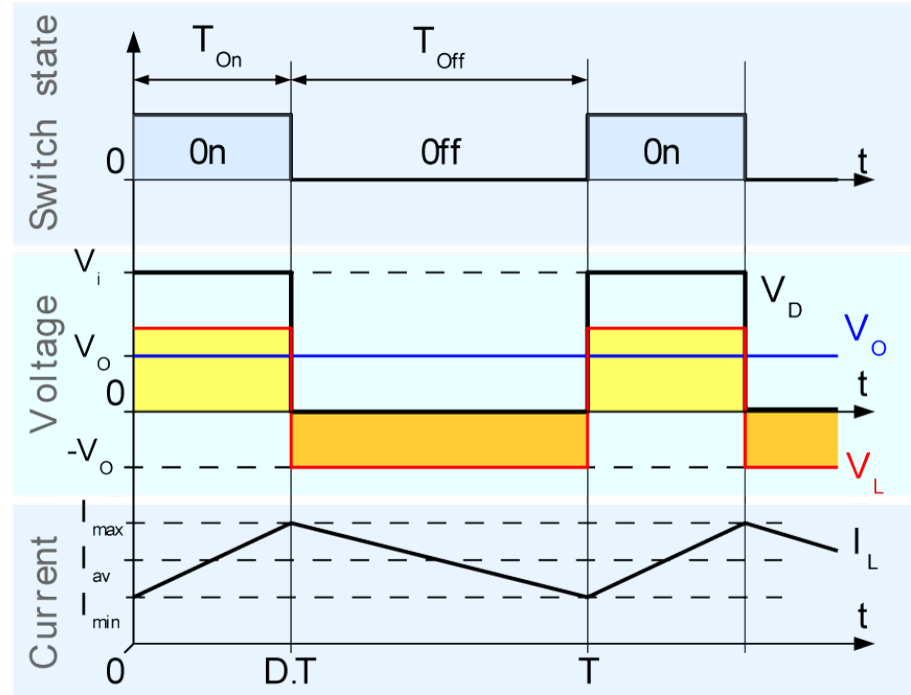


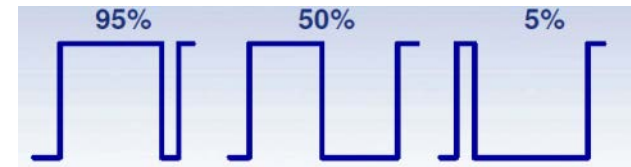The output voltage can be controlled by playing with the duty cycle a .



Power electronics basic concept

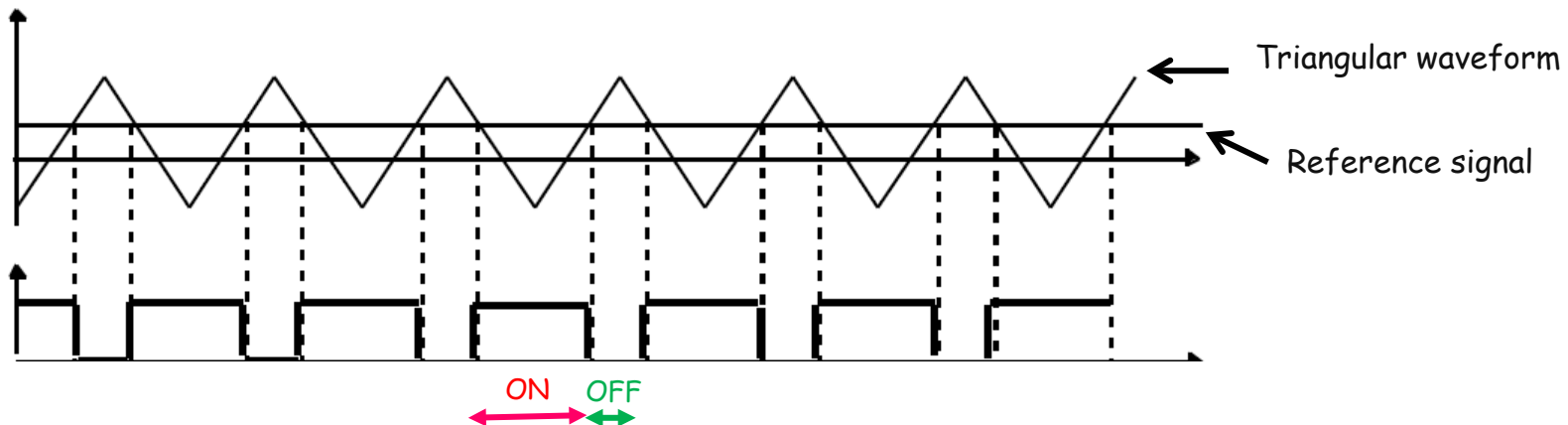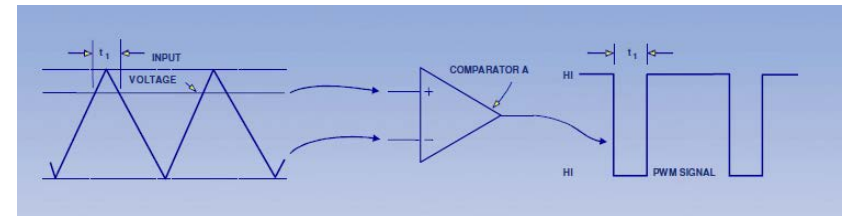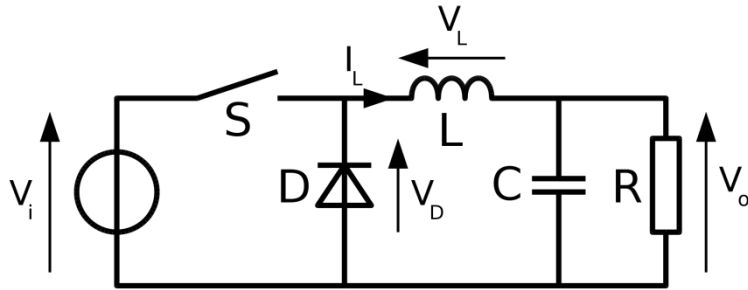Most of the time, PWM (Pulsed Width Modulation) technique is used to control the switches. A triangular waveform is compared to a reference signal, which generates the PWM command of the switch.





Topologies based on IGBT

The magnets need DC current.

The magnet power supplies are AC/DC.




The topologies are with multi-stages of conversion.

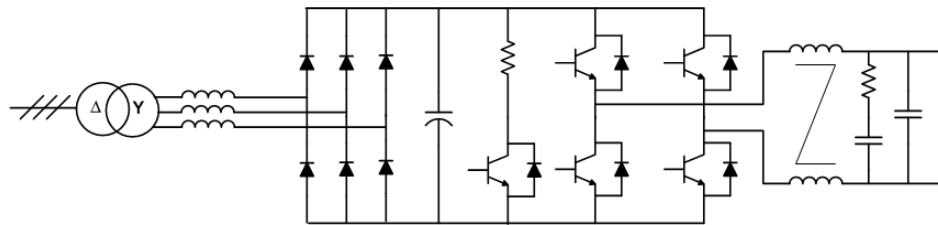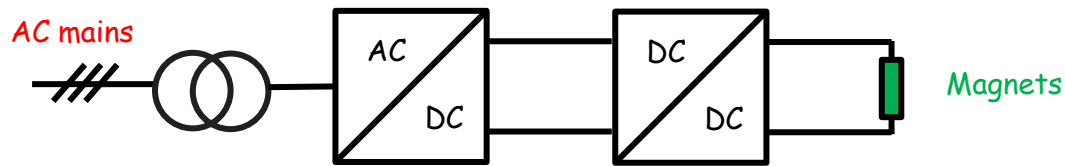The magnets need a galvanic isolation from the mains: cases with 50Hz transformer





Switch-mode converters

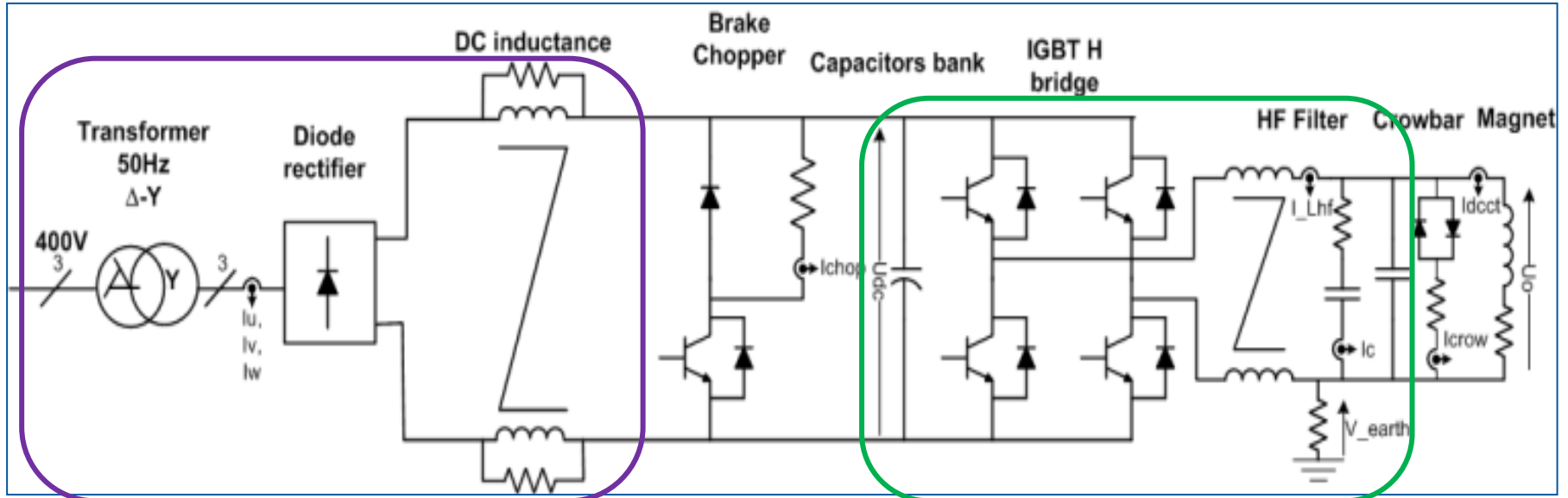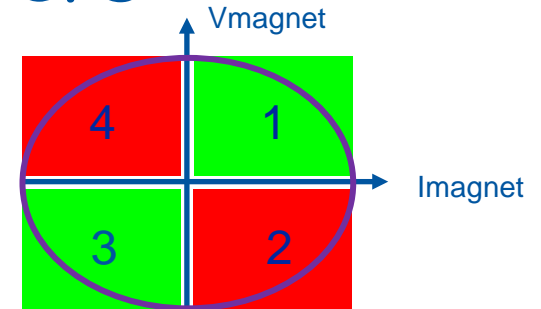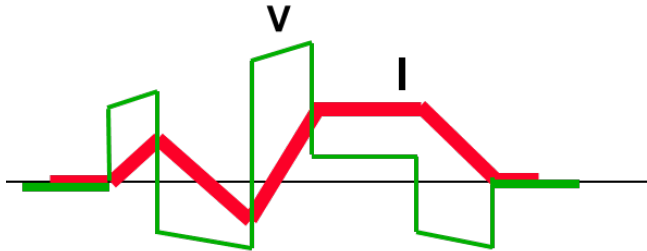Example: PS converter: PR.WFNI, $\pm 250\text{A}/\pm 600\text{V}$



50Hz AC/DC stage



High-frequency DC/DC stage

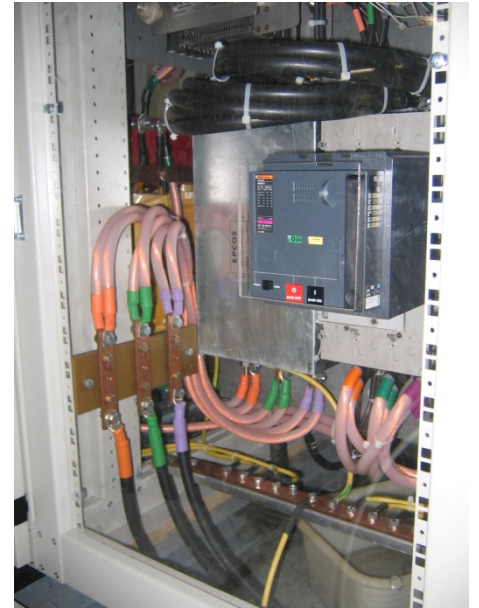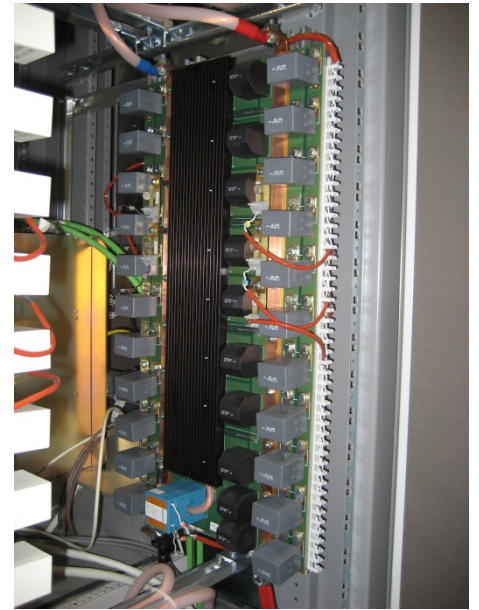

Transformer technologies



Two technologies are used for power transformers:
laminated magnetic core (like magnet):

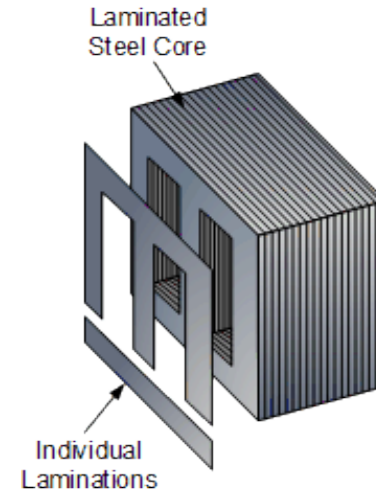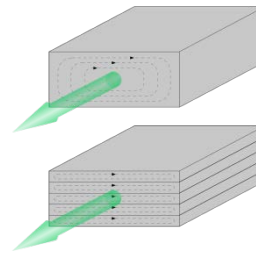- 50Hz technology
- High field (1.8T)
- Limitation due to eddy current
- Low power density
- High power range





Ferrite core (like kicker):

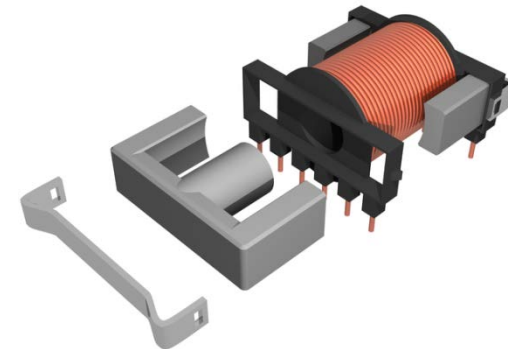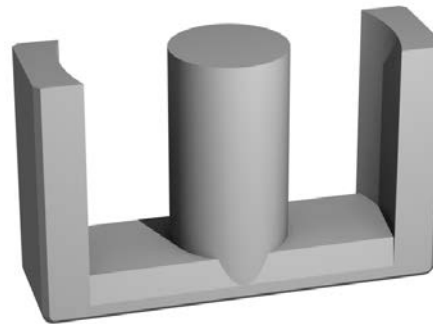- kHz technology
- Low field (0.3T)
- Nonconductive magnetic material, very low eddy current
- High power density
- Low power range (<100kW)






Topologies with HF transformer


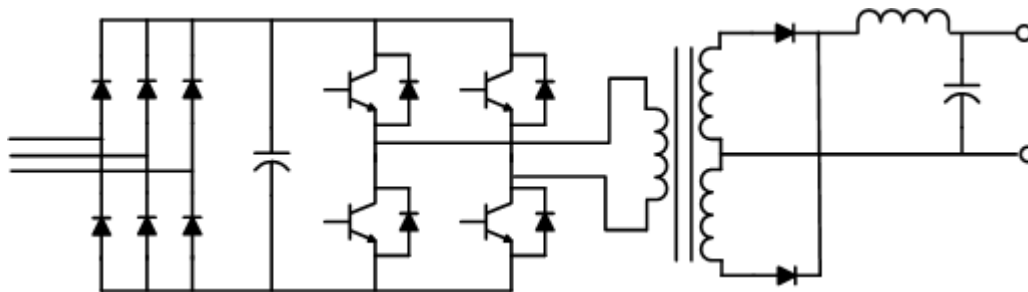
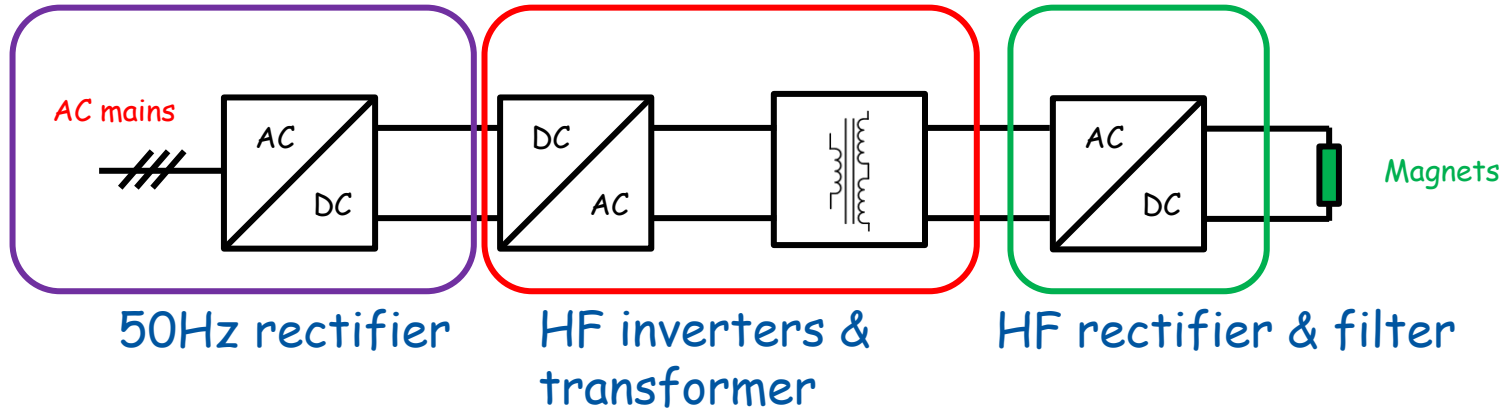
In this case, it is multi-stages converter with high-frequency inverters



Switch-mode converter with HF inverter

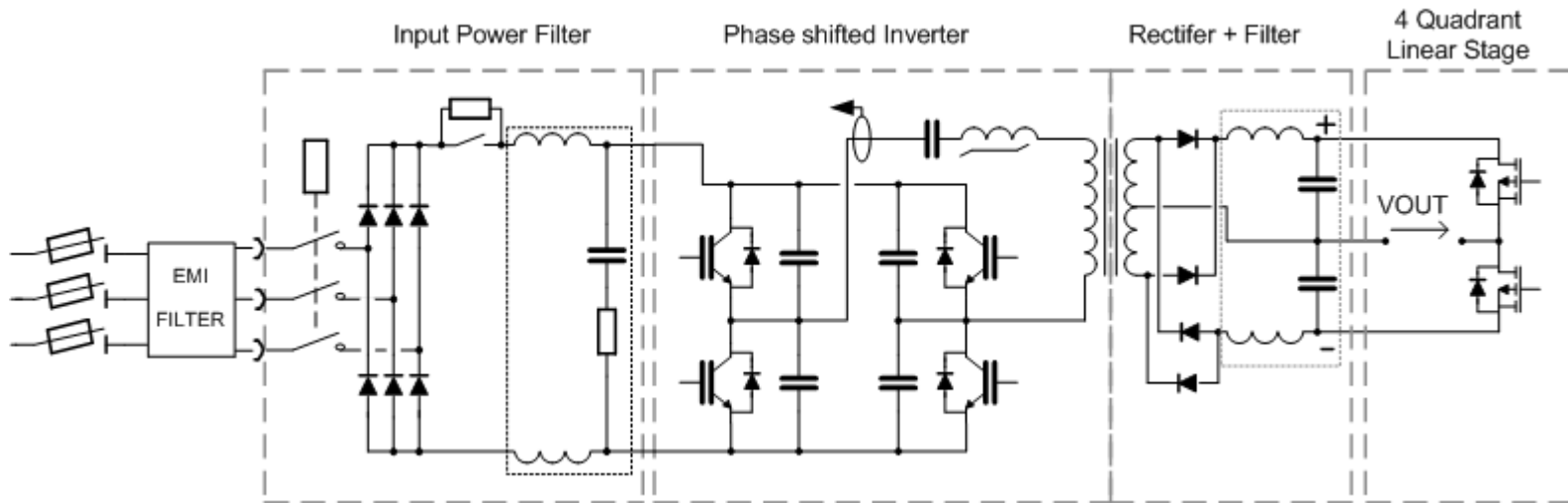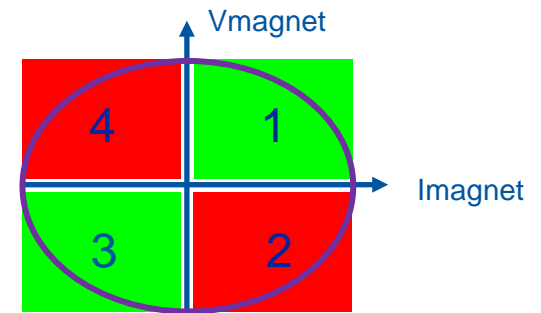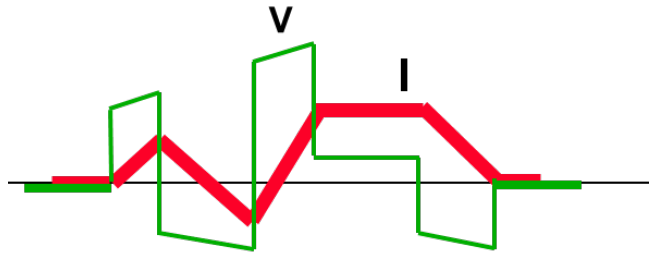
Example: LHC orbit corrector, $\pm 120\text{A}/\pm 10\text{V}$



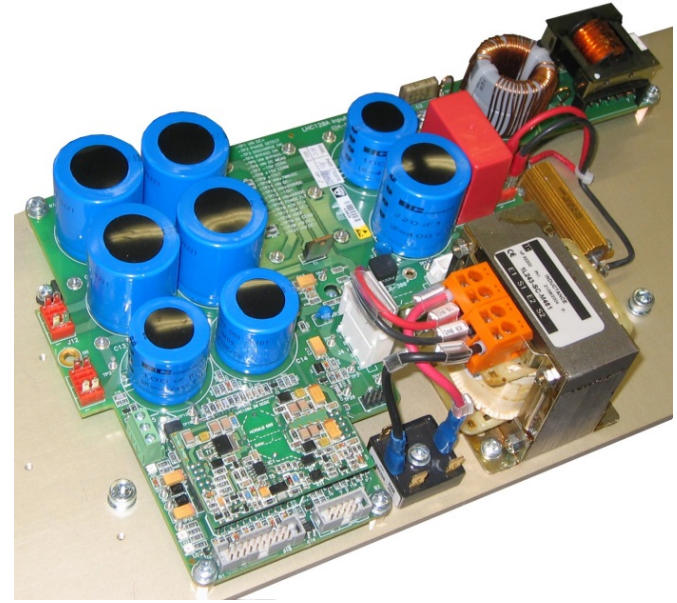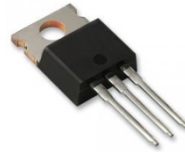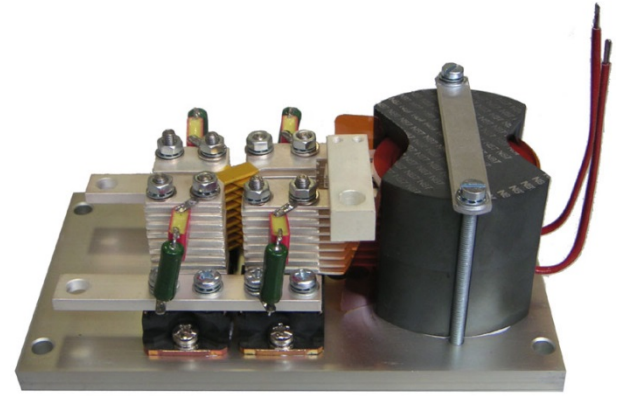

Converter association

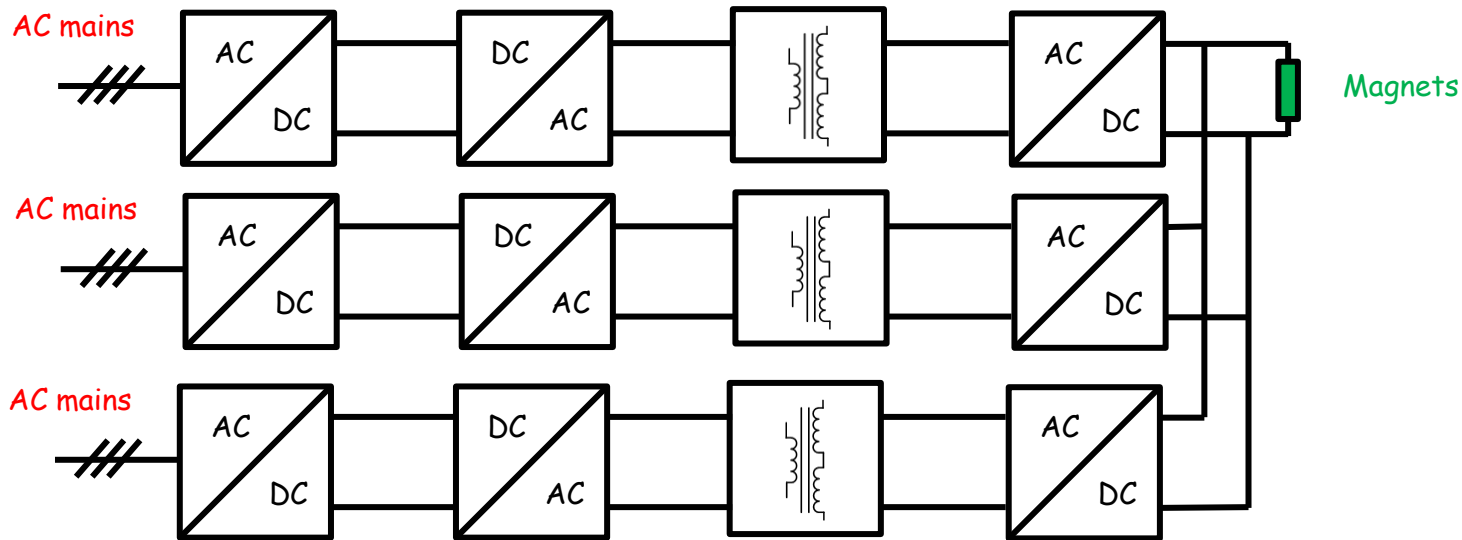When the power demand increases above the rating of the power semiconductor, the only solution is to build a topology with parallel or series connection of sub-system.





Parallel connection of sub-converters



Example: Atlas toroid magnet converter 20.5kA/18V



3.25kA/18V sub-converter

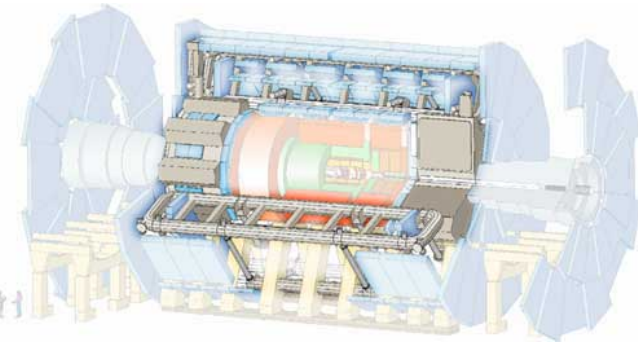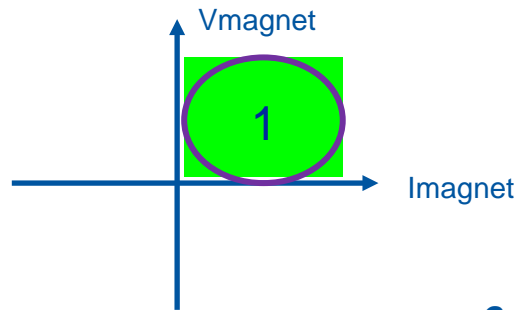



8 sub-converters in parallel

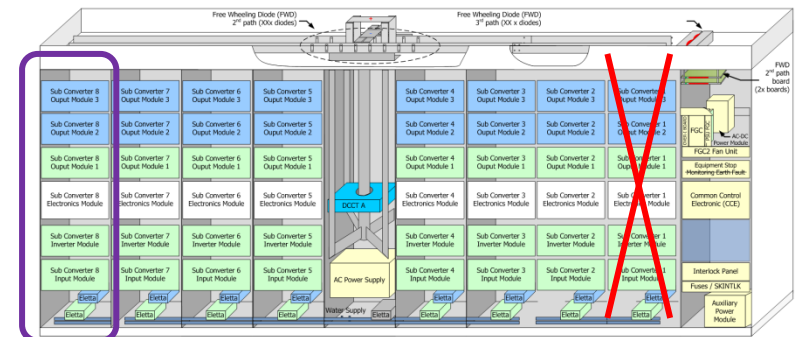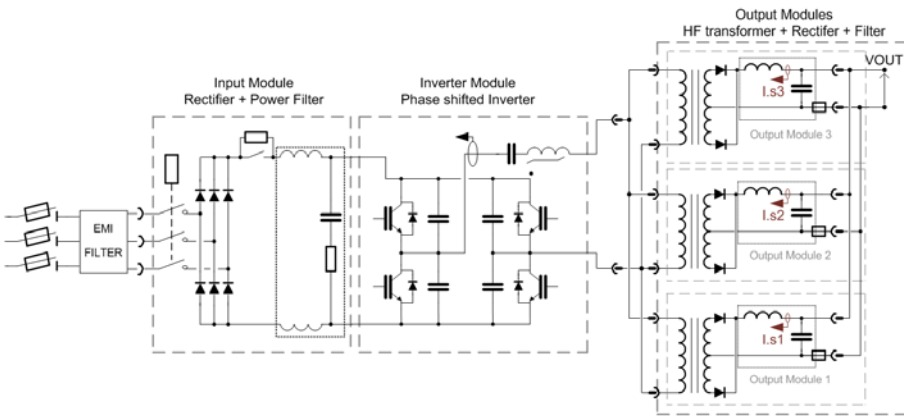

3.25kA/18V



Redundancy implementation, n+1 sub-converters

Can work with only n sub-converters

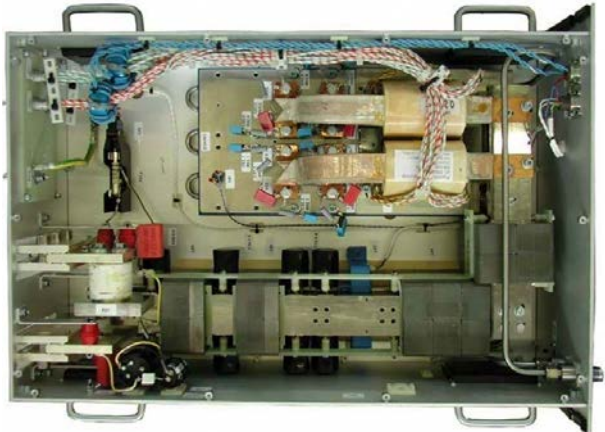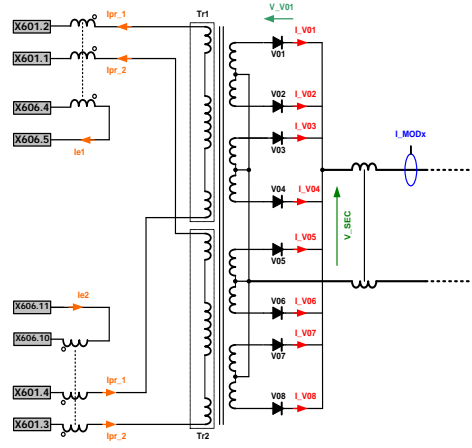


Parallel connection with thyristor rectifier

Example: Alice Dipole, 31kA/150V

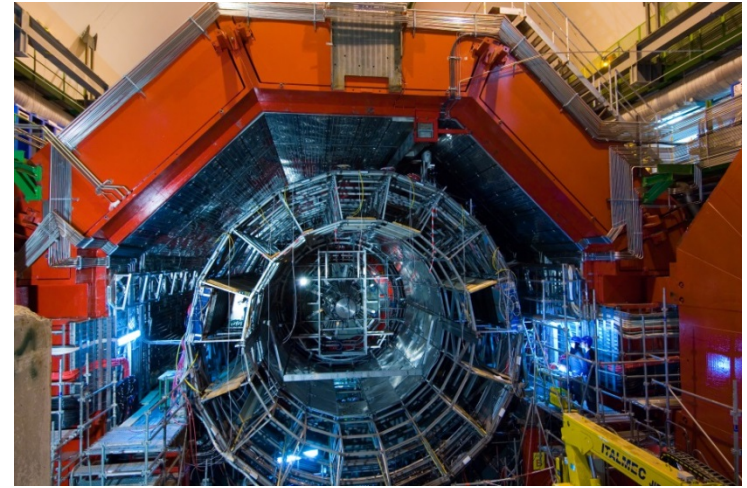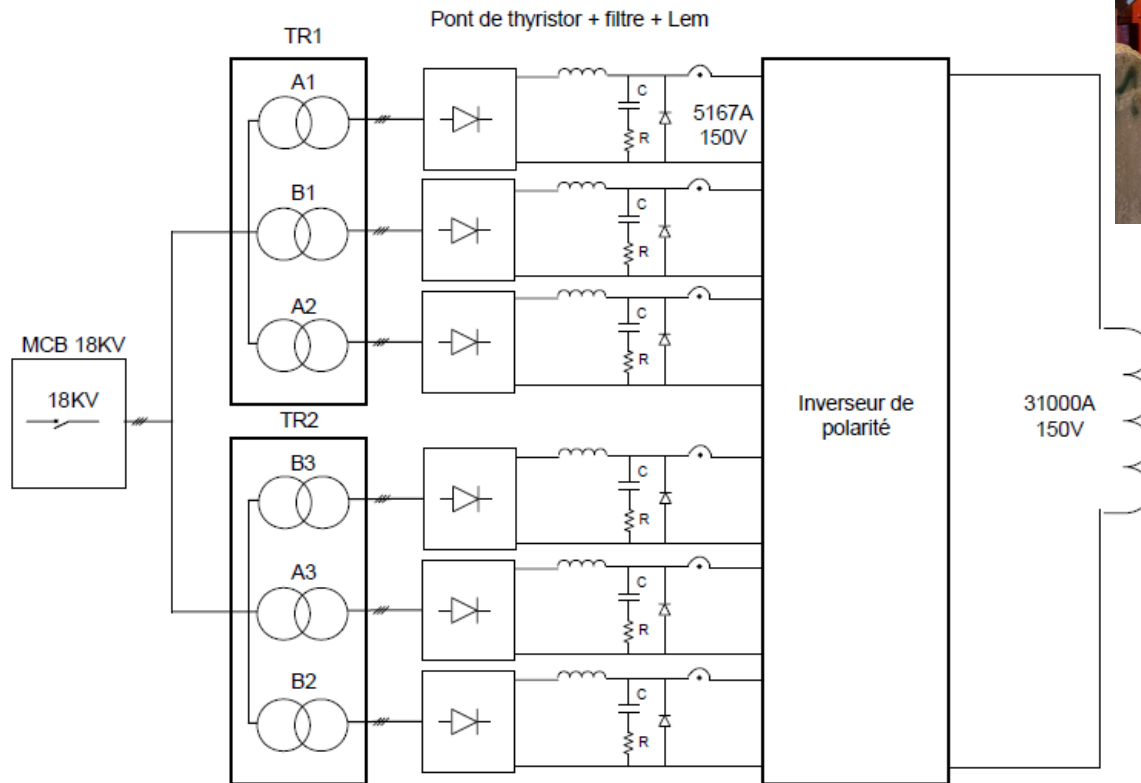



Series connection of sub-converters

Example: SPS dipole converter, 6kA/24kV

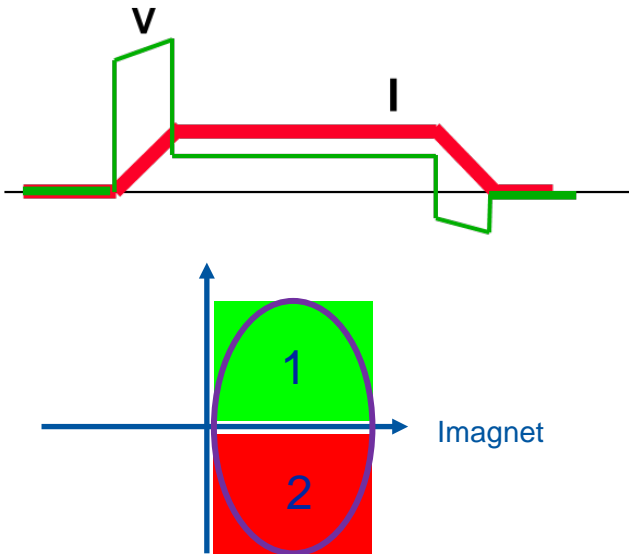

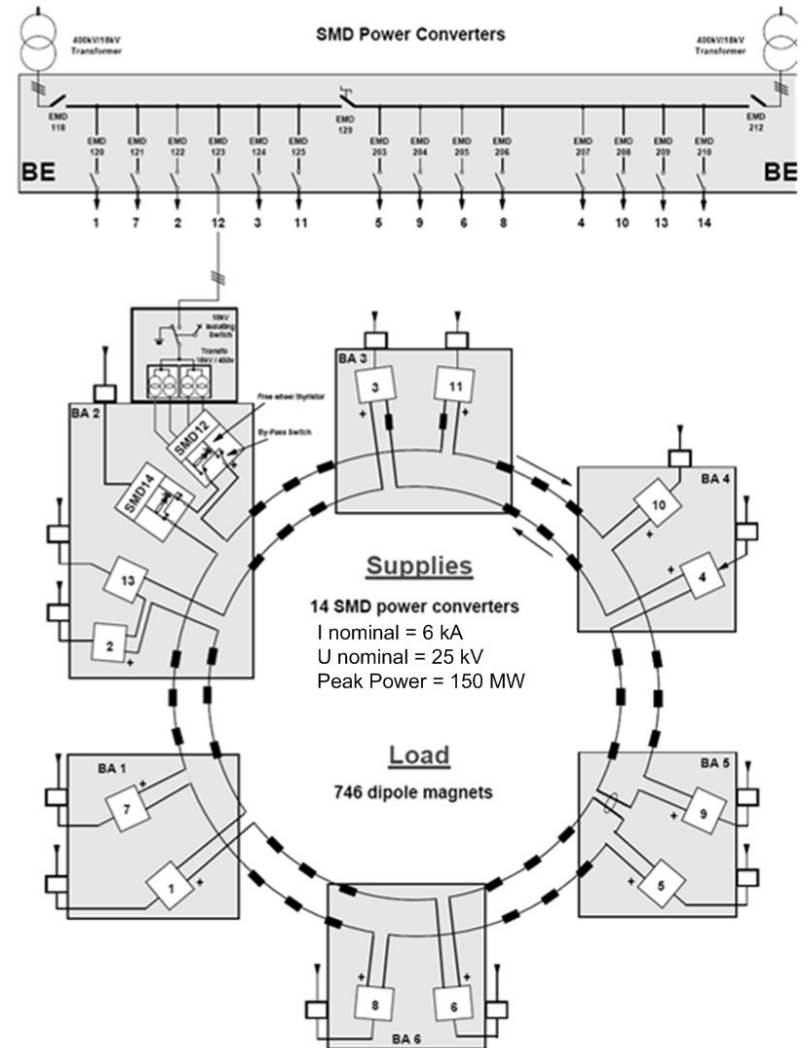12 converters in series between magnets.
Each converter gives 6kA/2kV.



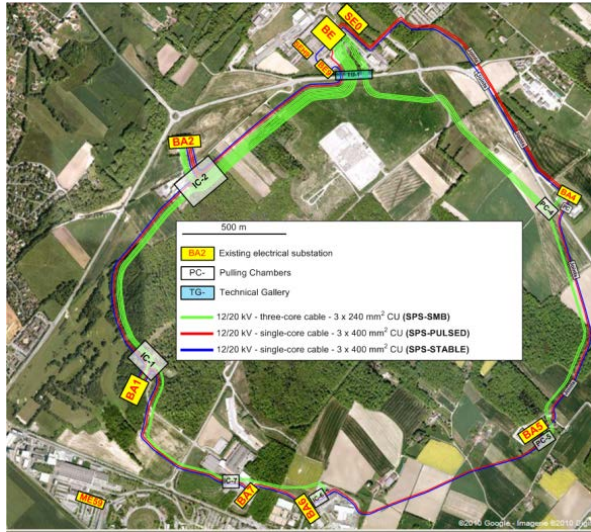


Nested circuits

Nested powering scheme is popular with accelerator physicists and magnet designers.

Allows association of different magnets or to correct local deviation over a long series of magnets.

Main reasons: saving on DC cables, current leads, lower power converter rating,...

Example, LHC inner triplet

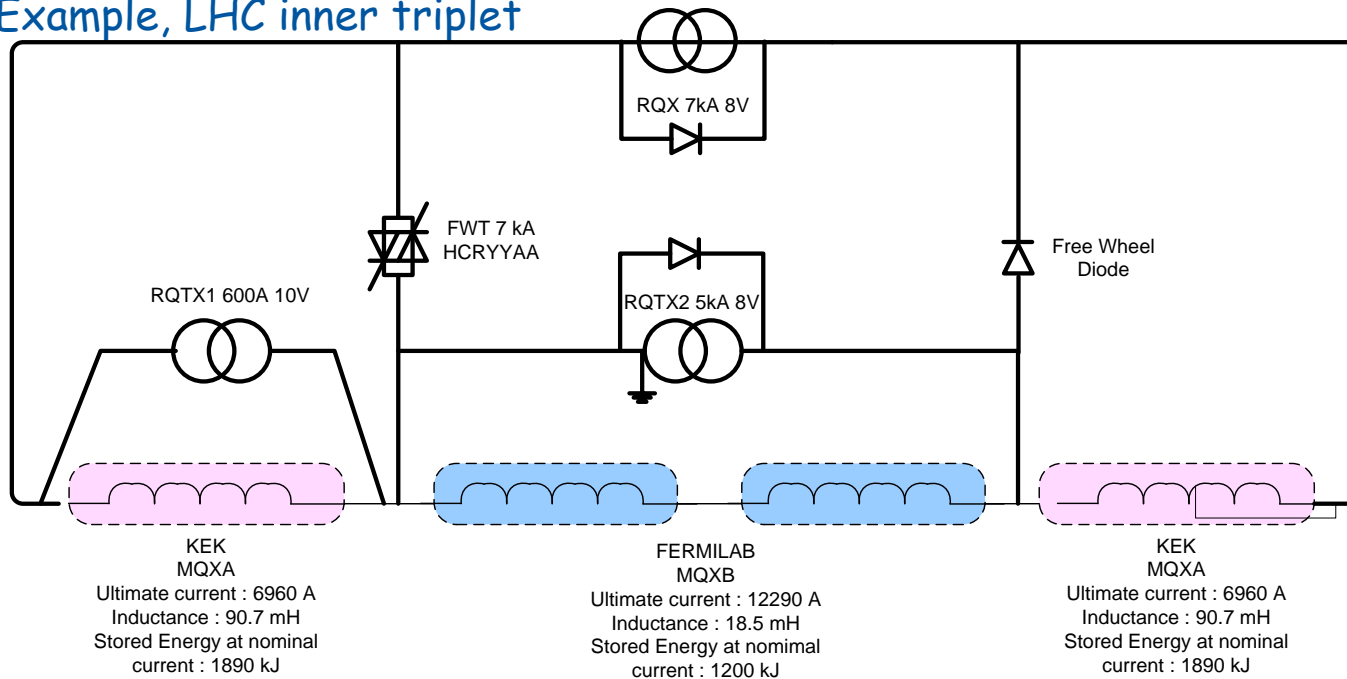

Nested circuits

Nested powering scheme is a nightmare for power engineers !!

Very complex control, it is like a car with many drivers having a steering wheel acting on only one wheel.



Coupled circuits

Nested circuits





Very difficult to operate and repair, long MTTR.

Reduce investment but decrease availability!


All converters have to talk each others.

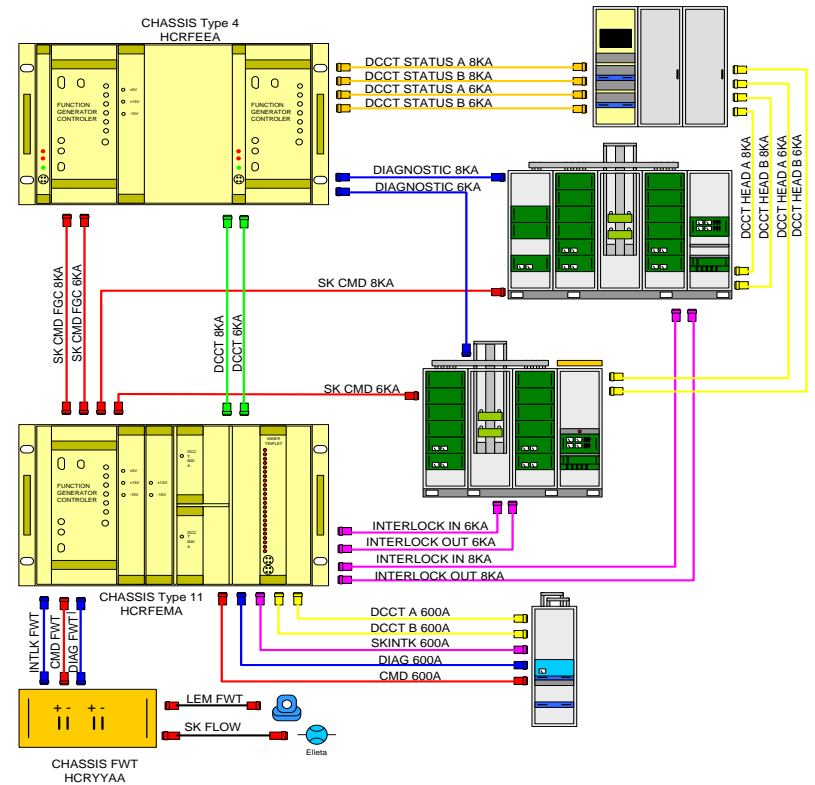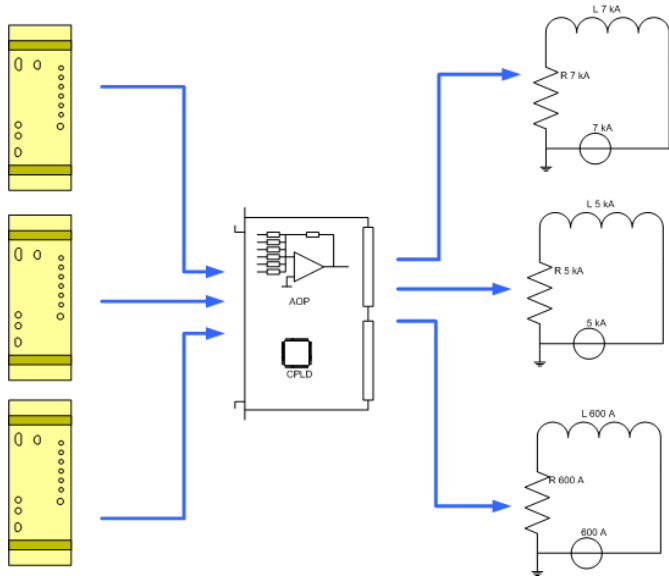Need a decoupling control to avoid fight between converters !



Nested circuits

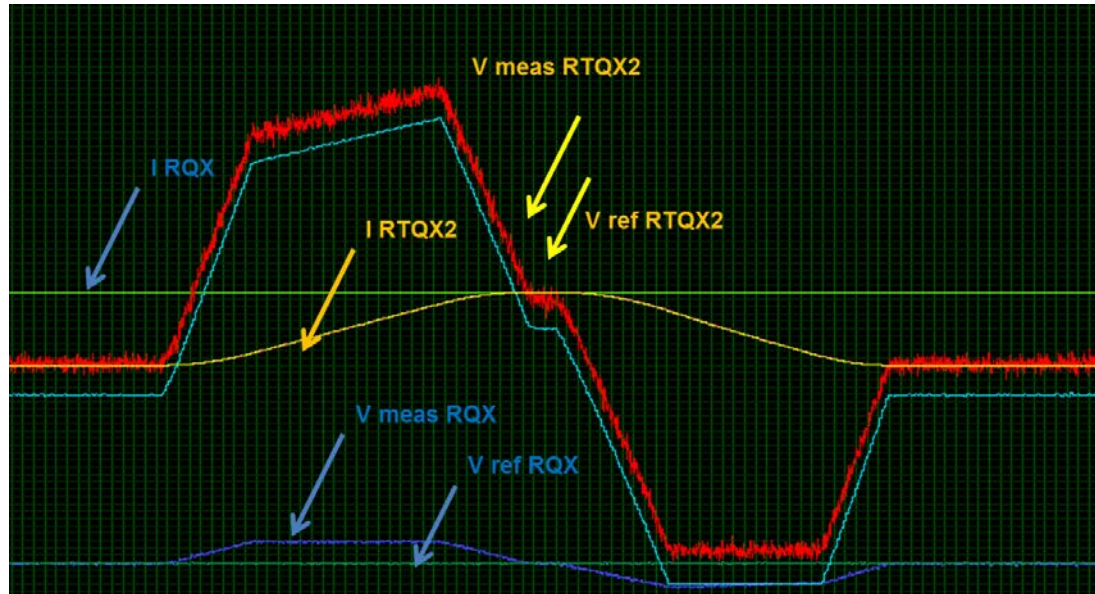Look at the current and voltage of RQX while RTQX2 current is changing!



Nested circuits aren't **RECOMMENDED** !

LHC inner triplet works perfectly well but MTTR is very high.


RHIC had many difficulties with nested circuits.

Energy management


Magnets need voltage to move their current:

$$V_{\text{magnet}}(t) = R_{\text{mg}} * I_{\text{mg}}(t) + L_{\text{mg}} * dI_{\text{mg}}(t)/dt$$

Example with the PS main magnets

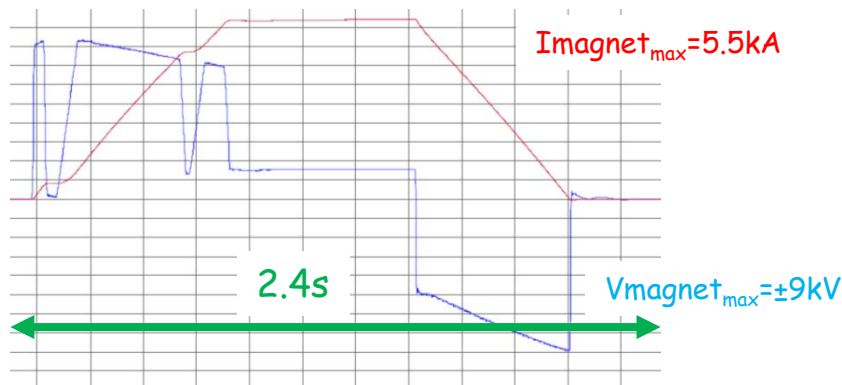

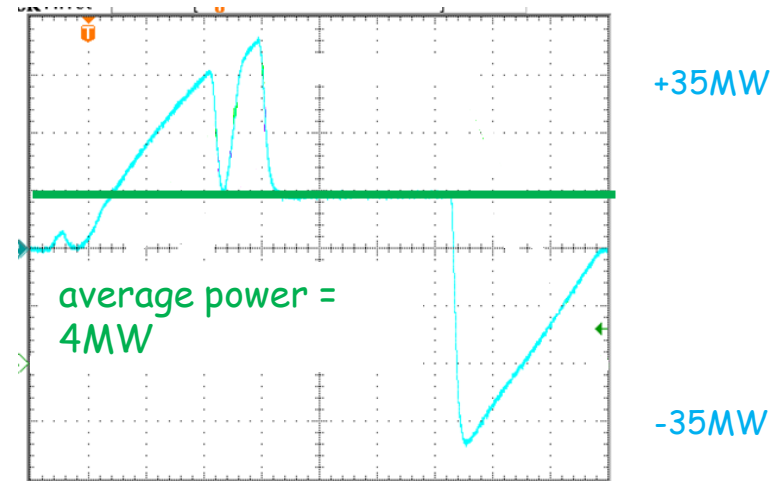Blue: U_{magnet} 1 kV / div
Red: I_{magnet} 500A / div



Light blue: Power_to_magnet 10 MW / div

$$\text{Power}(t) = I_{\text{magnet}}(t) \times V_{\text{magnet}}(t)$$

The peak power needed for the main magnets is $\pm 40 \text{ MW}$ with a dynamic of 1 MW/ms

The average power is only 4 MW !!!

The challenge: Power a machine which needs a peak power 10 times the average power with a very high dynamic !!!

New concept for energy management


The energy to be transferred to the magnets is stored in capacitors
 The capacitor banks are integrated in the power converter

- DC/DC converters transfer the power from the storage capacitors to the magnets.
- Four flying capacitor banks are not connected directly to the mains. They are charged via the magnets
- Only two AC/DC converters (called chargers) are connected to the mains and supply the losses of the system and of the magnets.

Patent

The global system with dedicated control has been filed as a patent application. European Patent Office, Appl. Nr: 06012385.8 (CERN & EPFL)


Flying capacitors

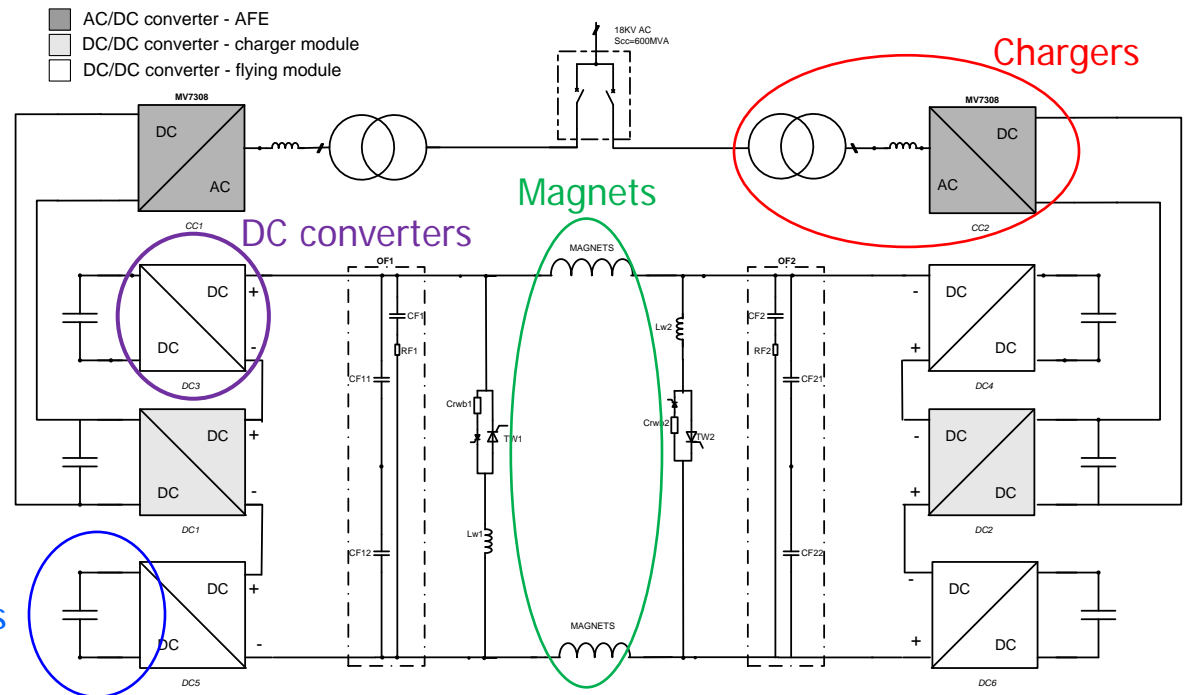

Energy management



Magnets current and voltage

Voltage and current of the magnets

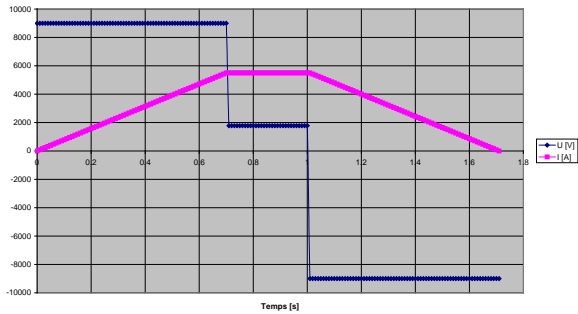


Stored magnetic energy

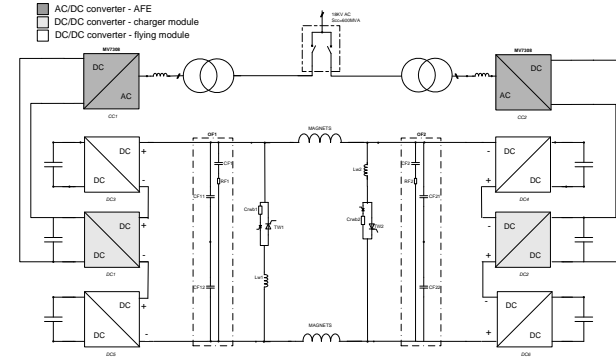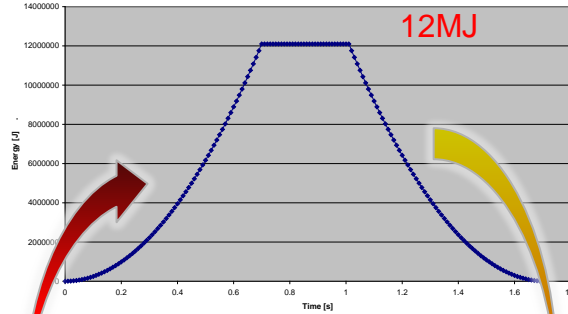Inductive Stored Energy of the magnets [J]




Power to the magnets

Active power of the magnets

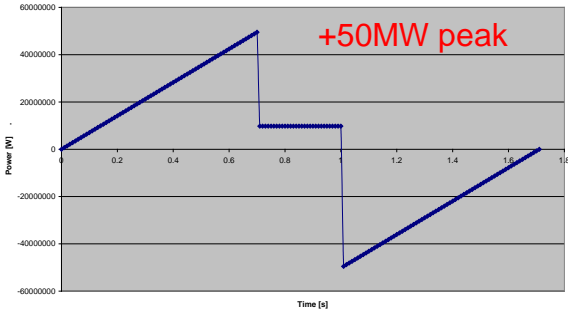


Capacitor banks voltage

Capacitors banks voltage

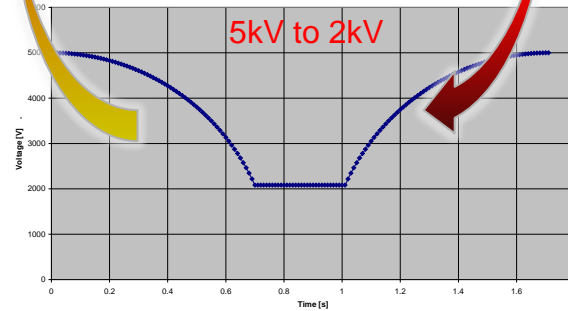

Power from the mains = Magnet resistive losses

Resistive Losses and charger power

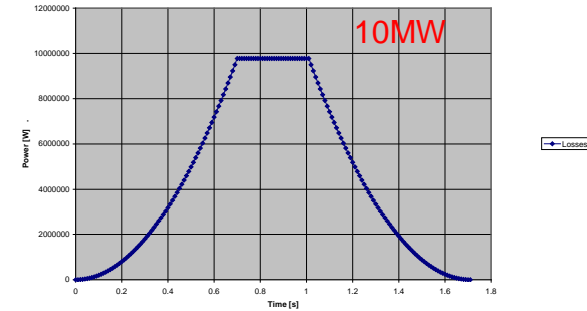

POPS: POver converter for the PS main magnets.

Energy management

Example: POPS 6kA/±10kV

Control room

Electrical room

Cooling tower

Power transformers

Capacitor banks



Energy management

Capacitor banks

- 5kV Dry capacitors
 - Polypropylene metalized self healing
 - Outdoor containers: 2.5m x 12m, 18 tons
 - 0.247F per bank, 126 cans
 - 1 DC fuse
 - 1 earthing switch
 - 3 MJ stored per bank
-
- 60 tons of capacitors divided in 6 capacitor banks making in total 18.5MJ
 - Up to 14MJ can be extracted during a cycle!
 - The capacitors represent 20% of the total system cost.




Energy management


Best optimization : Max power taken on the mains # magnet average power

Resistive losses of the magnets

Power demand on the mains

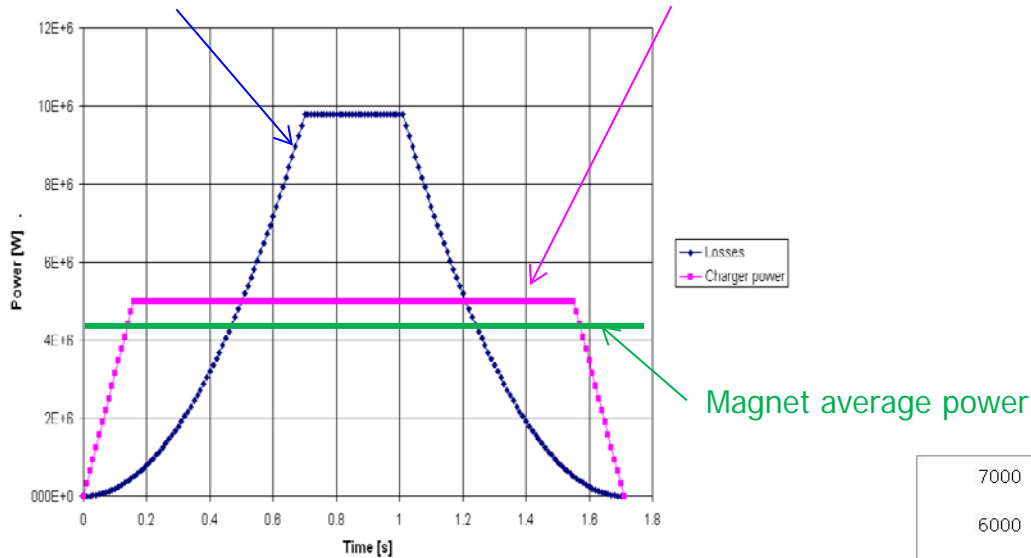


POPS energy management

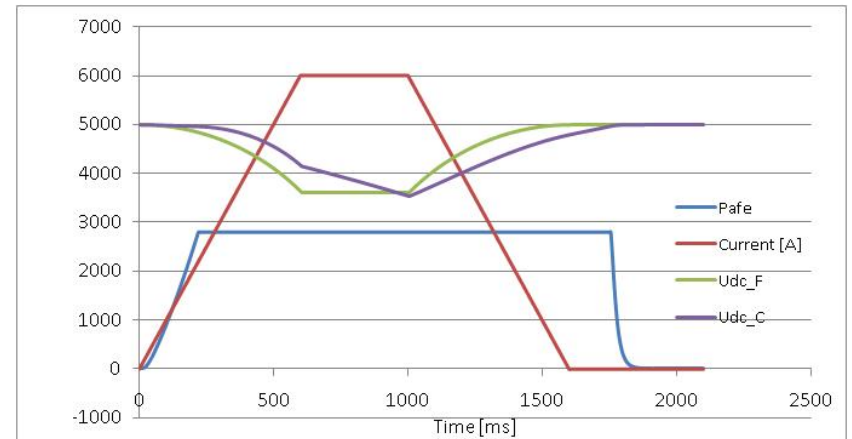

Discharged converter

Synchrotrons

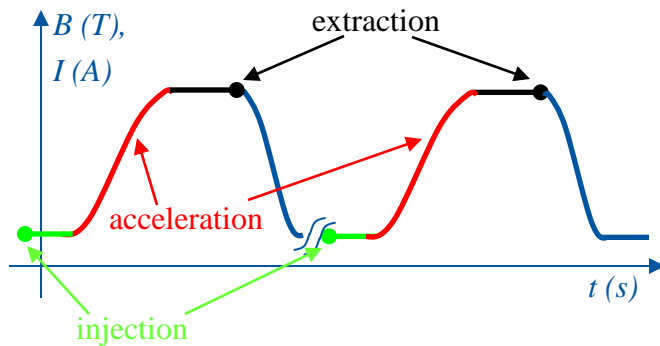
Beam is injected, accelerated and extracted in several turns



Rise and fall time < few ms




Linac's and transfer lines

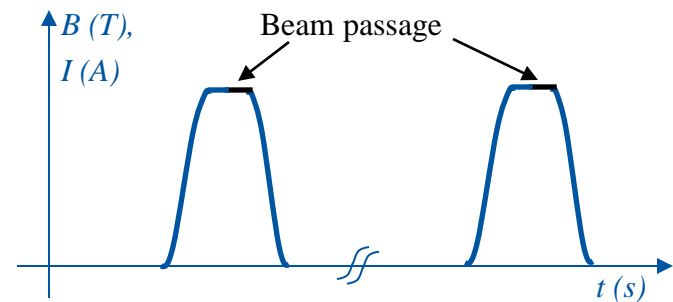Beam is passing through in one shot, with a given time period;




Direct Energy transfer from mains is not possible:
Intermediate storage of energy
Peak power : could be > MW
Average power kW

Discharged converter

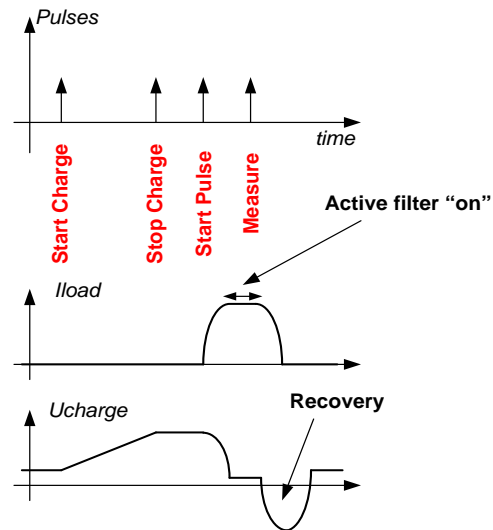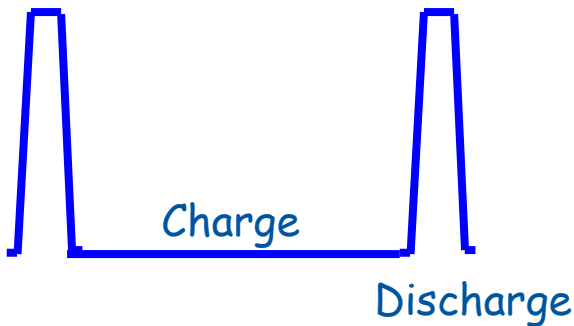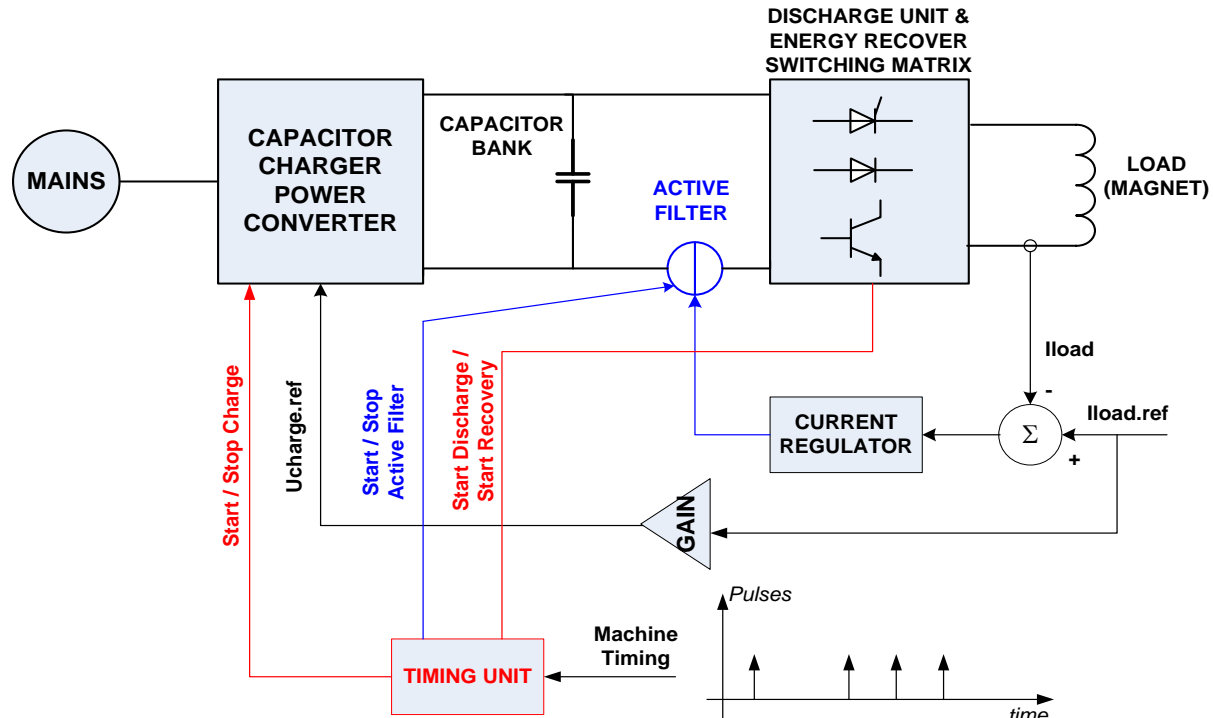


Example of LINAC4 Klystron modulator


Specification	symbol	Value	unit
Output voltage	V_{kn}	110	kV
Output current	I_{out}	50	A
Pulse length	$t_{rise}+t_{set}+t_{flat}+t_{fall}$	1.8	ms
Flat-Top stability	FTS	<1	5
Repetition rate	$1/T_{rep}$	2	Hz

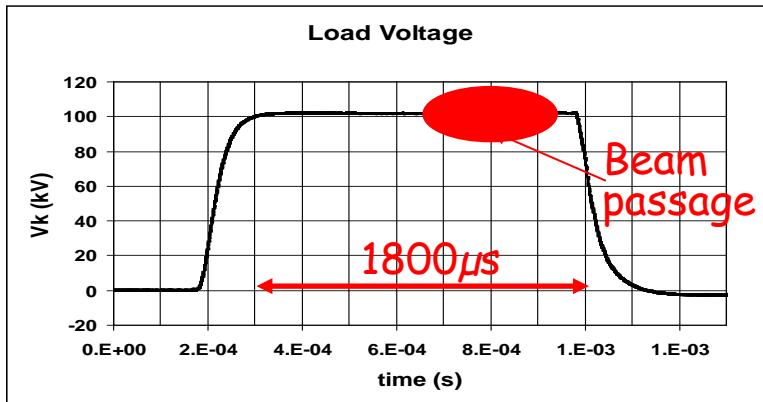

Peak power : 5.5MW
Average power: 20kW

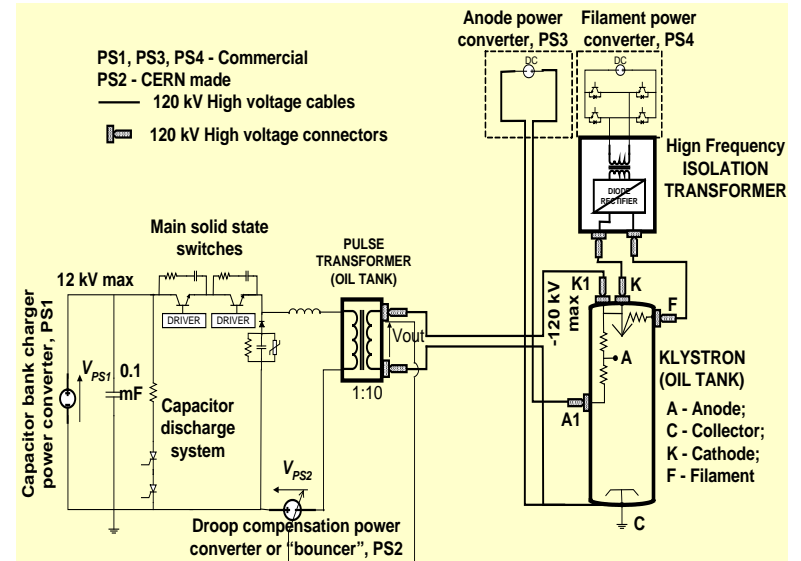

Power supply control

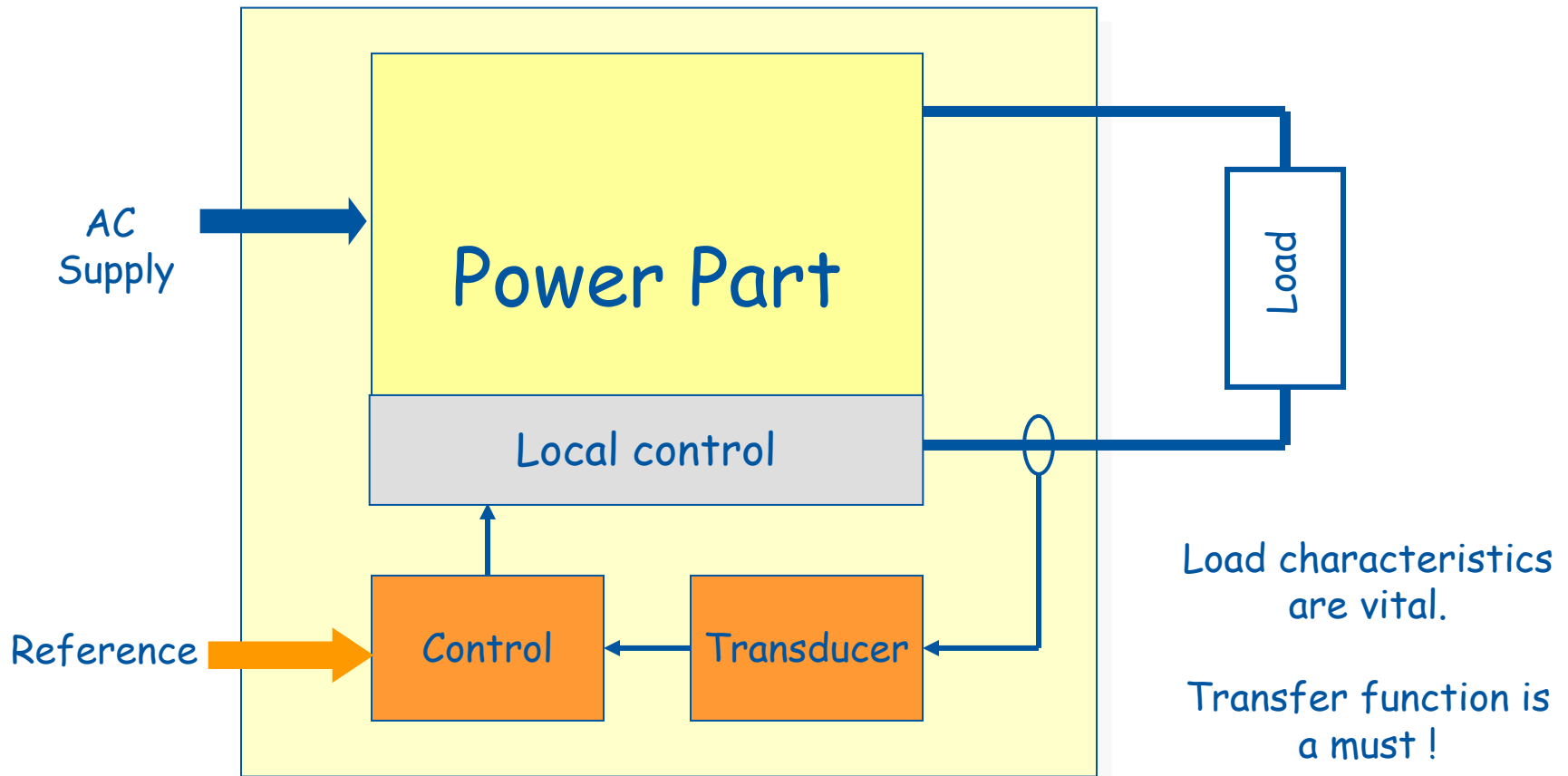

Power supply control

The power supply are controlled by the global control system.

They need to be synchronized => Timing


Locally, a fieldbus (must be deterministic) is used to communicate with a gateway,

WORLDFIP in the LHC


ETHERNET for LINAC4

In each power supply, an electronic box (FGC) manages the communication, the state machine and do the current control.

Real time software is implemented.

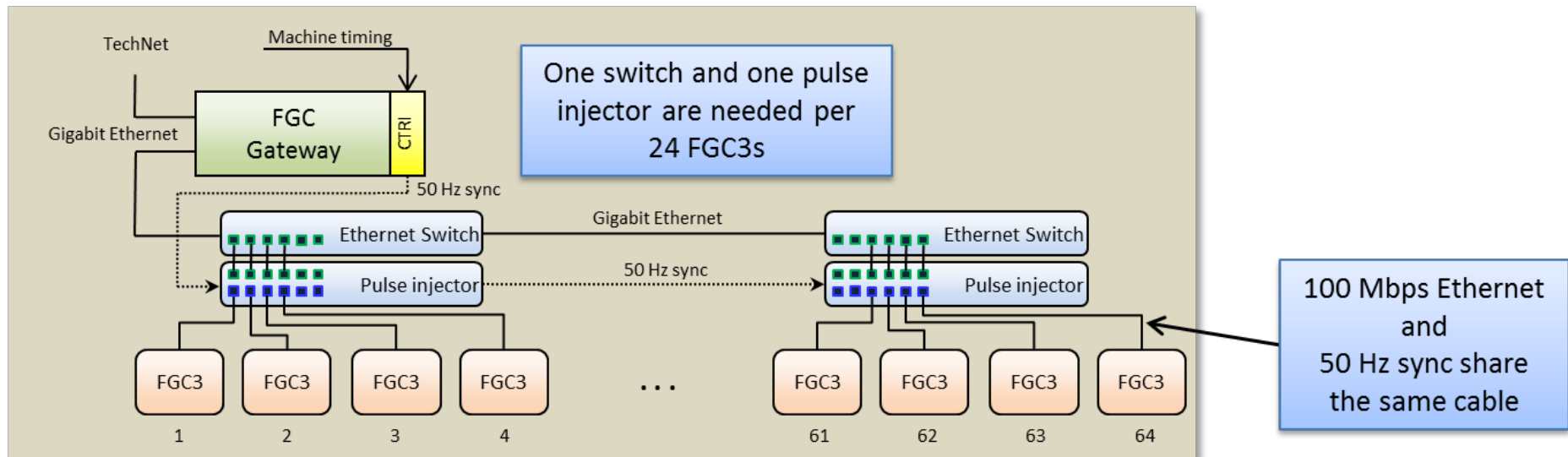

Power supply control

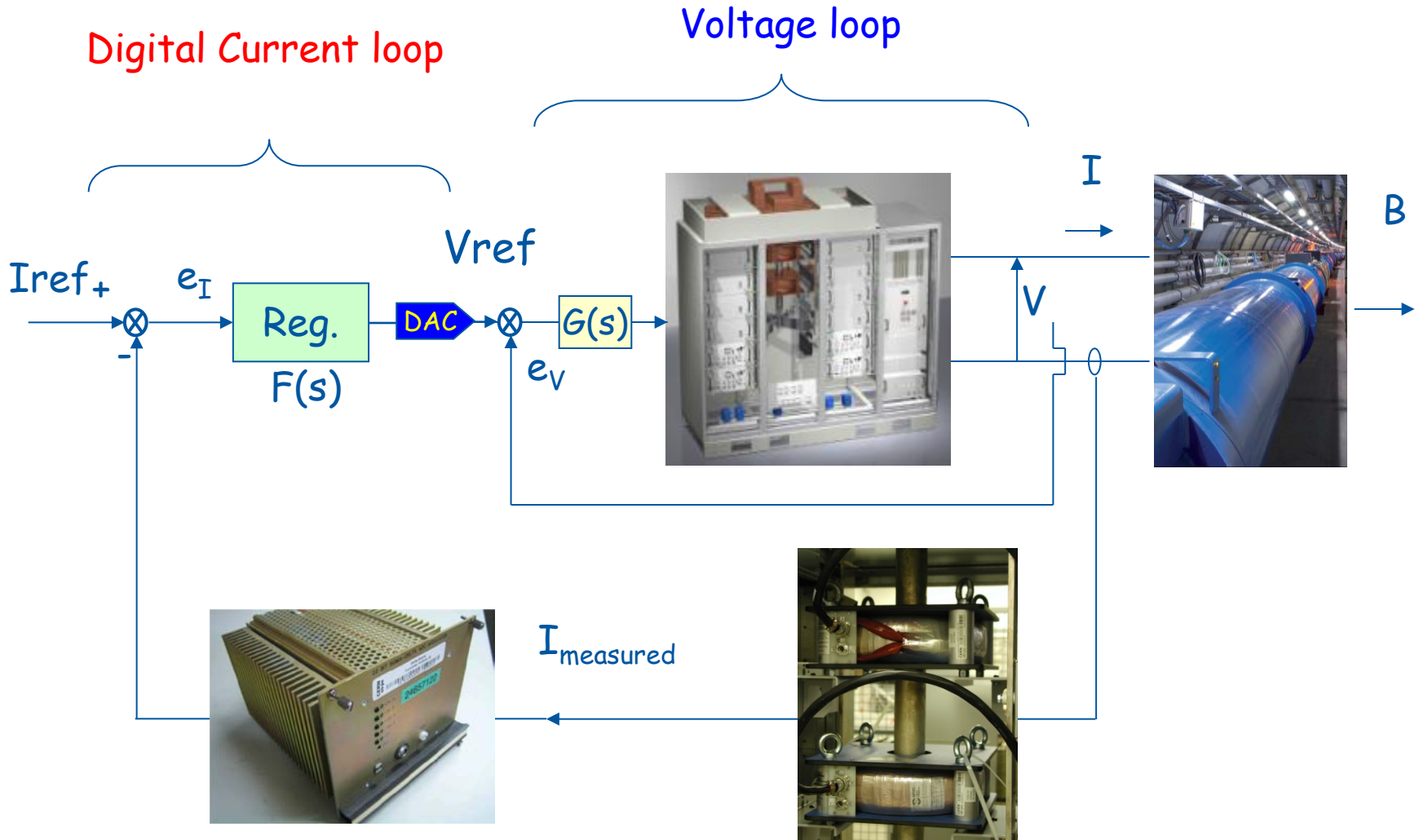


High-precision definition

Accuracy

The closeness of agreement between a test result and the accepted reference value. (ISO)




Reproducibility

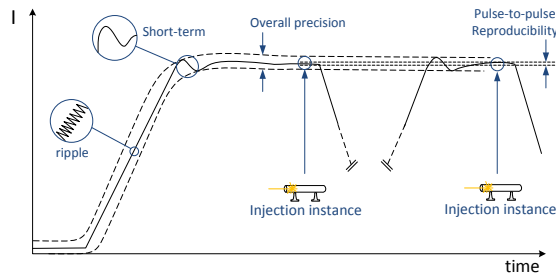Uncertainty when returning to a set of previous working values from cycle to cycle of the machine.



Stability

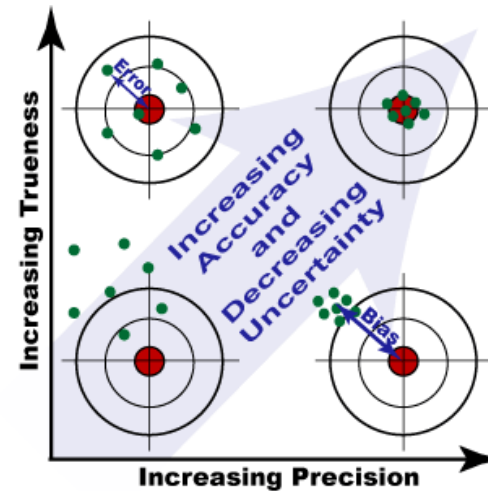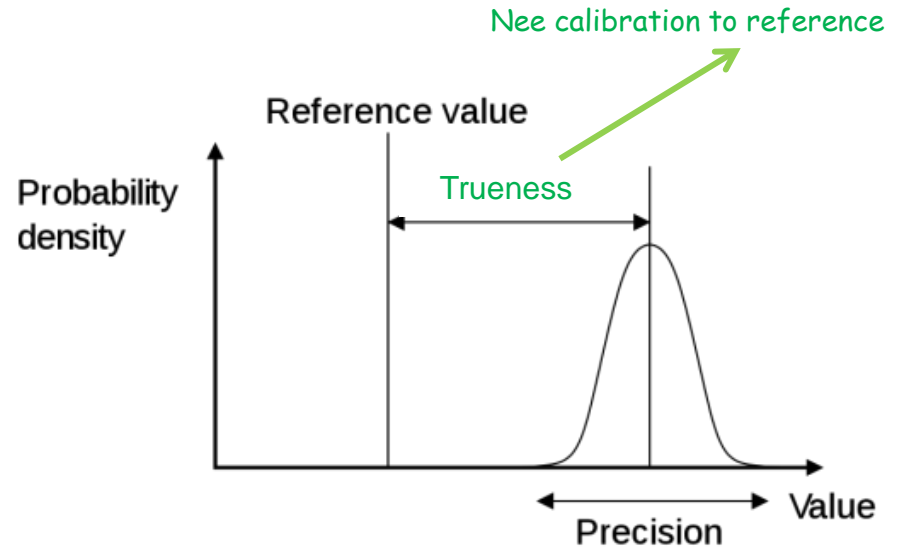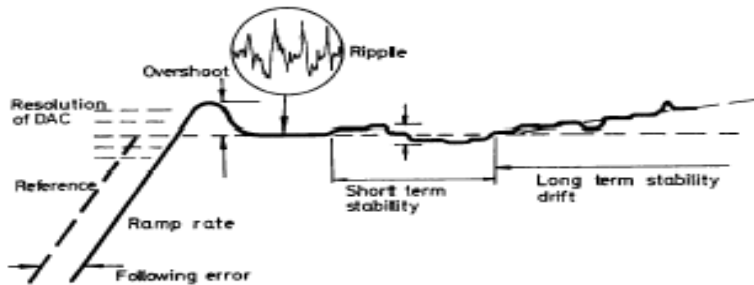Maximum deviation over a period with no changes in operating conditions.



Accuracy characterisation

The term Accuracy is a qualitative concept, used to describe the quality of a measurement. At CERN (and elsewhere) a measurement's systems capability is often characterized in terms of Gain and Offset errors, Linearity, Repeatability, Reproducibility and Stability.

Linearity:

Difference in the systematic error of a measuring device, throughout its range.

Gain and Offset errors:


They are systematic errors that relate to the trueness of a measurement.

The offset error refers to the systematic error at zero and the gain error to the systematic error at full scale.

Stability:






Measurement of the change in a measurement system's Systematic errors with time. We can more specifically refer to Gain Stability or Offset Stability.

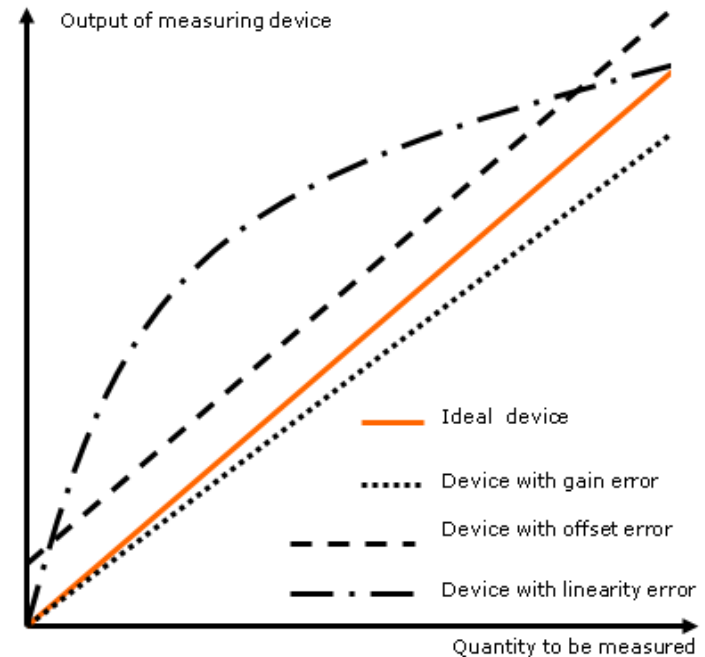Noise can also be seen as a measurement of a device's stability, although normally the term stability is used only for the low frequency range (\leq Hz).




<http://te-epc-lpc.web.cern.ch/te-epc-lpc/sensors/definitions.stm>

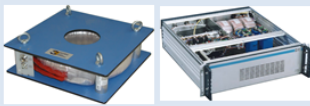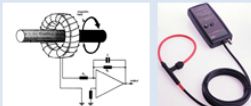
Current measurement technologies

	DCCTs	Hall effect	CTs	Rogowsky	Shunts
					
Principle	Zero flux detection	Hall effect	Faraday's law	Faraday's law	Ohm's law
Output	Voltage or current	Voltage or current	Voltage	Voltage	Voltage
Accuracy	Best devices can reach a few ppm stability and repeatability	Best devices can reach 0.1%	Typically not better than 1%	Typically %, better possible with digital integrators	Can reach a few ppm for low currents, <% for high currents
Ranges	50A to 20kA	hundreds mA to tens of kA	50A to 20kA	high currents possible, up to 100kA	From <mA up to to several kA
Bandwidth	DC ..kHz for the higher currents, DC..100kHz for lower currents	DC up to couple hundred kHz	Typically 50Hz up to a few hudreds of kHz	Few Hz possible, up to the MHz	Up to some hundreds of kHz with coaxial assemblies
Isolation	Yes	Yes	Yes	Yes	No
Error sources	<p>Magnetic (remanence, external fields, centering)</p> <p>Burden resistor (thermal settling, stability, linearity, tempco)</p> <p>Output amplifier (stability, noise, CMR, tempco)</p>	<p>Magnetic</p> <p>Burden resistor</p> <p>Output amplifier</p> <p>Hall sensor stability (tempco, piezoelectric effect)</p>	<p>Magnetic (remanence, external fields, centering, magnetizing current)</p> <p>Burden resistor</p>	<p>Magnetic</p> <p>Integrator (offset stability, linearity, tempco)</p>	<p>Power coefficient, tempco, ageing, thermal voltages</p>


High-precision Current measurement chain

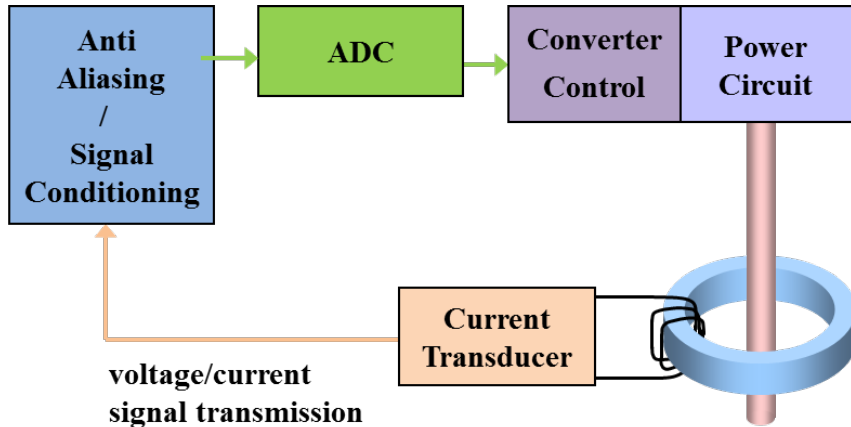


Precision amplifier and burden

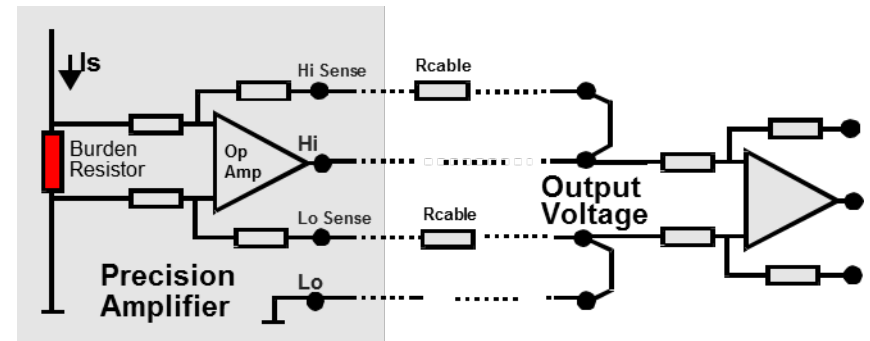

Signal conditioning and filtering

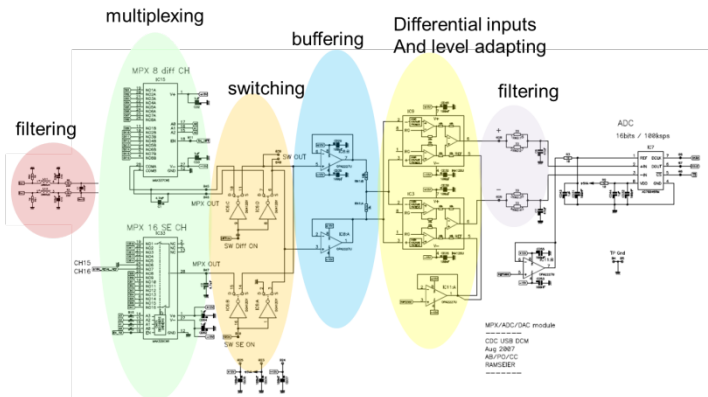

High-resolution ADC

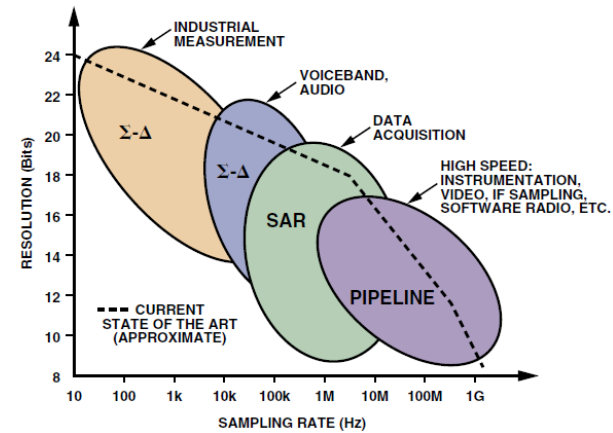

LHC class specification

Converter category	Accuracy Class	½ hour stability	24h stability	1 year stability
Main Dipoles	Class 1	3	5	50
Main quadrupoles	Class 1	3	5	50
Inner Triplets	Class 1	3	5	50
Separation dipoles, Insertion quadrupoles	Class 2	5	10	70
600A multipole correctors	Class 3	10	50	200
120A orbit correctors	Class 4	50	100	1000
60A orbit correctors	Class 4	50	100	1000



LHC class 1 DCCT



13kA DCCT
Magnetic Head



13kA DCCT
Electronics

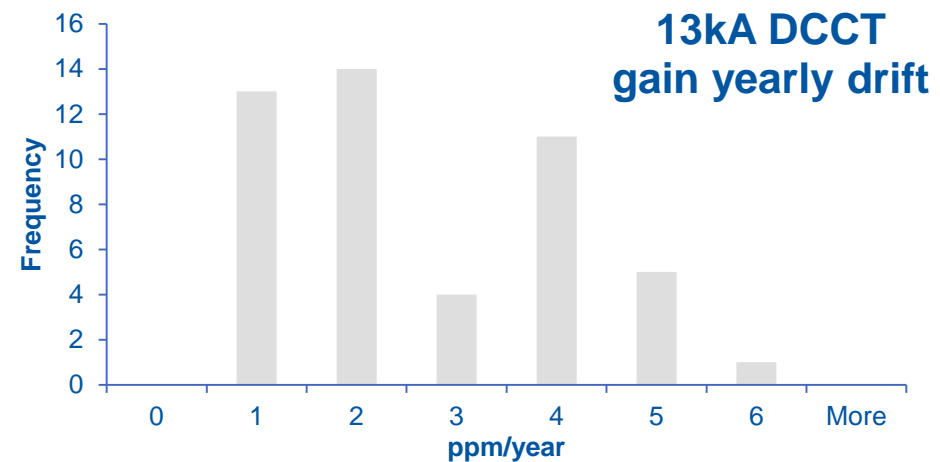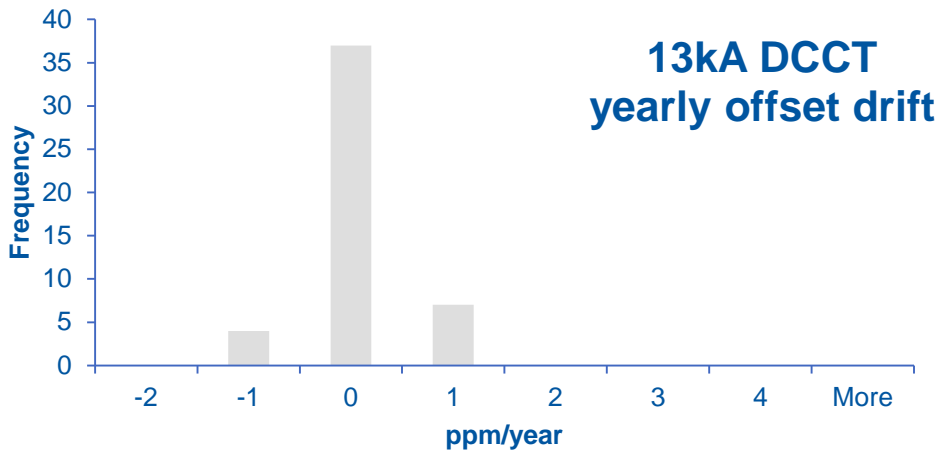



DCCT specification

Gain drift 1 year	5 ppm
Offset drift 1 year	5 ppm

LHC class 1 ADC



*The CERN 22
bit Delta
Sigma ADC*

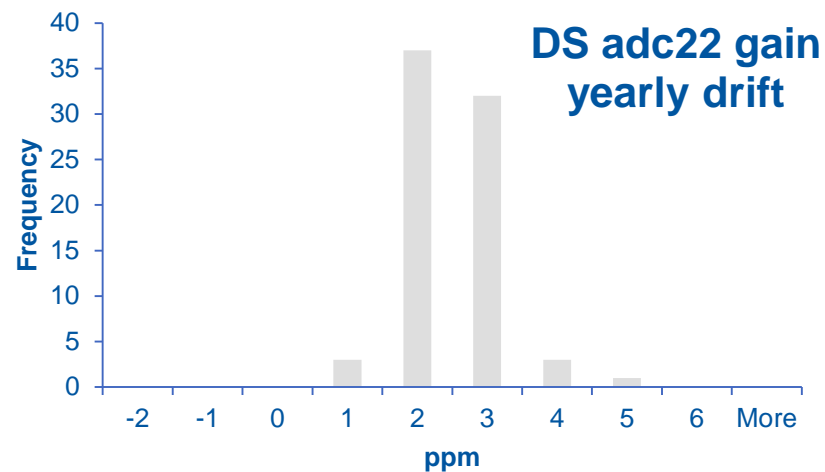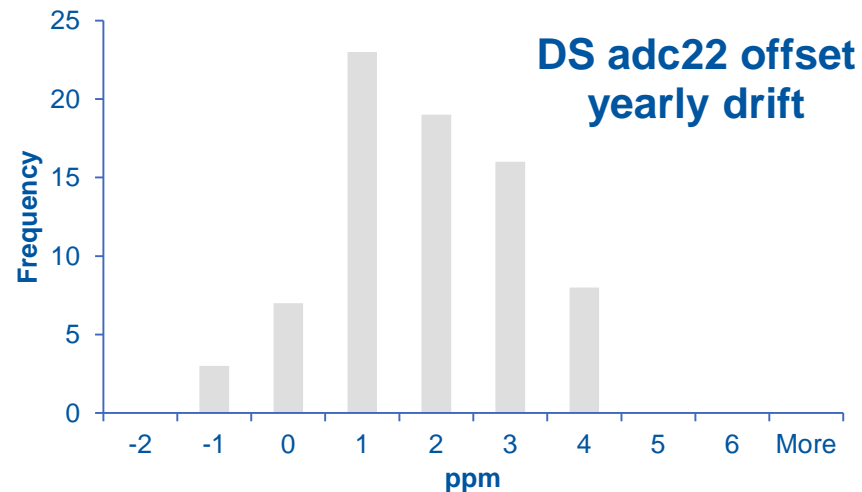

DS22 specification

Gain drift 1 year 20 ppm

Offset drift 1 year 10 ppm

LHC class 1 global accuracy

Converter category	Accuracy Class	1 year stability
Main Dipoles	Class 1	50

LHC specification



50ppm/year

LHC result

< 10ppm/year with annual calibration

Possible improvement


< 2ppm/year with monthly calibration

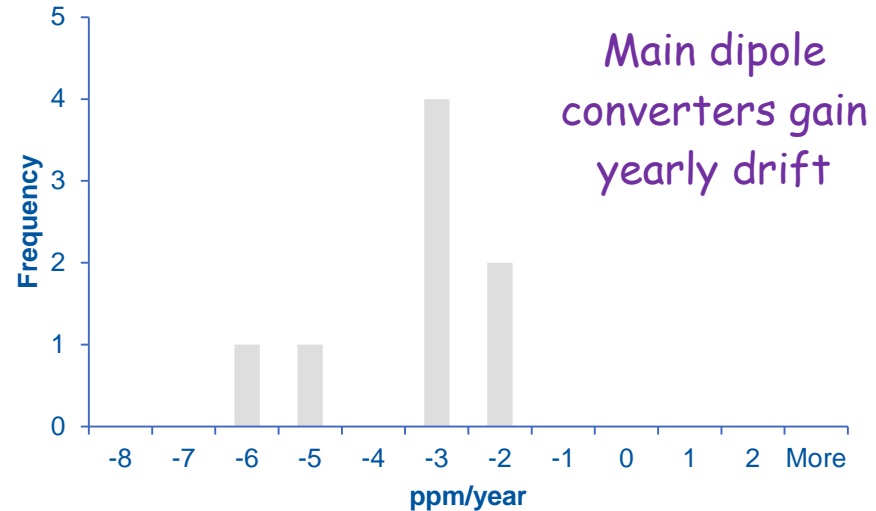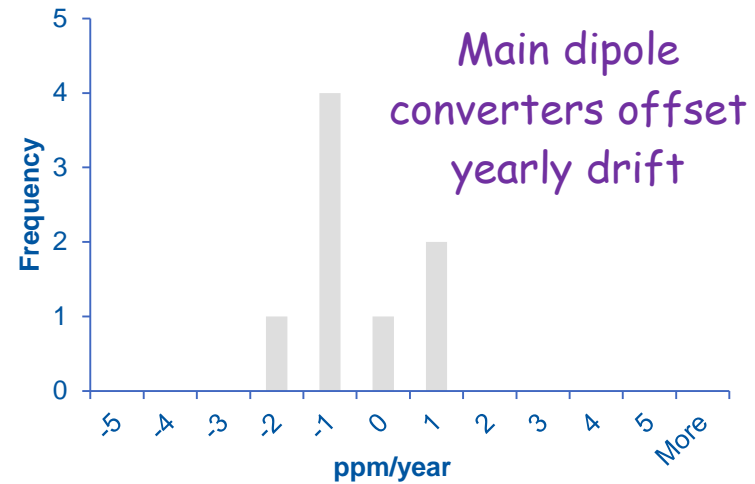

LHC resolution


Smallest increment that can be induced or discerned.

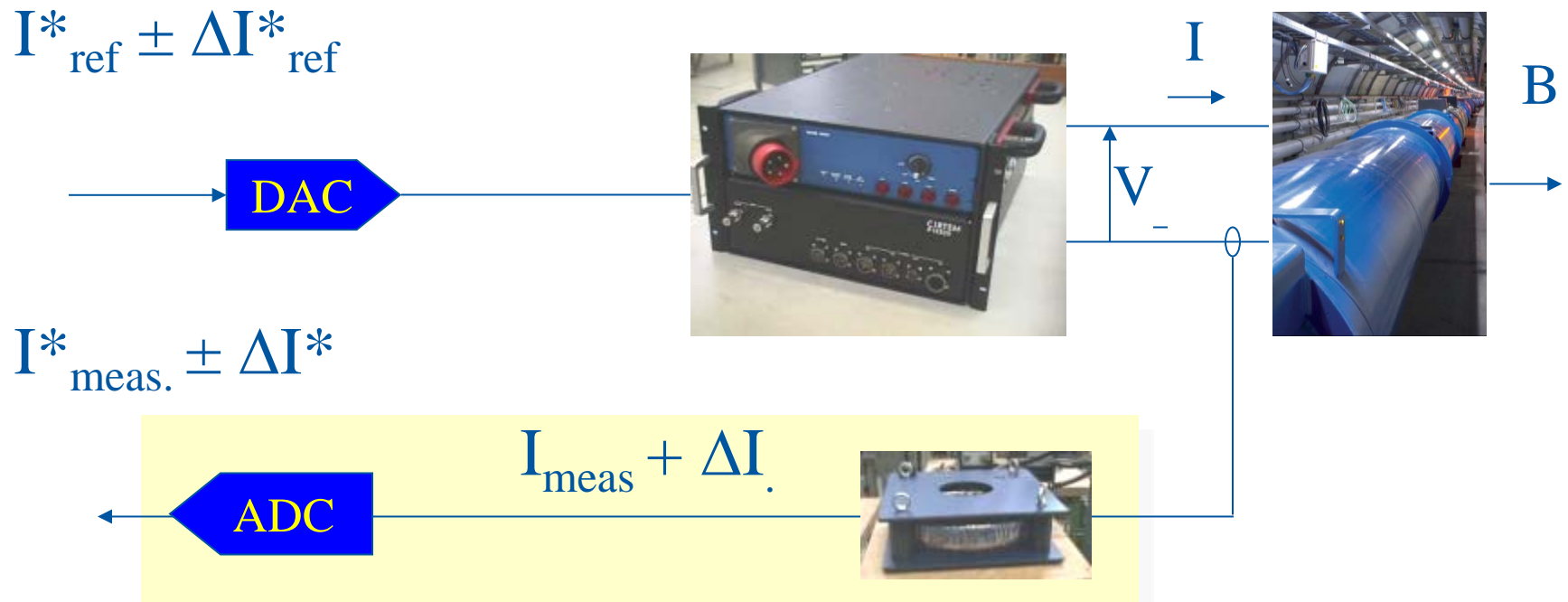The resolution is expressed in ppm of maximum DCCT current.
Resolution is directly linked to A/D system.



LHC resolution




Best resolution achieved = 1ppm

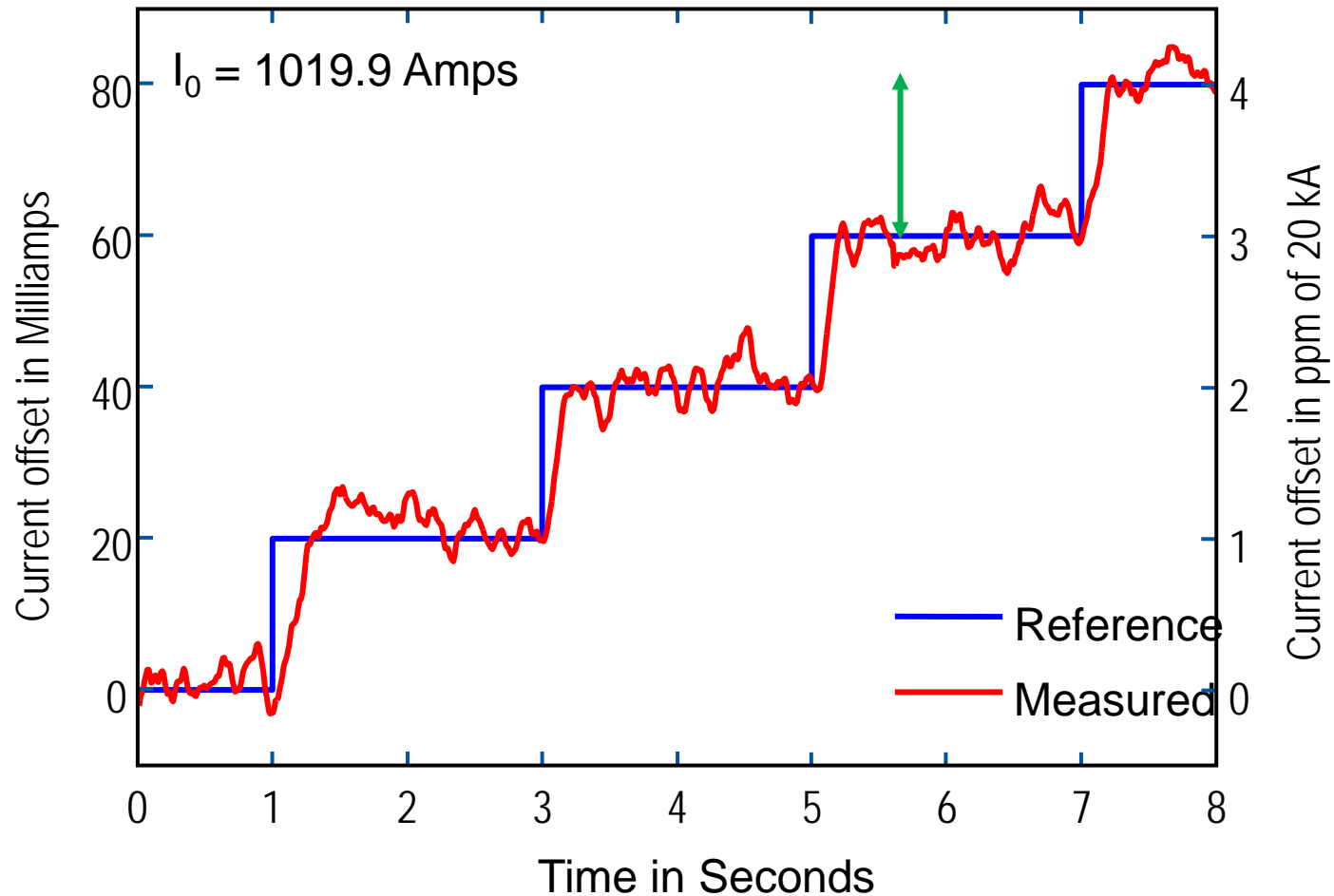

Current regulation

The performance of the current regulation is critical for a machine. Can be a nightmare for operators!

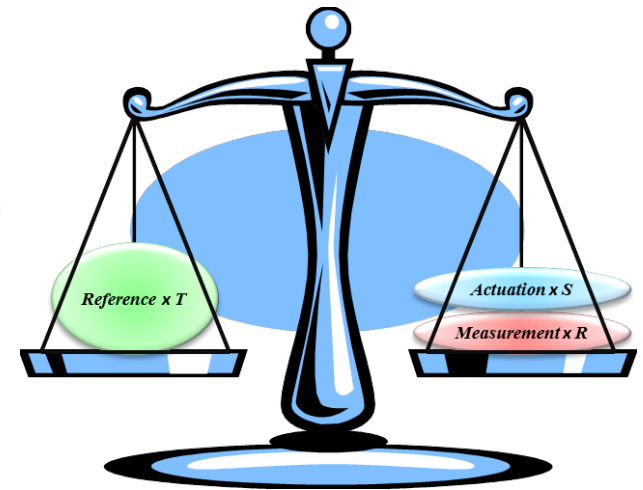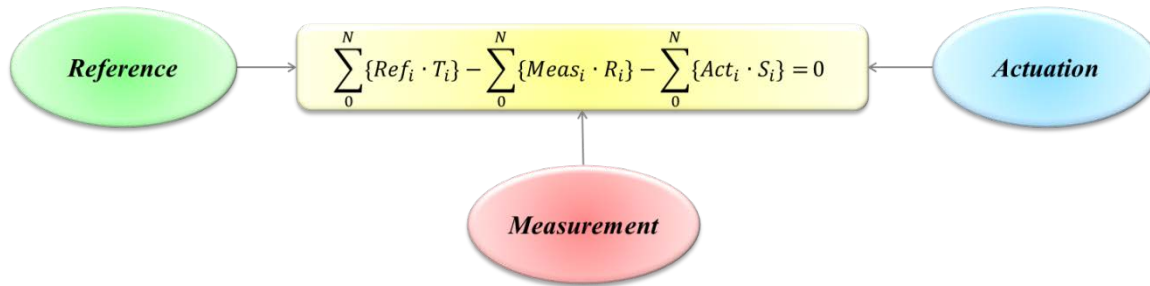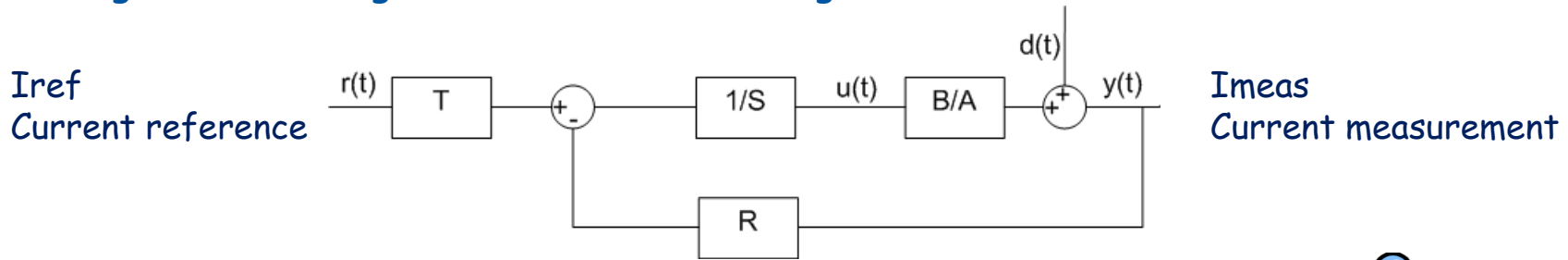RST controller provides very powerful features:
Manage the tracking error as well as the regulation.




Current regulation

Anti-windup is needed to control the saturation of the loop.



complex control loop

The real controller is shown below:

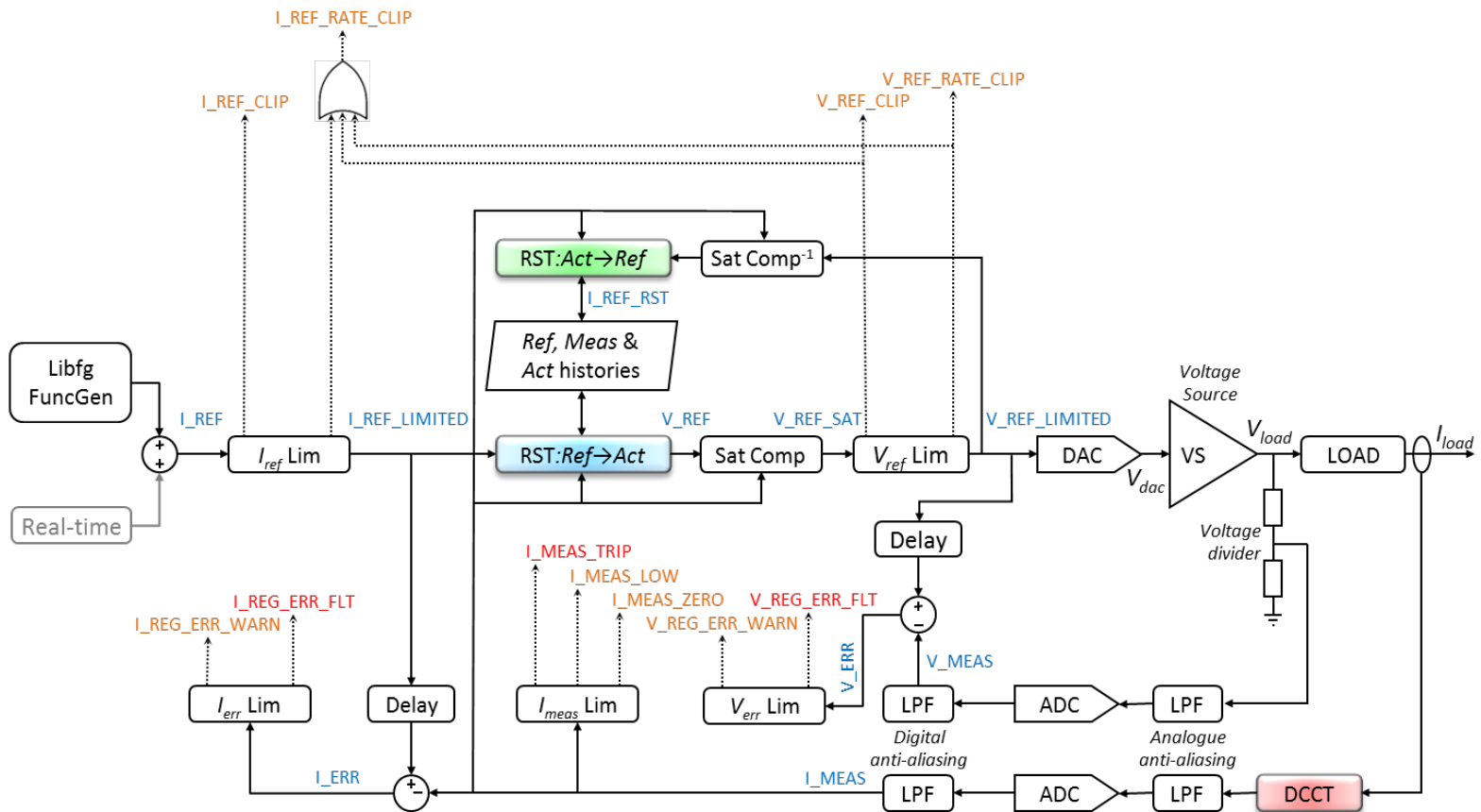

Current regulation

Tutorial is proposed here on the FGC current regulation


https://project-cclibs.web.cern.ch/project-cclibs/download_tutorial.htm

Here you can find some examples

<https://project-cclibs.web.cern.ch/project-cclibs/plots/tests/>



ripples

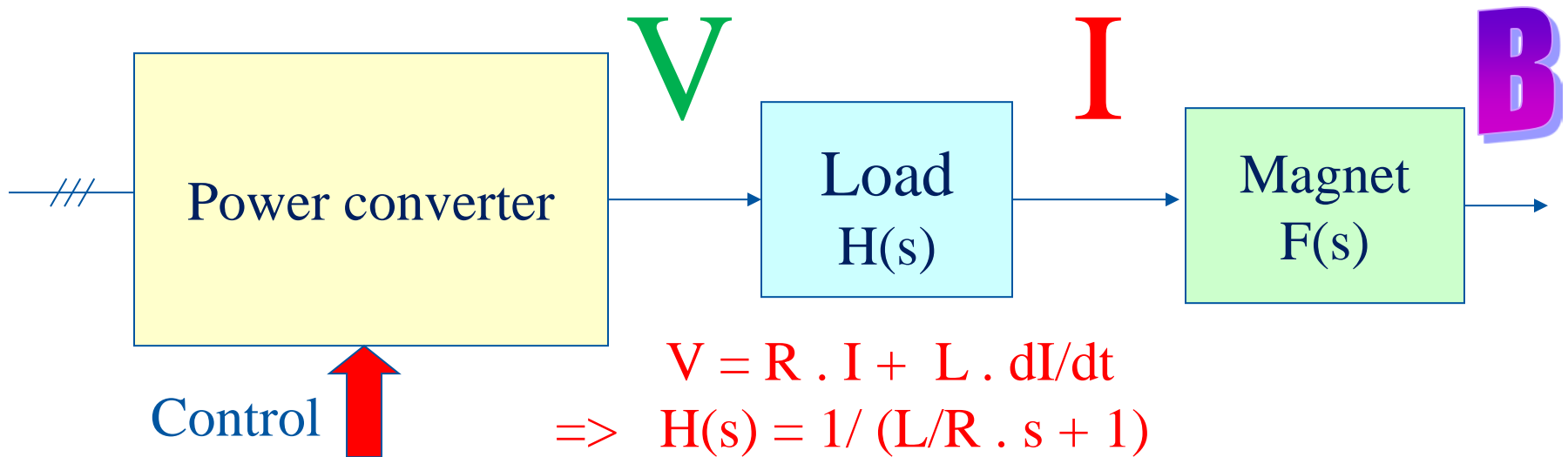

Voltage ripple is defined by the power supply

Current ripple : load transfer function (cables & magnet)

B-Field ripple : magnet transfer function (vacuum chamber,...)




Current ripple
Depends of the load


Grounding

Particles accelerators are very sensitive to EMC (conducted and radiated noise).


Need a meshed earth !

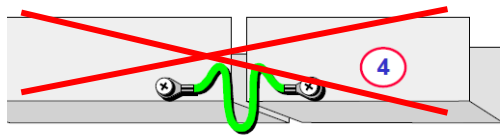

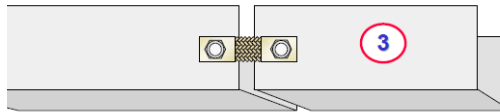Wires only provide bonds that are effective up to 1kHz





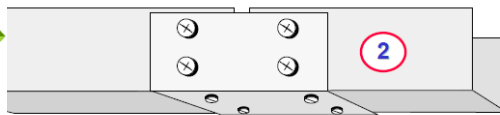Short, wide braid straps could bond up to MHz
Use as many as practical, spread along the joint and at both ends



U-brackets with RF-bonds every $3/f$ metres along the join and at both ends (f in MHz) are effective up to f

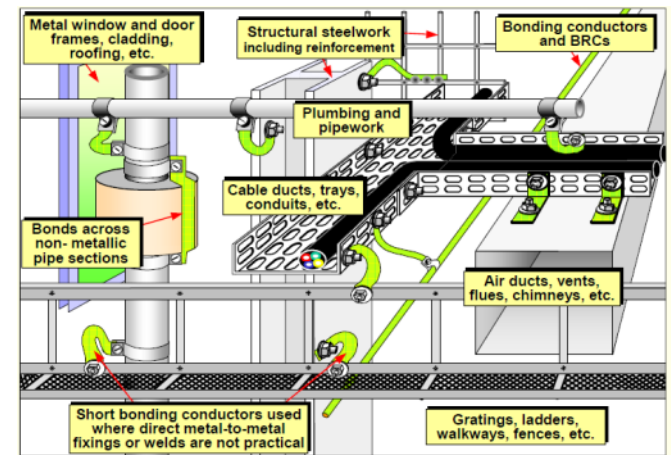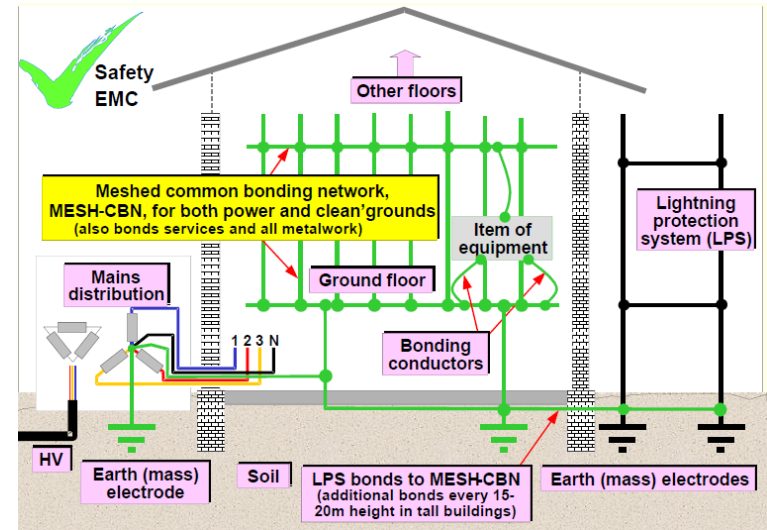
But continuously seam-welded or conductively-gasketed joints are best (1)



<http://indico.cern.ch/getFile.py/access?contribId=44&sessionId=9&resId=0&materialId=slides&confId=85851>

Grounding

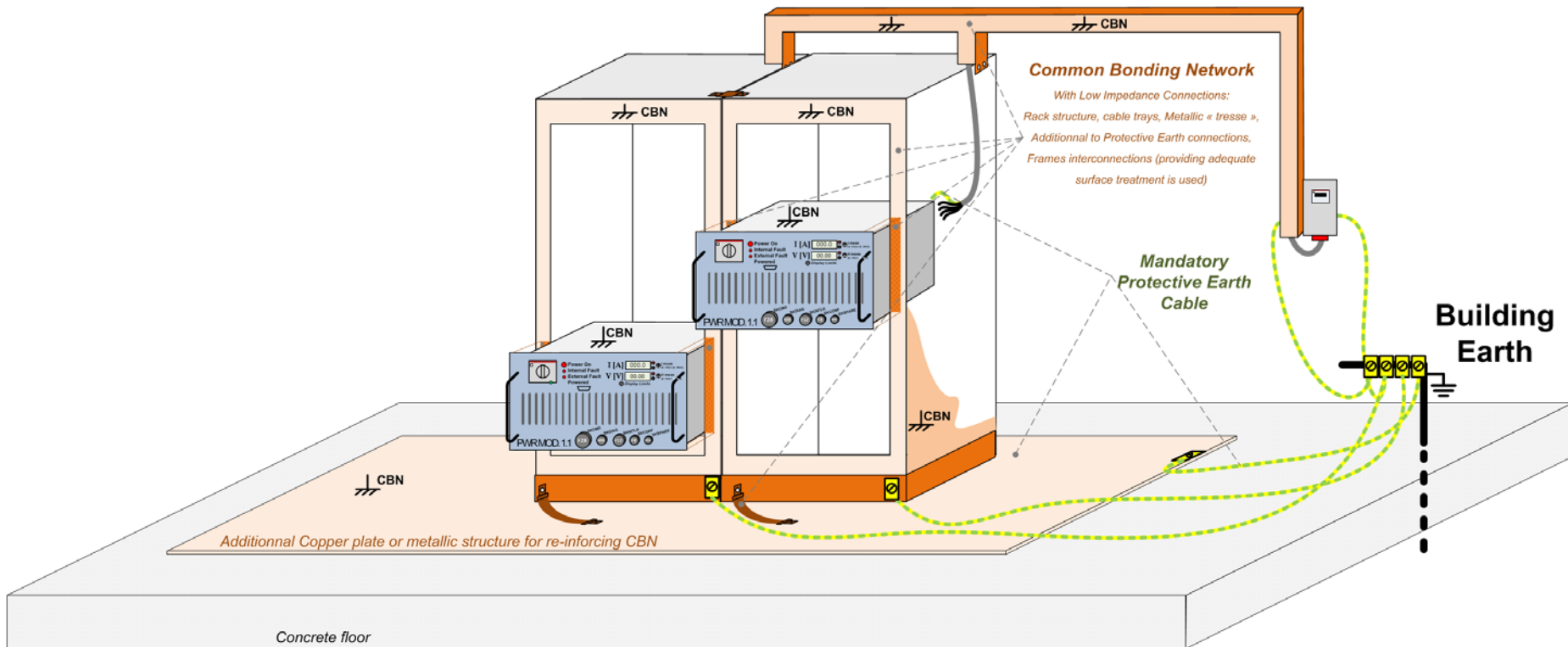Applying good EMC rules to power supplies:



What do an accelerator physicist should specify ?

If you have already designed the magnets without including power supply engineer, you have already made a mistake!

Powering optimization plays with magnet parameters


The power engineer has to be included in the accelerator design from the beginning!

What do an accelerator physicist should specify ?


Magnet parameters:

- Inductance, in mH
- Resistance, in $m\Omega$
- Maximum current
- Voltage rating
- DC cable resistance, in $m\Omega$

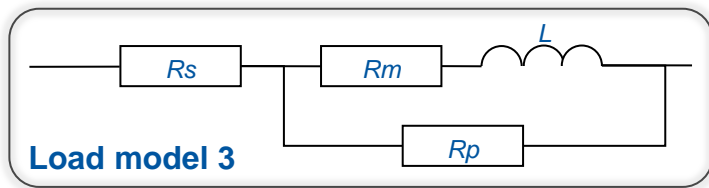much better, magnet model including saturation effect



Load Saturation model

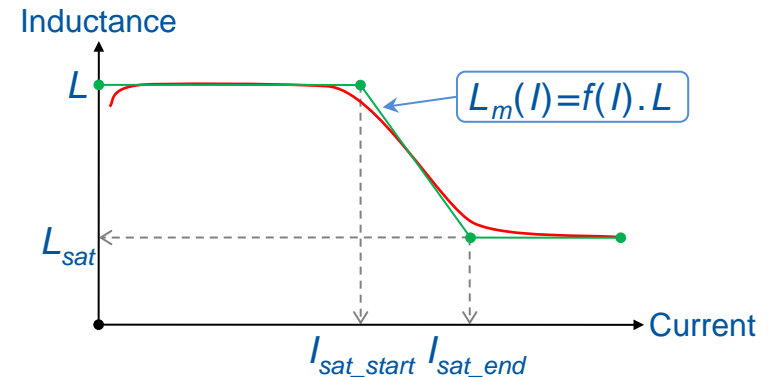


What do an accelerator physicist should specify ?

Magnet operation:

- Precision class
- Type of control: Current / B-field
- Maximum current ripple
- Complete cycle
 - Injection current
 - Maximum dI/dt , ramp-up
 - Maximum flat top current
 - Maximum dI/dt , ramp-down
 - Return current
 - Cycle time
- Degauss cycle / pre-cycle
- Magnet protection system



Power supply functional specification

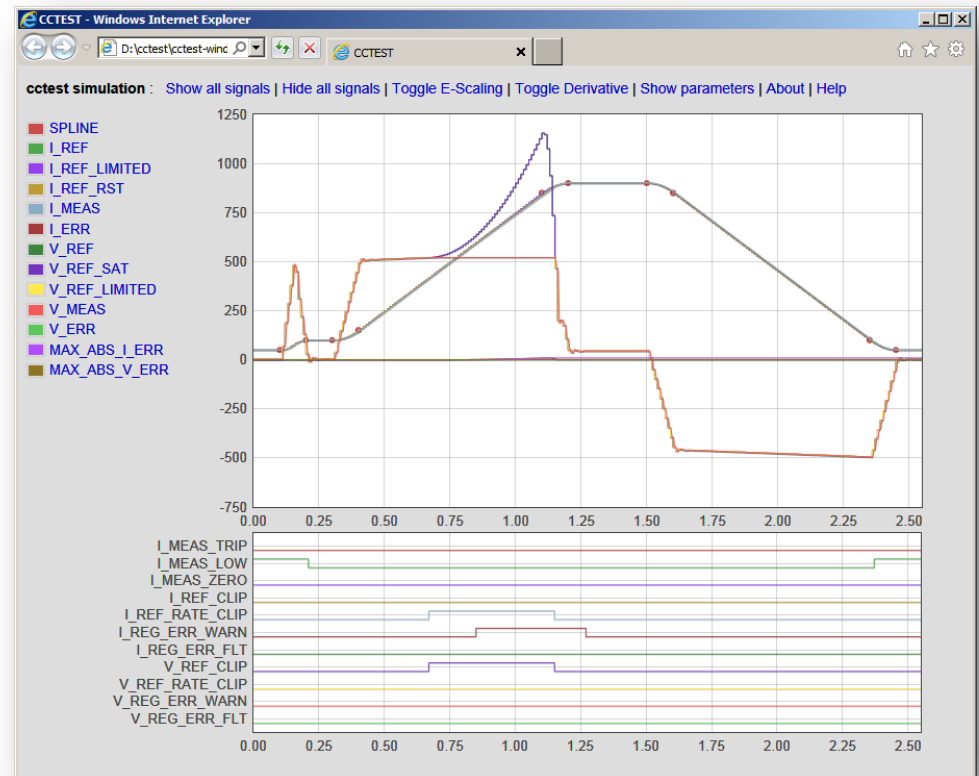


Power supply delivery

From power supply functional specification

<https://edms.cern.ch/document/829344/3>

Power supply design

simulation

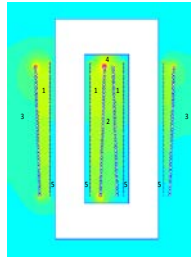



Component design

3D mechanical integration


Production

Laboratory Tests

On site commissioning

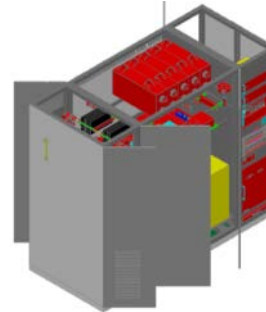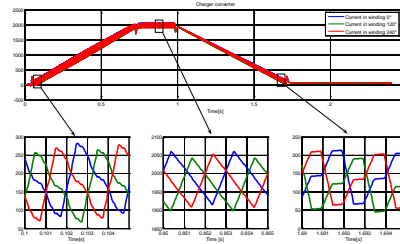

Minimum 18 months

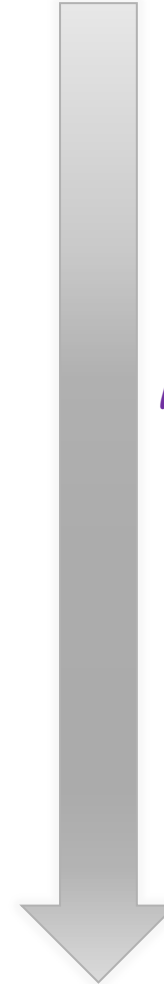


Summary

Power supplies are the main actuators of a particles accelerator.
The performances for particles accelerators are very challenging.

Creativity on many technical fields are required!

More training :

Special CAS on power converters

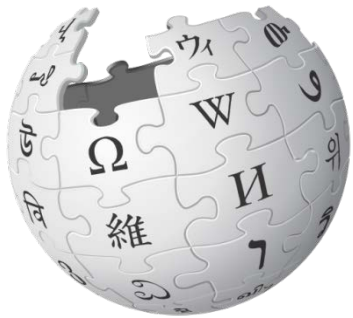

WikipediA
The Free Encyclopedia

7 - 14 May 2014

Baden (CH)

