

RF Engineering Basic Concepts

Fritz Caspers, Peter McIntosh, Tom Kroyer

CAS 2007, Daresbury

Contents

- ◆ S parameters
- ◆ Signal flow graph
- ◆ Properties of the S matrix of an N-port
- ◆ Basic properties of striplines, microstrip- and slotlines
- ◆ Application of the Smith Chart

S-parameters (1)

- ◆ The abbreviation S has been derived from the word *scattering*.
- ◆ For high frequencies, it is convenient to describe a given network in terms of *waves* rather than voltages or currents. This permits an easier definition of reference planes.
- ◆ For practical reasons, the description in terms of in- and outgoing waves has been introduced.
- ◆ Now, a 4-pole network becomes a 2-port and a $2n$ -pole becomes an n -port. In the case of an odd pole number (e.g. 3-pole), a common reference point may be chosen, attributing one pole equally to two ports. Then a 3-pole is converted into a $(3+1)$ pole corresponding to a 2-port.
- ◆ As a general conversion rule for an odd pole number one more pole is added.

S-parameters (2)

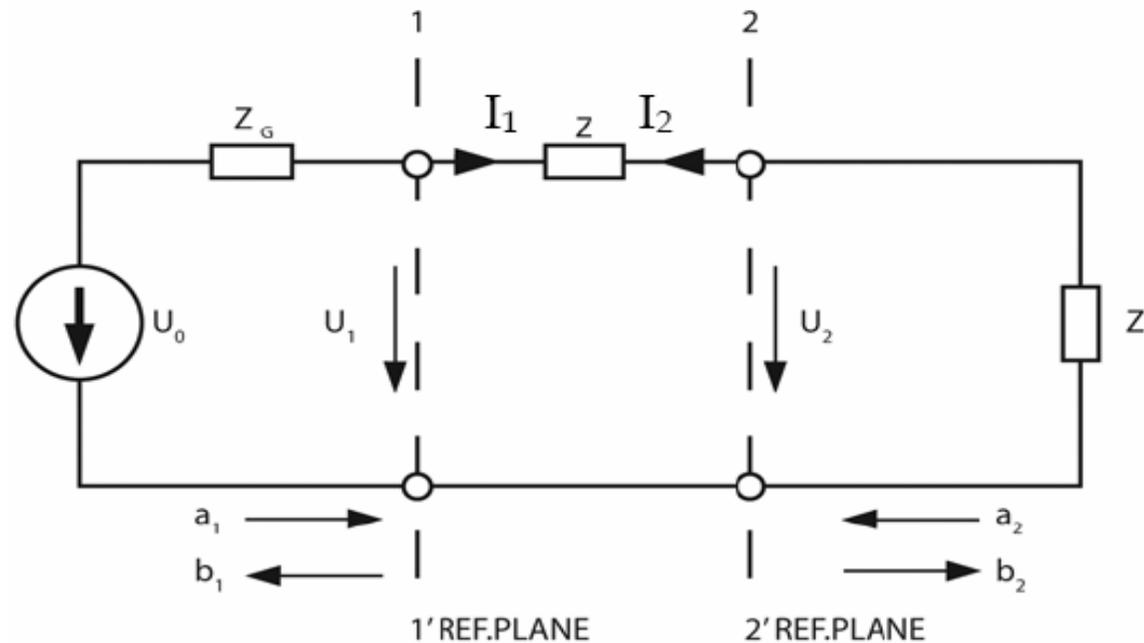


Fig. 1 2-port network

- ◆ Let us start by considering a simple 2-port network consisting of a single impedance Z connected in series (Fig. 1). The generator and load impedances are Z_G and Z_L , respectively. If $Z = 0$ and $Z_L = Z_G$ (for real Z_G) we have a matched load, i.e. *maximum available power* goes into the load and $U_1 = U_2 = U_0/2$.
- ◆ Please note that *all the voltages and currents are peak values*. The lines connecting the different elements are supposed to have zero electrical length. Connections with a finite electrical length are drawn as double lines or as heavy lines. Now we need to relate U_0 , U_1 and U_2 with a and b .

Definition of “power waves”(1)

- ◆ The waves going *towards* the n-port are $a = (a_1, a_2, \dots, a_n)$, the waves travelling *away* from the n-port are $b = (b_1, b_2, \dots, b_n)$. By definition currents going *into* the n-port are counted positively and currents flowing out of the n-port negatively. The wave a_1 is going into the n-port at port 1 is derived from the voltage wave going into a matched load.
- ◆ In order to make the definitions consistent with the conservation of energy, the voltage is normalized to Z_0 . Z_0 is in general an arbitrary reference impedance, but usually the characteristic impedance of a line (e.g. $Z_0 = 50 \Omega$) is used and very often $Z_G = Z_L = Z_0$. In the following we assume Z_0 to be real. The definitions of the waves a_1 and b_1 are



$$a_1 = \frac{U_0}{2\sqrt{Z_0}} = \frac{\text{incident voltage wave (port 1)}}{\sqrt{Z_0}} = \frac{U_1^{inc}}{\sqrt{Z_0}}$$

(2.1)

$$b_1 = \frac{U_1^{refl}}{\sqrt{Z_0}} = \frac{\text{reflected voltage wave (port 1)}}{\sqrt{Z_0}}$$

- ◆ Note that a and b have the dimension $\sqrt{\text{power}}$ [1].

Definition of “power waves”(2)

- ◆ The power travelling towards port 1, P_1^{inc} , is simply the available power from the source, while the power coming out of port 1, P_1^{refl} , is given by the reflected voltage wave.

$$P_1^{inc} = \frac{1}{2}|a_1|^2 = \frac{|U_1^{inc}|^2}{2Z_0} = \frac{|I_1^{inc}|^2}{2} Z_0 \quad (2.2)$$

$$P_1^{refl} = \frac{1}{2}|b_1|^2 = \frac{|U_1^{refl}|^2}{2Z_0} = \frac{|I_1^{refl}|^2}{2} Z_0$$

- ◆ Please note the factor 2 in the denominator, which comes from the definition of the voltages and currents as peak values (“European definition”). In the “US definition” effective values are used and the factor 2 is not present, so for power calculations it is important to check how the voltages are defined. For most applications, this difference does not play a role since ratios of waves are used.
- ◆ In the case of a mismatched load Z_L there will be some power reflected towards the 2-port from Z_L

(2.3)

$$P_2^{inc} = \frac{1}{2}|a_2|^2$$

Definition of “power waves”(3)

- ◆ There is also the outgoing wave of port 2 which may be considered as the superimposition of a wave that has gone through the 2-port from the generator and a reflected part from the mismatched load. We have defined with the incident voltage wave U^{inc} . In analogy to that we can also quote with the incident current wave I^{inc} . We obtain the *general definition* of the waves a_i travelling into and b_i travelling *out of* an n-port:
- ◆ Solving these two equations, U_i and I_i can be obtained for a given a_i and b_i as

$$\begin{aligned} a_i &= \frac{U_i + I_i Z_0}{2\sqrt{Z_0}} \\ b_i &= \frac{U_i - I_i Z_0}{2\sqrt{Z_0}} \end{aligned} \quad (2.4)$$

$$\begin{aligned} U_i &= \sqrt{Z_0} (a_i + b_i) = U_i^{inc} + U_i^{refl} \\ I_i &= \frac{1}{\sqrt{Z_0}} (a_i - b_i) = \frac{U_i^{refl}}{Z_0} \end{aligned} \quad (2.5)$$

- ◆ For a harmonic excitation $u(t) = \text{Re}\{U e^{j\omega t}\}$ the power going *into* port i is given by

$$\begin{aligned} P_i &= \frac{1}{2} \text{Re}\{U_i I_i^*\} \\ P_i &= \frac{1}{2} \text{Re}\left\{\left(a_i a_i^* - b_i b_i^*\right) + \left(a_i^* b_i - a_i b_i^*\right)\right\} \end{aligned} \quad (2.6)$$

- ◆ The term $(a_i^* b_i - a_i b_i^*)$ $P_i = \frac{1}{2} (a_i a_i^* - b_i b_i^*)$ and vanishes when the real part is taken

The S-Matrix (1)

- ◆ The relation between a_i and b_j ($i = 1 \dots n$) can be written as a system of n linear equations (a_i being the independent variable, b_j the dependent variable)

$$\begin{aligned} b_1 &= S_{11}a_1 + S_{12}a_2 \\ b_2 &= S_{21}a_1 + S_{22}a_2 \end{aligned} \quad (2.7) \text{ Or in matrix formulation} \quad \mathbf{b} = \mathbf{S}\mathbf{a} \quad (2.8)$$

- ◆ The physical meaning of S_{11} is the input reflection coefficient with the output of the network terminated by a matched load ($a_2 = 0$). S_{21} is the forward transmission (from port 1 to port 2), S_{12} the reverse transmission (from port 2 to port 1) and S_{22} the output reflection coefficient.
- ◆ When measuring the S parameter of an n -port, *all* n ports must be terminated by a matched load (not necessarily equal value for all ports), including the port connected to the generator (matched generator).
- ◆ Using Eqs. 2.4 and 2.7 we find the reflection coefficient of a single impedance Z_L connected to a generator of source impedance Z_0 (Fig. 1, case $Z_G = Z_0$ and $Z = 0$)

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = \frac{U_1 - I_1 Z_0}{U_1 + I_1 Z_0} = \frac{Z_L - Z_0}{Z_L + Z_0} = \rho = \frac{(Z_L / Z_0) - 1}{(Z_L / Z_0) + 1} \quad (2.9)$$

- ◆ which is the familiar formula for the reflection coefficient ρ (often also denoted Γ).

The S-Matrix (2)

- ◆ Let us now determine the S parameters of the impedance Z in Fig. 1, assuming again $Z_G = Z_L = Z_0$. From the definition of S_{11} we have

$$S_{11} = \frac{b_1}{a_1} = \frac{U_1 - I_1 Z_0}{U_1 + I_1 Z_0}$$

$$U_1 = U_0 \frac{Z_0 + Z}{2Z_0 + Z}, \quad U_2 = U_0 \frac{Z_0}{2Z_0 + Z}, \quad I_1 = \frac{U_0}{2Z_0 + Z} = -I_2 \quad (2.10)$$

$$\Rightarrow S_{11} = \frac{Z}{2Z_0 + Z}$$

- ◆ and in a similar fashion we get

$$S_{21} = \frac{b_2}{a_1} = \frac{U_2 - I_2 Z_0}{U_1 + I_1 Z_0} = \frac{2Z_0}{2Z_0 + Z} \quad (2.11)$$

- ◆ Due to the symmetry of the element $S_{22} = S_{11}$ and $S_{12} = S_{21}$. Please note that for this case we obtain $S_{11} + S_{21} = 1$. The full S matrix of the element is then

$$\mathbf{S} = \begin{pmatrix} \frac{Z}{2Z_0 + Z} & \frac{Z_0 + Z}{2Z_0 + Z} \\ \frac{Z_0 + Z}{2Z_0 + Z} & \frac{Z}{2Z_0 + Z} \end{pmatrix} \quad (2.12)$$

The transfer matrix (T-matrix)

- ◆ The S matrix introduced in the previous section is a very convenient way to describe an n-port in terms of waves. It is very well adapted to measurements. However, it is not well suited to for characterizing the response of a number of cascaded 2-ports. A very straightforward manner for the problem is possible with the T matrix (transfer matrix), which directly relates the waves on the input and on the output [2]

$$\begin{pmatrix} b_1 \\ a_1 \end{pmatrix} = \begin{pmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{pmatrix} \begin{pmatrix} a_2 \\ b_2 \end{pmatrix} \quad (2.10)$$

- ◆ The conversion formulae between S and T matrix are given in Appendix I. While the S matrix exists for any 2-port, in certain cases, e.g. no transmission between port 1 and port 2, the T matrix is not defined. The T matrix \mathbf{T}_M of m cascaded 2-ports is given by (as in [2, 3]):

$$\mathbf{T}_M = \mathbf{T}_1 \mathbf{T}_2 \dots \mathbf{T}_m \quad (2.11)$$

- ◆ Note that in the literature different definitions of the T matrix can be found and the individual matrix elements depend on the definition used.

The signal flow graph

- ◆ The SFG is a graphical representation of a system of linear equations having the general form:


$$\mathbf{y} = \mathbf{M}\mathbf{x} + \mathbf{M}'\mathbf{y}$$

- ◆ \mathbf{M} and \mathbf{M}' are square matrices with n rows and columns
- ◆ \mathbf{x} represent the n independent variables (sources) and \mathbf{y} the n dependent variables.
- ◆ The elements of \mathbf{M} and \mathbf{M}' appear as transmission coefficients of the signal path.
- ◆ When there are no direct signal loops, this simplifies to $\mathbf{y} = \mathbf{M}\mathbf{x}$, which is equivalent to the usual S parameter definition

$$\mathbf{b} = \mathbf{S}\mathbf{a}$$




Drawing the SFG

- ◆ The SFG can be drawn as a directed graph. Each wave a_i and b_i is represented by a node, each arrow stands for an S parameter
- ◆ Nodes with no arrows pointing towards them are *source nodes*. All other nodes are *dependent signal nodes*.
- ◆ Example: A 2-port with given S_{ij} . At port 2 a not matched load ρ_L is connected.
- ◆ Question: What is the input reflection coefficient S_{11} of this circuit?


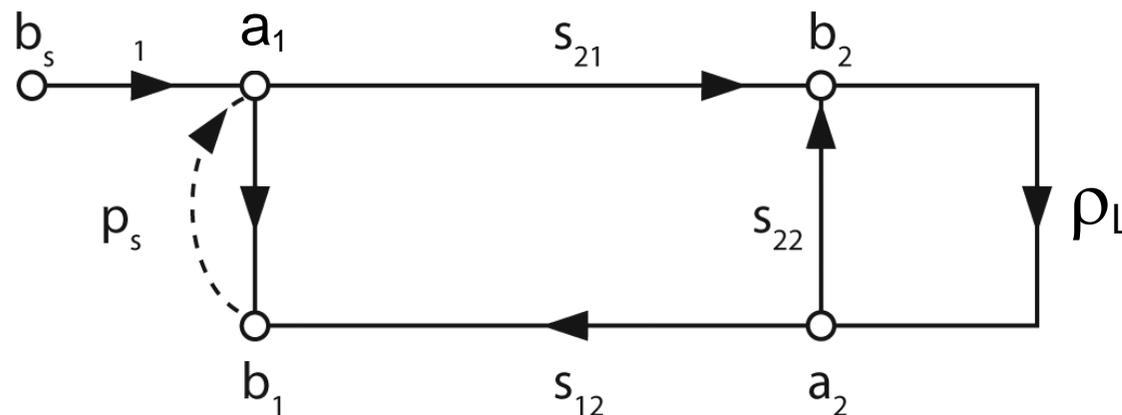


Simplifying the signal flow graph

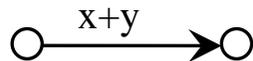
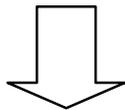
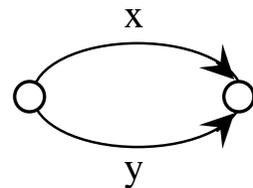
- ◆ For general problems the SFG can be solved for applying Mason's rule (see Appendix of lecture notes). For not too complicated circuits there is a more intuitive way by simplifying the SFG according to three rules
 1. Add the signal of parallel branches
 2. Multiply the signals of cascaded branches
 3. Resolve loops



1. Parallel branches

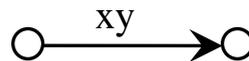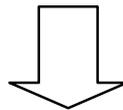

2. Cascaded signal paths

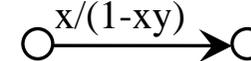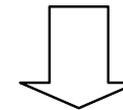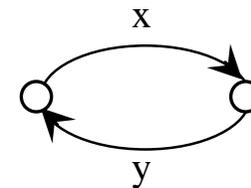


3. Loops

Solving problems with the SFG

- ◆ The loop at port 2 involving S_{22} and ρ_L can be resolved. It gives a branch from b_2 to a_2 with the coefficient $\rho_L/(1-\rho_L * S_{22})$
- ◆ Applying the cascading rule to the right path and finally the parallel branch rule we get

$$\frac{b_1}{a_1} = S_{11} + S_{21} \frac{\rho_L}{1 - S_{22}\rho_L} S_{12}$$

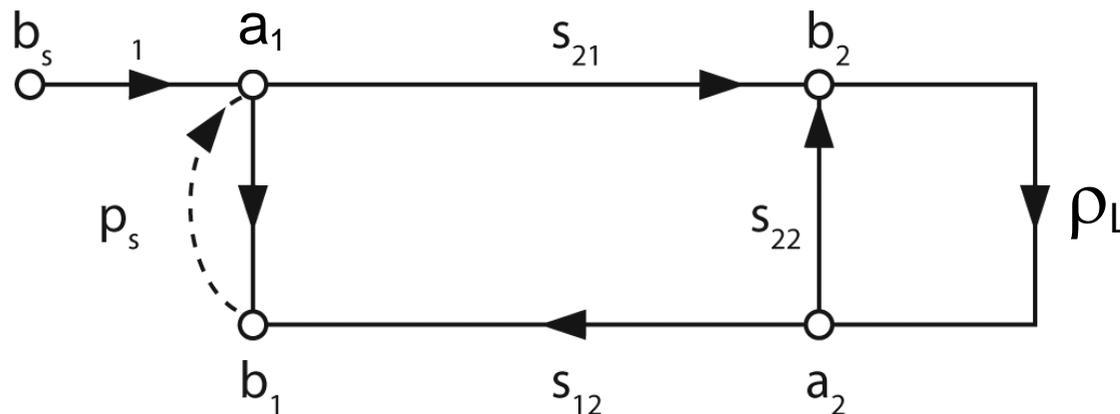- ◆ More complicated problems are usually solved by computer code using the matrix formulations mentioned before



Properties of the S matrix of an N-port

- ◆ A generalized n-port has n^2 scattering coefficients. While the S_{ij} may be all independent, in general due to symmetries etc the number of independent coefficients is much smaller.
- ◆ An n-port is *reciprocal* when $S_{ij} = S_{ji}$ for all i and j . Most passive components are reciprocal, active components such as amplifiers are generally non-reciprocal.
- ◆ A two-port is *symmetric*, when it is reciprocal ($S_{21} = S_{12}$) and when the input and output reflection coefficients are equal ($S_{22} = S_{11}$).
- ◆ An N-port is *passive and lossless* if its S matrix is *unitary*, i.e. $S^\dagger S = 1$, where $x^\dagger = (x^*)^T$ is the conjugate transpose of x .

Unitarity of an N-port

For a two-port the unitarity condition gives

$$(S^*)^T S = \begin{pmatrix} S_{11}^* & S_{21}^* \\ S_{12}^* & S_{22}^* \end{pmatrix} \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} = \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix}$$

which yields the three conditions

$$\begin{aligned} |S_{11}|^2 + |S_{21}|^2 &= 1 \\ |S_{12}|^2 + |S_{22}|^2 &= 1 \\ S_{11}^* S_{12} + S_{21}^* S_{22} &= 0 \end{aligned}$$

From the last equation we get, writing out amplitude and phase

$$|S_{11}| |S_{12}| = |S_{21}| |S_{22}| \quad \text{and}$$

$$-\arg S_{11} + \arg S_{12} = -\arg S_{21} + \arg S_{22} + \pi$$

and combining the equations for the modulus (amplitude)

$$\begin{aligned} |S_{11}| &= |S_{22}|, \quad |S_{12}| = |S_{21}| \\ |S_{11}| &= \sqrt{1 - |S_{12}|^2} \end{aligned}$$

Thus any lossless two-port can be characterized by one amplitude and three phases.

General properties

- ◆ In general the S parameters are complex and frequency dependent.
- ◆ Their phases change when the reference plane is moved. Therefore it is important to clearly define the reference planes used
- ◆ For a given structure, often the S parameters can be determined from considering mechanical symmetries and, in case of lossless networks, from energy conservation.

Examples of S matrices: 1-ports

- ◆ Simple lumped elements are 1-ports, but also cavities with one test port, long transmission lines or antennas can be considered as 1-ports
- ◆ 1-ports are characterized by their reflection coefficient ρ , or in terms of S parameters, by S_{11} .
- ◆ Ideal short: $S_{11} = -1$
- ◆ Ideal termination: $S_{11} = 0$
- ◆ Active termination (reflection amplifier): $|S_{11}| > 1$

Examples of S matrices: 2-ports (1)

- ◆ Ideal transmission line of length l

$$\mathbf{S} = \begin{pmatrix} 0 & e^{-\gamma l} \\ e^{-\gamma l} & 0 \end{pmatrix}$$

where $\gamma = \alpha + j\beta$ is the complex propagation constant, α the line attenuation in [Neper/m] and $\beta = 2\pi/\lambda$ with the wavelength λ . For a lossless line $|S_{21}| = 1$.

- ◆ Ideal phase shifter

$$\mathbf{S} = \begin{pmatrix} 0 & e^{-j\varphi_{12}} \\ e^{-j\varphi_{21}} & 0 \end{pmatrix}$$

For a reciprocal phase shifter $\varphi_{12} = \varphi_{21}$, while for the gyrator $\varphi_{12} = \varphi_{21} + \pi$. An ideal gyrator is lossless ($\mathbf{S}^\dagger \mathbf{S} = \mathbf{1}$), but it is not reciprocal. Gyration is often implemented using active electronic components, however in the microwave range passive gyrators can be realized using magnetically saturated ferrite elements.

Examples of S matrices: 2-ports (2)

- ◆ Ideal, reciprocal attenuator

$$\mathbf{S} = \begin{pmatrix} 0 & e^{-\alpha} \\ e^{-\alpha} & 0 \end{pmatrix}$$

with the attenuation α in Neper. The attenuation in Decibel is given by $A = -20 \cdot \log_{10}(S_{21})$, $1 \text{ Np} = 8.686 \text{ dB}$. An attenuator can be realized e.g. with three resistors in a T circuit or with resistive material in a waveguide.

- ◆ Ideal isolator

$$\mathbf{S} = \begin{pmatrix} 0 & 0 \\ 1 & 0 \end{pmatrix}$$

The isolator allows transmission in one direction only, it is used e.g. to avoid reflections from a load back to the generator.

- ◆ Ideal amplifier


$$\mathbf{S} = \begin{pmatrix} 0 & 0 \\ G & 0 \end{pmatrix}$$

with the voltage gain $G > 1$. Please note the similarity between an ideal amplifier and an ideal isolator!

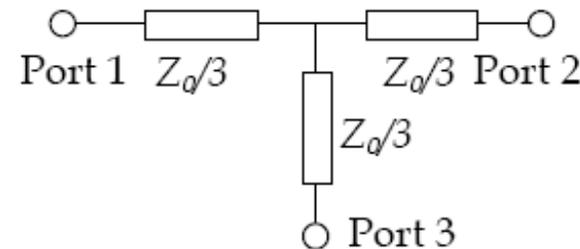Examples of S matrices: 3-ports (2)

- ◆ It can be shown that a 3-port cannot be lossless, reciprocal and matched at all three ports at the same time. The following components have two of the above characteristics.
- ◆ Resistive power divider: It consists of a resistor network and is reciprocal, matched at all ports but lossy. It can be realized with three resistors in a triangle configuration.



$$\mathbf{S} = \begin{pmatrix} 0 & 1/2 & 1/2 \\ 1/2 & 0 & 1/2 \\ 1/2 & 1/2 & 0 \end{pmatrix}$$



- ◆ The T splitter is reciprocal and lossless but not matched at all ports. Using the losslessness condition and symmetry considerations one finds for E and H plane splitters


$$S_H = \frac{1}{2} \begin{pmatrix} 1 & -1 & \sqrt{2} \\ -1 & 1 & \sqrt{2} \\ \sqrt{2} & \sqrt{2} & 0 \end{pmatrix}$$
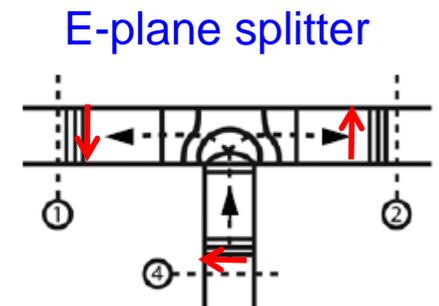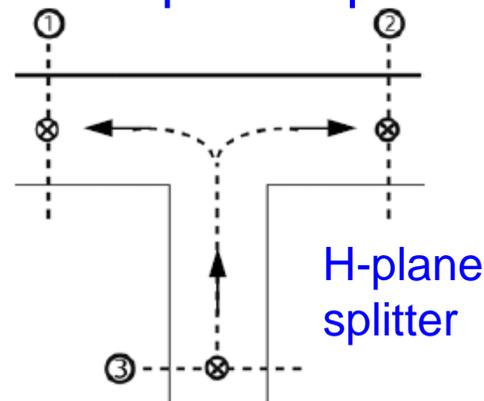
$$S_E = \frac{1}{2} \begin{pmatrix} 1 & 1 & \sqrt{2} \\ 1 & 1 & -\sqrt{2} \\ \sqrt{2} & -\sqrt{2} & 0 \end{pmatrix}$$



Circulators

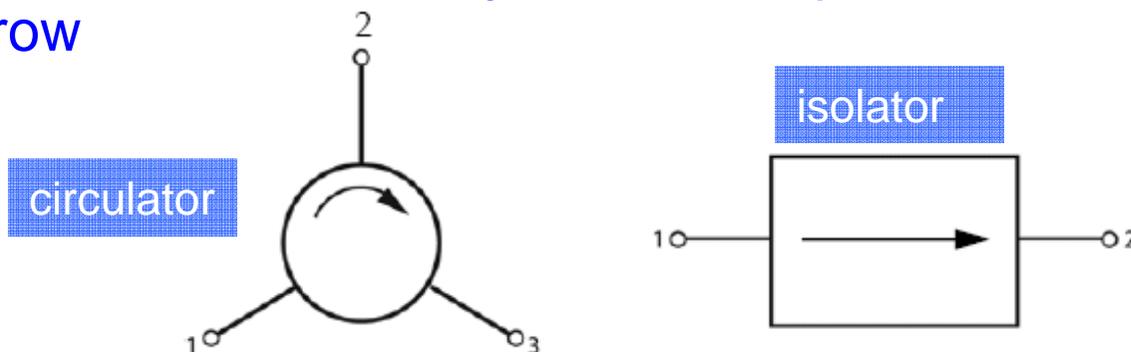- ◆ The ideal circulator is lossless, matched at all ports, but not reciprocal. A signal entering the ideal circulator at one port is transmitted *exclusively* to the next port in the sense of the arrow




- ◆ Its S matrix has a very simple form:

$$\mathbf{S} = \begin{pmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{pmatrix}$$

- ◆ When port 3 of the circulator is terminated with a matched load we get a two-port called isolator, which lets power pass only from port 1 to port 2



Ferrites for circulators

- ◆ A circulator, like the gyrator and other passive non-reciprocal elements contains a volume of ferrite. This ferrite is normally magnetized into saturation by an external magnetic field.
- ◆ The magnetic properties of a saturated RF ferrite have to be characterized by a μ -tensor. The real and imaginary part of each complex element μ are μ' and μ'' . They are strongly dependent on the bias field.
- ◆ The μ_+ and μ_- represent the permeability seen by a right- and left-hand circular polarized wave traversing the ferrite

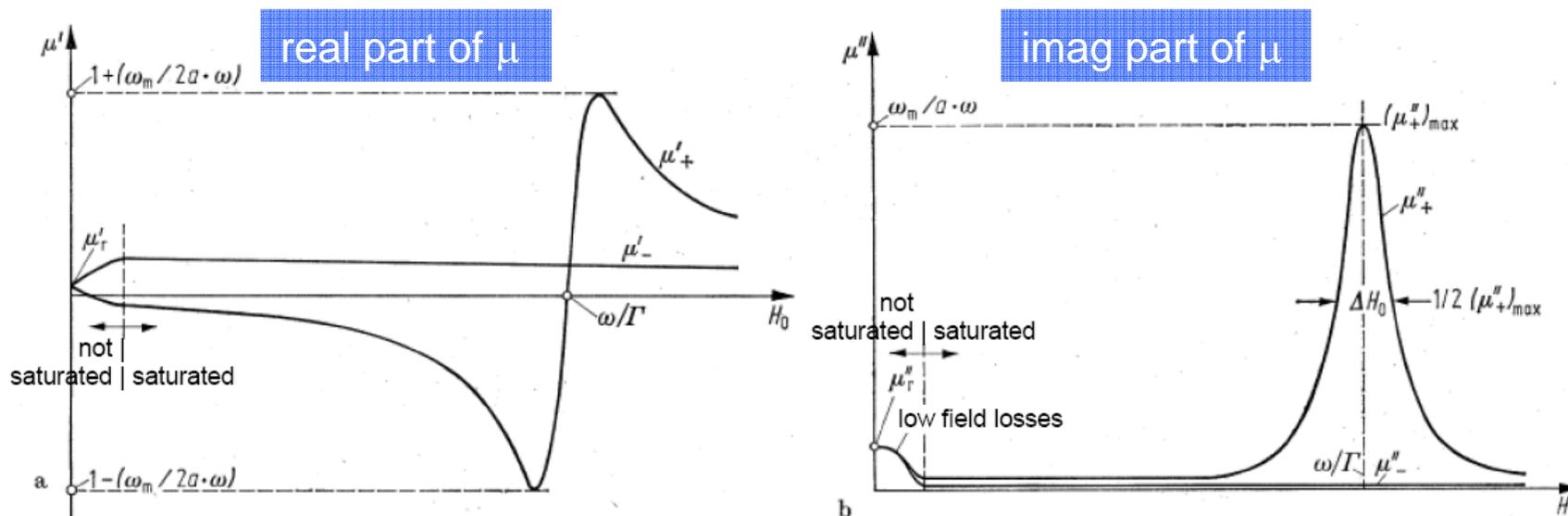


Practical Implementations of circulators

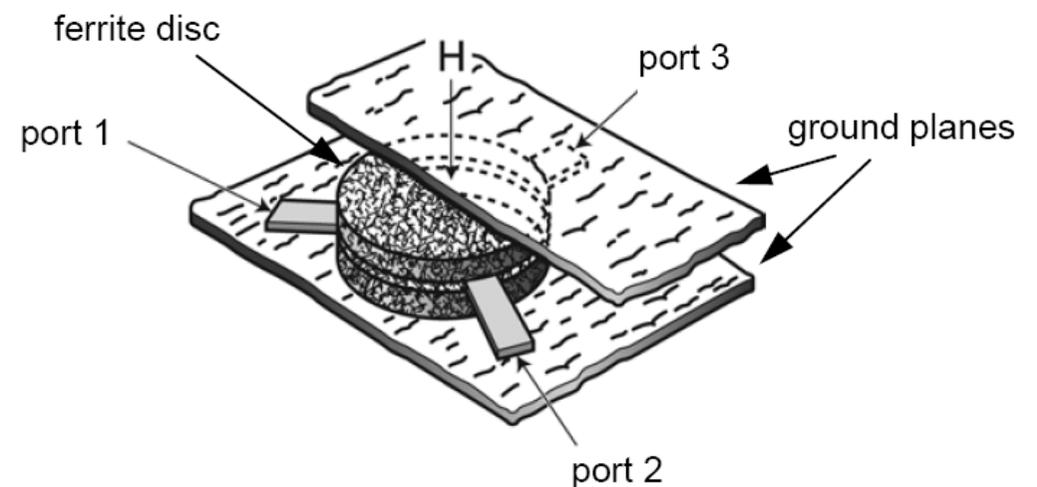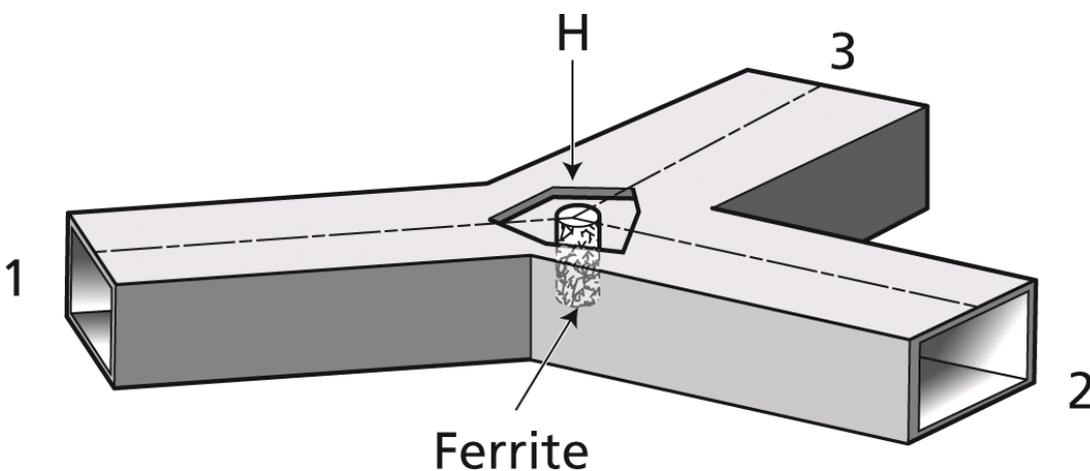- ◆ The magnetically polarized ferrite provides the required nonreciprocal properties. As a result, power is only transmitted from port 1 to port 2, from port 2 to port 3 and from port 3 to port 1.
- ◆ Circulators can be built with e.g. with waveguides (left) or with striplines (right)



The Faraday isolator


- ◆ The Faraday isolator is based on the Faraday rotation of a polarized wave in the presence of a magnetically polarized ferrite
- ◆ Running along the ferrite the TE_{10} wave coming from left is rotated counterclockwise by 45 degrees. It can then enter unhindered the waveguide on the right
- ◆ A wave coming from the right is rotated clockwise (as seen from the right); the wave then has the wrong polarization. It gets damped by the horizontal damping foil.

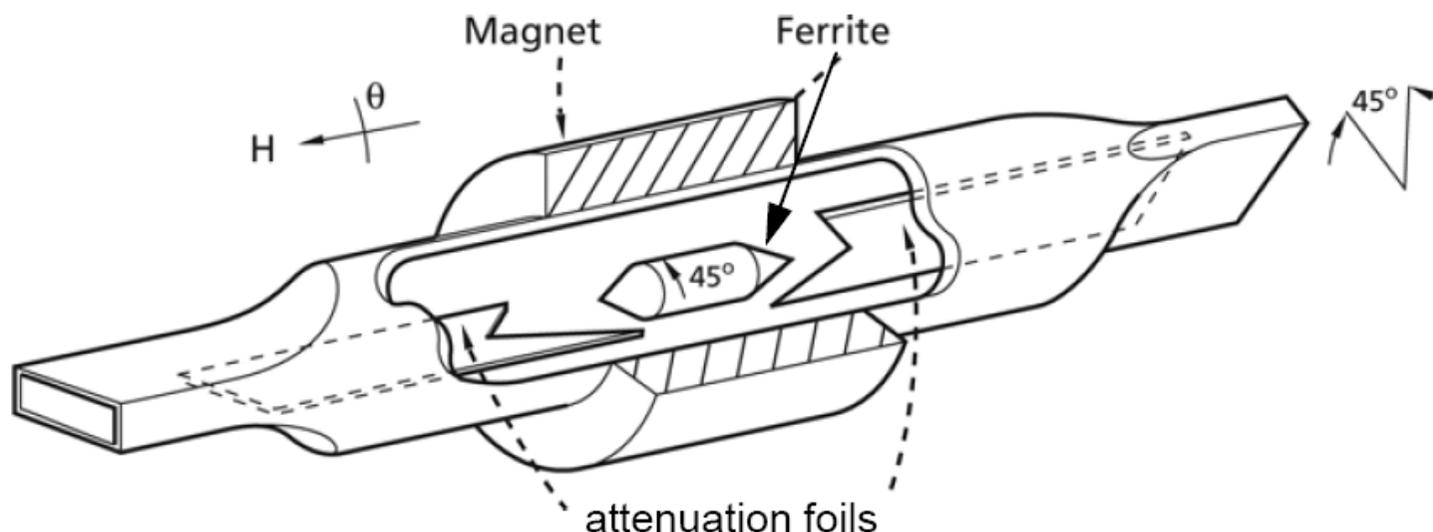

The Magic T

- ◆ A combination of a E-plane and H-plane waveguide T is a very special 4-port: A “magic” T. The coefficients of the S matrix can be found by using the unitary condition and mechanical symmetries.
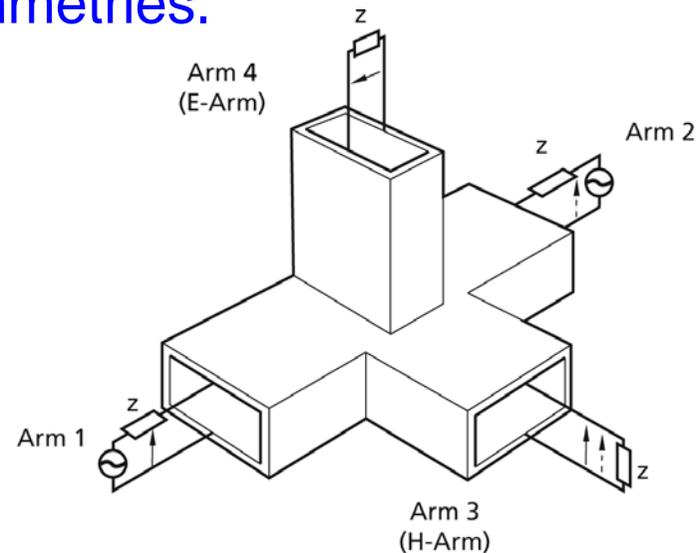
$$\mathbf{S} = \frac{1}{\sqrt{2}} \begin{pmatrix} 0 & 0 & 1 & 1 \\ 0 & 0 & 1 & -1 \\ 1 & 1 & 0 & 0 \\ 1 & -1 & 0 & 0 \end{pmatrix}$$




- ◆ Ideally there is no transmission between port 3 and port 4 nor between port 1 and port 2, even though you can look straight through it!
- ◆ Magic Ts are often produced as coaxial lines and printed circuits. They can be used taking the sum or difference of two signals. The bandwidth of a waveguide magic ‘T’ is around one octave or the equivalent H10-mode waveguide band. Broadband versions of 180° hybrids may have a frequency range from a few MHz to some GHz.

The directional coupler (1)

- ◆ Another very important 4-port is the directional coupler.
- ◆ General principle: We have two transmission lines, and a coupling mechanism is adjusted such that part of the power in line 1 is transferred to line 2. The coupler is *directional* when the power in line 2 travels mainly in one direction.
- ◆ In order to get directionality at least two coupling mechanisms are necessary, i.e. many holes or electric and magnetic coupling, as in the Bethe coupler.
- ◆ The $\lambda/4$ coupler has two holes at a distance $\lambda/4$. The two backwards coupled waves cancel while the forward coupled waves add up in phase

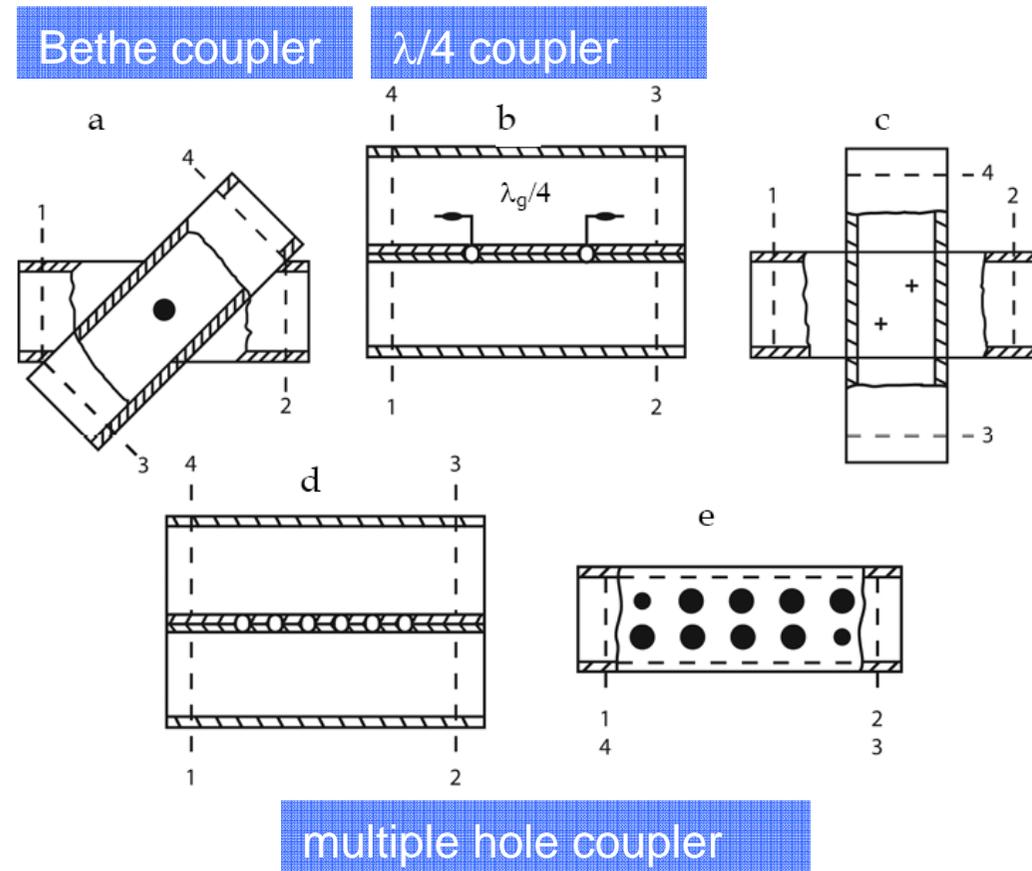Directional couplers with coupling holes in waveguide technology



The directional coupler (2)

- ◆ The *directivity* is defined as the ratio of the desired over the undesired coupled wave. For a forward coupler, in decibel,

$$\alpha_d = 20 \log \frac{|S_{31}|}{|S_{41}|}$$


- ◆ Practical numbers for the coupling are 3 dB, 6 dB, 10 dB, and 20 dB with directivities usually better than 20 dB
- ◆ The S matrix of the 3 dB coupler ($\pi/2$ -hybrid) can be derived as

$$S_{3dB} = \frac{1}{\sqrt{2}} \begin{pmatrix} 0 & 1 & \pm j & 0 \\ 1 & 0 & 0 & \pm j \\ \pm j & 0 & 0 & 1 \\ 0 & \pm j & 1 & 0 \end{pmatrix}$$

- ◆ Please note that this element is lossless, reciprocal and matched at all ports. This is possible for 4-ports.

General N-ports



- ◆ A general N-ports may included ports in different technologies, i.e. waveguides, coaxial lines, microstrip lines etc.
- ◆ In a given frequency range different modes may propagate at each physical port, e.g. several waveguide modes in a rectangular waveguide or higher order modes on a coaxial line.
- ◆ Each mode must then be represented by a distinct port.
- ◆ The number of ports needed generally increases with frequency, as more waveguide modes can propagate. In numerical simulations neglecting higher order modes in the model can lead to questionable results.

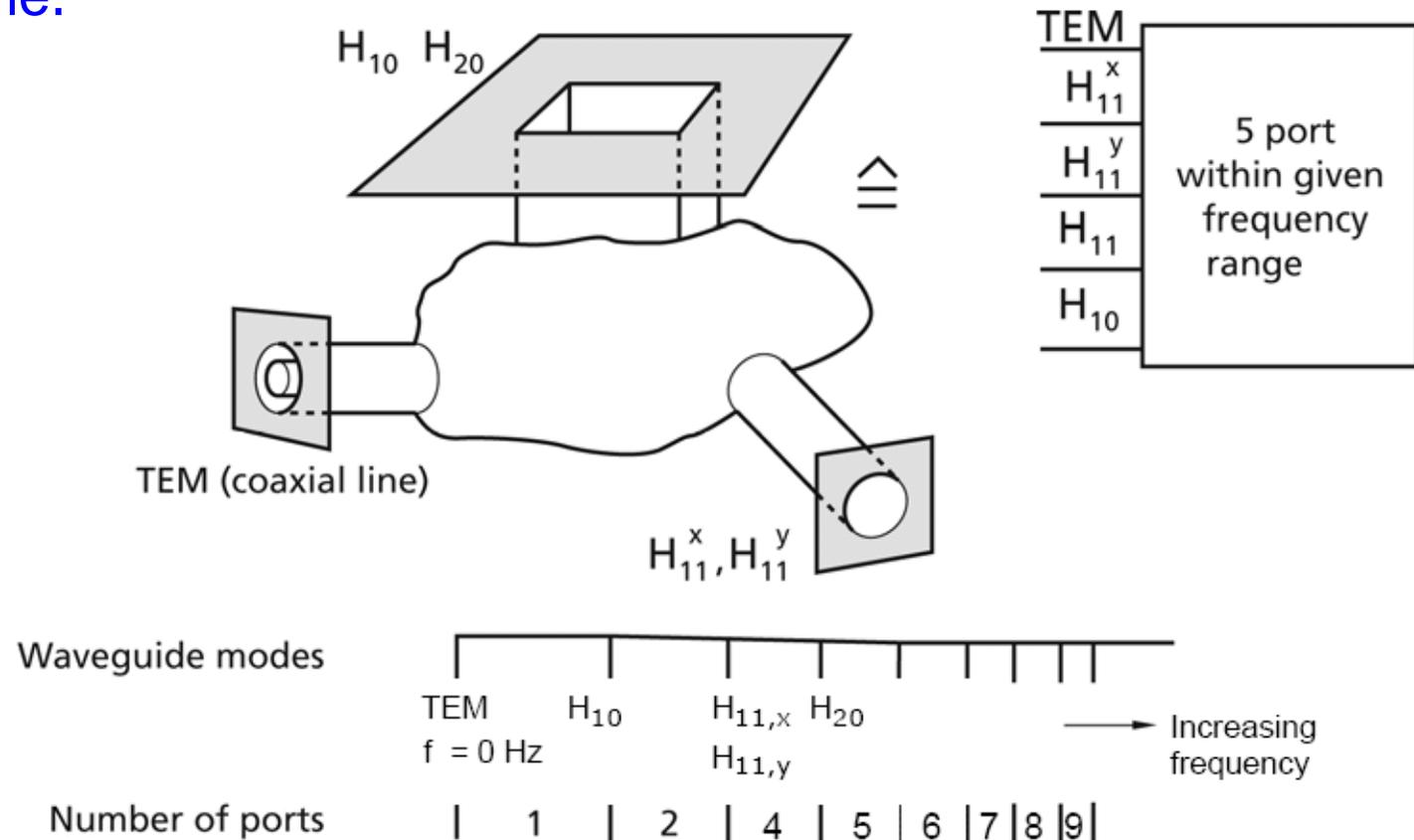



Directional couplers in microstrip technology

- ◆ Most of the RF elements shown can be produced at low price in printed circuit technology

90° 3-dB coupler

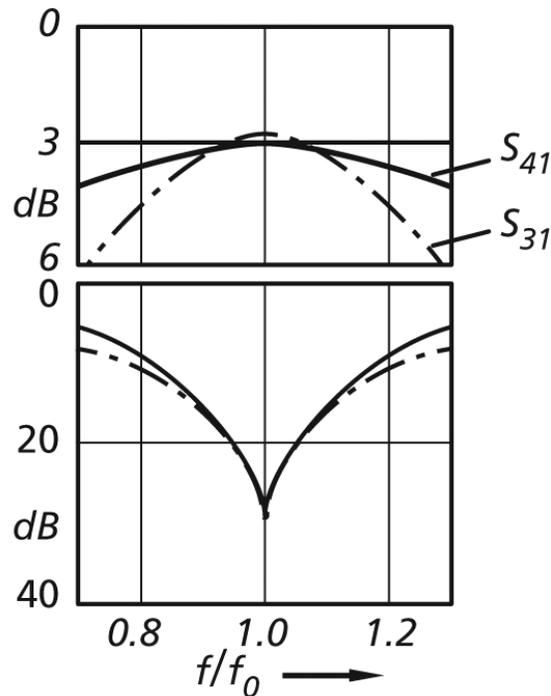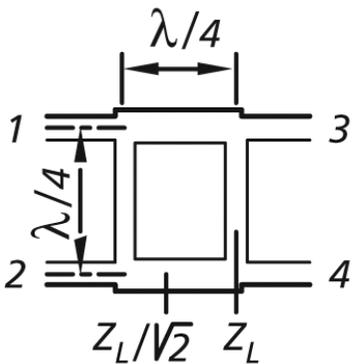


Magic T
(rat-race 180°)

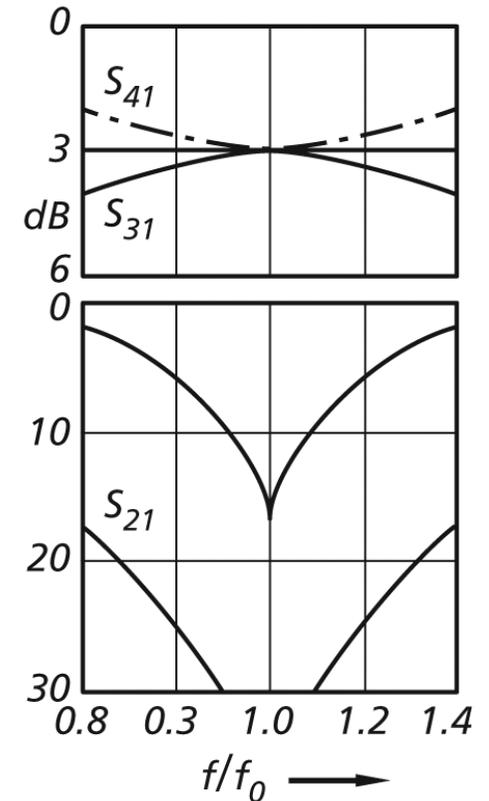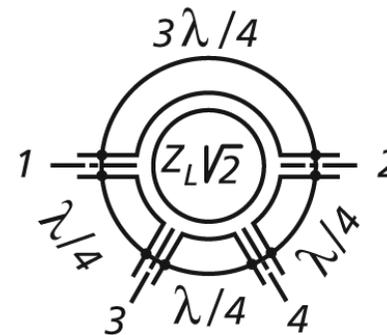

Striplines (1)

- ◆ A stripline is a flat conductor between a top and bottom ground plane. The space around this conductor is filled with a homogeneous dielectric material. This line propagates a pure TEM mode. With the static capacity per unit length, C' , the static inductance per unit length, L' , the relative permittivity of the dielectric, ϵ_r and the speed of light c the characteristic impedance Z_0 of the line is given by

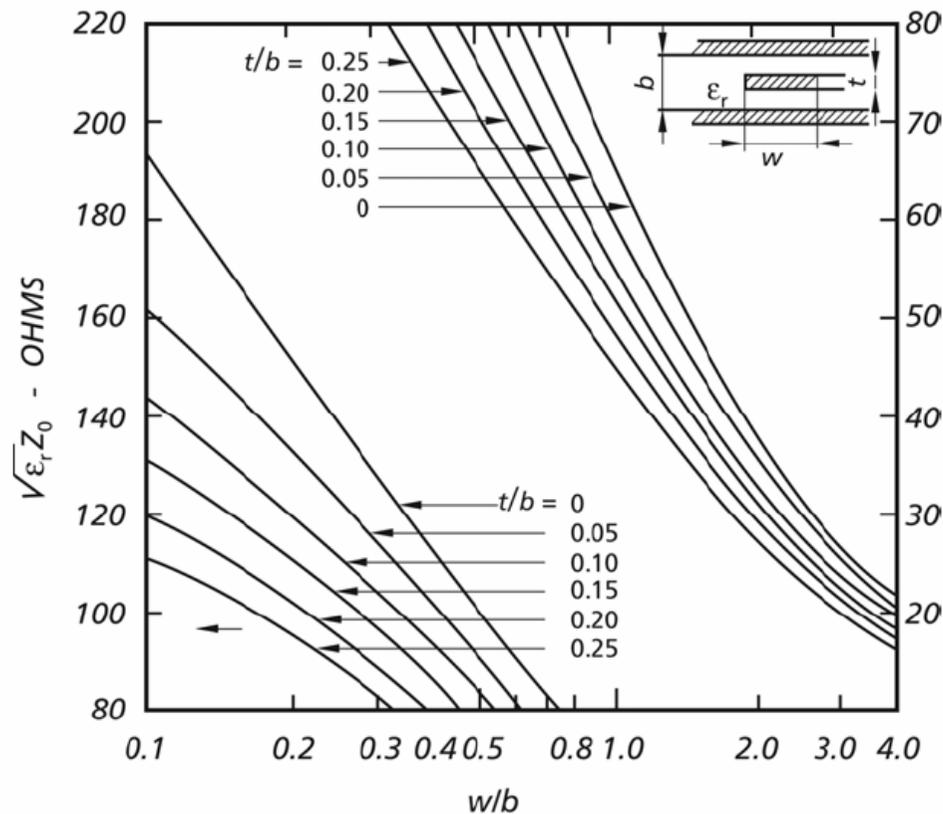

$$Z_0 = \sqrt{\frac{L'}{C'}}$$


$$v_{ph} = \frac{c}{\sqrt{\epsilon_r}} = \frac{1}{\sqrt{L'C'}}$$

$$Z_0 = \sqrt{\epsilon_r} \cdot \frac{1}{C'c} \quad (5.1)$$

Fig 19: char.impedance of striplines

Striplines (2)

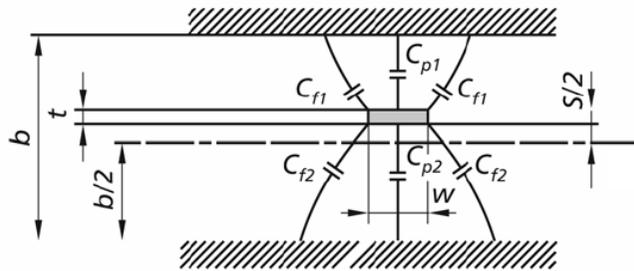- ◆ For a mathematical treatment, the effect of the fringing fields may be described in terms of static capacities (see Fig. 20) [14]. The total capacity is the sum of the principal and fringe capacities C_p and C_f .



$$C_{tot} = C_{p1} + C_{p2} + 2C_{f1} + 2C_{f2} \quad (5.2)$$

Fig. 20: Design, dimensions and characteristics for offset center-conductor strip transmission line [14]

- ◆ For striplines with an homogeneous dielectric the phase velocity is the same, and frequency independent, for all TEM-modes. A configuration of two coupled striplines (3-conductor system) may have two independent TEM-modes, an odd mode and an even mode (Fig. 21).

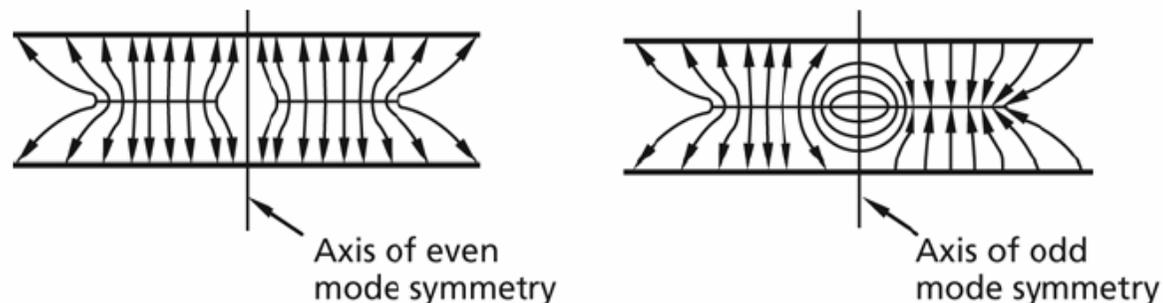


Fig. 21: Even and odd mode in coupled striplines [14]

Striplines (3)

- ◆ The analysis of coupled striplines is required for the design of directional couplers. Besides the phase velocity the odd and even mode impedances $Z_{0,odd}$ and $Z_{0,even}$ must be known. They are given as a good approximation for the side coupled structure (Fig. 22, left) [14]. They are valid as a good approximation for the structure shown in Fig. 22.

$$Z_{0,even} = \frac{1}{\sqrt{\epsilon_r}} \cdot \frac{94.15 \Omega}{\frac{w}{b} + \frac{\ln 2}{\pi} + \frac{1}{\pi} \ln \left(1 + \tanh \left(\frac{\pi s}{2b} \right) \right)}$$

$$Z_{0,odd} = \frac{1}{\sqrt{\epsilon_r}} \cdot \frac{94.15 \Omega}{\frac{w}{b} + \frac{\ln 2}{\pi} + \frac{1}{\pi} \ln \left(1 + \coth \left(\frac{\pi s}{2b} \right) \right)}$$

(5.3)

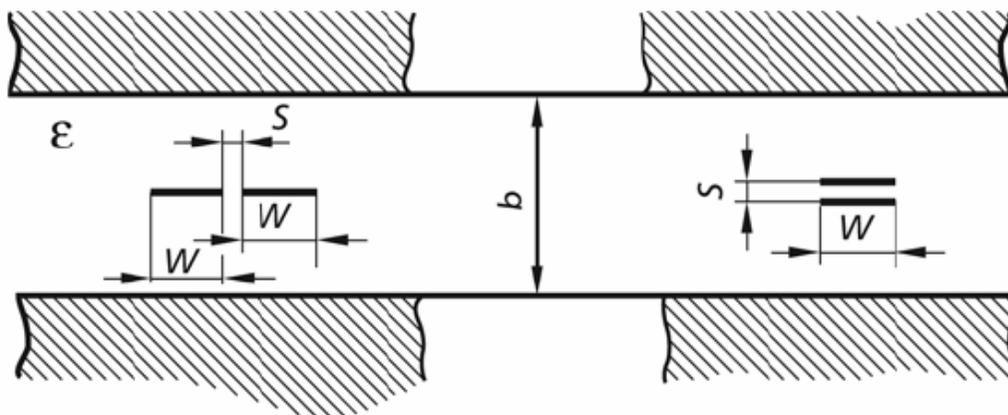


Fig. 22: Types of coupled striplines [14]: left: side coupled parallel lines, right: broad-coupled parallel lines

Striplines (4)

- ◆ A graphical presentation of Equations 5.3 is also known as the Cohn nomographs [14]. For a quarter-wave directional coupler (single section in Fig. 16) very simple design formulae can be given

$$\begin{aligned}Z_{0,odd} &= Z_0 \sqrt{\frac{1+C_0}{1-C_0}} \\Z_{0,even} &= Z_0 \sqrt{\frac{1-C_0}{1+C_0}} \\Z_0 &= \sqrt{Z_{0,odd} Z_{0,even}}\end{aligned}\tag{5.4}$$

where C_0 is the voltage coupling ratio of the $\lambda/4$ coupler.

- ◆ In contrast to the 2-hole waveguide coupler this type couples backwards, i.e. the coupled wave leaves the coupler in the direction opposite to the incoming wave. The stripline coupler technology is rather widespread by now, and very cheap high quality elements are available in a wide frequency range. An even simpler way to make such devices is to use a section of shielded 2-wire cable.

Microstrip (1)

- ◆ A microstripline may be visualized as a stripline with the top cover and the top dielectric layer taken away (Fig. 23). It is thus an asymmetric open structure, and only part of its cross section is filled with a dielectric material. Since there is a transversely inhomogeneous dielectric, only a quasi-TEM wave exists. This has several implications such as a frequency-dependent characteristic impedance and a considerable dispersion (Fig. 24).

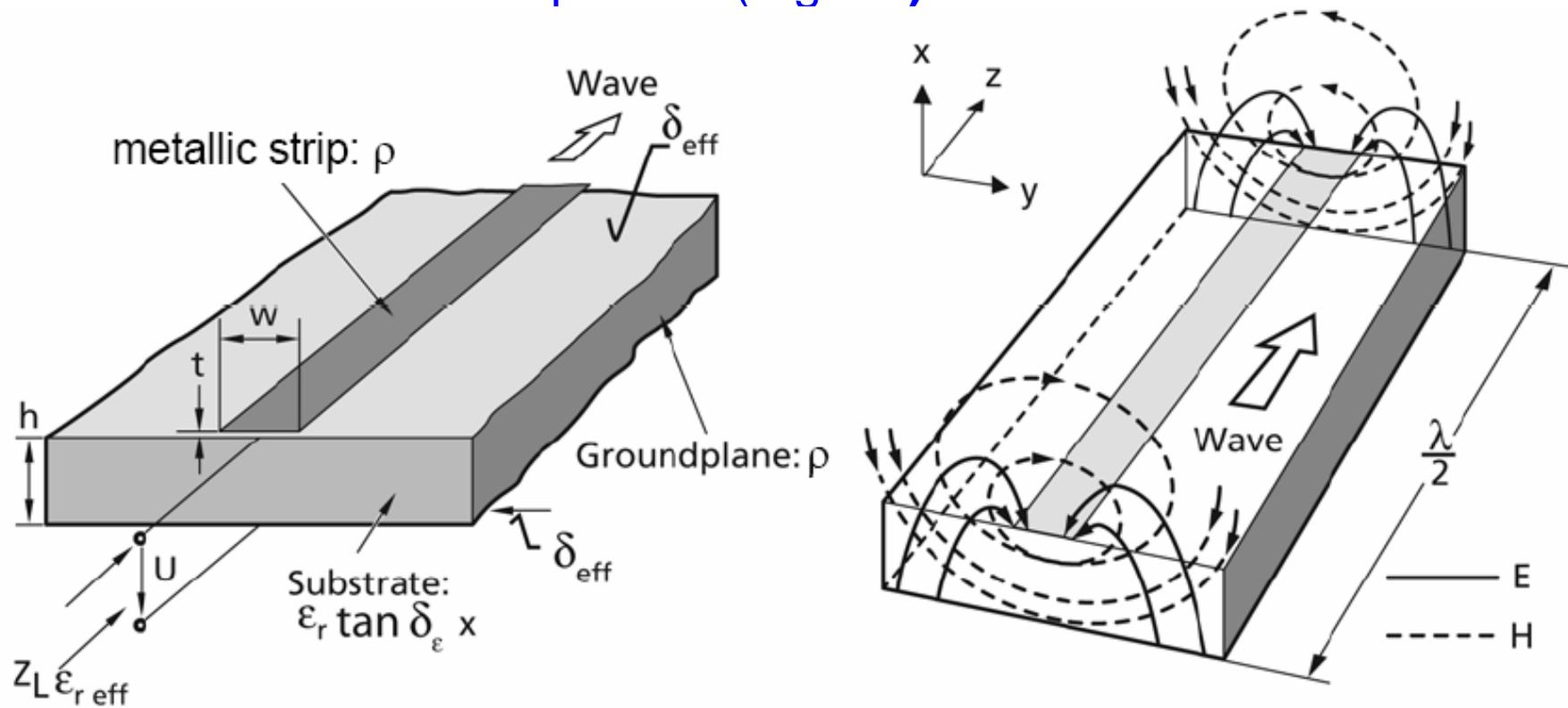


Fig.23 Microstripline: left: Mechanical construction, right: static field approximation [16].

Microstrip (2)

- ◆ An exact field analysis for this line is rather complicated and there exist a considerable number of books and other publications on the subject [16, 17]. Due to the dispersion of the microstrip, the calculation of coupled lines and thus the design of couplers and related structures is also more complicated than in the case of the stripline. Microstrips tend to radiate at all kind of discontinuities such as bends, changes in width, through holes etc.
- ◆ With all the disadvantages mentioned above in mind, one may question why they are used at all. The mains reasons are the cheap production, once a conductor pattern has been defined, and easy access to the surface for the integration of active elements. Microstrip circuits are also known as Microwave Integrated Circuits (MICs). A further technological step is the MMIC (Monolithic Microwave Integrated Circuit) where active and passive elements are integrated on the same semiconductor substrate.
- ◆ In Figs. 25 and 26 various planar printed transmission lines are depicted. The microstrip with overlay is relevant for MMICs and the strip dielectric wave guide is a 'printed optical fibre' for millimeter-waves and integrated optics [17].

Microstrip (3)

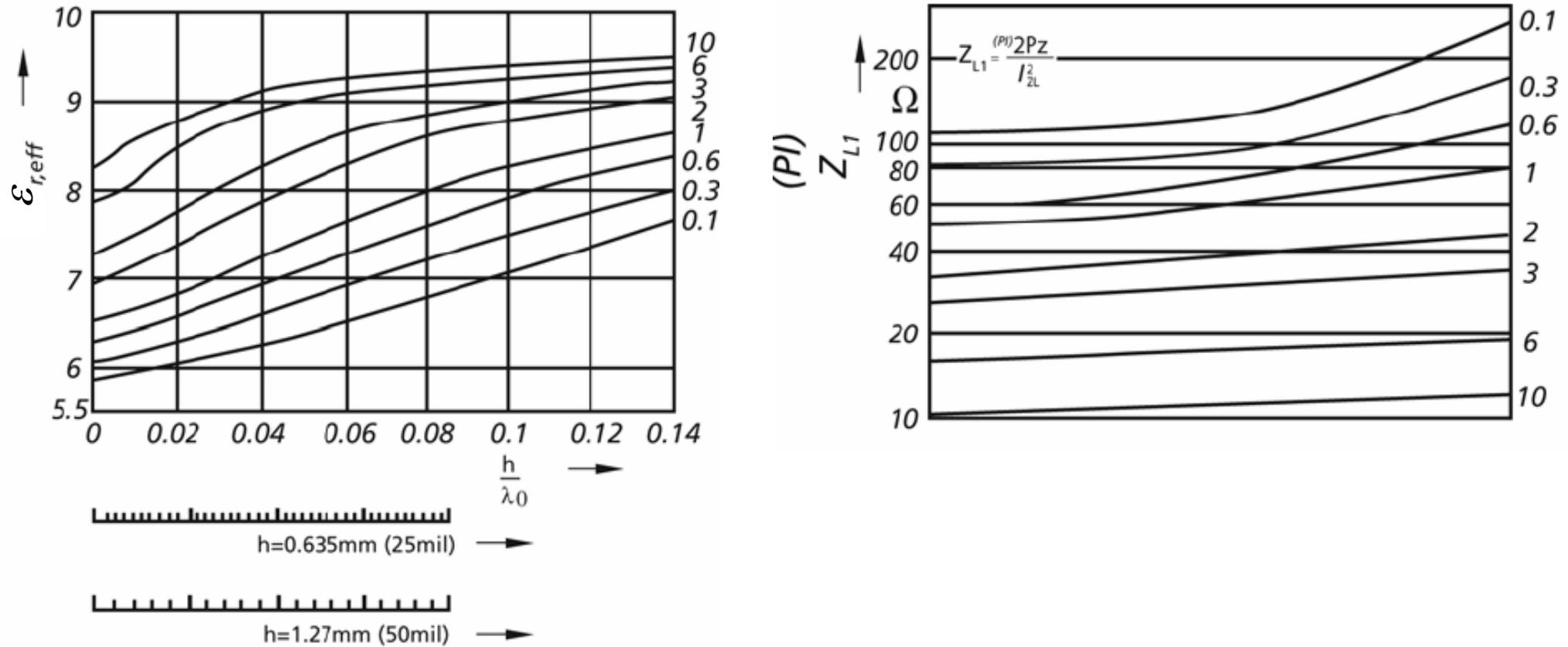


Fig. 24: Characteristic impedance (current/power definition) and effective permittivity of a microstrip line [16]

Microstrip (4)

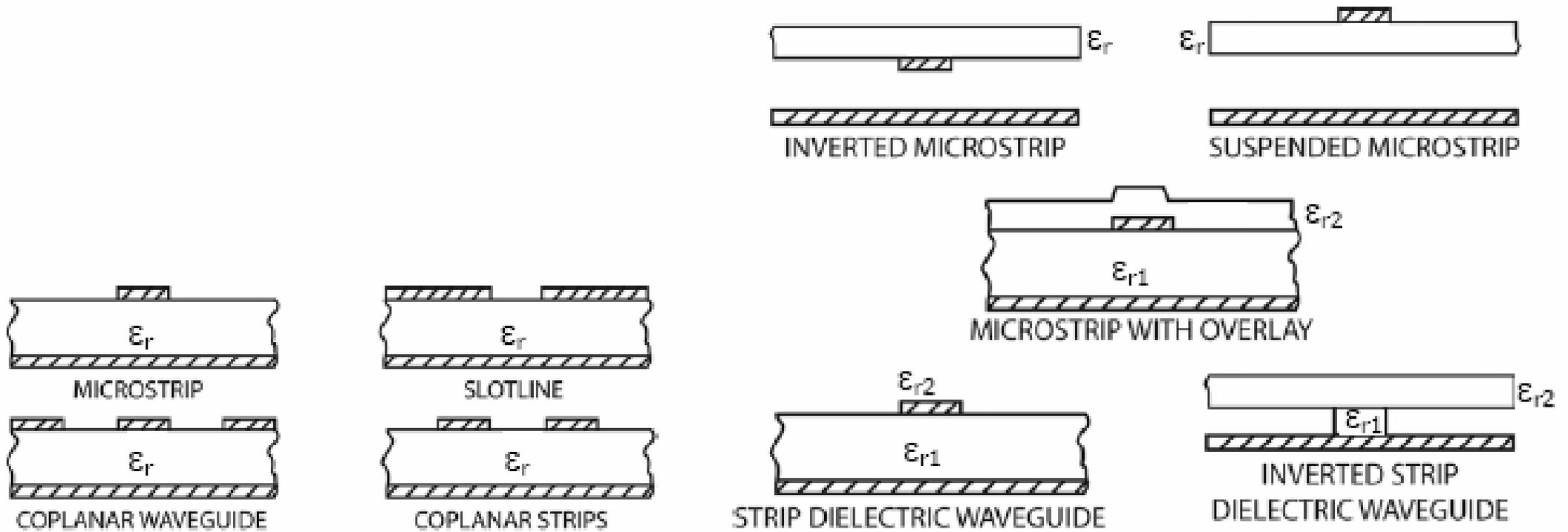


Fig. 25 (left): Planar transmission lines used in MICs; Fig 26 (right): various Transmission lines derived from microstrip

Slotlines (1)

- ◆ The slotline may be considered as the dual structure of the microstrip. It is essentially a slot in the metallization of a dielectric substrate as shown in Fig. 27. The characteristic impedance and the effective dielectric constant exhibit similar dispersion properties to those of the microstrip line. A unique feature of the slotline is that it may be combined with microstrip lines on the same substrate. This, in conjunction with through holes, permits interesting topologies such as pulse inverters in sampling heads (e.g. for sampling scopes).

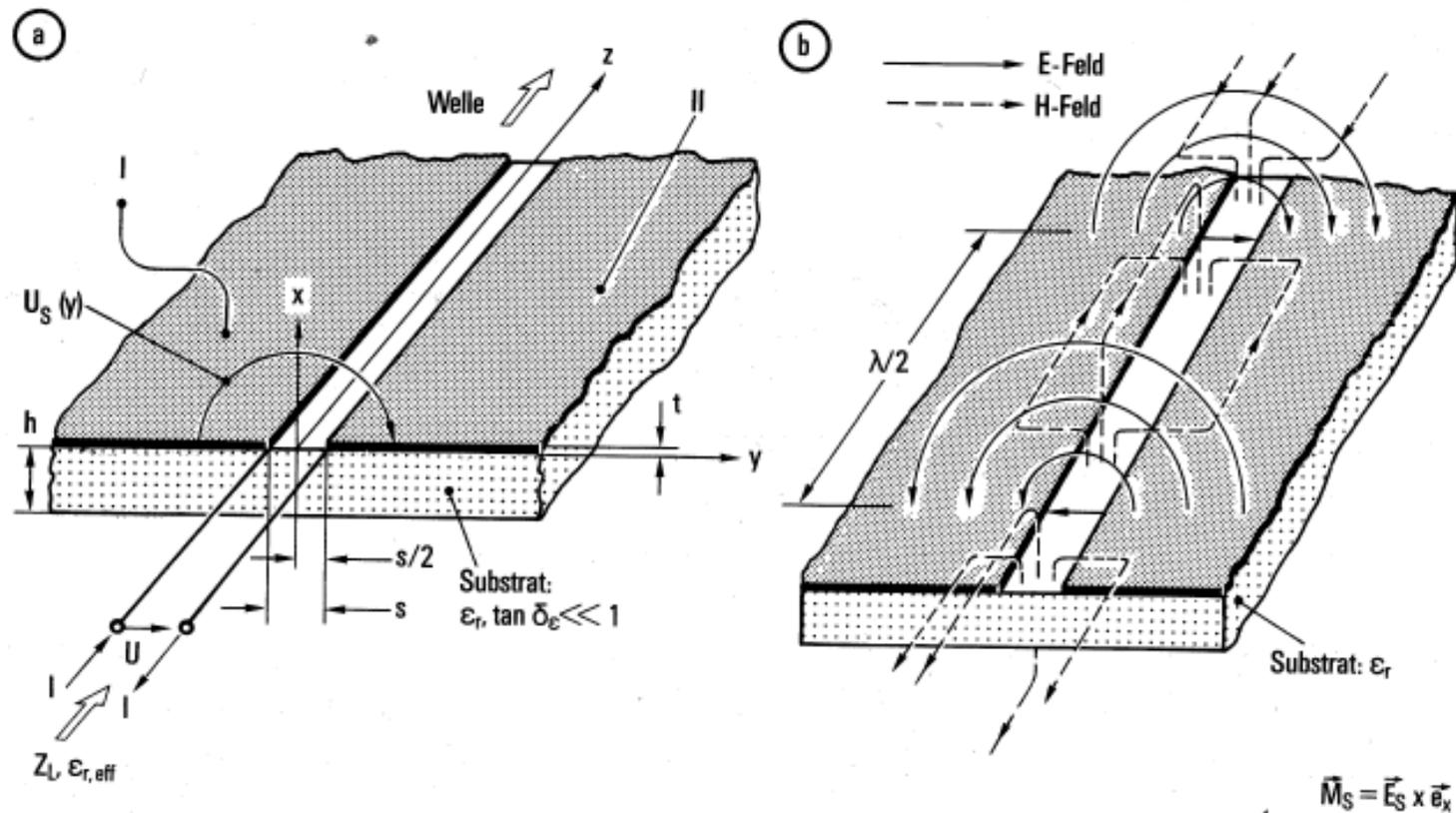


Fig 27 part 1: Slotlines a) Mechanical construction, b) Field pattern (TE-approximation)

Slotlines (3)

- ◆ Fig. 28 shows a broadband (decade bandwidth) pulse inverter. Assuming the upper microstrip to be the input, the signal leaving the circuit on the lower microstrip is inverted since this microstrip ends on the opposite side of the slotline compared to the input. Printed slotlines are also used for broadband pickups in the GHz range, e.g. for stochastic cooling [15].

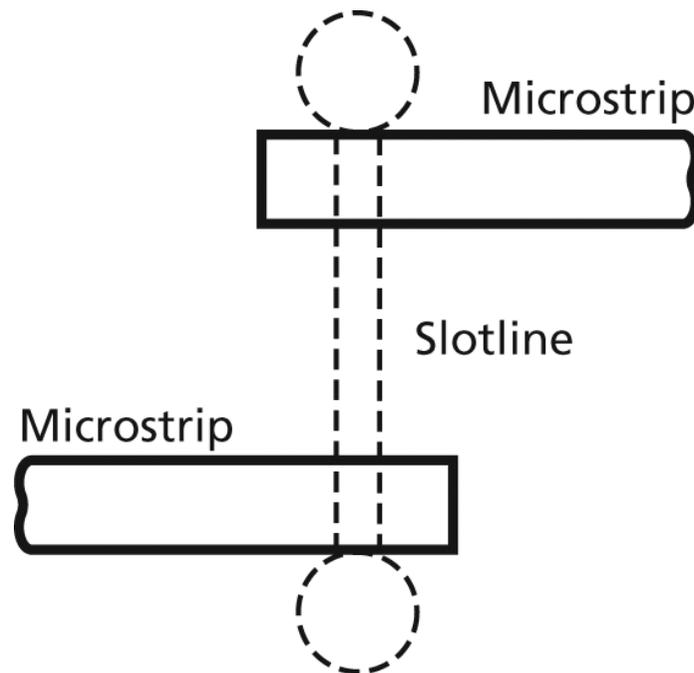


Fig 28. Two microstrip-slotline transitions connected back to back for 180° phase change [17]

The Smith Chart - definition

- ◆ The Smith Chart is a very handy tool for visualizing and solving RF problems
- ◆ It indicates in the plane of the complex reflection coefficient ρ the corresponding value of the complex impedance $Z = R + jX$. Often the normalized impedance z is used, with $z = Z/Z_0$, where Z_0 is an arbitrary characteristic impedance, e.g. $Z_0 = 50 \Omega$. The reflection coefficient is given as

$$\rho = \frac{Z - Z_0}{Z + Z_0} = \frac{z - 1}{z + 1} \quad (6.1)$$


or in terms of admittance $Y = 1/Z = G + jB$, with the normalized admittance $y = Y/Y_0$, where $Y_0 = 1/Z_0$

$$\rho = -\frac{Y - Y_0}{Y + Y_0} = -\frac{y - 1}{y + 1} \quad (6.2)$$

Equations 6.1 and 6.2 define *conformal mappings* from the z and the y plane to the ρ plane.


The Smith Chart - construction

- ◆ A very basic use of the Smith Chart is to graphically convert values of ρ into z and vice versa. To this purpose in the ρ plane a grid is drawn that allows to find the value of z at a given point ρ .
- ◆ An important property of conformal mappings is that general circles are mapped to general circles. Straight lines are considered as circle with infinite radius
- ◆ Below the loci of constant resistance and constant reactance are drawn in the ρ plane
- ◆ The origin of the ρ plane is marked with a red dot, the diameter of the largest circle is $|\rho|=1$

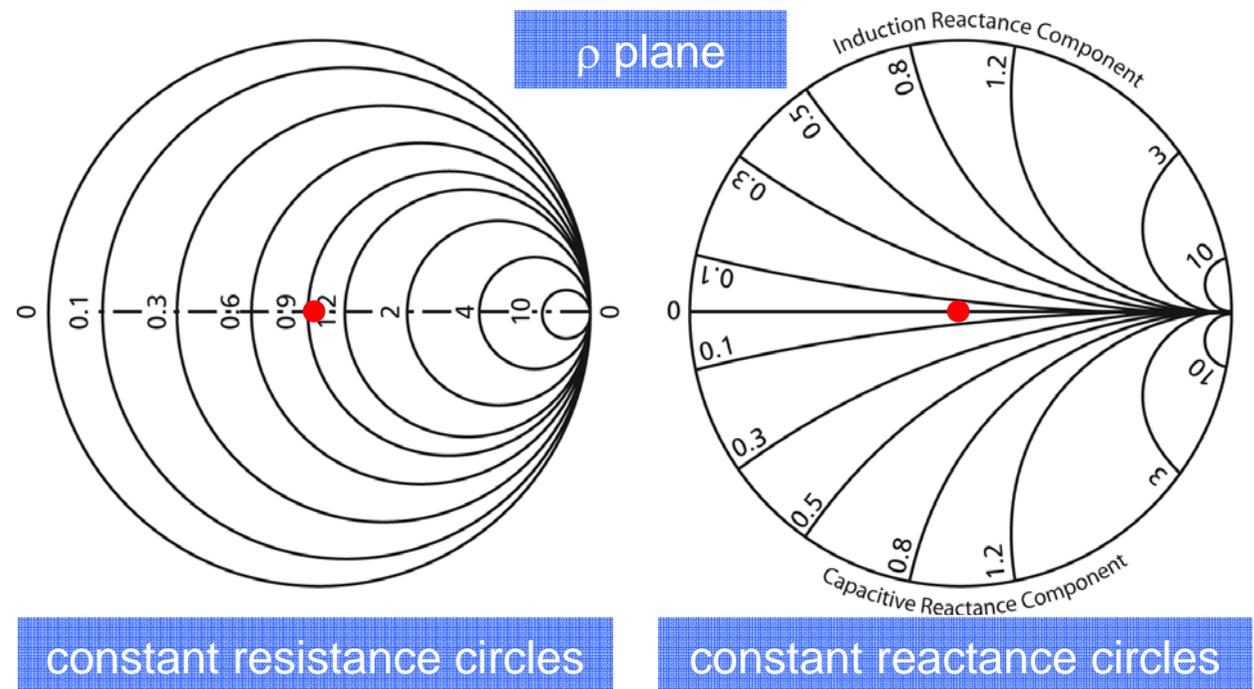

The Smith Chart


- ◆ The Smith Chart is simply the ρ plane with overlaid circles that help to find the z for each point. The radius in is general $\rho = 1$.
- ◆ Important points:
 - Center of the Smith Chart: matched load. $\rho = 0, z = 1$
 - Open circuit: $\rho = +1, z = \infty$
 - Short circuit: $\rho = -1, z = 0$
- ◆ Lossless elements lie on the circle $|\rho|=1$; active elements, such as reflection amplifiers, lie outside this circle.

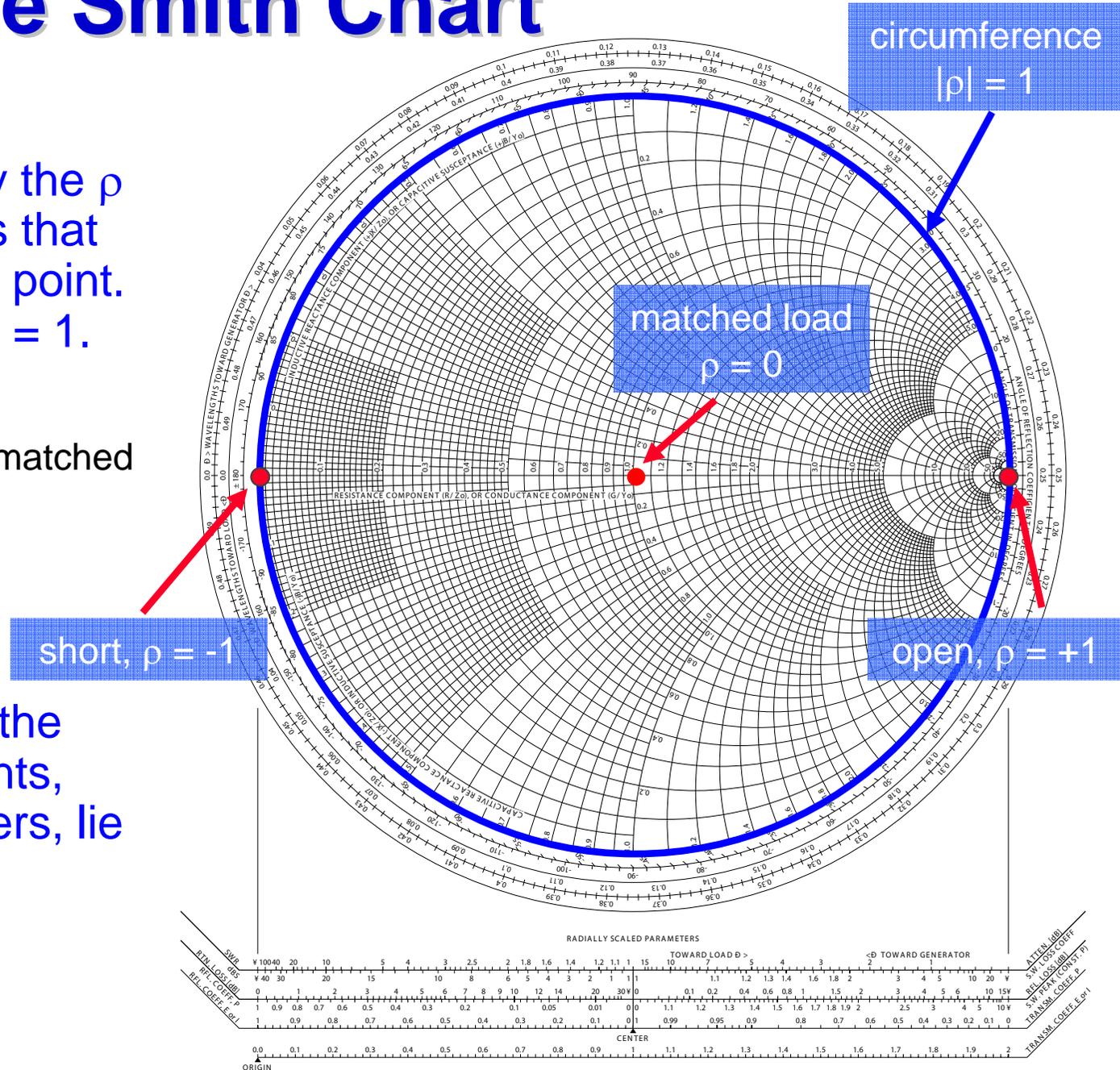

Downloaded from <http://www.sss-mag.com/smith.html>

Navigation in the Smith Chart 1

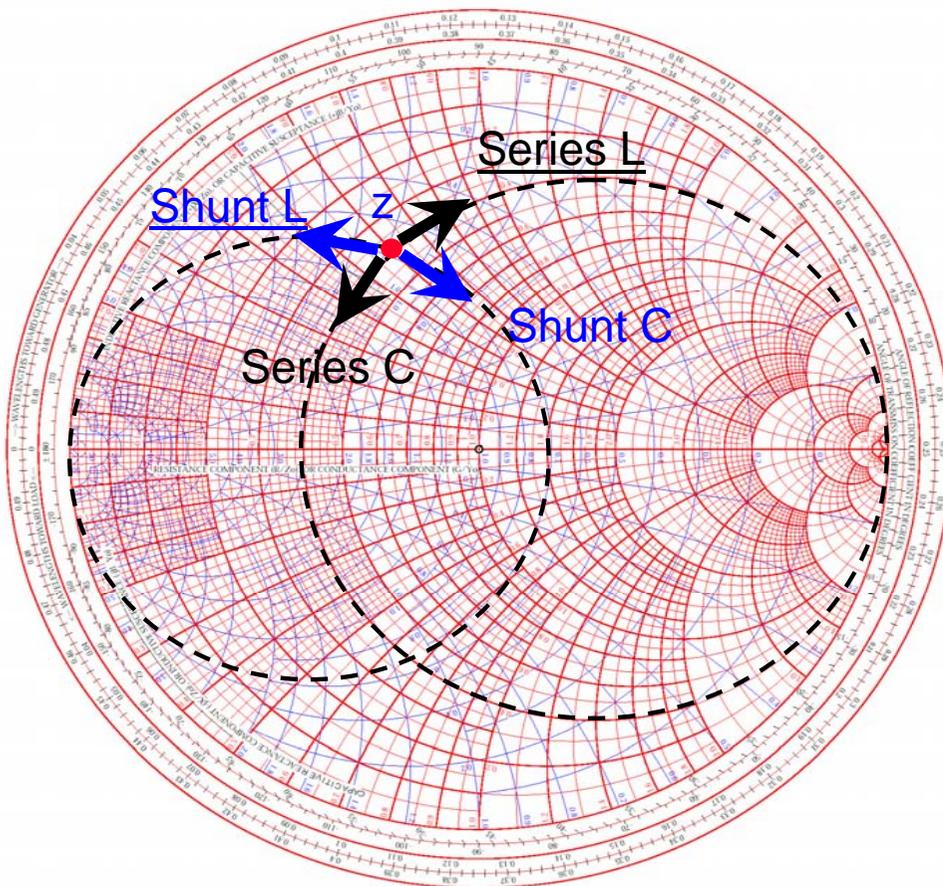
- ◆ When a lossless element is added *in series* to an impedance z , one moves along the constant resistance circles ($R = \text{const}$)
- ◆ When a lossless element is added *in parallel (shunt)* to an impedance z , one moves along the circles conductance ($G = \text{const}$)



	<u>Up</u>	Down
Black circles	<u>Series L</u>	Series C
Blue circles	<u>Shunt L</u>	Shunt C

Navigation in the Smith Chart 2

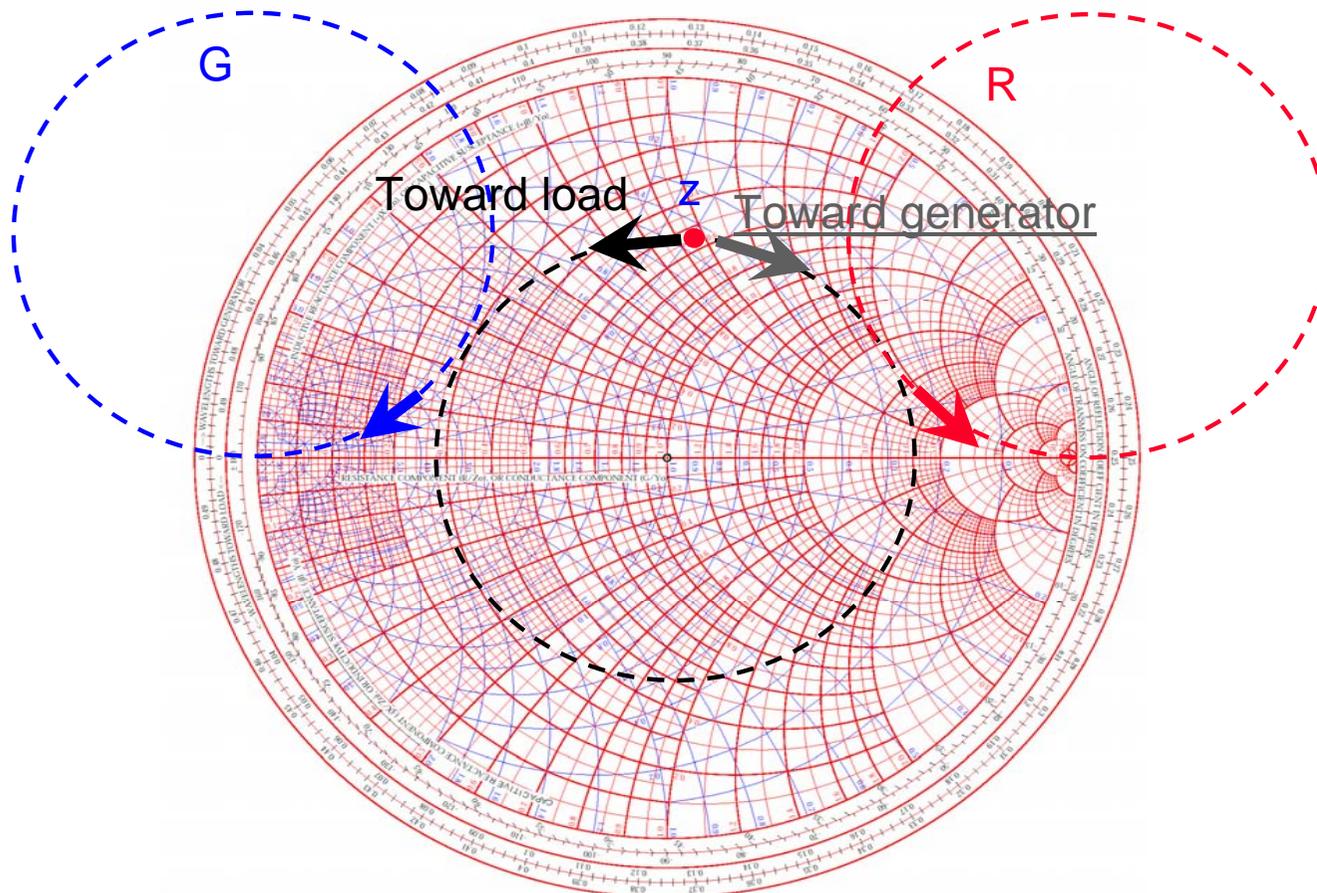- ◆ An ideal lossless transmission line only changes the phase of $\rho \Rightarrow$ a transmission line gives a rotation about the center of the Smith Chart
- ◆ For a line of length $\lambda/4$ we get a rotation by 180 degrees \Rightarrow a short circuit is converted into an open circuit and vice versa. Such a line is called $\lambda/4$ transformer.



Red arcs	Resistance R in series
Blue arcs	Conductance G in parallel
Concentric circle	Transmission line going Toward load <u>Toward generator</u>

The quality factor

- ◆ The quality (Q) factor of a resonant circuit is defined as the ratio of the stored energy W over the energy dissipated P in one cycle.

$$Q = \frac{\omega W}{P}$$

- ◆ Q_0 : *Unloaded Q factor* of the unperturbed system, e.g. a closed cavity
- ◆ Q_L : *Loaded Q factor* with measurement circuits etc connected
- ◆ Q_{ext} : *External Q factor* of the measurement circuits etc
- ◆ These Q factors are related by


$$\frac{1}{Q_L} = \frac{1}{Q_0} + \frac{1}{Q_{ext}}$$

- ◆ The Q factor of a resonance peak or dip can be calculated from the center frequency f_0 and the 3 dB bandwidth Δf as

$$Q = \frac{f_0}{\Delta f}$$

Q factor measurement in the Smith Chart

- ◆ The typical locus of a resonant circuit in the Smith chart is illustrated as the dashed red circle
- ◆ From the different marked frequency points the 3 dB bandwidth and thus the quality factors Q_0 , Q_L and Q_{ext} can be determined (see lecture notes)
- ◆ The larger the circle, the stronger the coupling
- ◆ In practise, the circle may be rotated around the origin due to transmission lines between the resonant circuit and the measurement device

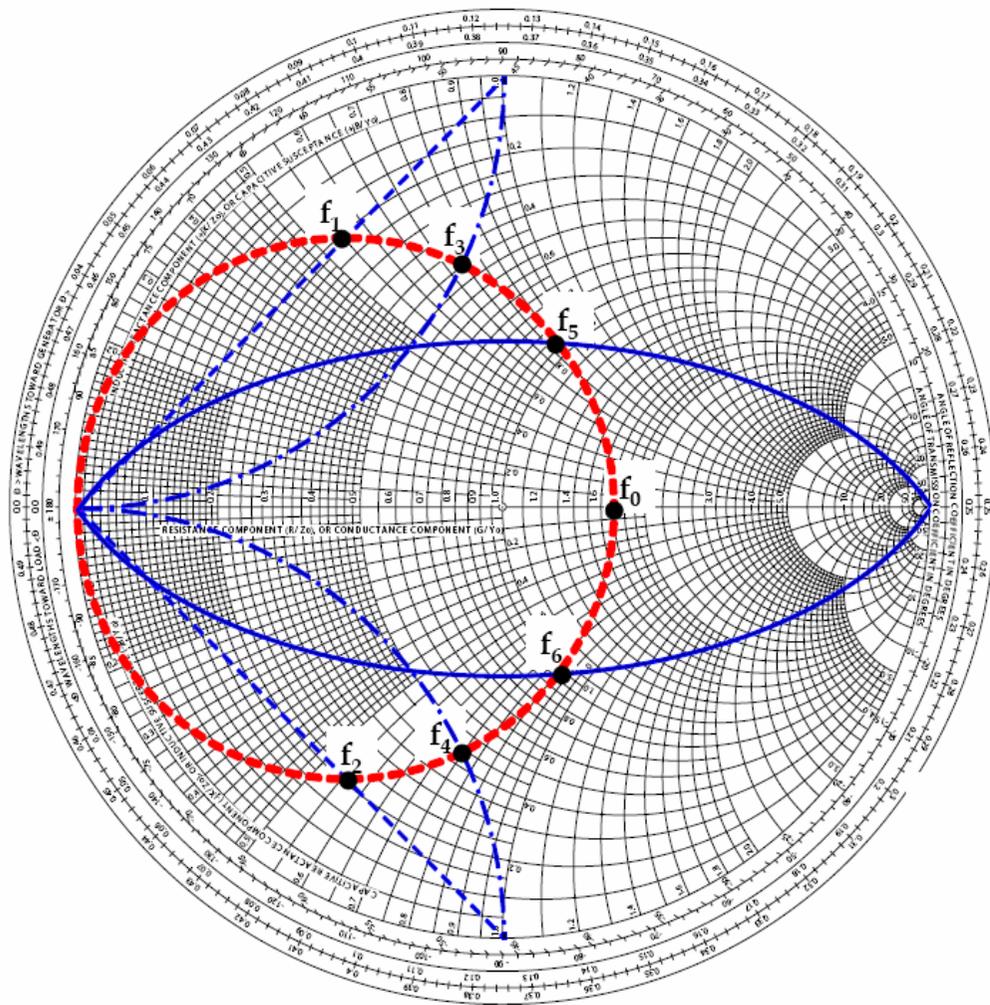

Q factor measurement in the Smith Chart 2

- ◆ f_0 gives the center frequency of the resonator. Condition: $|S_{11}| \rightarrow \min$. Procedure in Smith Chart:
 - ◆ Resonator in “detuned short” position
 - ◆ Marker format: S_{11} (amplitude and phase)
 - ◆ Search for the minimum of $|S_{11}|$
 - ◆ Read f_0 and the resonator shunt impedance $R = \text{Re}\{S_{11}\}$
- ◆ The unloaded Q_0 can be determined from f_5 and f_6 . Condition: $\text{Re}\{Z\} = \text{Im}\{Z\}$ in detuned short position.
 - ◆ Resonator in “detuned short” position
 - ◆ Marker format: Z
 - ◆ Search for the two points where $\text{Re}\{Z\} = \text{Im}\{Z\} \Rightarrow f_5$ and f_6
- ◆ The loaded Q_L can be calculated from the “half-power” points f_1 and f_2 . Condition: $|\text{Im}\{S_{11}\}| \rightarrow \max$
 - ◆ Resonator in “detuned short” position
 - ◆ Marker format: $\text{Re}\{S_{11}\} + j\text{Im}\{S_{11}\}$
 - ◆ Search for the two points where $|\text{Im}\{S_{11}\}| \rightarrow \max \Rightarrow f_1$ and f_2
- ◆ The external Q_E can be calculated from f_3 and f_4 . Condition: $Z = \pm j$ in detuned open position
 - ◆ Resonator in “detuned open” position
 - ◆ Marker format: Z
 - ◆ Search for the two points where $Z = \pm j \Rightarrow f_3$ and f_4