



CERN

European Organization for Nuclear Research

Organisation Européenne pour la Recherche Nucléaire

# ***Power converters***

***Definitions and classifications  
Converter topologies***

***Frédéric BORDRY  
CERN***

**"Introduction to Accelerator Physics"  
19<sup>th</sup> September – 1<sup>st</sup> October, 2010  
Варна - Varna - Bulgaria**






# Menu


- Power converter definition
- Power converter topologies: *commutation*  
Sources, switches,...semiconductors
- Special case for magnet powering  
(Voltage source - Current source)
- Pulsed power converters
- Control and precision
- Conclusion

In 1 hour ????

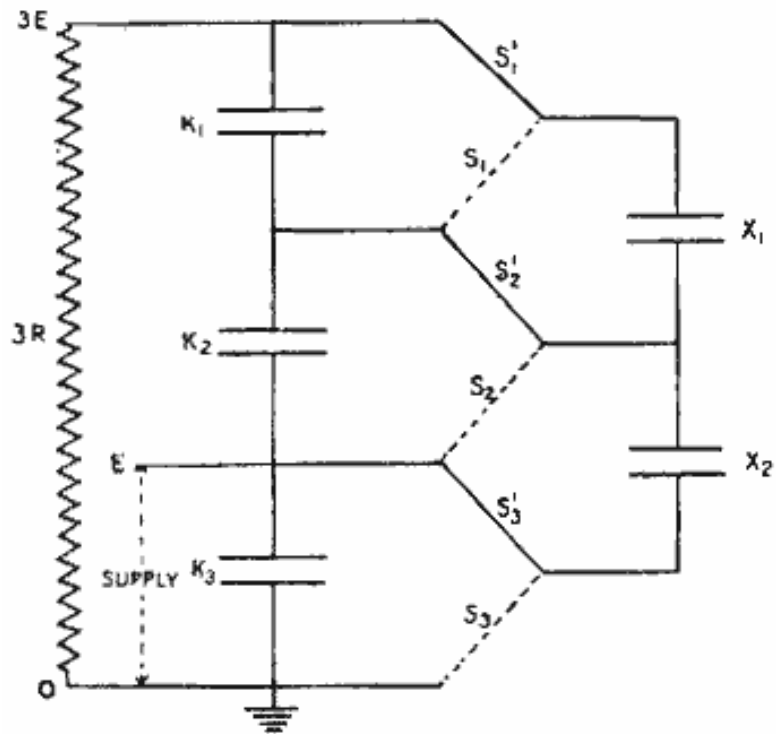

Schematic of Cockcroft and Walton's voltage multiplier. **Opening and closing the switches S transfers charge** from capacitor K3 through the capacitors X up to K1.

**Voltage multiplier : switches...**

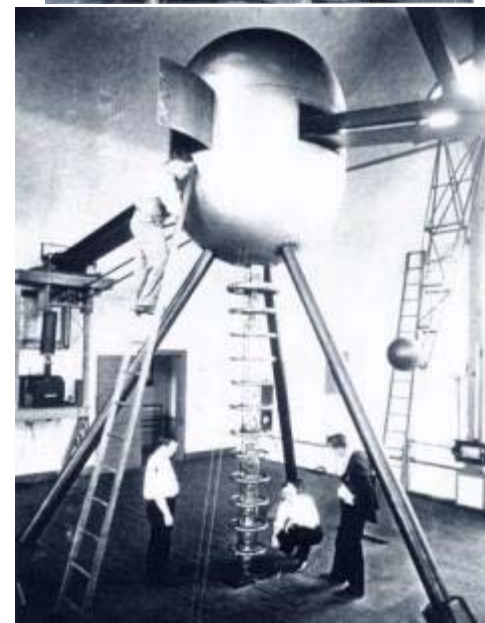



“On a new principle for the production of higher voltages.”


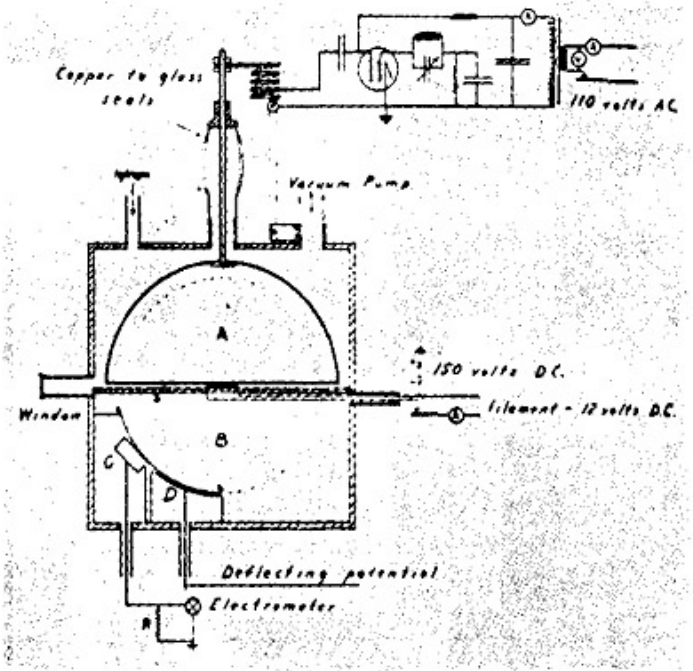


Diagram of the first successful cyclotron constructed by Lawrence and M. S. Livingston. The single dee is five inches in diameter.

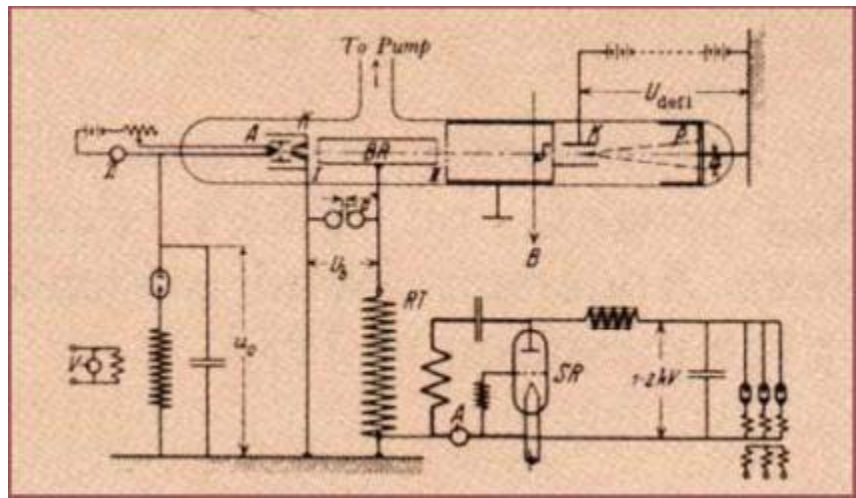

The difficulties of maintaining high voltages led several physicists to propose accelerating particles by using a lower voltage more than once. Lawrence learned of one such scheme in the spring of 1929, while browsing through an issue of *Archiv für Elektrotechnik*, a German journal for electrical engineers. Lawrence read German only with great difficulty, but he was rewarded for his diligence: he found an article by a Norwegian engineer, Rolf Wideröe, the title of which he could translate as “On a new principle for the production of higher voltages.” The diagrams explained the principle and Lawrence skipped the text.



# ***Power converters : Definitions***

**The source of the beam blow-up when we could not prove it was the RF** (Control room operator)

**A powerful (small) black box able to convert MAD files into currents** (Accelerator Physics group member)

**An equipment with three states, ON, OFF and FAULT** (Another operator)

**Is it the same thing as a power supply?** (Person from another physics lab)

**A big box with wires and pipes everywhere and blinking lamps. Occasionally it goes BANGG!** (Former CERN Power Converter Group secretary view)



# ***Power converters : Definitions (cont'd)***

**That which feeds the magnets** (a visitor)

**A stupid installation taking a non-sinusoidal current at poor power factor** (Power distribution engineer)

**A standard piece of equipment available from industry off-the-shelf**  
(a higher management person, not in in this room !)


**Ровер Цонвертер** (written in Cyrillic)


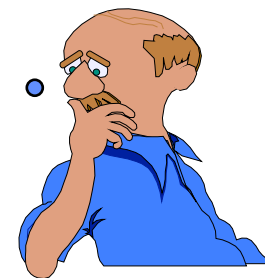
# Power converters specifications

**"Do you have one or two power converters for the test of magnet prototypes? 40 A will be enough ?  
Precision is not important for time being.  
Don't worry it's not urgent. Next month is OK "  
(Email received 05.12.08)**


**40A power converter:  
Size? Weight ? Cost?**





# [40A, 100 kV] klystron power converter

**DC Power: 4 MW**

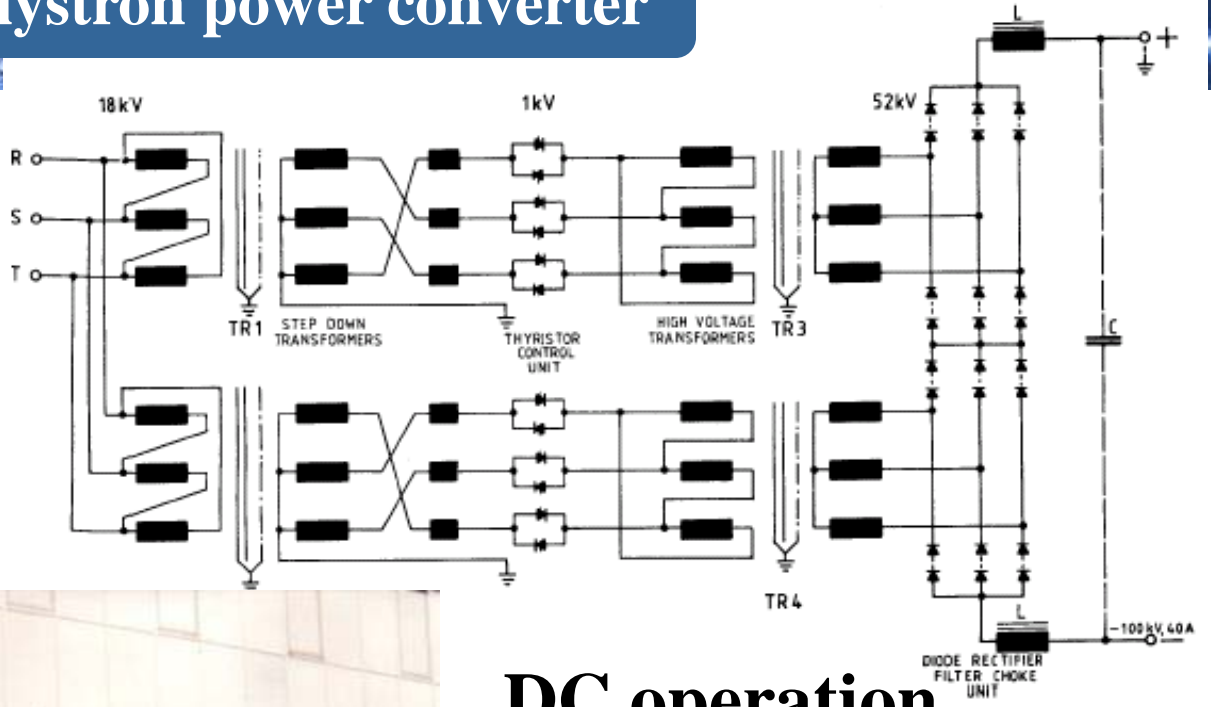

September 2010



## DC operation





## Characteristics :

- output voltage : 100 kV
- output current : 20 A
- pulse length : 700  $\mu$ s
- flat top stability : better than 1%
- 2 Hz repetition rate

**Peak power : 2 MW**

**Average power: 4 kW**





# LHC orbit corrector : [ $\pm 60A, \pm 8V$ ]

Magnet :  $L=7\text{ H}$  ;  $R = 30\text{ m}\Omega$  (60m of 35 mm<sup>2</sup>)

$T = L/R = 300\text{ s}$

$U_{\text{static}} = R.I = 1.8V$



6 V for the  $di/dt$  with  $L= 7\text{ H}$  ( $V = RI + L di/dt$ )

$\Rightarrow di/dt_{\text{max}} < 1A/s$

Small signal :  $f_{\text{CL}_B}^{\text{CL}} \cong 1\text{ Hz}$  :  $\Delta I = 0.13\text{ A} \cong 0.25\% I_{\text{max}}$   
( $L\omega\Delta I = 7 \times 2\pi \times f_{\text{CL}_B}^{\text{CL}} \times 0.13 \cong 6\text{ V}$ )

“The power converters involved in feedback of the local orbit may need to deal with correction rates between 10 and 500 Hz”;

$f_{\text{CL}_B}^{\text{CL}} \cong 50\text{Hz}$  ( $\Delta I = 2\%$  :  **$U_{\text{max}} = 2500\text{ V} \text{ ??????...$** )

( $U_{\text{max}} = 8V \Rightarrow \Delta I \cong 50\text{ ppm } I_{\text{max}}$  at 50 Hz)





# *Power converters specifications*

**"Do you have one or two power converters for the test of magnet prototypes? 40 A will be enough ?  
Precision is not important for time being.  
Don't worry it's not urgent. Next month is OK "  
(Email received 05.12.08)**

## **Need of more specification data**

**Output Voltage**

**DC or Pulsed (pulse length and duty cycle)**

**Output voltage and current reversibility**

**Precision (short and long term)**

**Ripple**

**Environment conditions: grid, volume, water ,....**



# Energy source




# Applications


## Power converter

The task of a power converter is to process and control the flow of electric energy by supplying voltages and currents in a form that is optimally suited for user loads.


Control

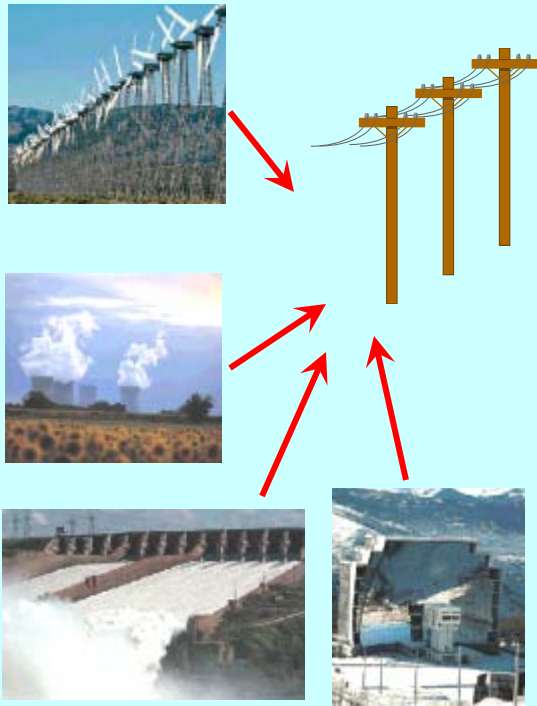

50 or 60 Hz ; AC

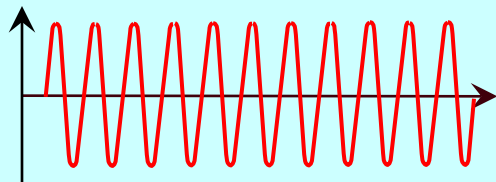


Traction and auxiliary

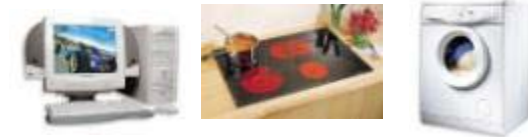

Domestic Appliance




Medical applications

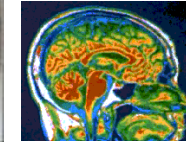


Industrial applications, Welding, Induction Heating, ....



DC current

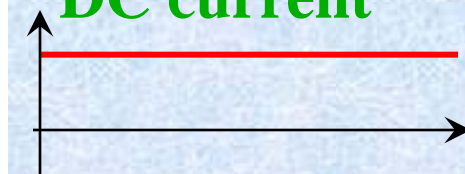



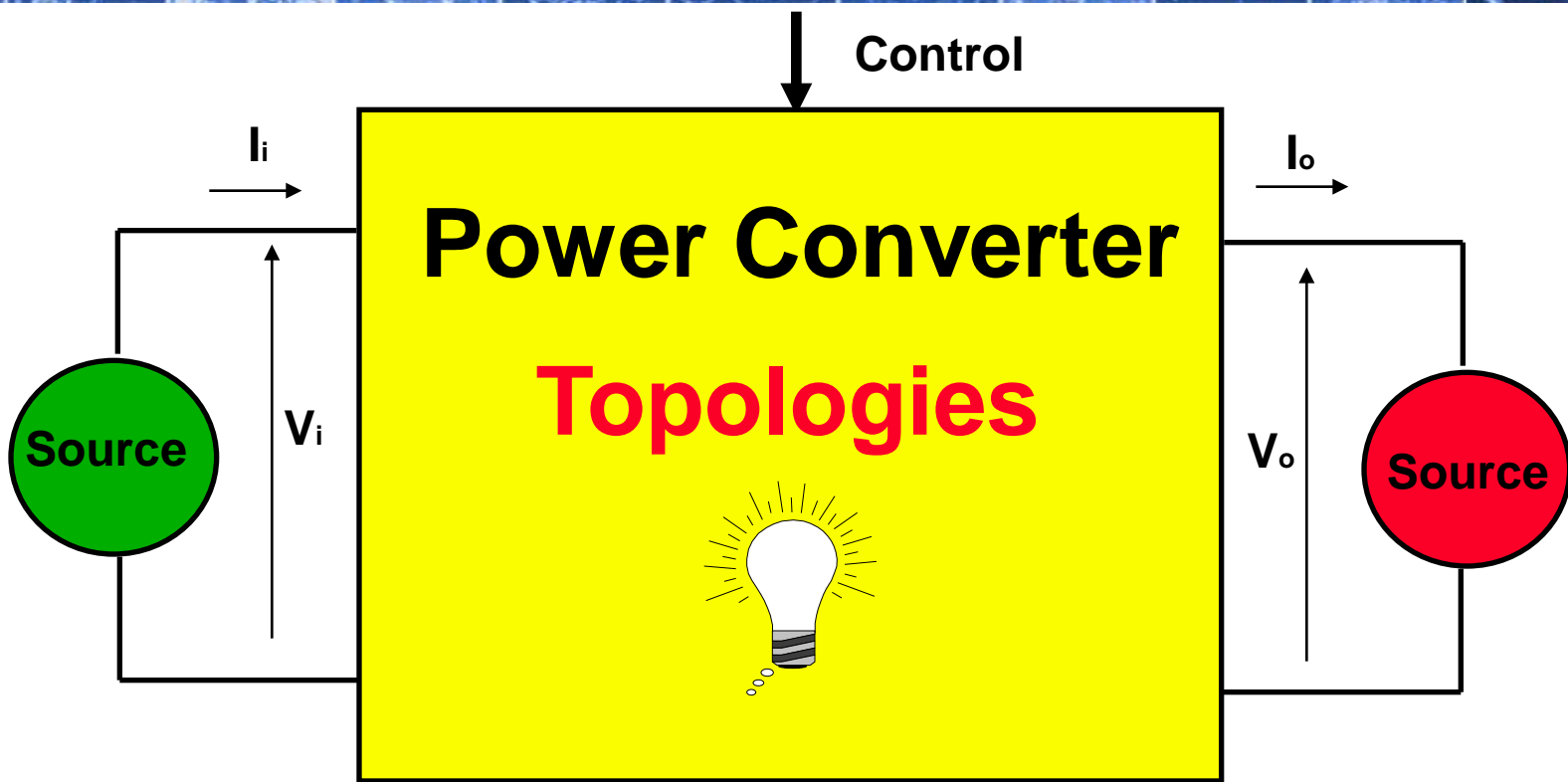

Electrical energy transfer



**Power Converter  
Design**

- performance
- efficiency
- reliability (MTBF), reparability (MTTR),
- effect on environment (RFI, noise,...)
- low cost



# Source definition

**Source definition:** any element able to impose a voltage or a current, independently of, respectively, the current flowing through, or the voltage imposed at its terminals.

**A source could be a generator or a receptor.**

Two types of sources:



## Voltage source

which imposes a voltage independently of the current flowing through it. This implies that the series impedance of the source is zero (or negligible in comparison with the load impedance)
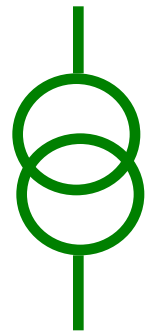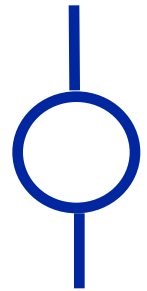
## Current source



which imposes a current independently of the voltage at its terminals.

This implies that the series impedance of the source is infinite (or very large in comparison with the load impedance)




# Energy conversion : transfer of energy between two sources

## Introductory example

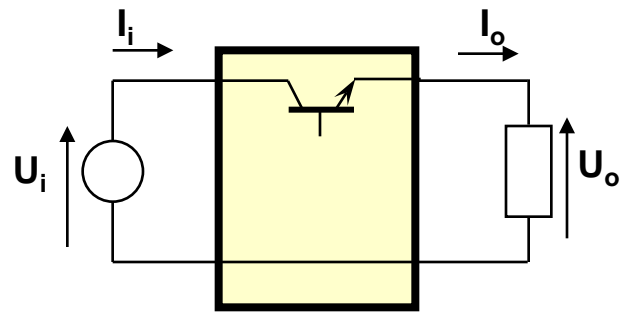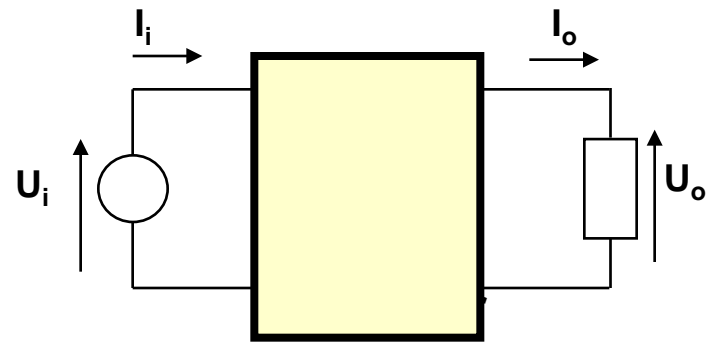

Linear solution

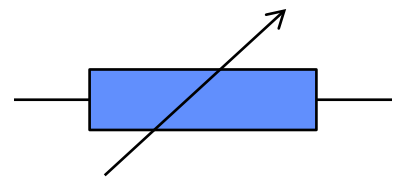


### Transfer of energy between

- DC source  $U_i$  ,  $I_i$
- DC source:  $U_o$  ,  $I_o$


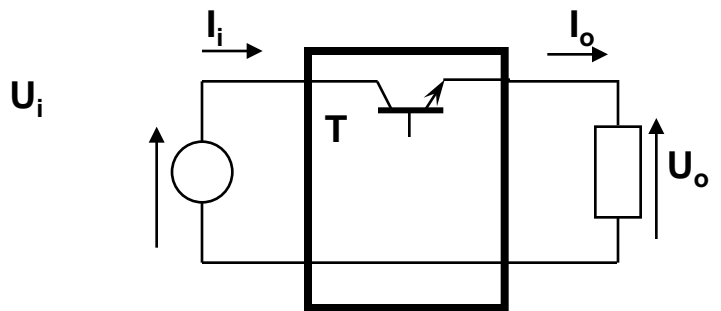
# Linear solution

$U_i = 24V ; U_o = 10 V$  and  $I_o = 600A$



$P_o = U_o \cdot I_o = 10 \cdot 600 = 6'000 W$

$P_T$  (power dissipated by the switch) =  $U_T \cdot I_T = (U_i - U_o) \cdot I_o = (24 - 10) \cdot 600 = 8'400 W$

Converter efficiency =  $P_o / (P_T + P_o) = 42 \%$  !!!!!


Furthermore, it'll be difficult to find a **component (semiconductor) able to dissipate 8'400 W** .

**Then impossible for medium and high power conversion**

# Commutation

$\left. \begin{array}{l} - U_T = 0 \text{ if } I_T \neq 0 \\ - I_T = 0 \text{ if } U_T \neq 0 \end{array} \right\} P_T = 0$


~~Linear mode~~

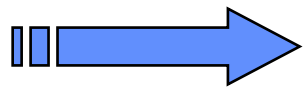


**switch mode  
(saturated-blocked)**




# Commutation

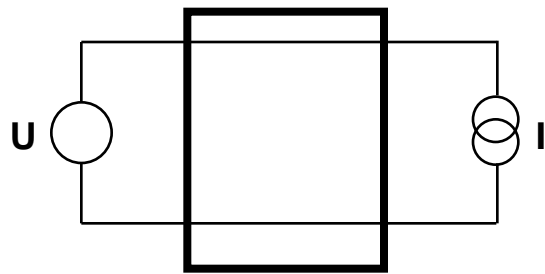

Direct Link

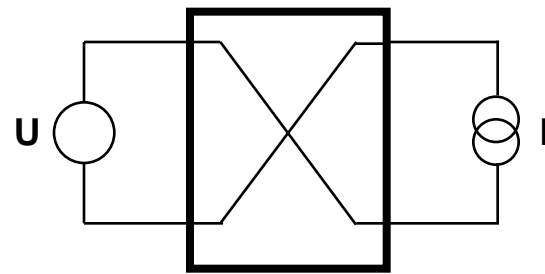


Inverse Link

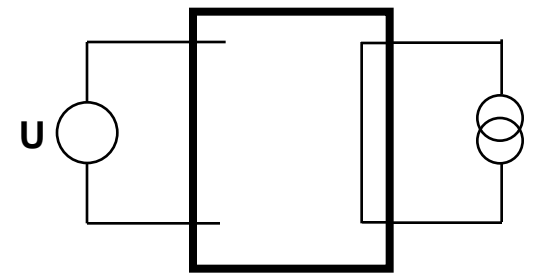

Open Link


**Active components used as switches to create a succession of link and no link between sources to assure an energy transfer between these sources with high efficiency.**
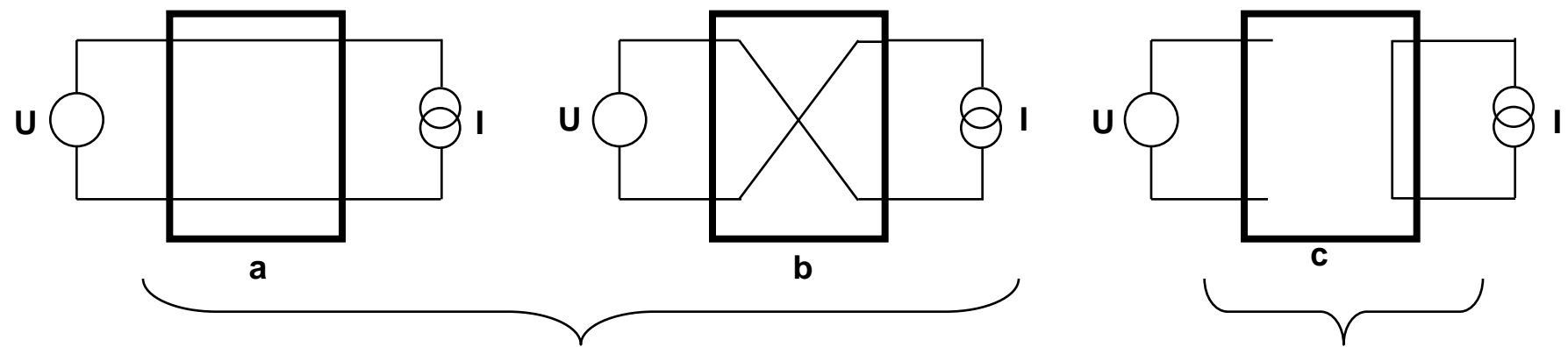
# Direct link configuration : Direct voltage-current converters



**Connexion**  
(energy flow between sources)

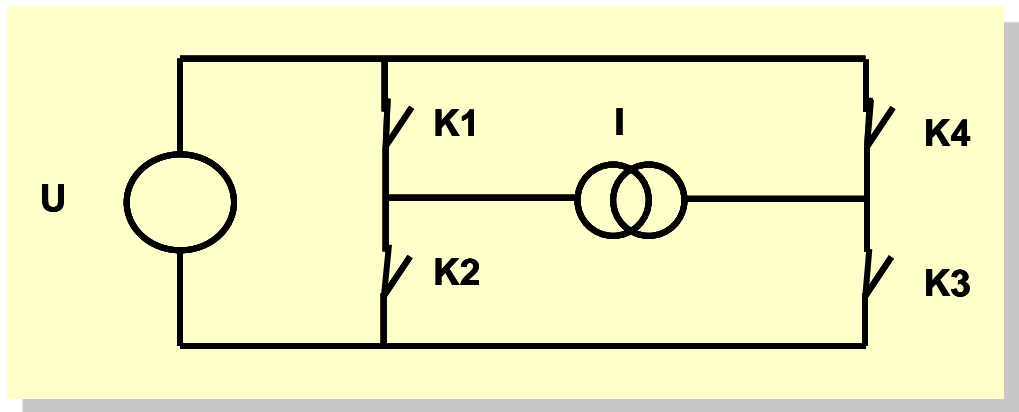
**Disconnexion**  
(current source short-circuited,  
voltage source open circuited)





- K1 and K3 closed => a
- K2 and K4 closed => b
- K1 and K4 (or K2 and K3) closed => c
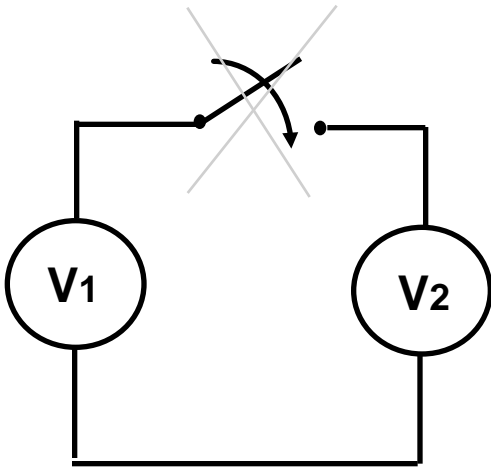
# Commutation rules

- *electronic switches modify the interconnection of impeding circuits*
- *any commutation leading instantaneous variations of a state variable is prohibited*



Turn On impossible

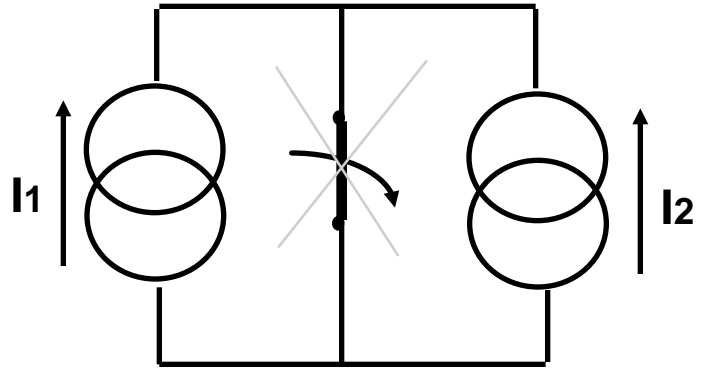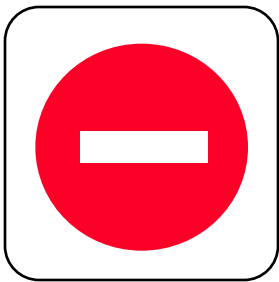


Turn Off impossible

Interconnection between two impeding networks can be modified only if :



- **the two networks are sources of different natures (voltage and current)**
- **the commutation is achieved by TWO switches. The states of the two switches must be different.**
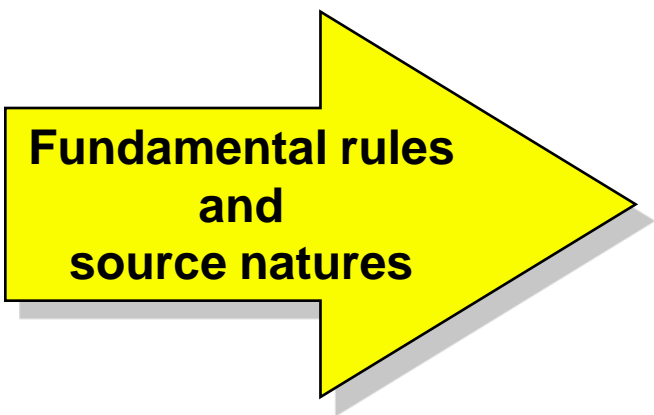
# Power Converter topology design: the problem

the interconnection of sources by switches




switch characteristics

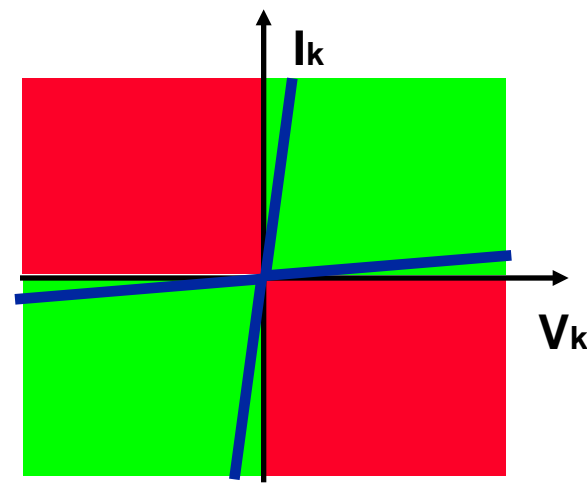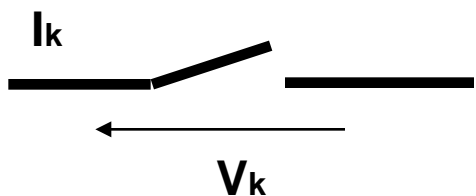




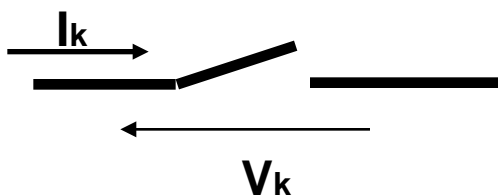**Switch** : *semiconductor device functioning in commutation*  
*The losses in the switch has to be minimized*  
*Zon very low*  
*Zoff very high*



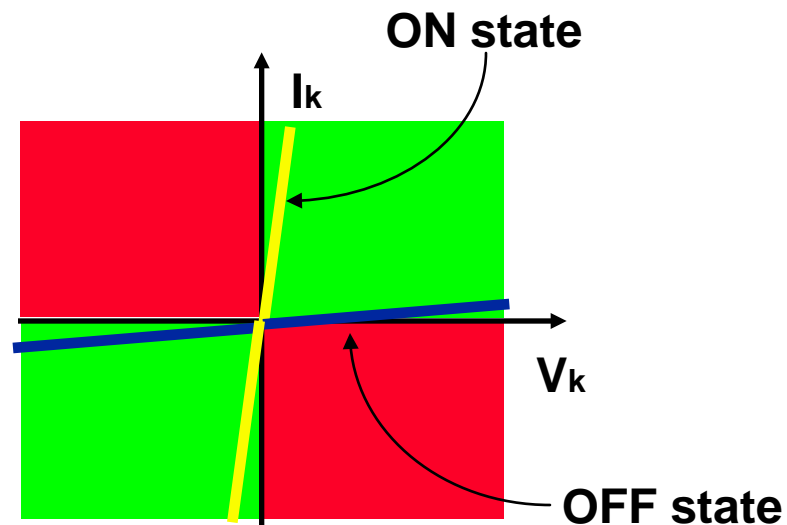
Switch : at least two orthogonal segments  
 (short and open circuit are not switches)



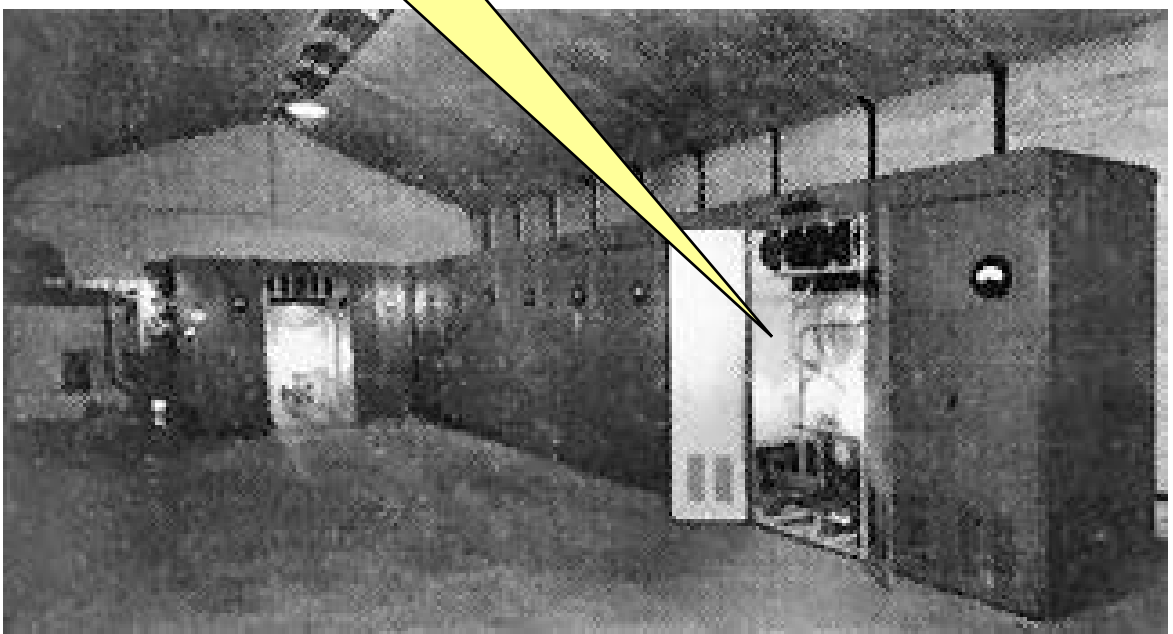
# Once upon a time... not so far



This is a 6-phase device, 150A rating with grid control. It measures 600mm high by 530mm diameter.



# Power Semiconductors

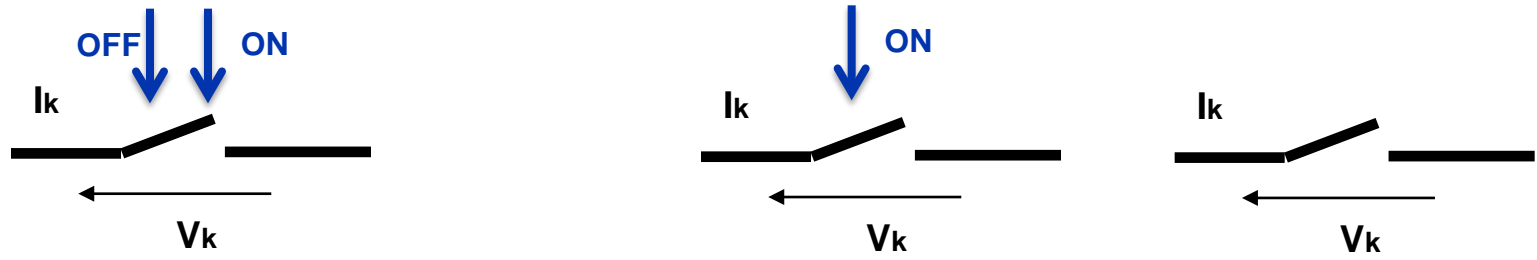

## Power Semiconductors

### Turn-off Devices

### Thyristors

### Diodes




#### Transistors

#### Thyristors


- Fast
- Line commutated
- Avalanche

- Line commutated
- Fast
- Bi-directional
- Pulse

- MOSFET
- Darling
- IGBTs

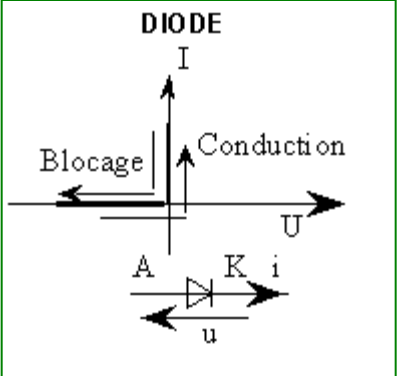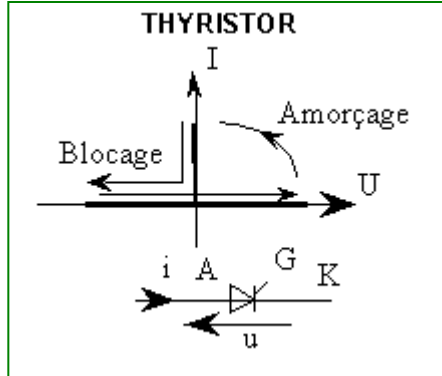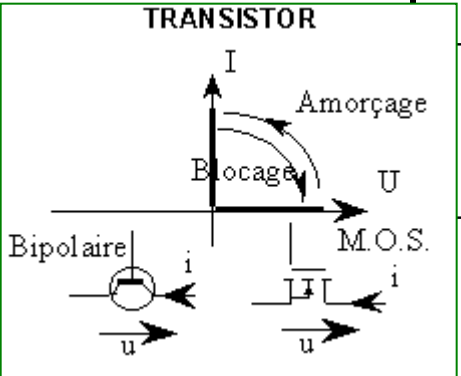

# Evolution of Power semiconductors

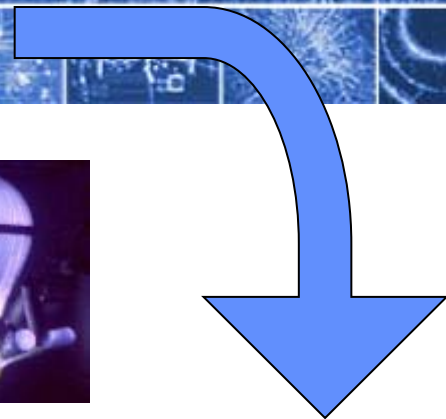

From mercury arc rectifier, grid-controlled vacuum-tube rectifier, inignitron ,....



## Power Electronics

**From 1960**

**Power Diode and Thyristor**

**or SCR (Silicon-Controlled Rectifier )**



**Link to frequency of the electrical network  
50 Hz (60 Hz)**

**From 1985**

**High frequency power semiconductors :**

**MosFet, IGBTs , GTOs, IGCTs,....**




**High frequency => high performances (ripple, bandwidth, perturbation rejection,...)  
small magnetic (volume, weight)**





# Power Converter for magnets

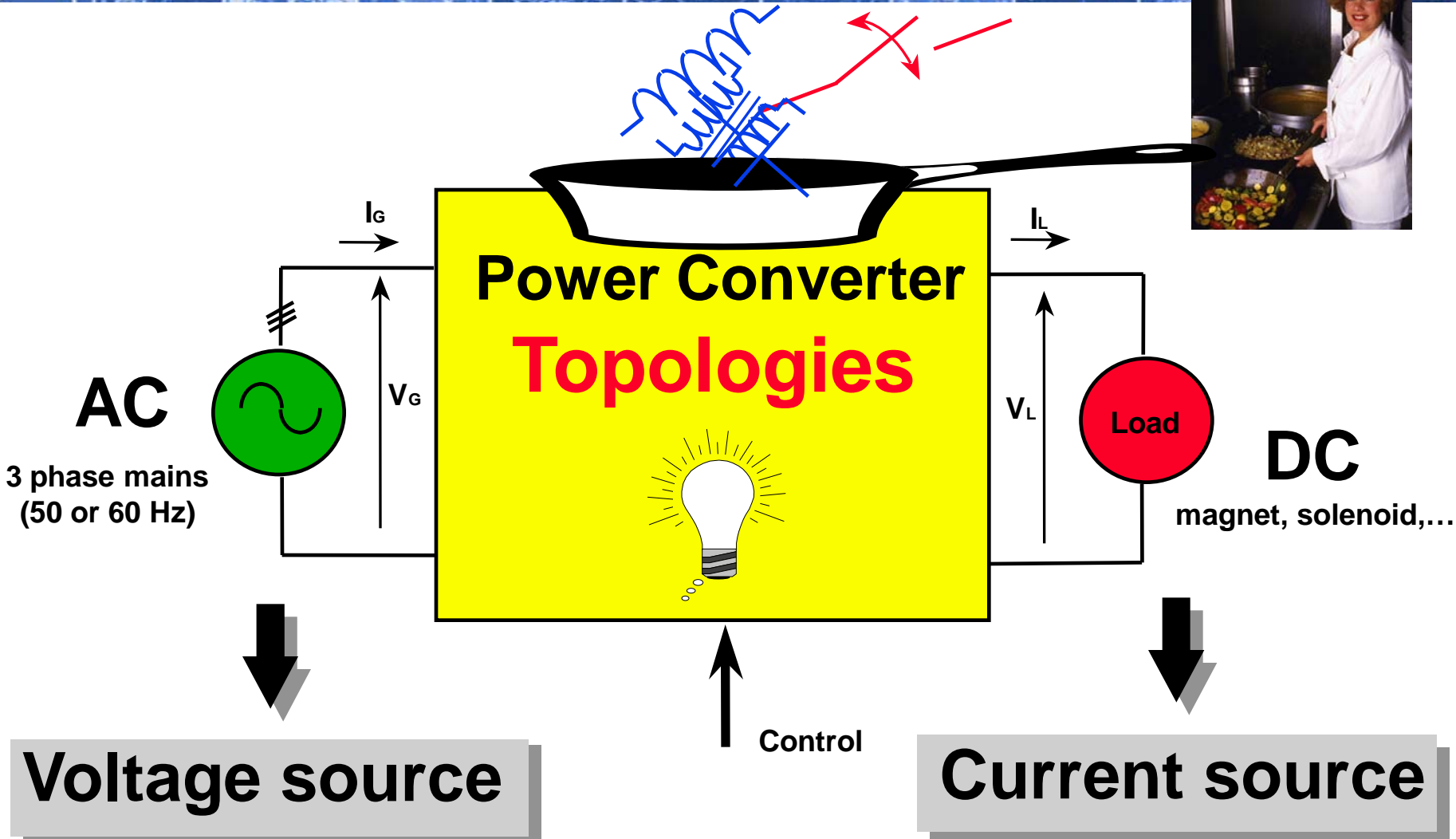






Achieving high performance : **COMPROMISE**






# Operating Modes


**Complexity**

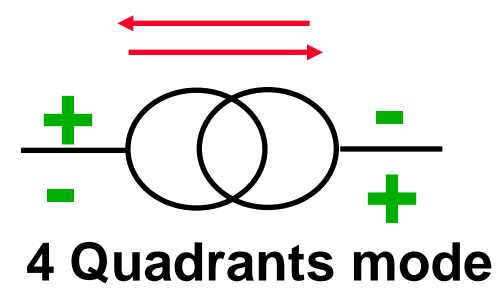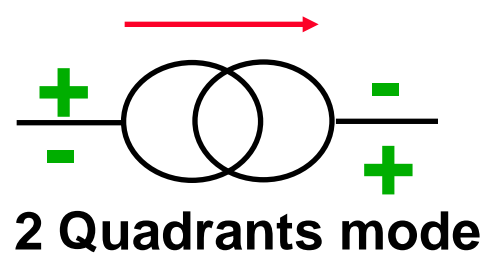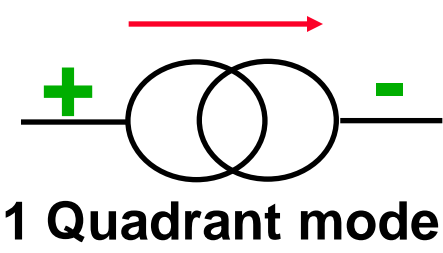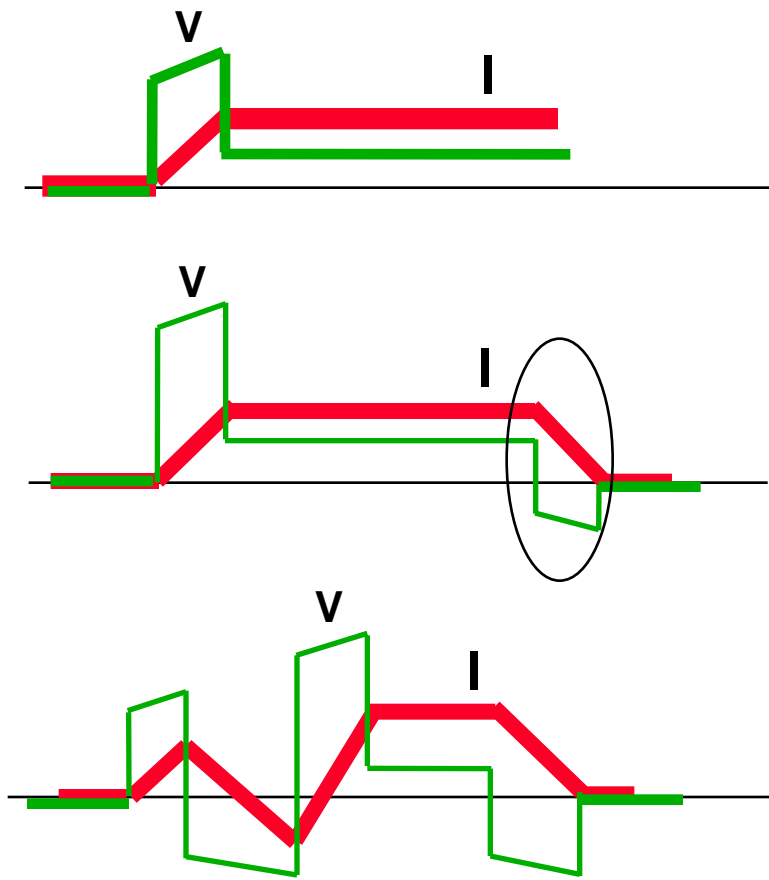 


**Output Source**

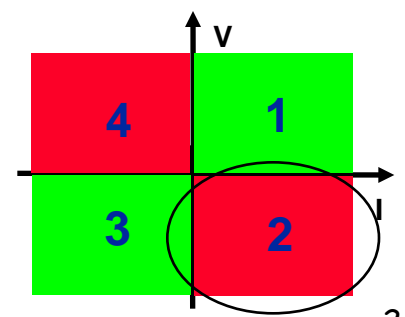

# Converter classification

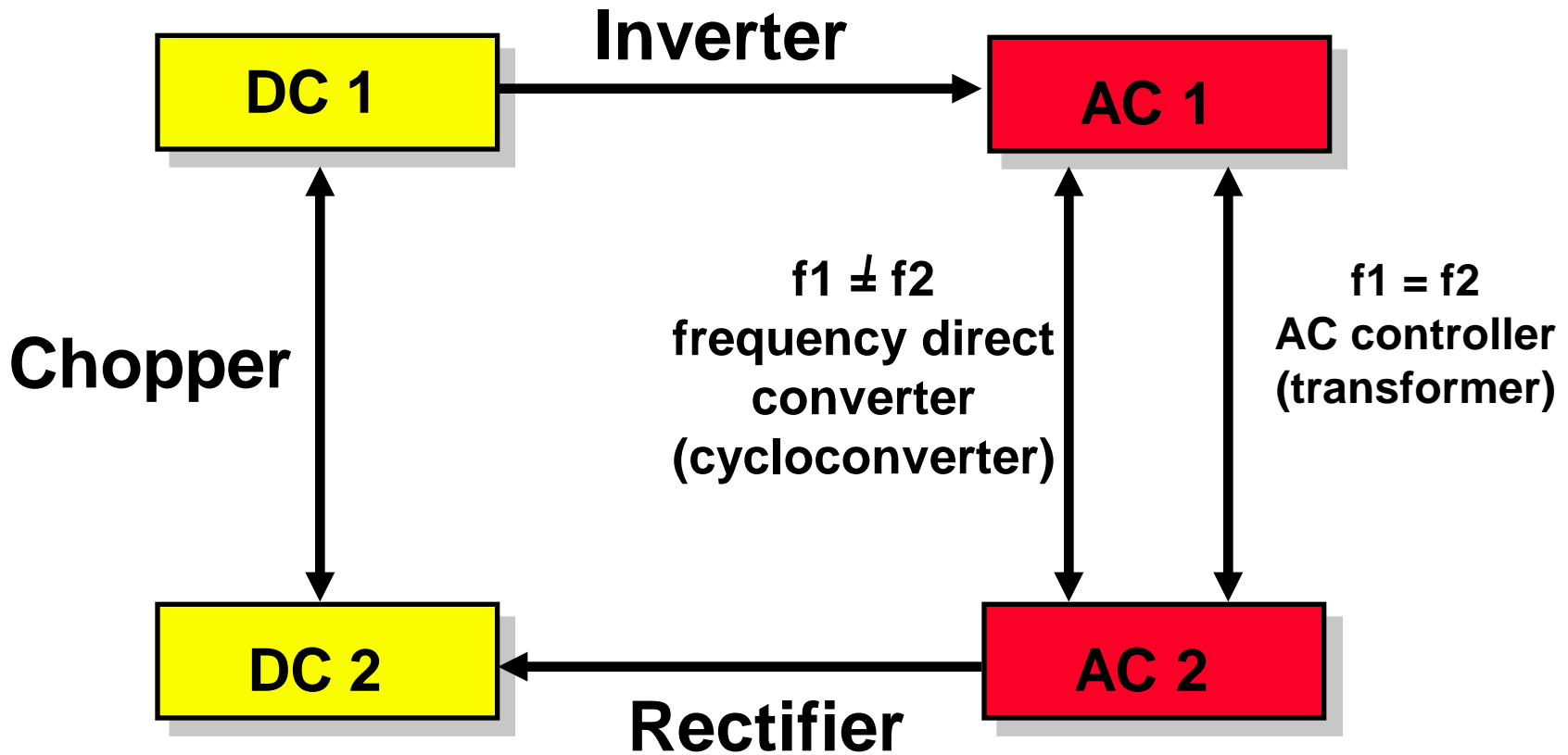





# General power converter topologies

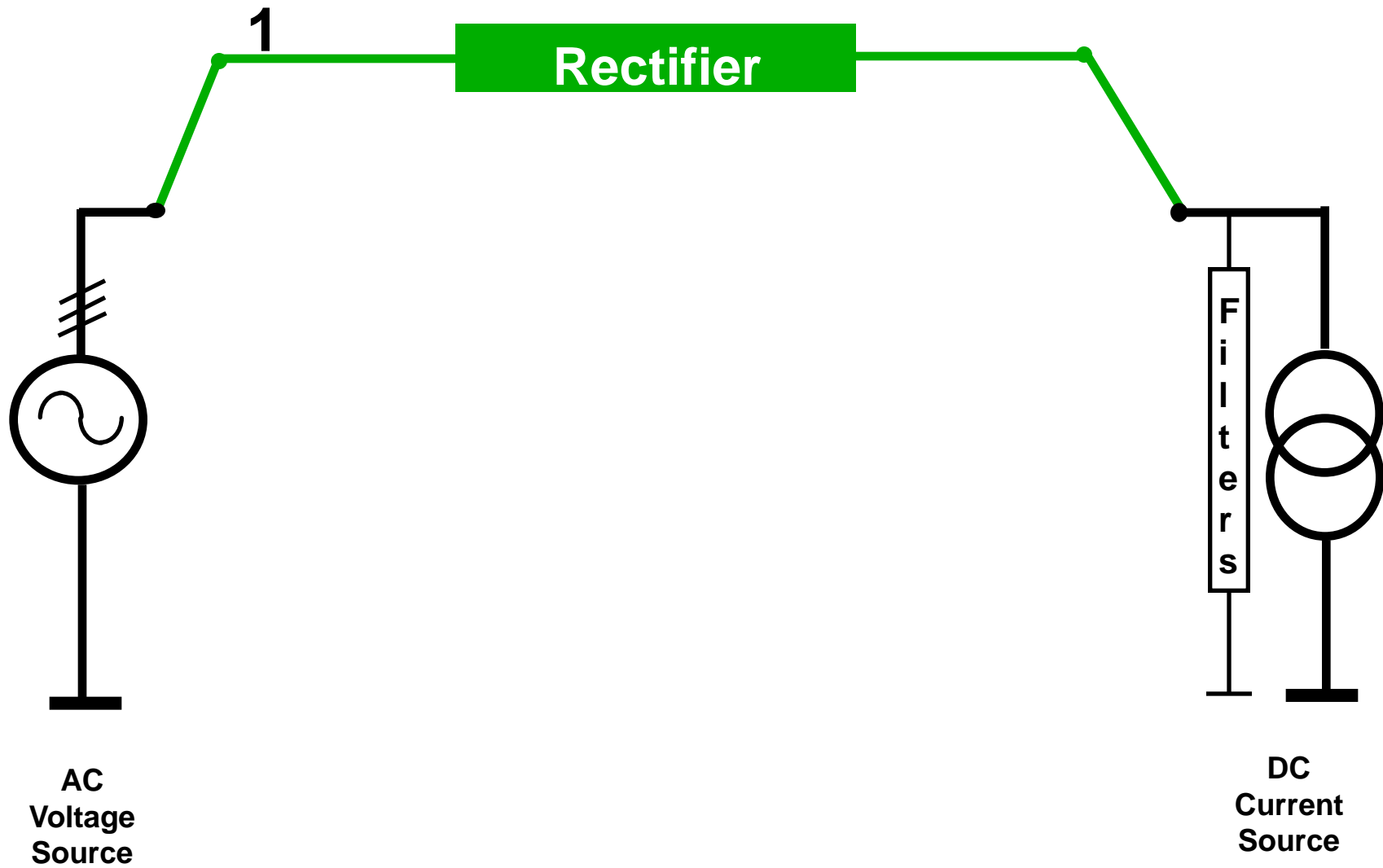







# Direct Converters : Rectifiers

September 2010

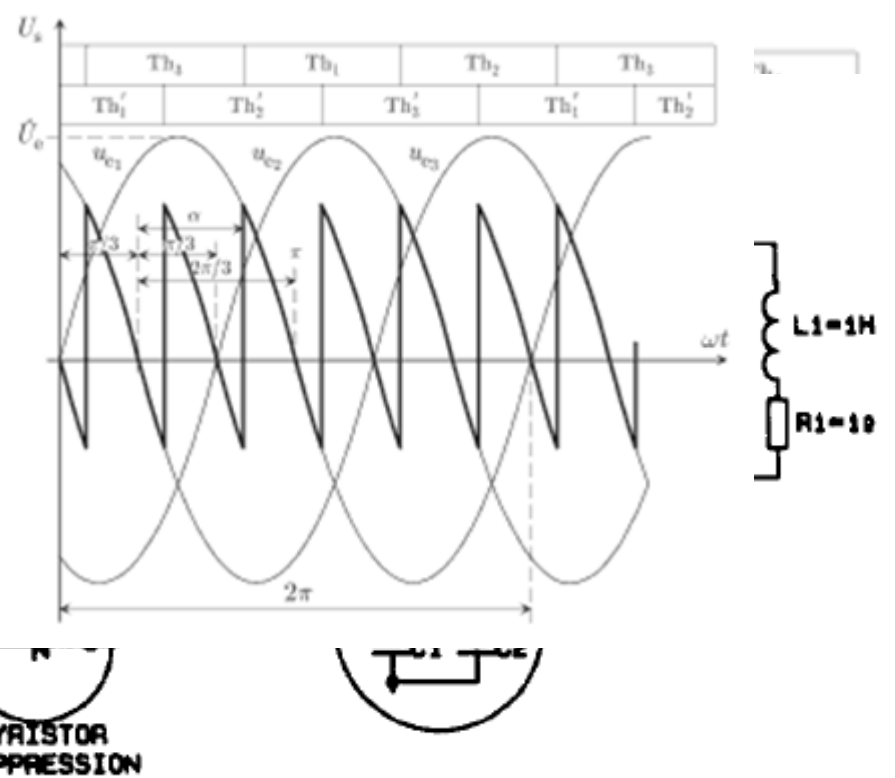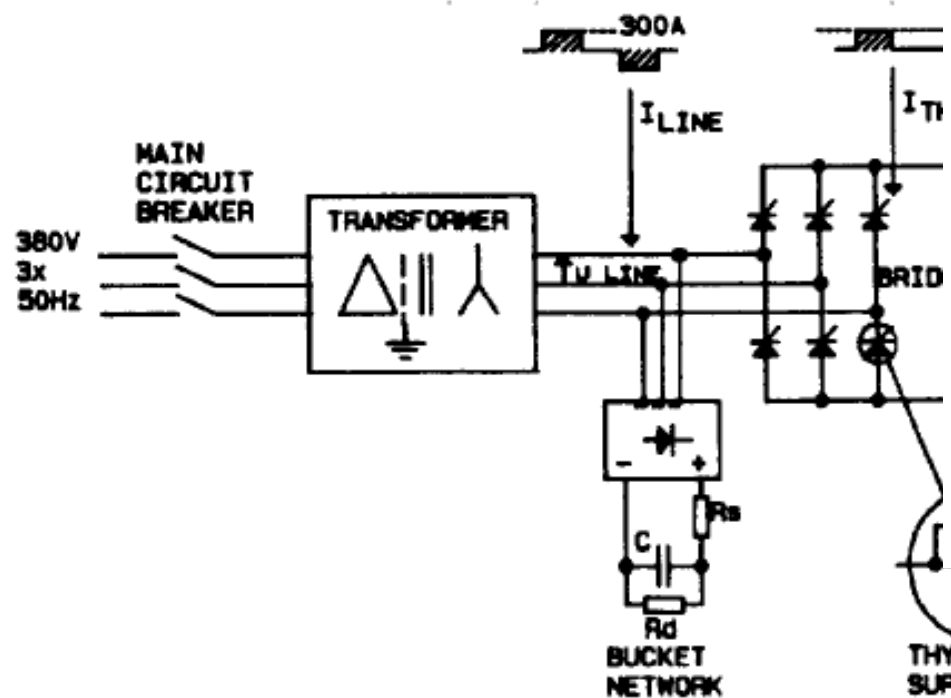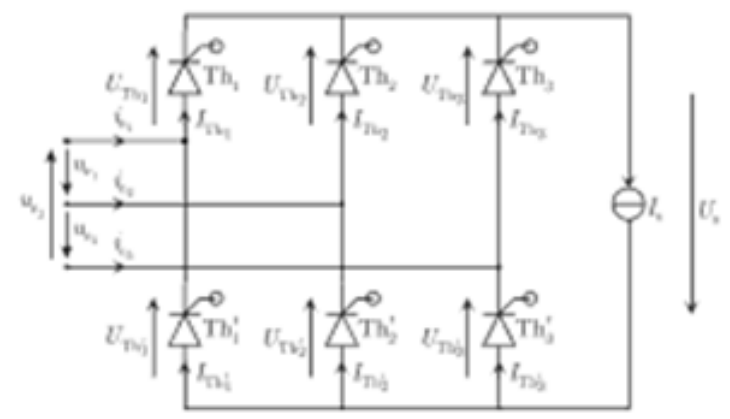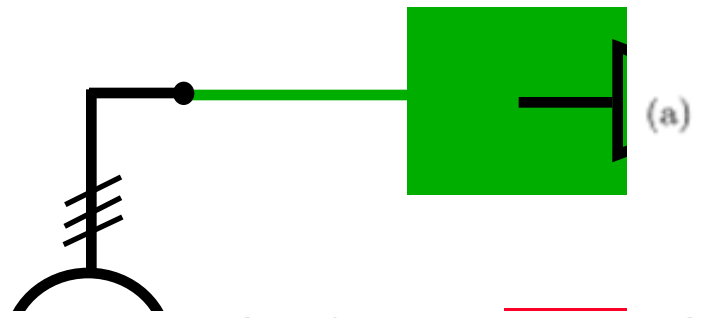

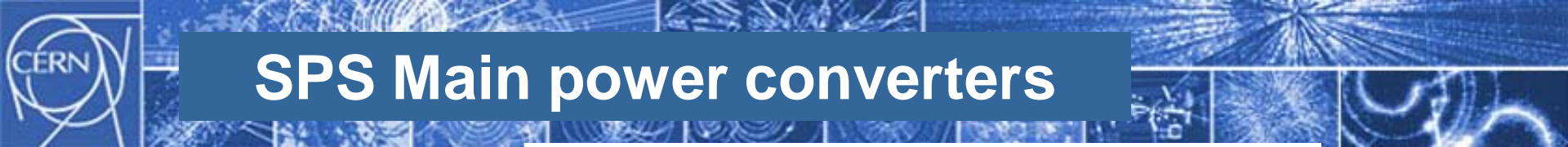


# SPS Main power converters

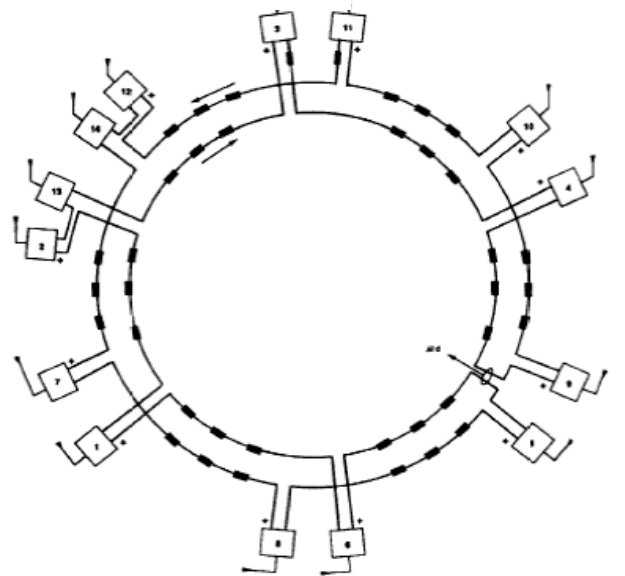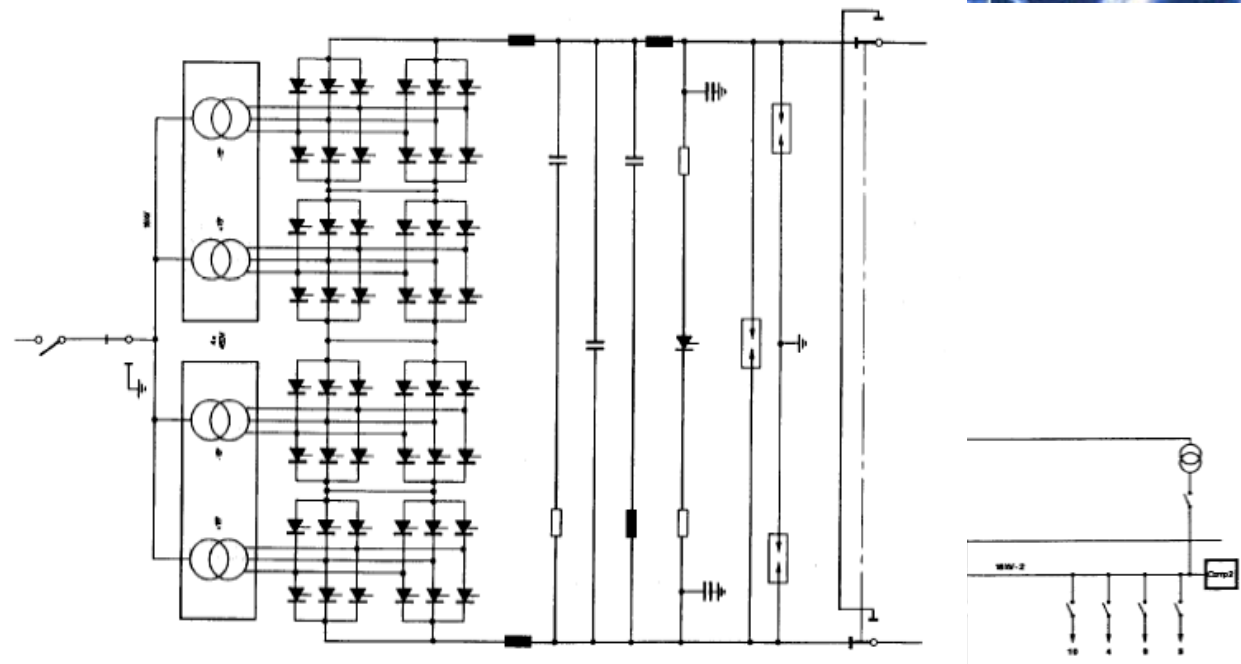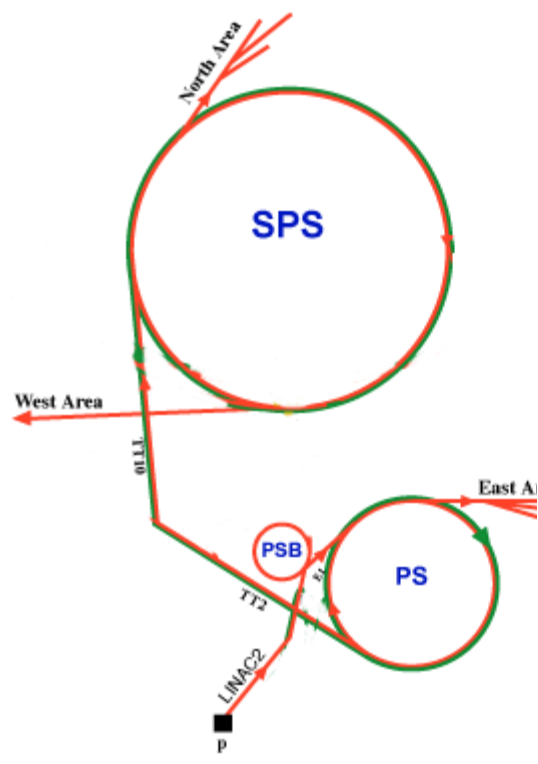

**Main power converters**  
**12 x [6kA, ± 2 kV]**


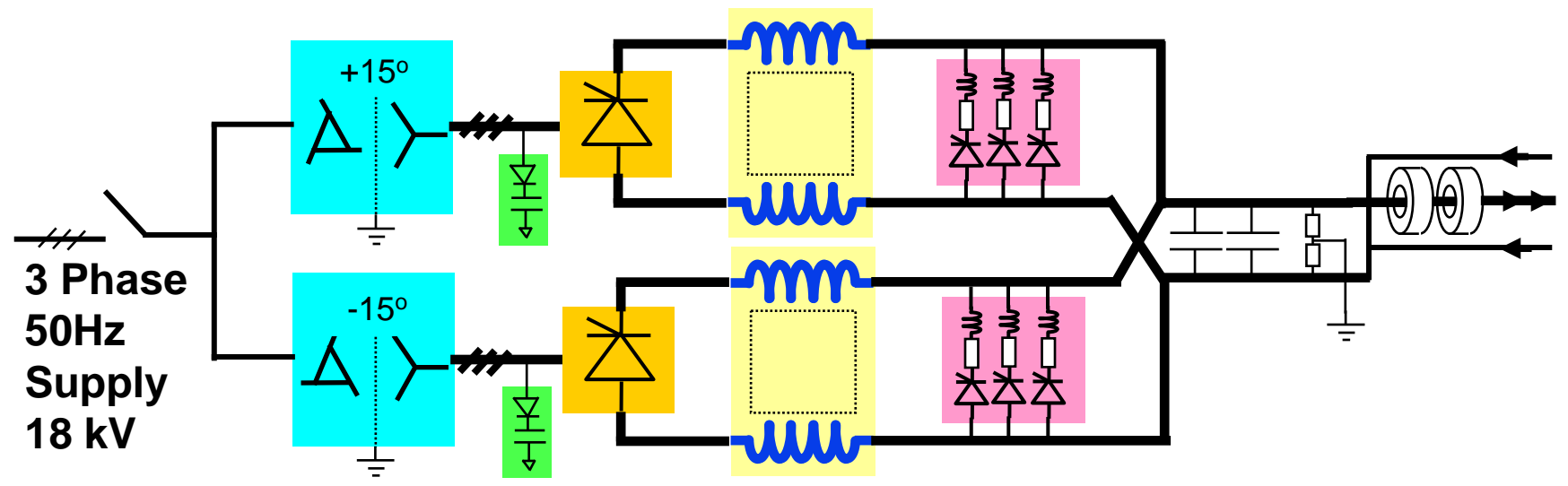
# Two Quadrant Phase Controlled Rectifiers for high current SC magnets



Fk. Bordry - Power Converters - CAS - VARNA - 30<sup>th</sup> September 2010




**[13kA, ± 200 V]**





# Direct Converters : Rectifiers

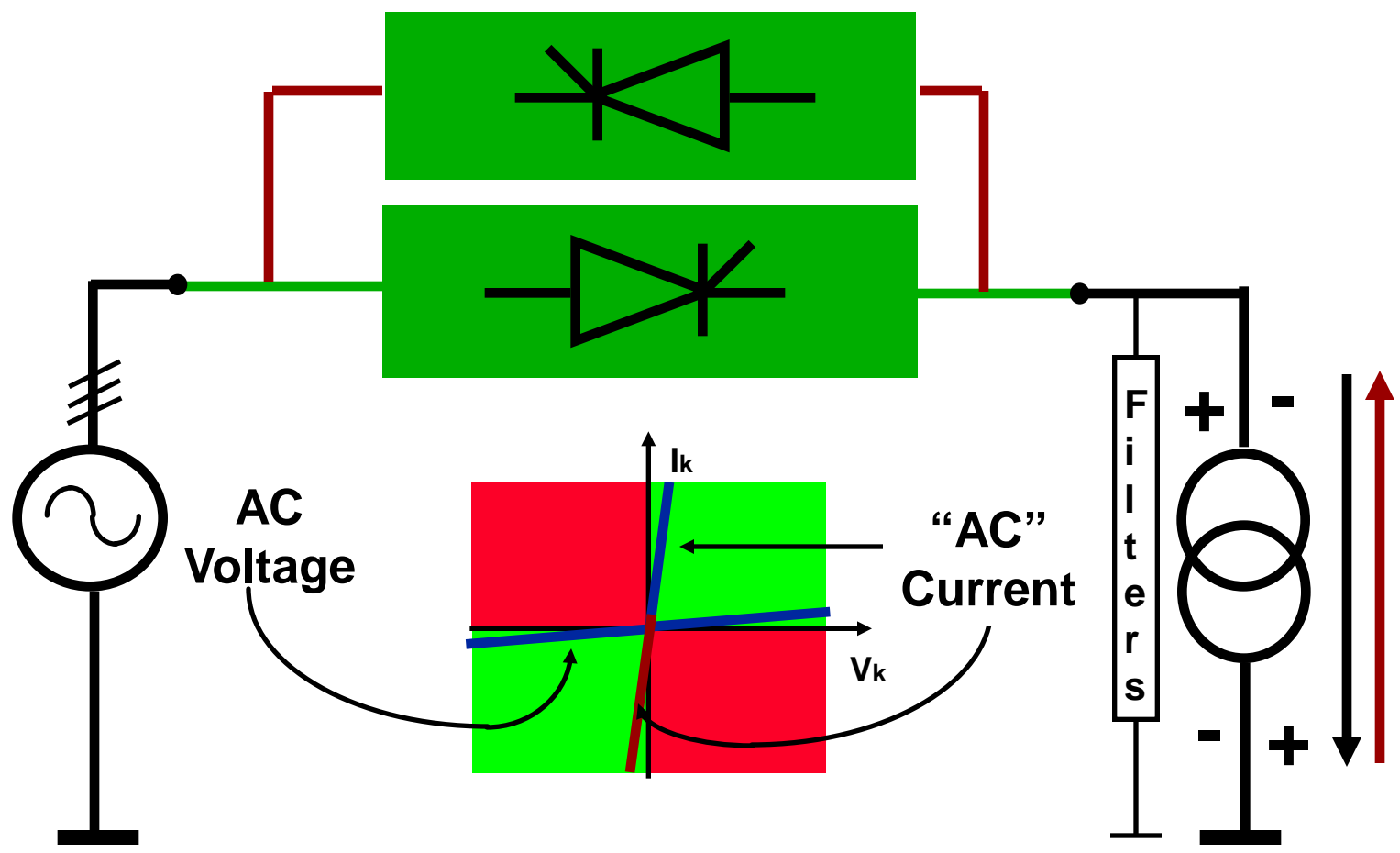

# Direct Converters : Phase Controlled Rectifiers


- ☺ very high power capability
- ☺ moderate prices and competitive market
- ☺ simple structure, well understood (but care needed with high currents)
- ☹ three phase transformer operates at low frequency (50 or 60 Hz)
- ☹ variable power factor from 0 to 0.8
- ☹ harmonic content on input current
- ☹ response time is large (ms)
- ☹ current ripple is large (passive or active filters)



passive (active) filters operating at low frequency

**Increase** of pulse number (3,6,12,24,48) but  
**complexity** (cost, control,...)


# General power converter topologies

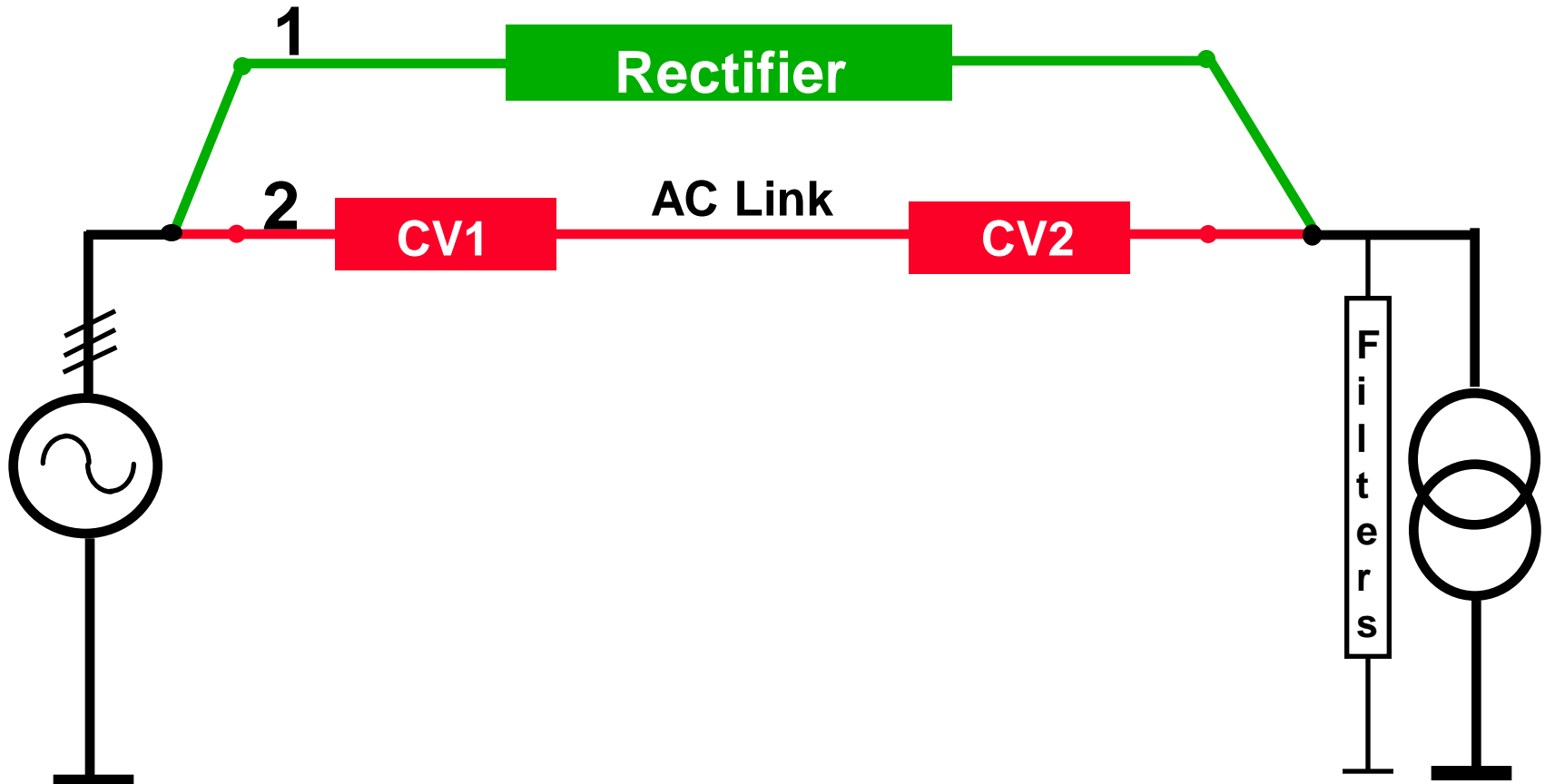


**Application :- very high currents with low voltages  
- (very high voltages with low currents)**


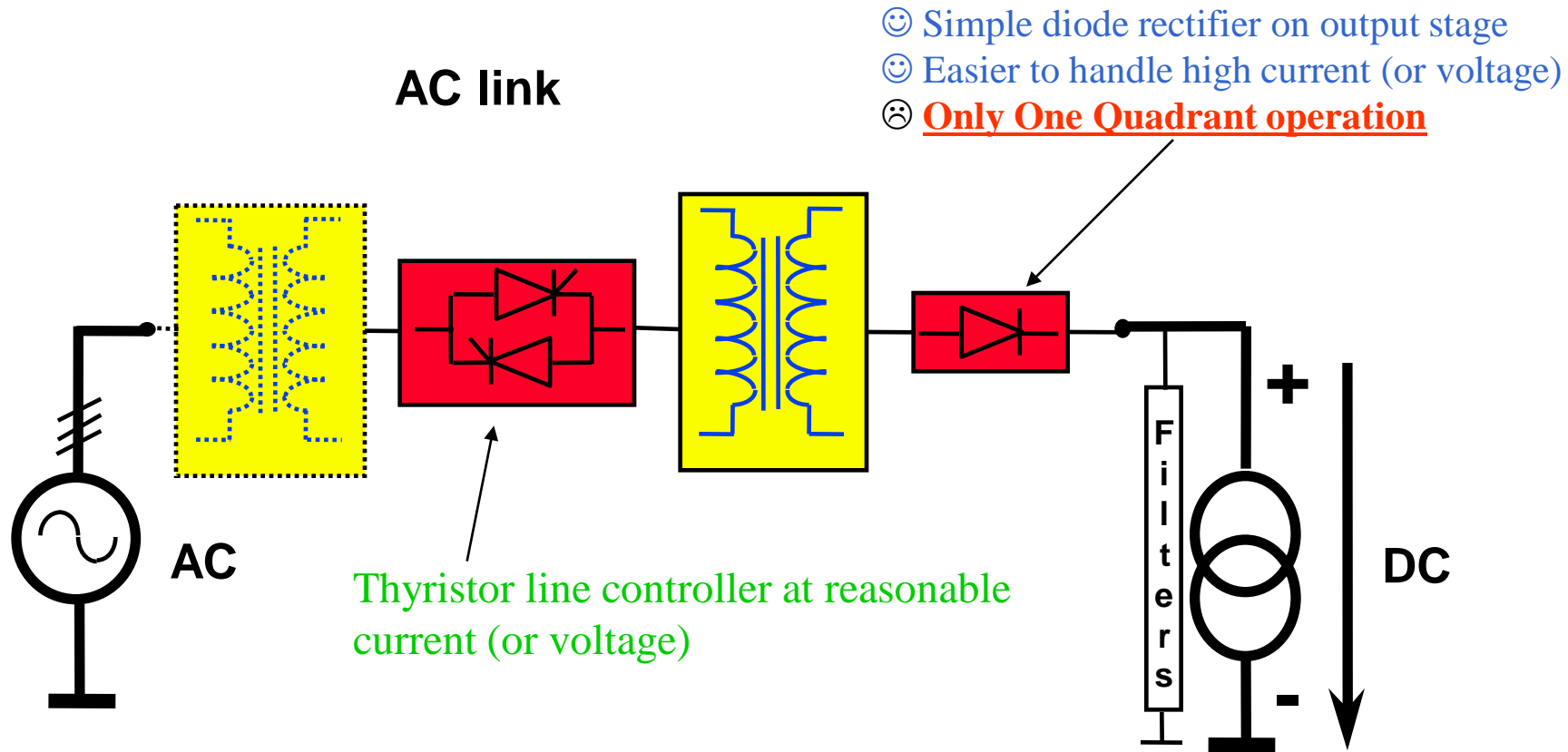
# Direct Converters : AC link (AC line controller)



# [100 kV, 40A] klystron power converter

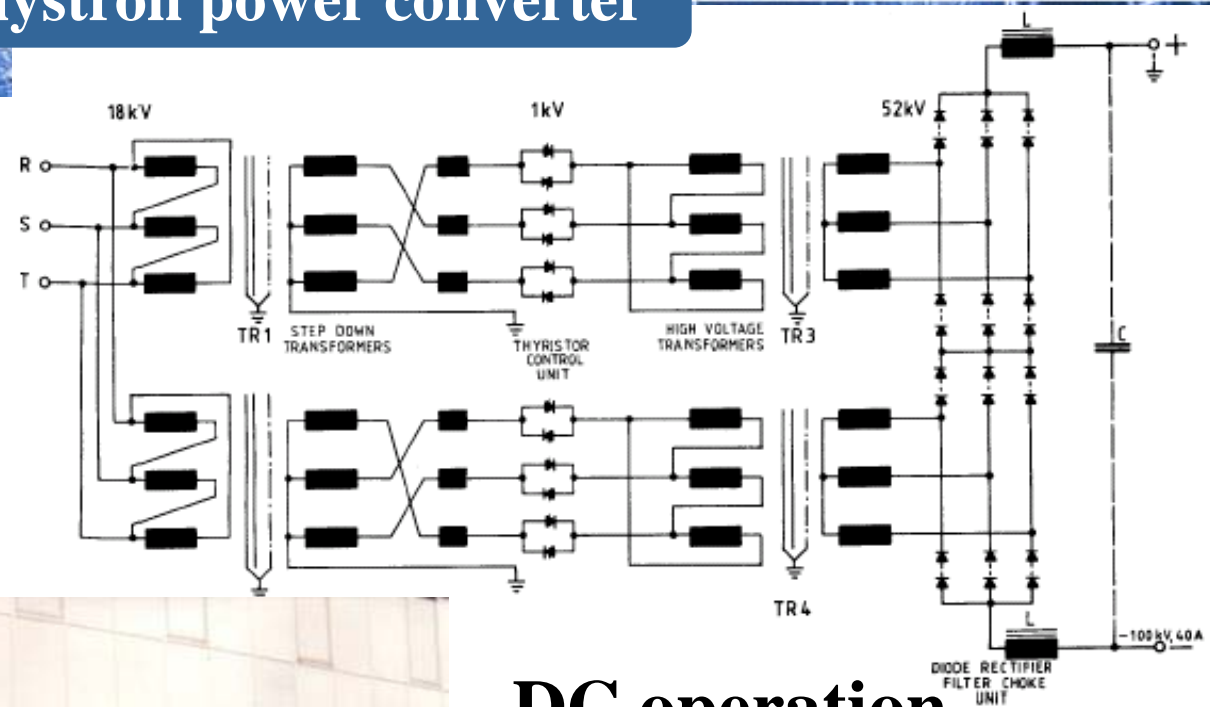


## DC operation


September 2010




# General power converter topologies

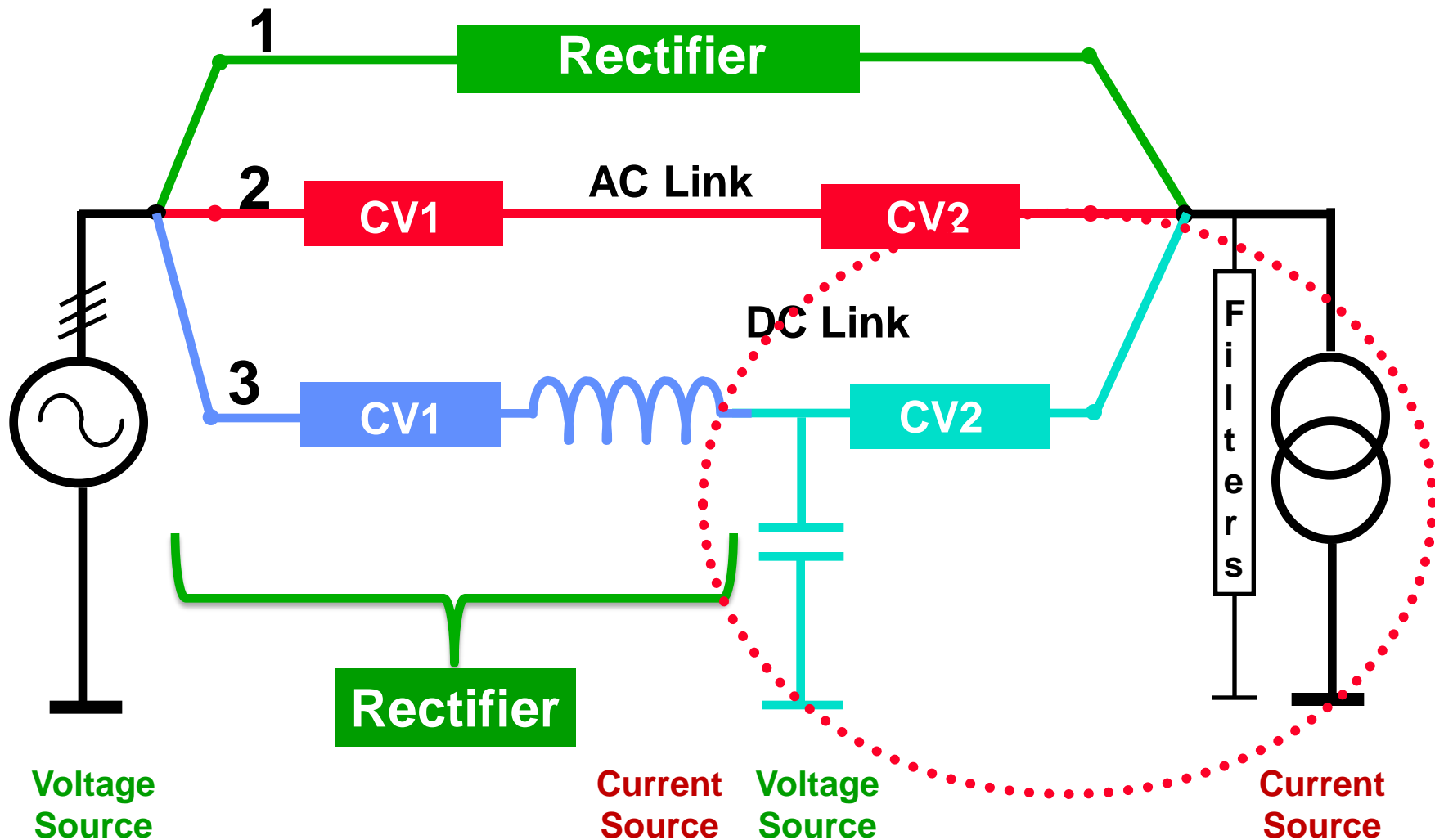

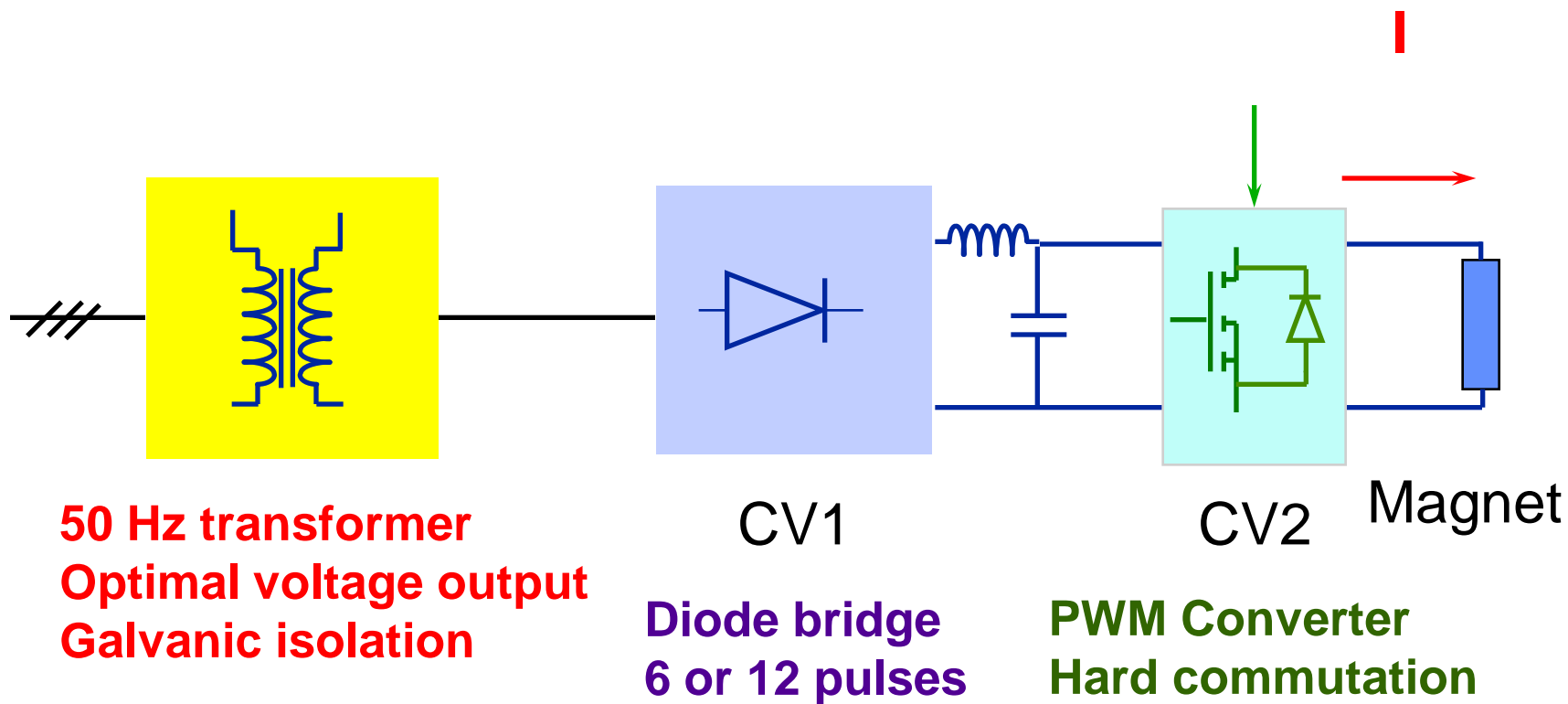
# Galvanic isolation at AC input source (50Hz transformer)



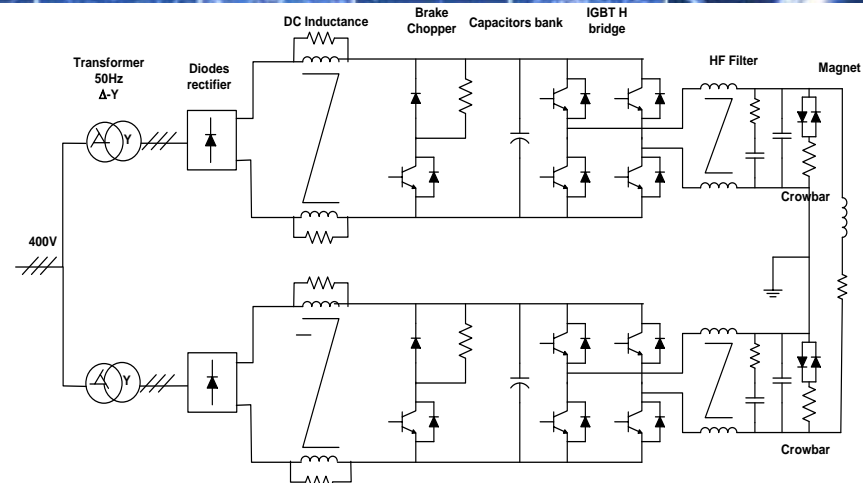**Peak Power:** 405 kW  
**Voltage:**  $\pm 900V$   
**Max Current:**  $\pm 450A$



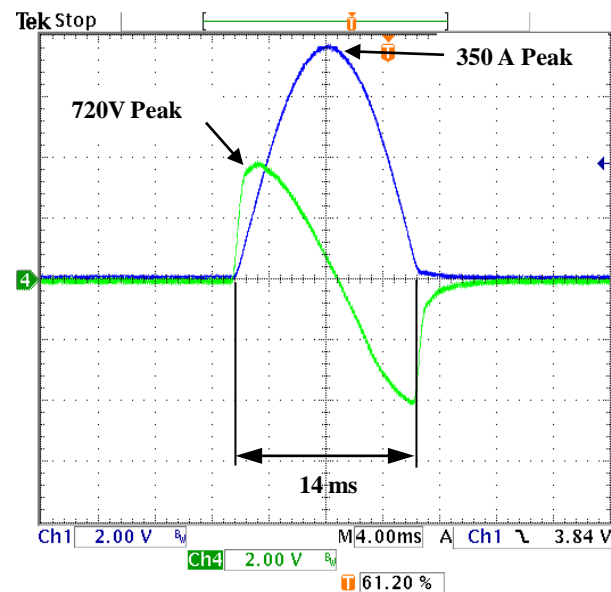Multi-Turn Extraction: Current/Voltage waveforms



27 Jun 2008  
10:29:37

Current Loop Bandwidth  $\approx 1kHz$




# Indirect AC-DC-AC-DC converter


Three cascade power conversion stages:

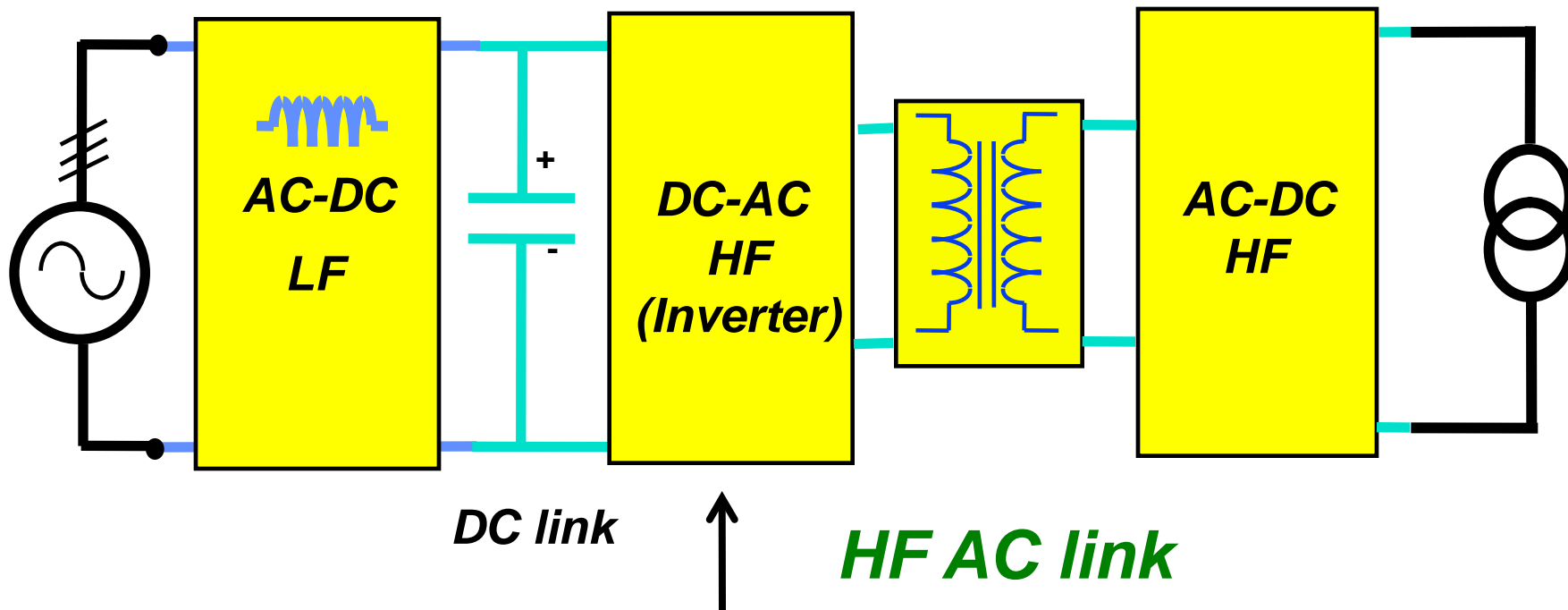- 1) Simple DC source (Diode (thyristor) rectifiers)
- 2) HF DC-AC converter (Inverter)
- 3) HF AC-DC converter (Rectifier) (often diode rectifier)

HF transformer to provide the galvanic isolation



# LHC Switch-Mode Power Converters

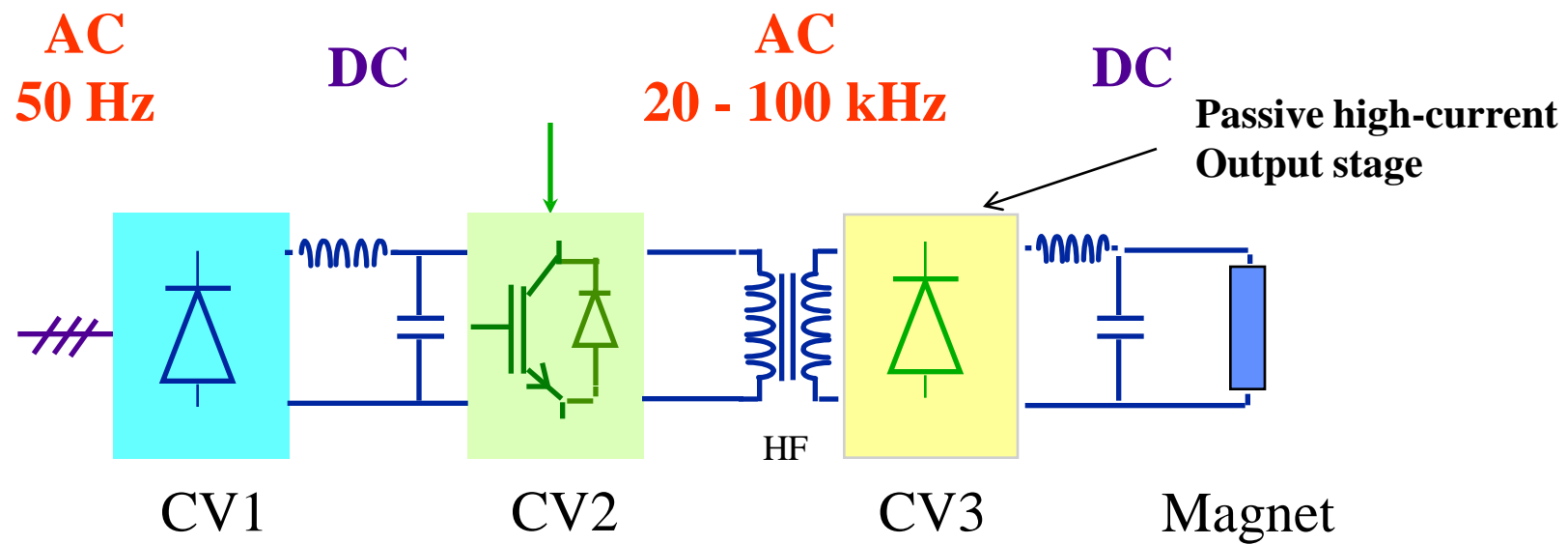

Voltage loop:  
bandwidth few kHz

- Fast power semiconductors (IGBT)
- Semiconductor losses :  
soft commutation
- HF transformer and output filter : ferrite

- light weight, reduced volume (HF transformers and filters)
- good power factor (0.95)
- high bandwidth and good response time
- Soft commutation gives low losses and low electrical noise
- small residual current ripple at output
- More complex structure, less well understood, limited number of manufacturers



# LHC:1-quadrant converter: modular approach




## 1-quadrant converters:

- [13kA,18V] : 5\*[3.25kA,18V]
- [8kA,8V] : 5\*[2kA,8V]
- [6kA,8V] : 4\*[2kA,8V]
- [4kA,8V] : 3\*[2kA,8V]



MTBF and MTTR optimization

# DC and slow pulsed converters

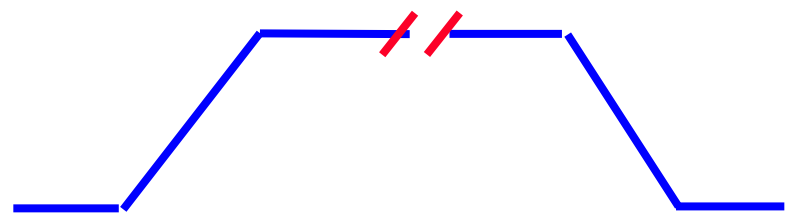

Rise and fall time < few ms

Control of the ramps

## High and medium power Phase Controlled Rectifiers


- Diodes and thyristors rectifiers
- 50Hz transformers and magnetic component (filters)
- 1-quadrant and 2-quadrants (but unipolar in current) : energy back to the mains
- 4-quadrant: back-to-back converters

## Low and Medium power Switch-mode power converters

- Mosfets , IGBTs, IGCTs,... turn-off semiconductors
- HF transformers and passive filters
- excellent for 1-quadrant converter
- 4-quadrant converters but with energy dissipation (very complex structure if energy has to be re-injected to mains)


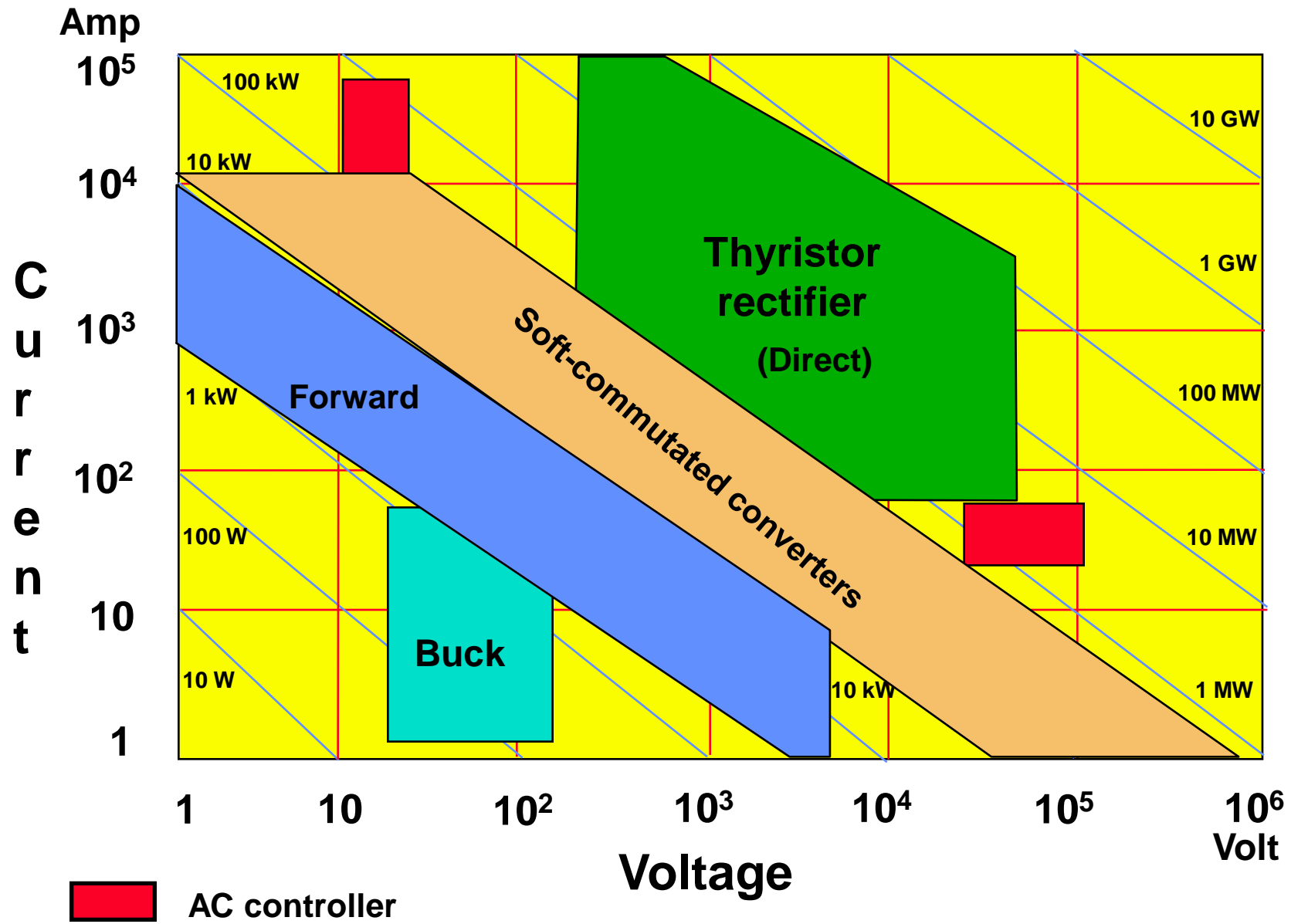
# Power converter : Operational domains for accelerators




Fk. Bordry - Power Converters - CAS - VARNA - 30<sup>th</sup> September 2010



# Pulsed converters

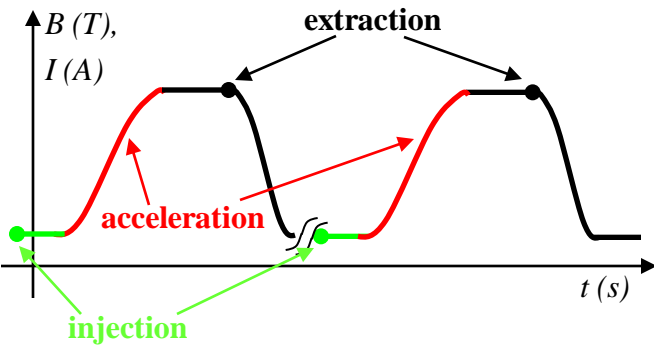
## Synchrotrons: injections and extractions

- Beam is injected, accelerated and extracted in several turns;


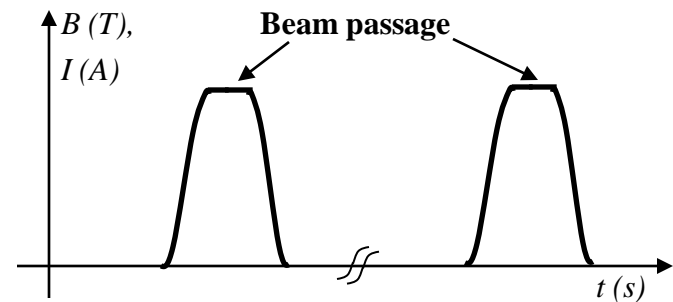
## Linac's and transfer lines

- Beam is passing through in one shot, with a given time period;



Rise and fall time < few ms


Direct Energy transfer  
from mains is not possible:

Intermediate storage of energy

Peak power : could be > MW ( average power kW)



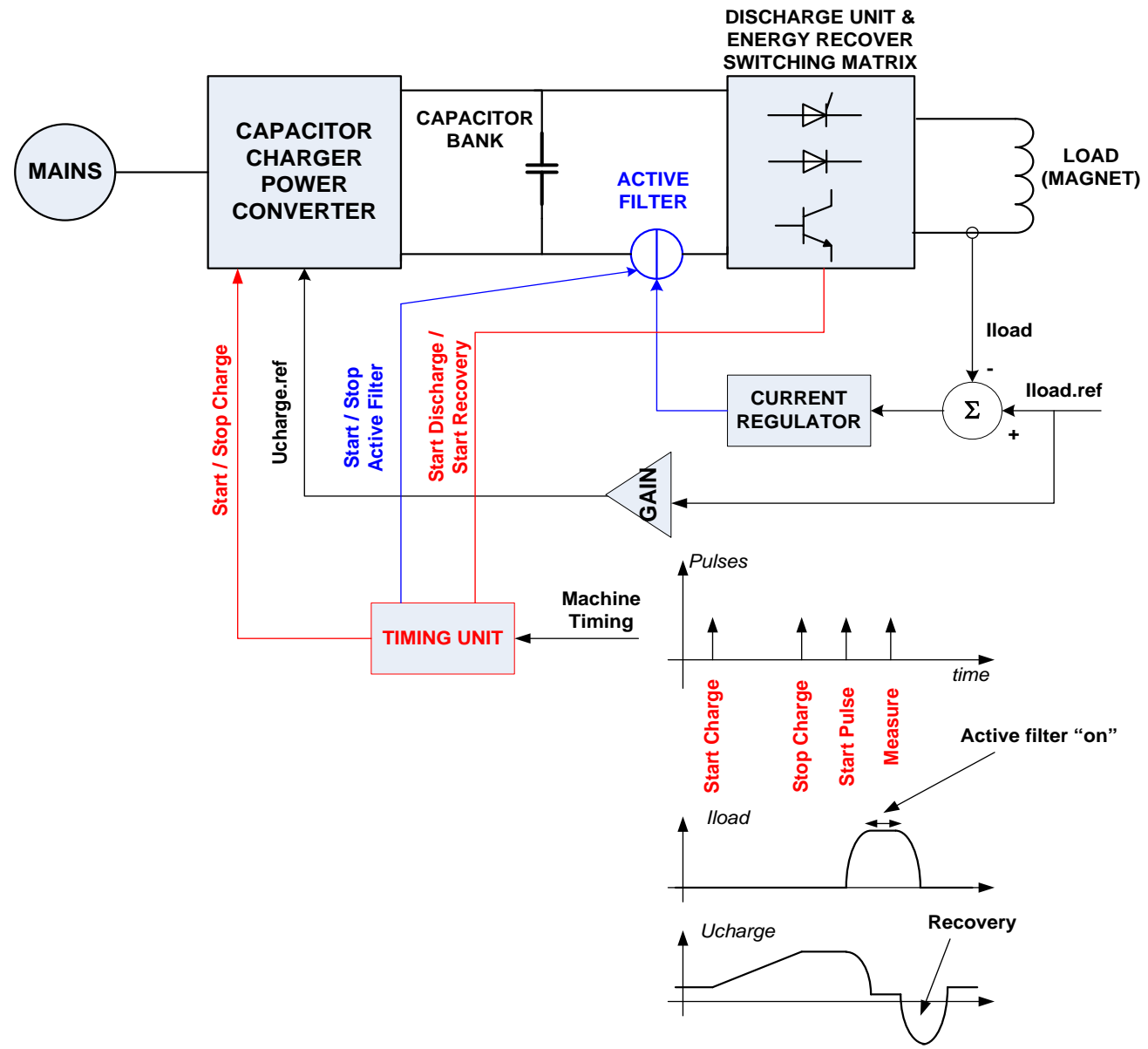
# Block schematic of a fast pulsed converter




## CNGS



Charging Unit  
10kV - 20A

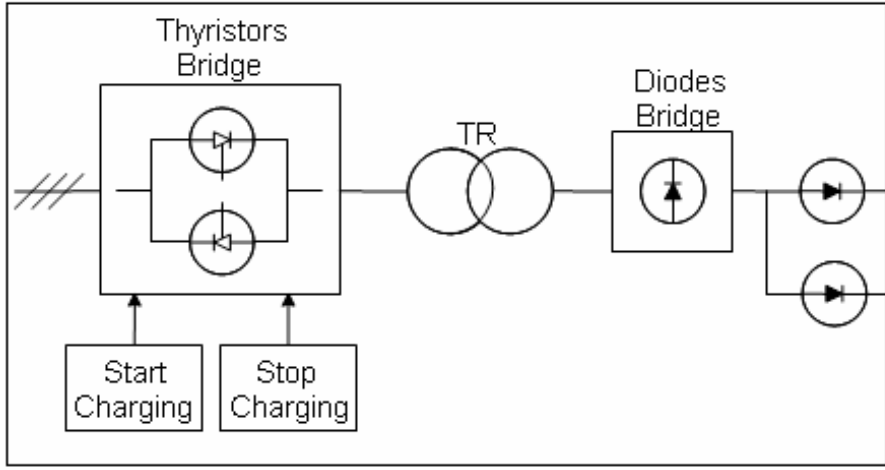

Discharge Circuit 1

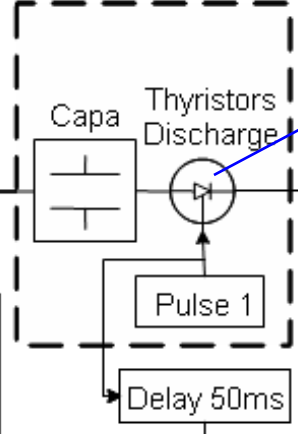


Discharge Circuit 2

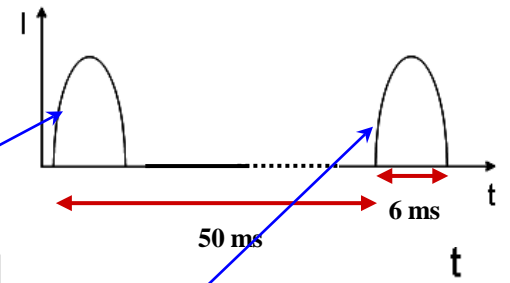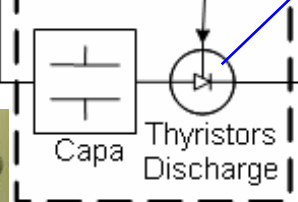

Polarity Changer  
Earthing

Power Cables  
(~1000m)


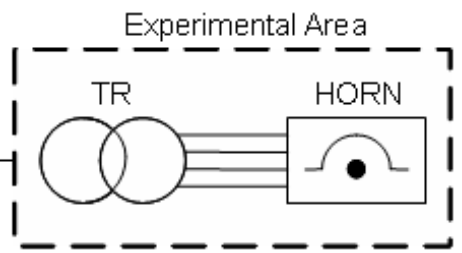


**150 kA for the horn**  
**180 kA for the reflector**




- Characteristics :
  - output voltage : 100 kV
  - output current : 20 A
  - pulse length : 700  $\mu$ s
  - flat top stability : better than 1%
  - 2 Hz repetition rate

**Peak power : 2 MW**

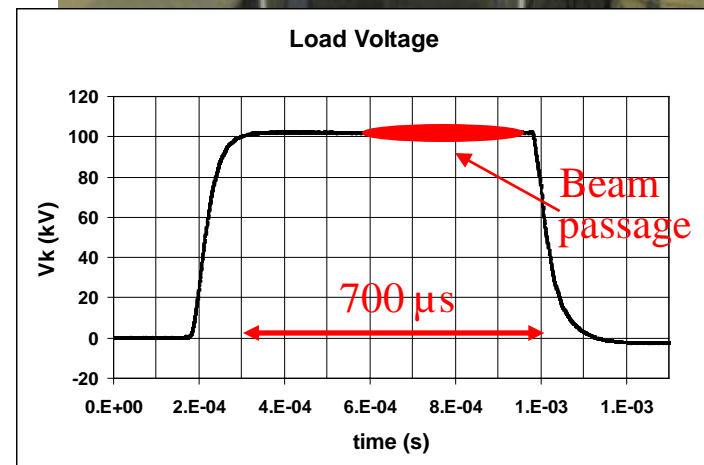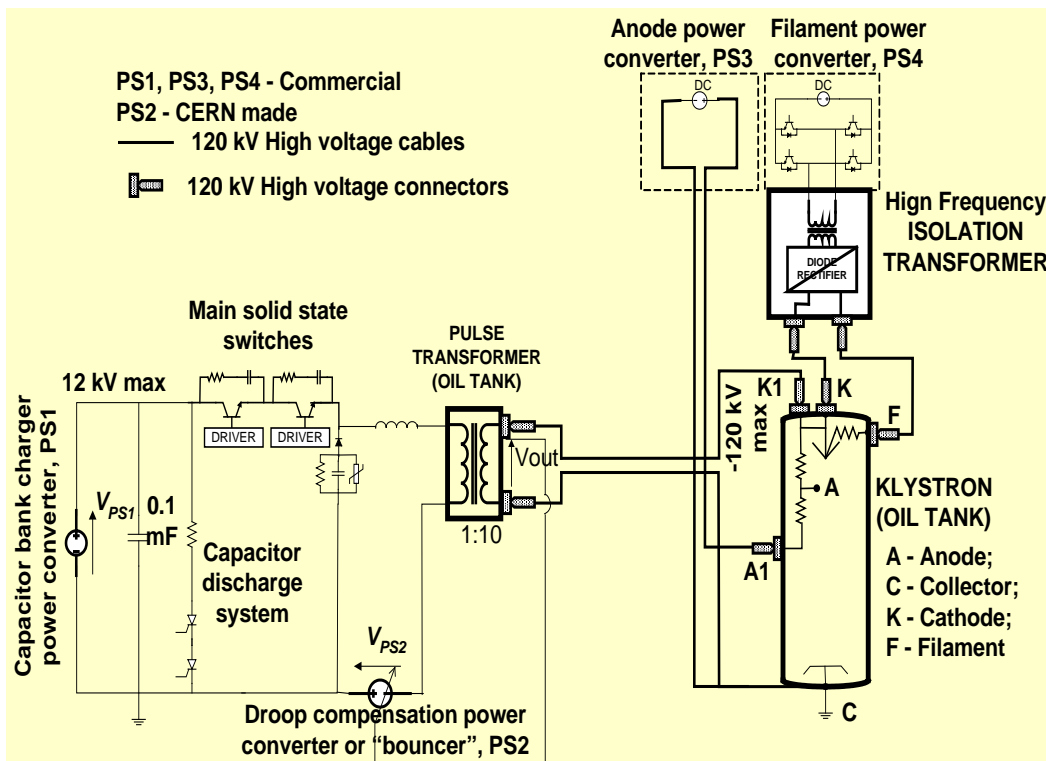


# Power Converter % Load

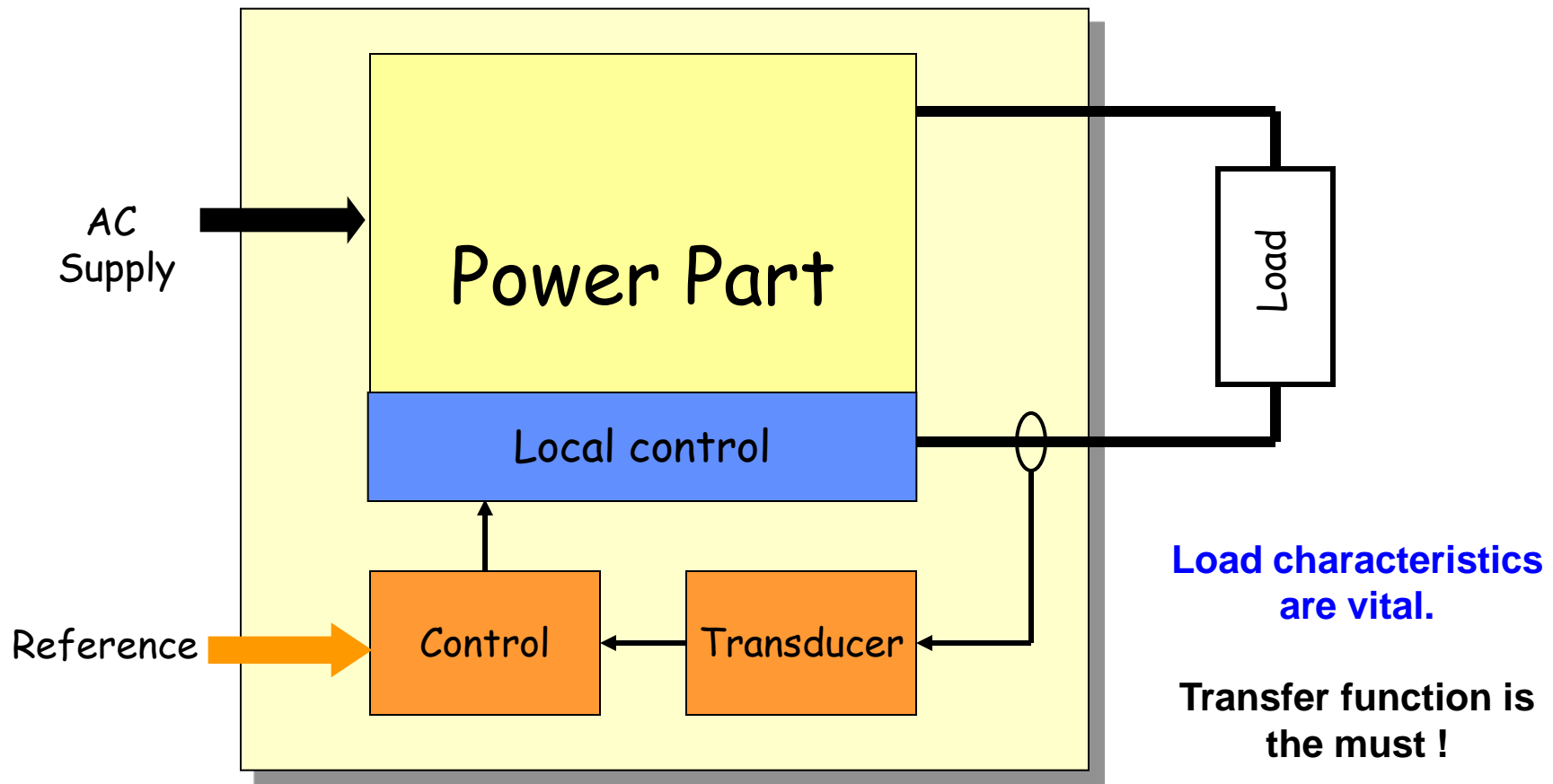

**Load characteristics are vital.**

**Transfer function is the must !**





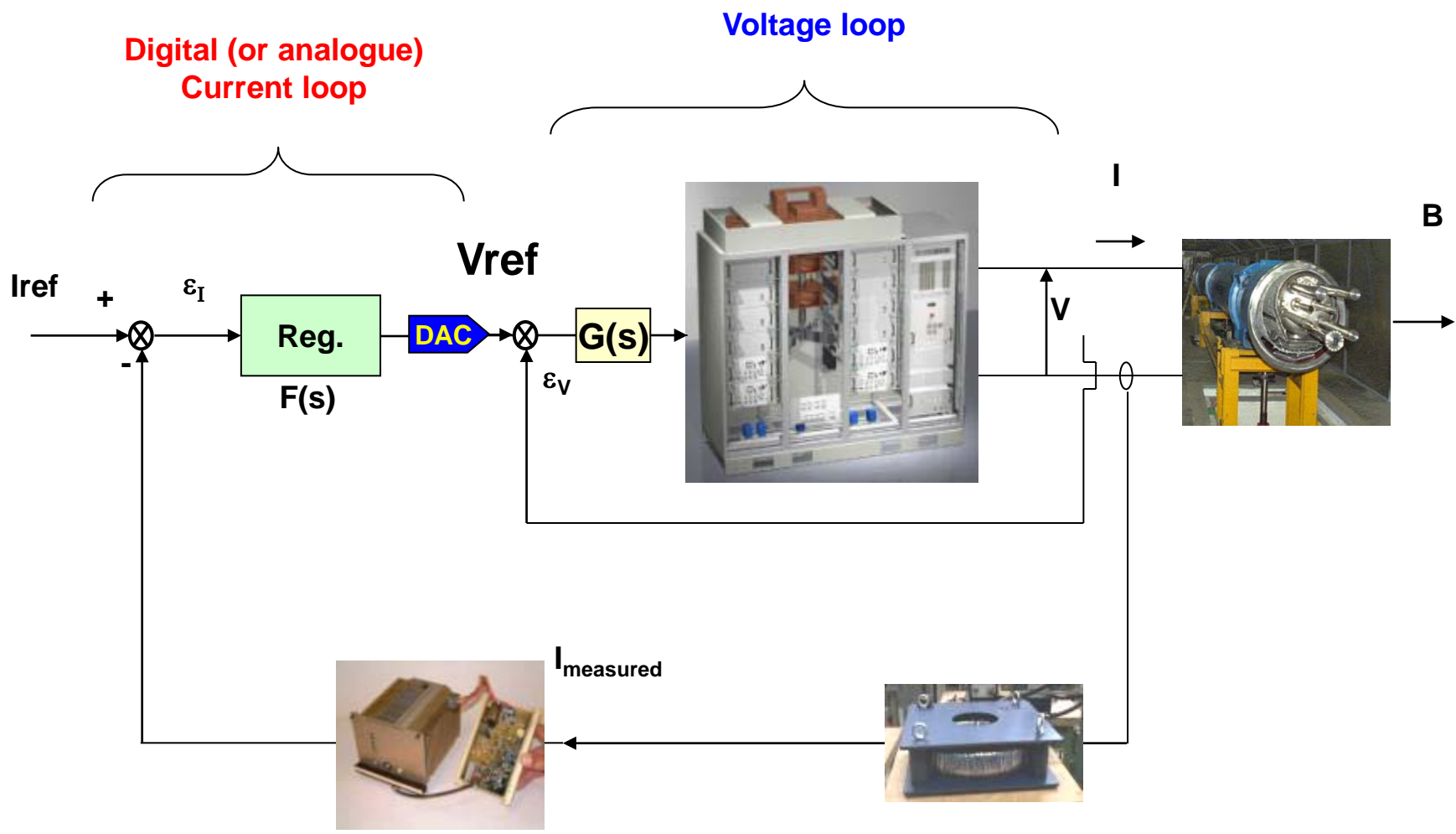



# Power converter : Performance requirements

**Overshoot**  
**Bandwidth**

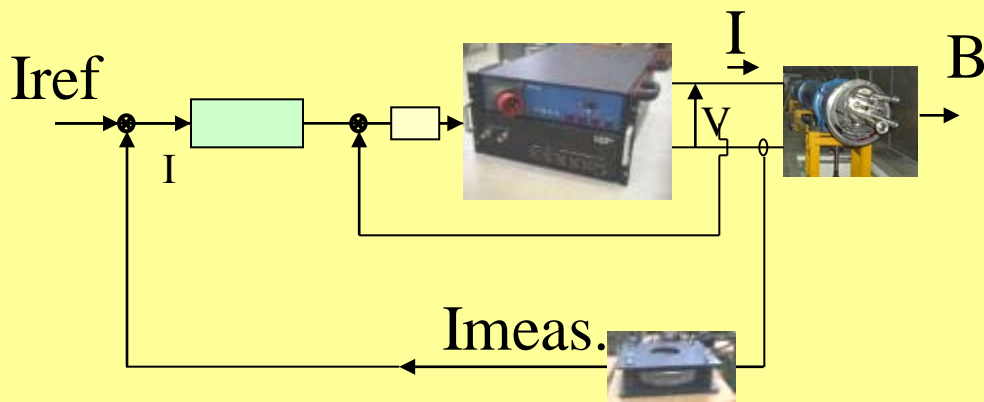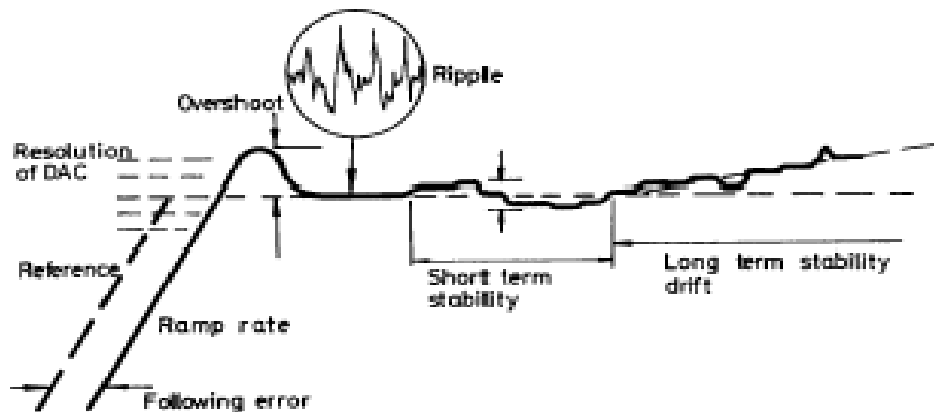

**Accuracy** **Reproducibility** **Stability** **Resolution** ?




# Glossary

## Precision

### – Accuracy


Long term setting or measuring uncertainty taking into consideration the full range of permissible changes\* of operating and environmental conditions.

\* requires definition

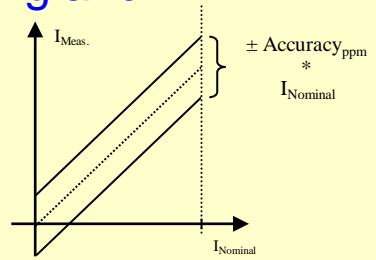

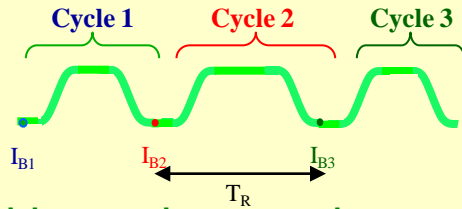
### – Reproducibility

Uncertainty in returning to a set of previous working values from cycle to cycle of the machine.


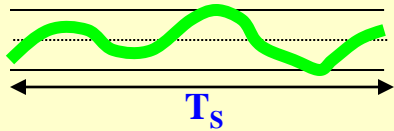
### – Stability

Maximum deviation over a period with no changes in operating conditions.



Accuracy, reproducibility and stability are defined for a given period


**Precision is qualitative . Accuracy, reproducibility, stability are quantitative.**



# Resolution

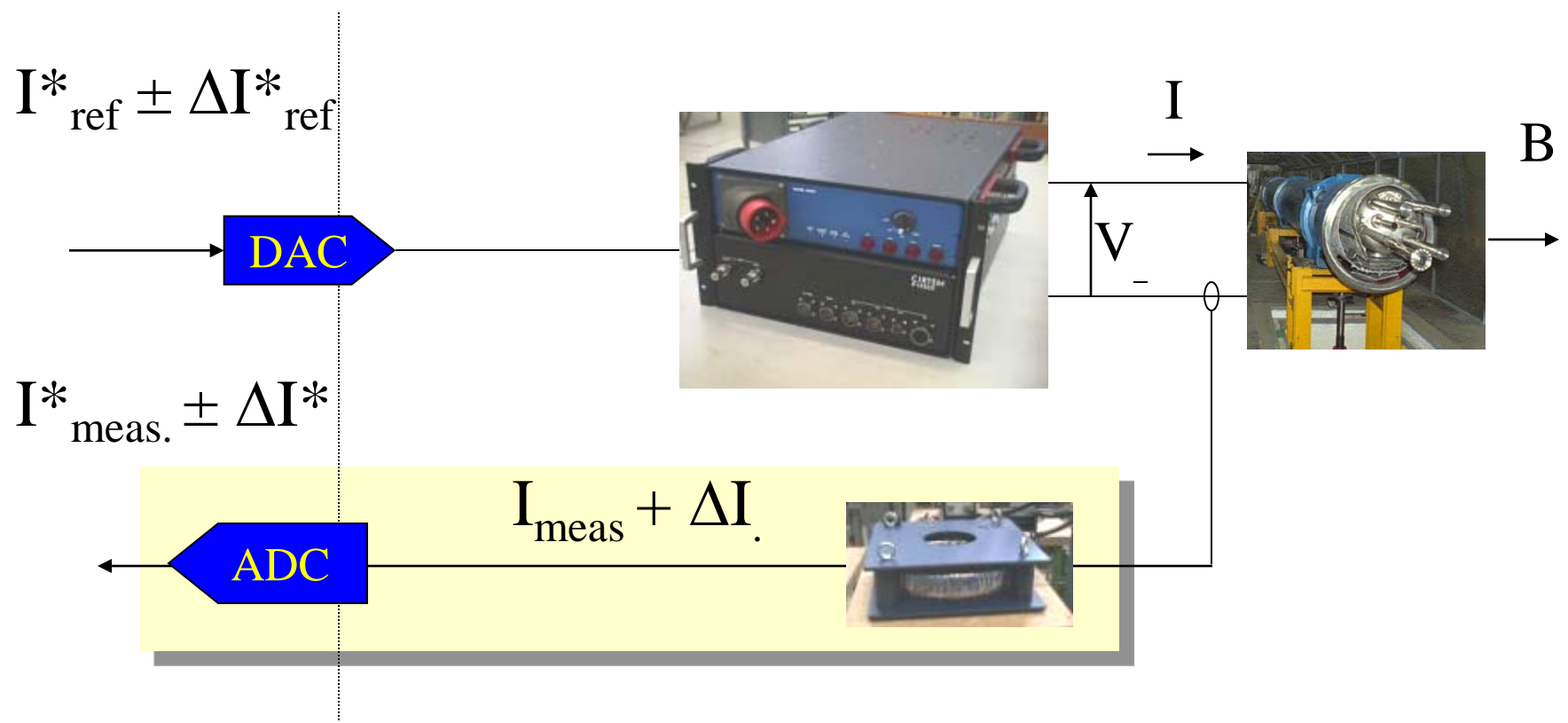
**Smallest increment that can be induced or discerned.**

**The resolution is expressed in ppm of  $I_{Nominal}$ .  
Resolution is directly linked to A/D system**





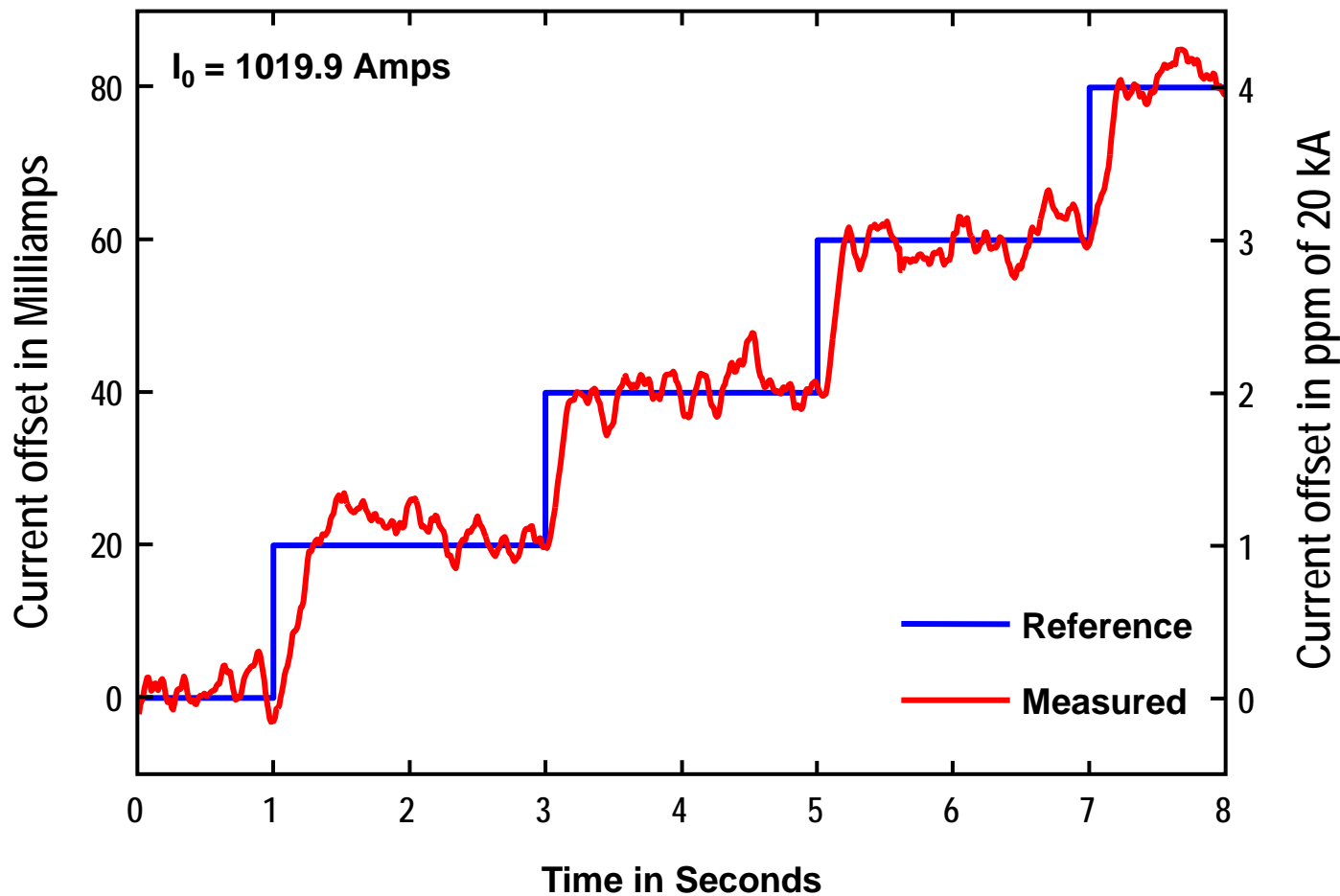
# Results of Resolution Test with the LHC Prototype Digital Controller







# RIPPLE

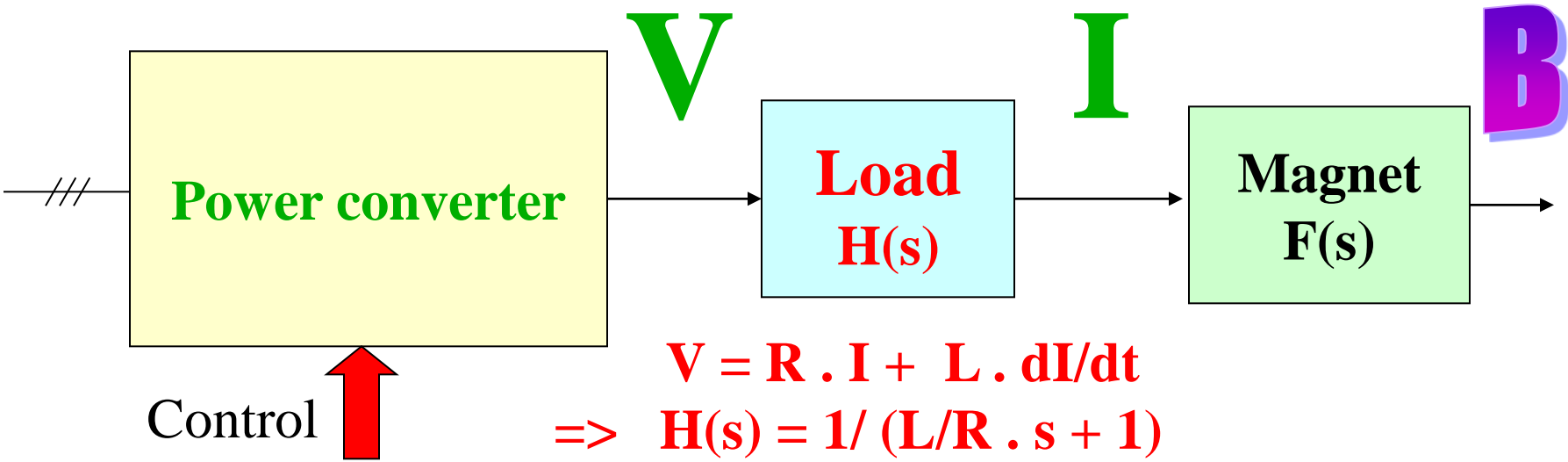

**Voltage ripple is defined by the power converter**

**Current ripple : load transfer function**

**(cables, magnet inductance,...)**

**(good identification is required if the load is a long string of magnets )**

**Field ripple : magnet transfer function (vacuum chamber,...)**

# EMC : ELECTROMAGNETIC COMPATIBILITY

## COMPATIBILITY : Emission - Immunity

IEC 61204-3

Norms for the power converters :

### Emission :

IEC 61204-3 ( replaced IEC-60478-3)  
(CISPR 11 ; EN 55011)


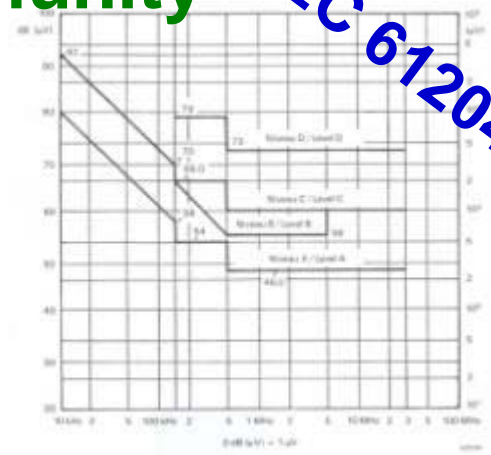


Figure 3 - Valeurs limites pour PEM par conduction  
Limit values for conducted EMI

### Immunity :

IEC 61000 - 4 :  
Burst 61000 - 4 - 4  
Surge 61000- 4 - 5

IEC 61000-4-4

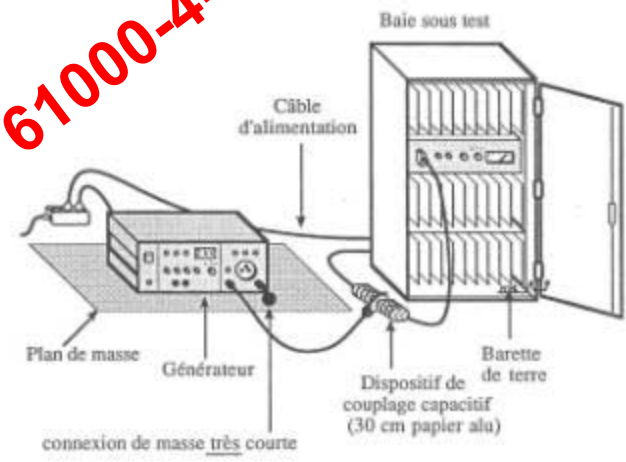



# Power converters specifications

**"Do you have one or two power converters for the test of magnet prototypes? 40 A will be enough ?  
Precision is not important for time being.  
Don't worry it's not urgent. Next month is OK "  
(Email received 05.12.08)**

**Load characteristics :** I and V reversibility ( 1 , 2 or 4-quadrants ? ) ;  
Transfer function (at least R, L, C) => will define V and then power

**Range :** I<sub>max</sub> (and I<sub>min</sub>)

**Rise and fall time (di/dt max; voltage constraint on the load);** is the precision an issue during the ramps (beam or no beam)

=> Pulsed converters with intermediate storage ?

=> bandwidth (topology and control strategy)

**Precision:** accuracy, reproducibility, stability - Resolution

**Ripple:**  $\Delta V(f)$  => passive (or active) filters ; control strategy (SMPC)


**Is the volume a constraint ? Is water cooling possible ?**

**Environment:** temperature and humidity; EMI conditions, radiation,...

**Hardware design and production take time.....**
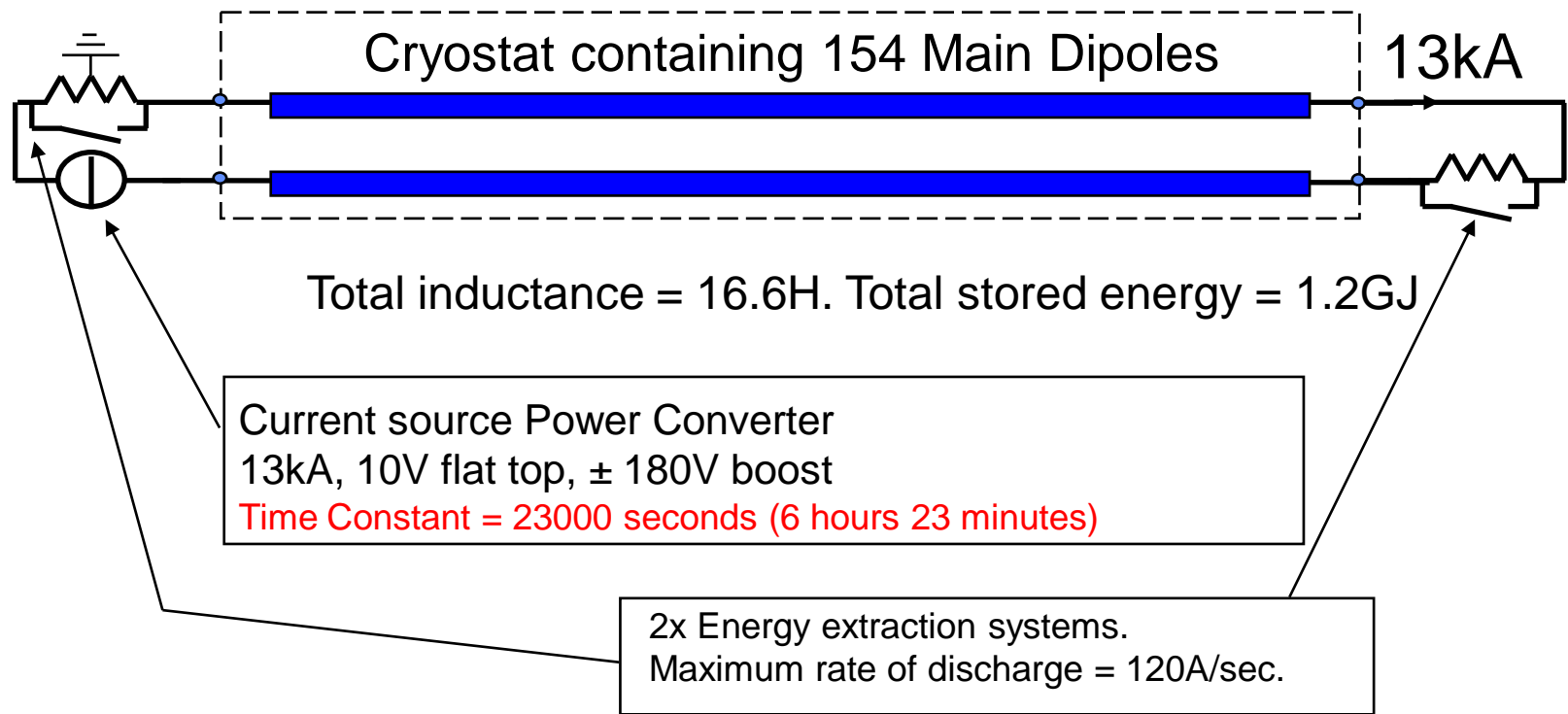
# One Sector (1/8) of the LHC Machine

*Need to think at circuit level : power converters, water cooled cables, extraction system (resistances and breakers), HTS current leads, cryogenics feed box, magnet string, diode, QPS,...*





# благодаря

**CAS - CERN Accelerator School :**

**Power converters for particle accelerators**

**26 - 30 Mar 1990, Switzerland**

**CERN Accelerator School and CLRC Daresbury Laboratory :**  
**Specialised CAS Course on**

**Power Converters for particle accelerators**

**12 - 18 May 2004 - Warrington, UK**

CERN ACCELERATOR SCHOOL AND THE INSTITUTE FOR NUCLEAR RESEARCH AND NUCLEAR ENERGY (INRNE - BULGARIAN ACADEMY OF SCIENCES) ARE ORGANISING A COURSE ON

## INTRODUCTION TO ACCELERATOR PHYSICS

19 SEPTEMBER - 1 OCTOBER 2010  
**GRAND HOTEL, VARNA**  
ST. KONSTANTINE & ELENA, VARNA, BULGARIA

This basic introductory course will be of interest to young staff from laboratories, universities and companies manufacturing accelerator equipment.

The course will focus on the basics of Accelerator Physics such as transverse and longitudinal dynamics, beam measurements and an introduction

to multi-particle dynamics. A series of topical seminars and tutorials will complete the programme.

Contact: CERN Accelerator School  
1211 Geneva 23 - Switzerland Fax: +41 22 767 9480 - [www.cern.ch/schools/CAS](http://www.cern.ch/schools/CAS)