

Switched Mode Converters (4 Quadrants)

Yves THUREL
CERN

4 Quadrant basic background

- 4Q. Conventions

- 4Q. Working area / loads

- 4Q. Basic schematics

4 Quadrant topologies Review

- Principle schematics (main ones presented)

- Advantages / Drawbacks

- Some realizations

4 Quadrant practical realization & example

- LHC Specifications

- LHC Topology choice explained

- LHC Converter principles

- Technical points highlighted (loops, circulating current,...)

- Realizations

4 Quadrant basic background

- 4Q. Conventions

- 4Q. Working area / loads

- 4Q. Basic schematics

4 Quadrant topologies Review

- Principle schematics (main ones presented)

- Advantages / Drawbacks

- Some realizations

4 Quadrant practical realization & example

- LHC Specifications




- LHC Topology choice explained

- LHC Converter principles



- Technical points highlighted (loops, circulating current,...)

- Realizations



4 Quadrant Operation: Definition (applied to R-L circuit)

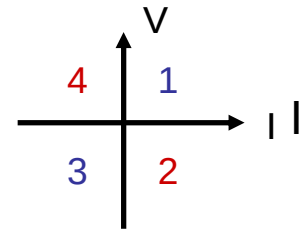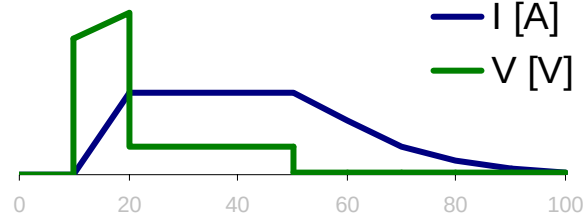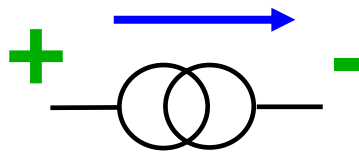1 Quadrant mode

Control of the decreasing current is still possible within drastic conditions and limits. (R_{CIRCUIT} acts as discharger.)

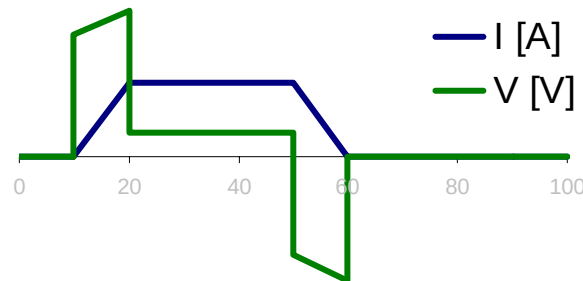
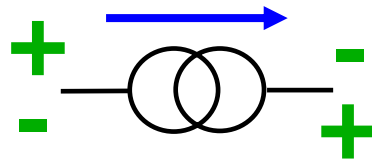
2 Quadrant mode

Current is controlled (being always in the same sense), when increasing or decreasing.

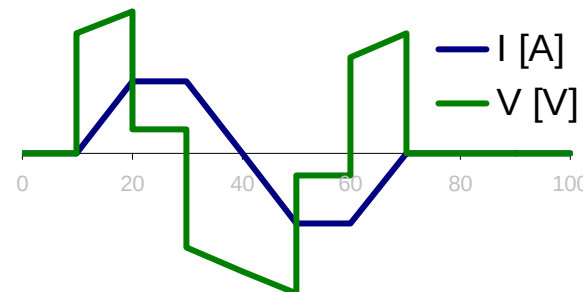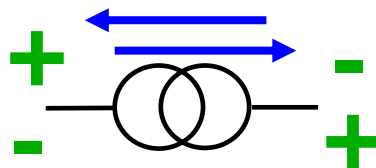4 Quadrant mode

No theoretical operation limitation.

4 Quadrant Operation: Loads Typical Cycle (R-L)

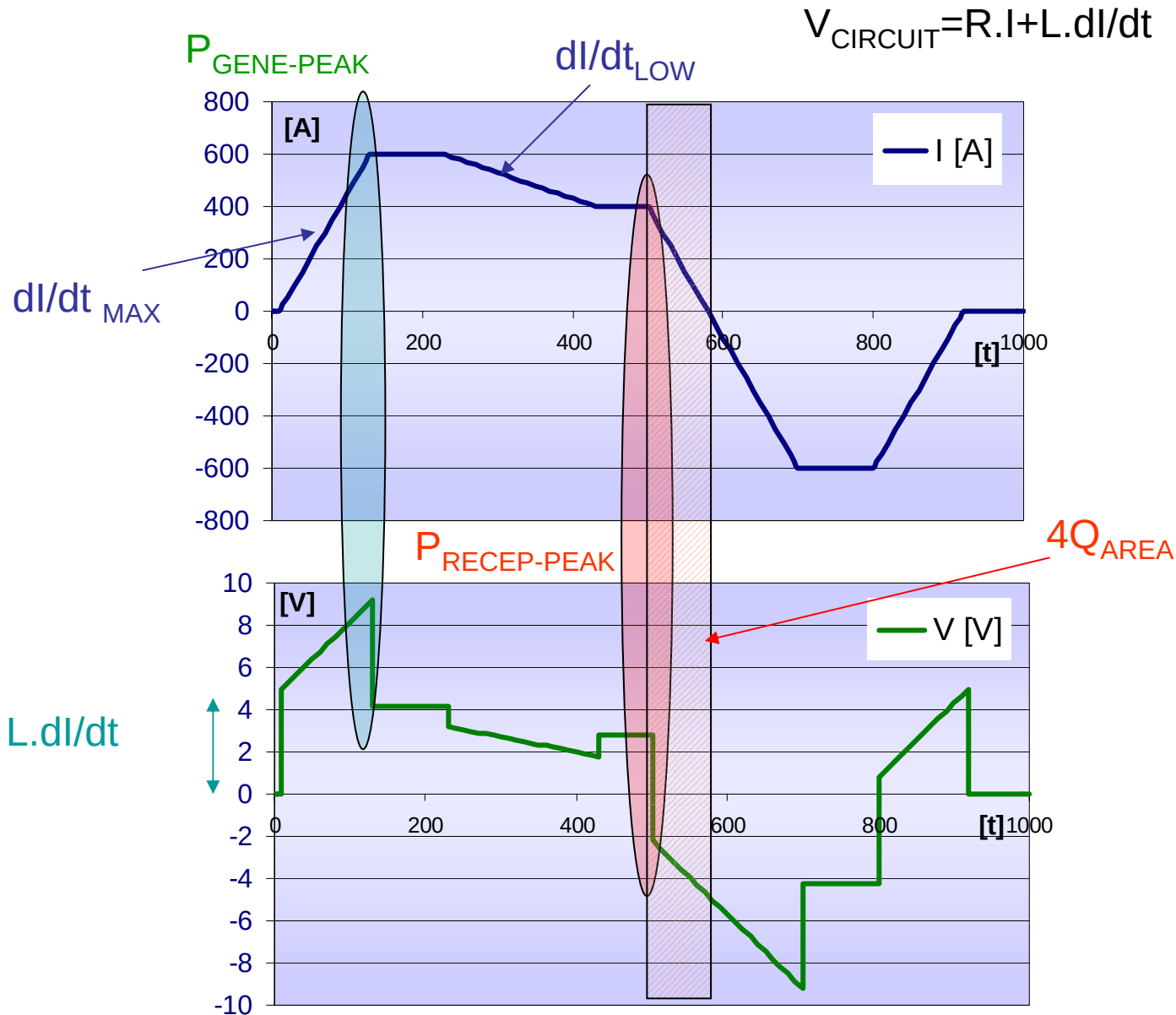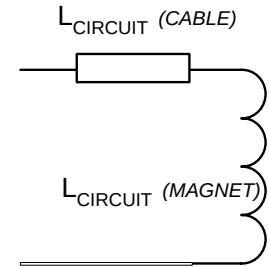CIRCUIT

$$L = 1\text{H}$$

$$R = 7\text{mOhms}$$

$$dI/dt_{\text{MAX}} = 5\text{A.s}^{-1}$$

$$I_{\text{MAX}} = 600\text{A}$$

KEY FEATURES


$$L.dI/dt = 5\text{V}$$

$$R.I_{\text{MAX}} = 4.2\text{V}$$


$$V_{\text{MAX}} = 9.2\text{V}$$

4 Quadrant Operation: Load Influence on topology

“Pulsed” Machine

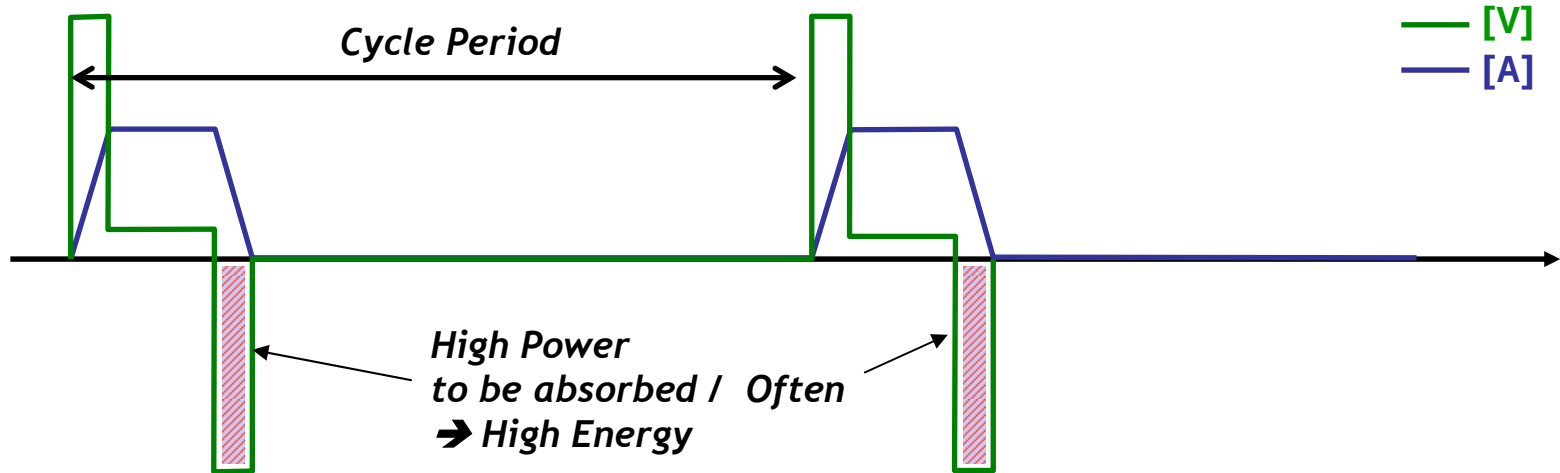

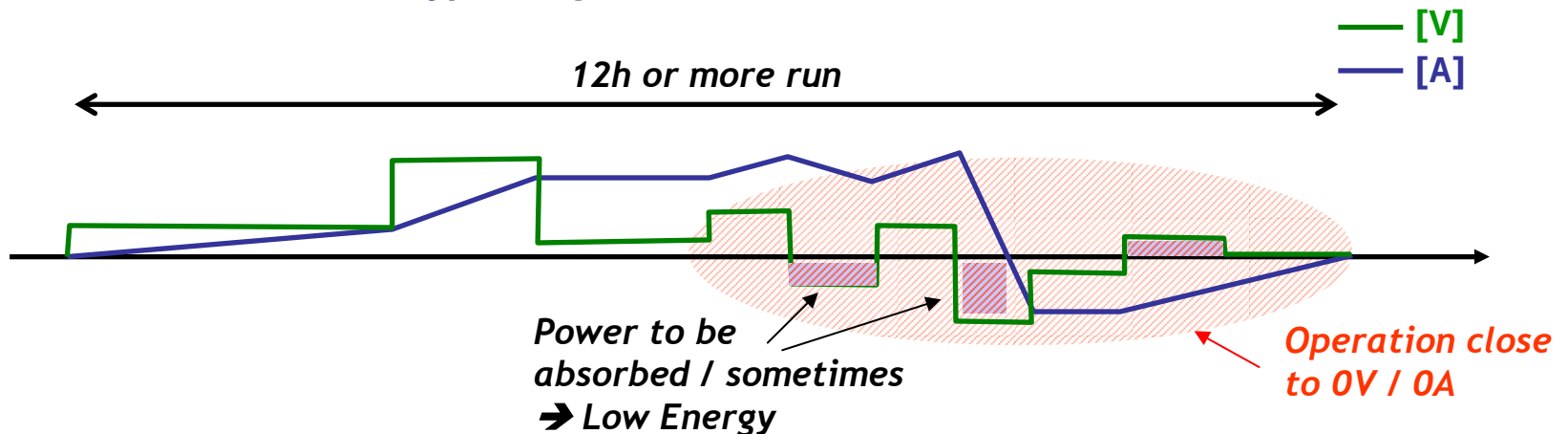“Slow” Machine: LHC Type / Magnet or orbit Correctors



4 Quadrant Operation: Load Impact on cost & design parameters

Circuit Characteristics


- $L = 1\text{H}$ *LHC Machine*
- $di/dt = 10\text{A.s-1}$ *LHC Machine*
- $I = [-600\text{A}; +600\text{A}]$ *LHC Machine*
- $P_{\text{Cable}} < 15\text{kW}$ *LHC Tunnel*

Circuit Key Features


- $L \cdot di/dt = 10\text{V}$
- $10\text{mOhms} < R_{\text{cable}} < 21\text{mOhms}$
- $6\text{V} < R_{\text{cable}} \cdot I_{\text{MAX}} < 12\text{V}$

20 mOhms

(V: Output Voltage Power converter)

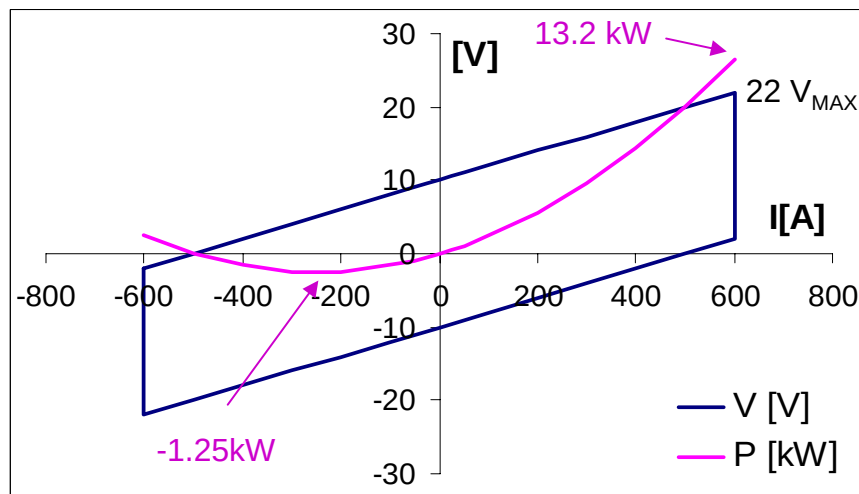10 mOhms

(P: Output power Power converter)

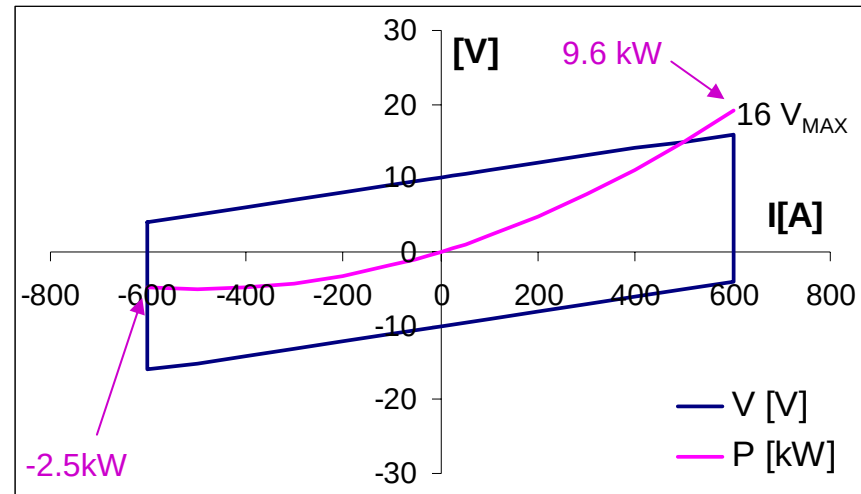

P_{MAX}	13.2kW	100%	P_{MAX}	9.6kW	73%
P_{ABSORBED}	1.25kW	100%	P_{ABSORBED}	2.5kW	200%
Cable Losses	14.4kW	100%	Cable Losses	7.2kW	50%

Price




4 Quadrant Operation: Receptor mode

Goals:





- Absorbing magnet energy
- Still regulating magnet reverse voltage, i.e di/dt

Solutions:


Ideal Magnet
No Resistance

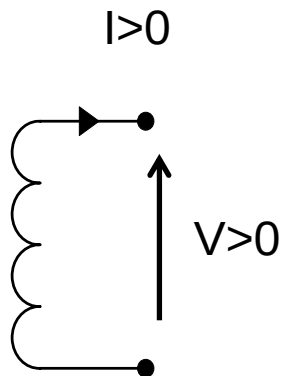

Energy Receptor Concepts

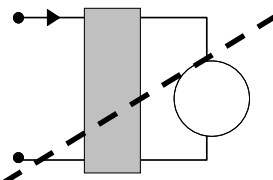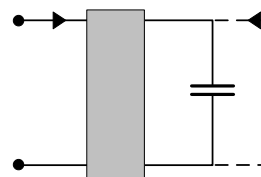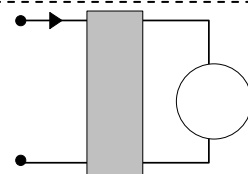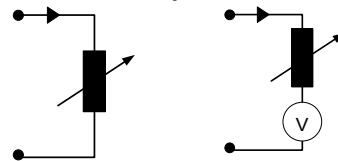

- Variable resistor (active)
- Voltage source added for 0 A transition: No voltage can be obtained when 0 Amp in the magnet.
- Converter magnet-mains, giving back energy to mains.
- Converter magnet-capacitor, storing the magnet energy.
- This capacitor is charged by the magnet and the needed generator converter
- *Alternative (not very used) solutions could be: rotative machine, or (supraconductor) inductor...not treated here.*

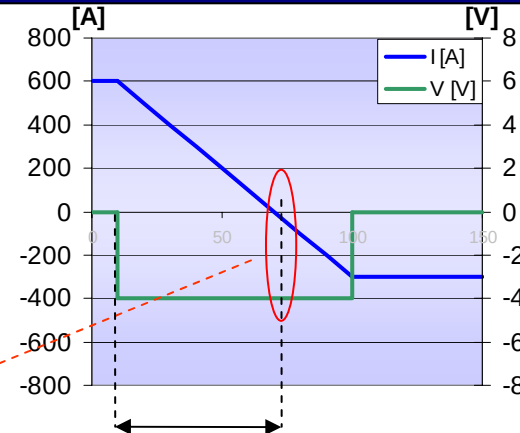

4 Q Stage: Main topologies

2x Thyristor bridge in anti//

Very well known


Power returned to mains

Linear dissipative Stage

Basic background known, (push-pull stage)

4Q operation to be explained later

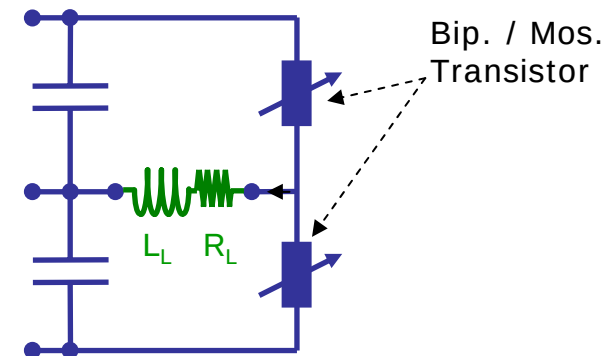
Dissipation in the transistors, acting as programmable resistor



Switching Stage

Conventional H bridge (L-C Filter)

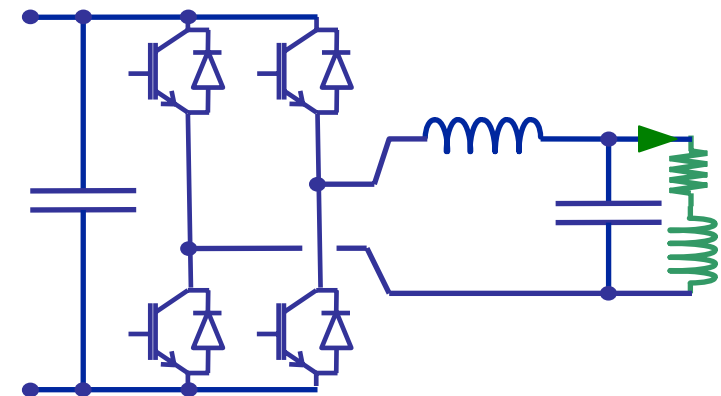
Power returned to capacitor or dissipated in brake chopper.



4Q Stage: Linear basic principle

(* The 2 voltages are always the same)


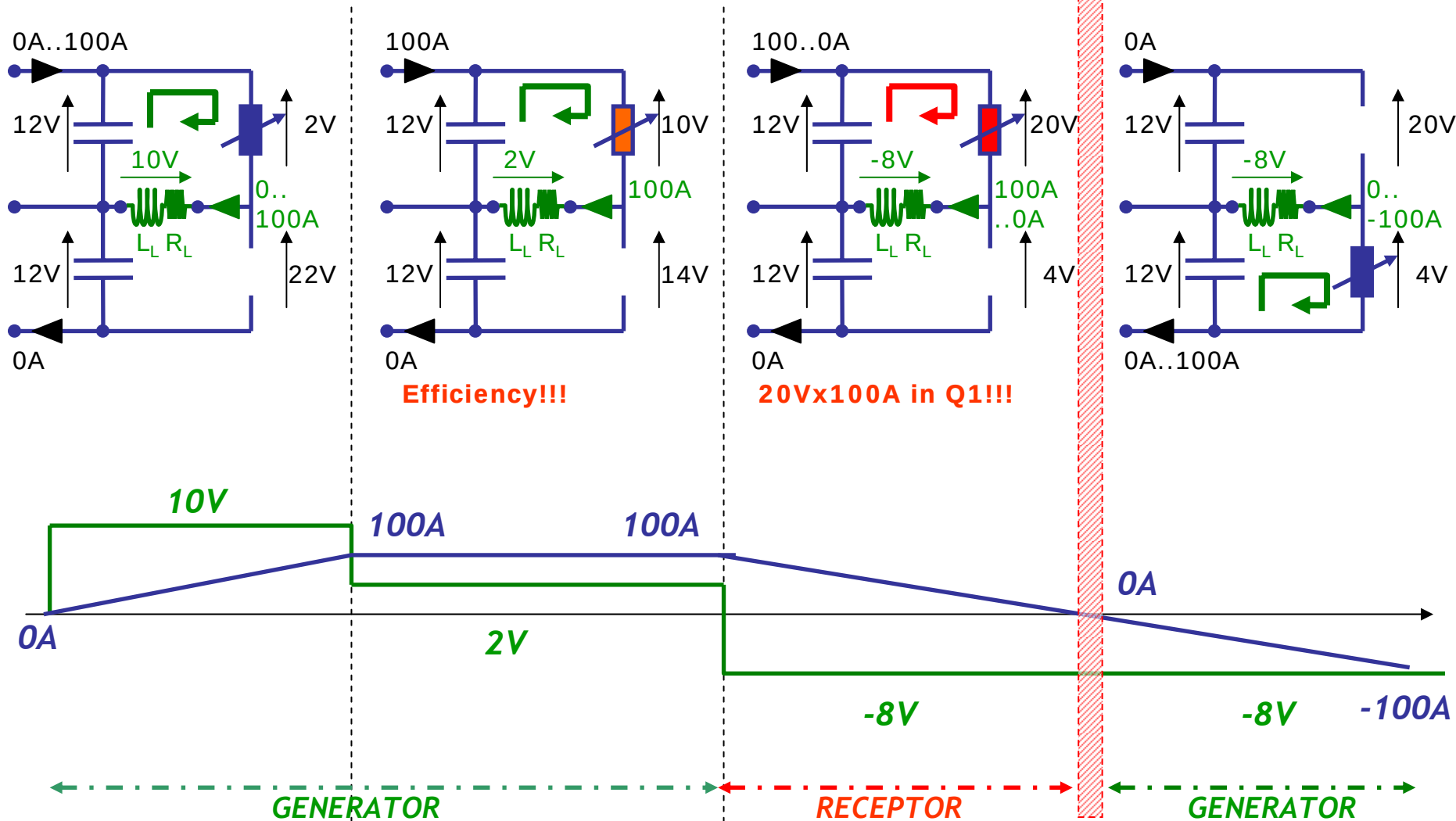
...Combined with double* DC fixed voltage output




4Q Stage: Linear basic principle

(* The 2 voltages are always the same)

...combined with double* DC variable voltage output
for better efficiency and losses reduced in receptor mode

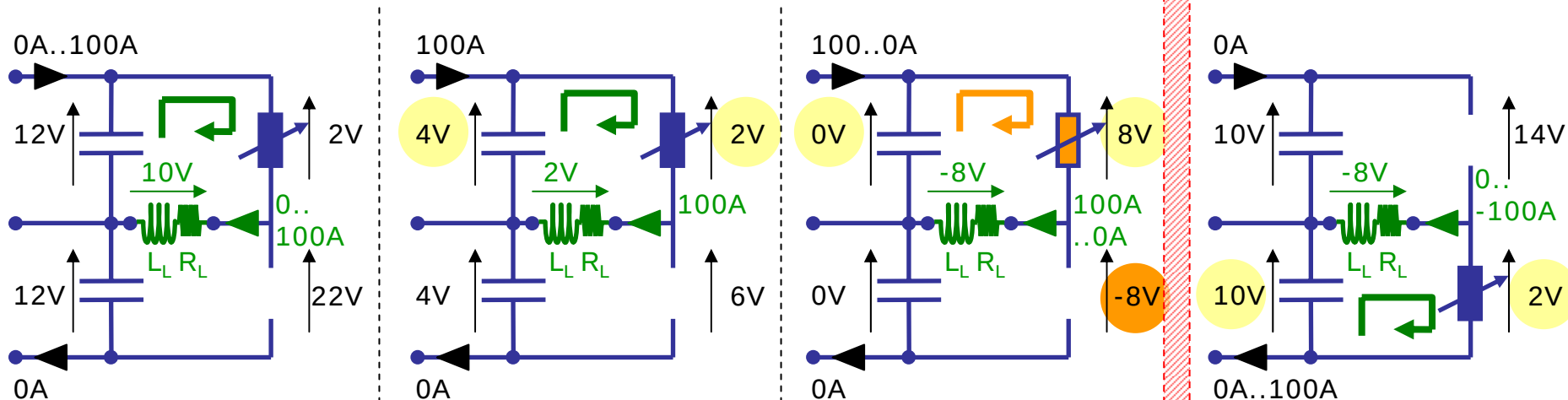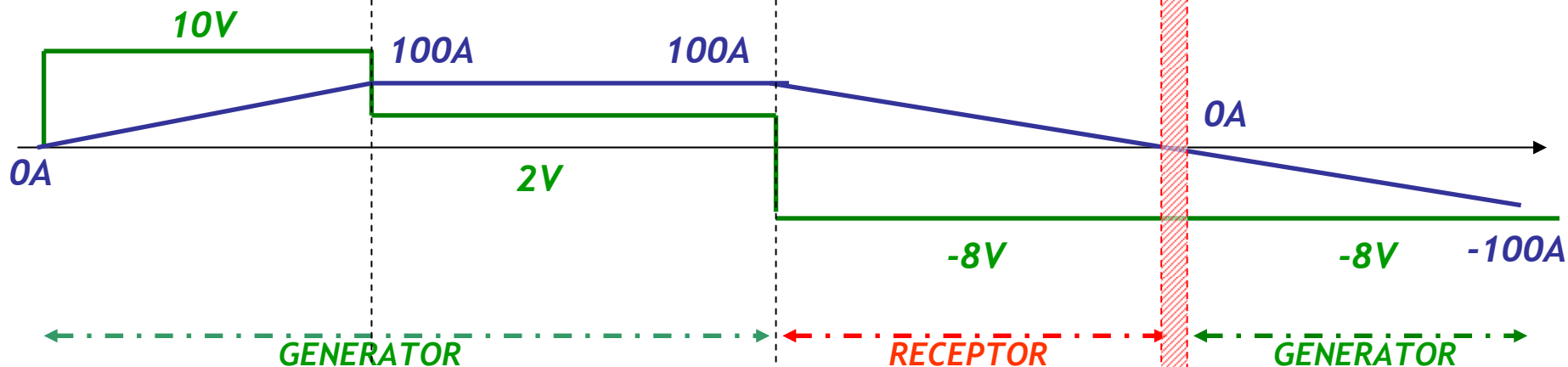Efficiency better8Vx100A in Q1

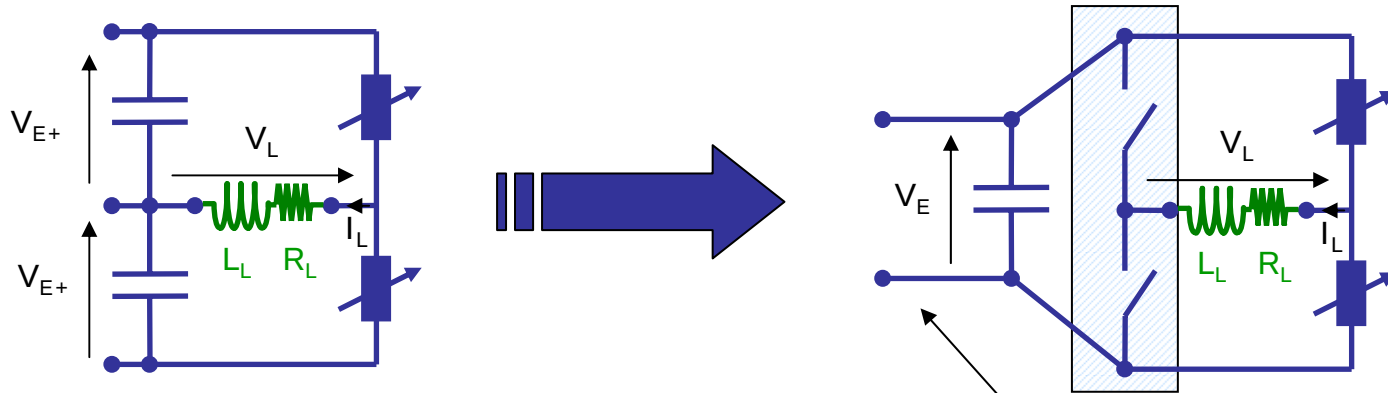4Q Stage: Linear basic principle (variation “linear” H bridge) ...combined with single DC variable voltage output




Remark:

This solution is easier, from the inverter side, but leads to polarity new transitions which can be source of distortion, and finally lead to a complex 4 quadrant stage

Polarity Switches

Single output inverter

4Q Stage: Switching basic principle

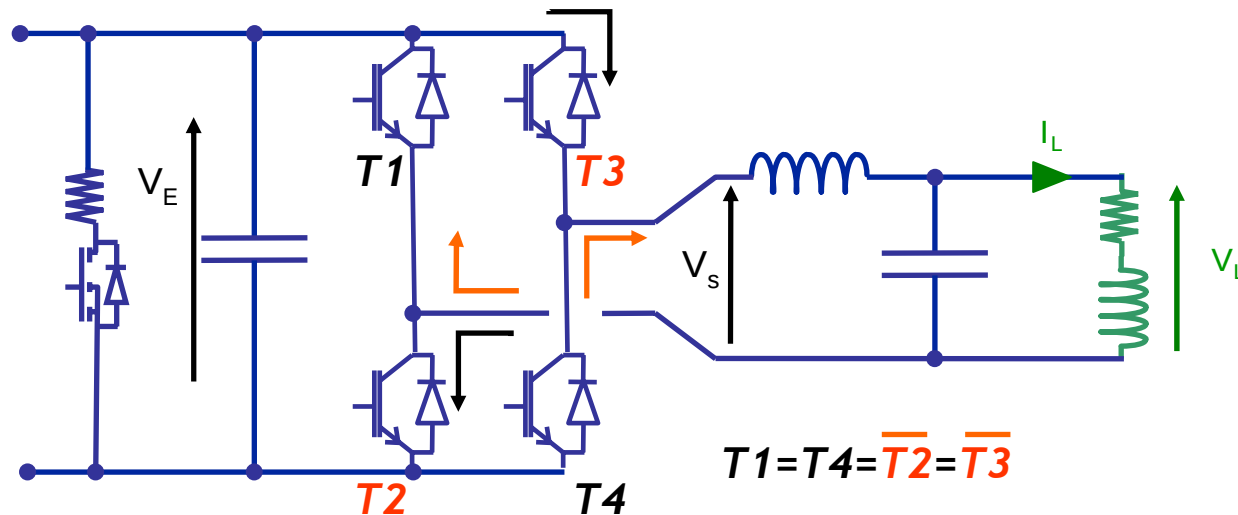

$$T1 = T4 = \overline{T2} = \overline{T3}$$


H Bridge: 2 modes

It is possible to work in Buck Mode so that both

- ΔI is reduced (HF output voltage ripple)
- Losses are reduced

Note:

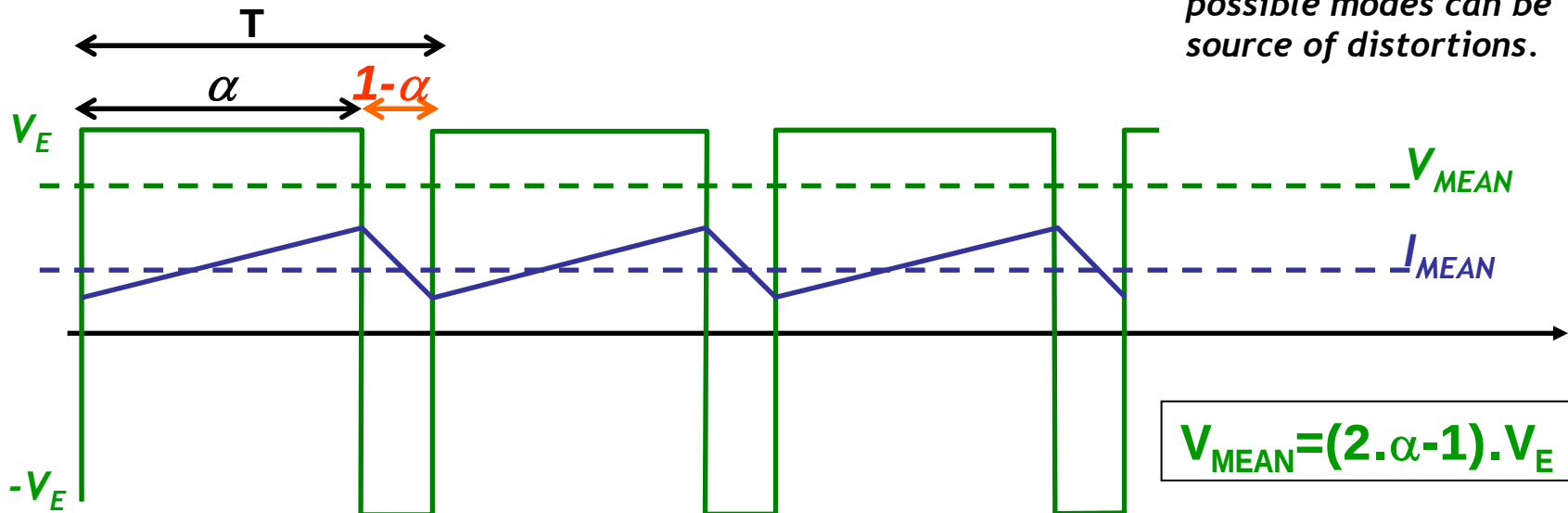transition between these 2 possible modes can be source of distortions.



4 Quadrant basic background

4Q. Conventions

4Q. Working area / loads

4Q. Basic schematics

4 Quadrant topologies Review

Principle schematics (main ones presented)

Advantages / Drawbacks

Some realizations

4 Quadrant practical realization & example

LHC Specifications

LHC Topology choice explained

LHC Converter principles


Technical points highlighted (loops, circulating current,...)

Realizations

Topologies: Key points, (how to classify them, how to select them?)

POWER RANGE,
DISSIPATIVE OR NOT,
EFFICIENCY

SIZE, WEIGHT,
COST

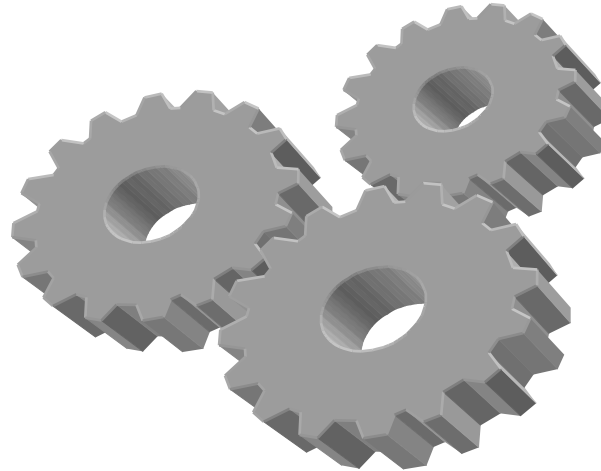


TOPOLOGY CHOICE ????


AC MAINS PERT. REJ.,
EMC, BF & HF RIPPLE

DISTORTION
BANDWIDTH

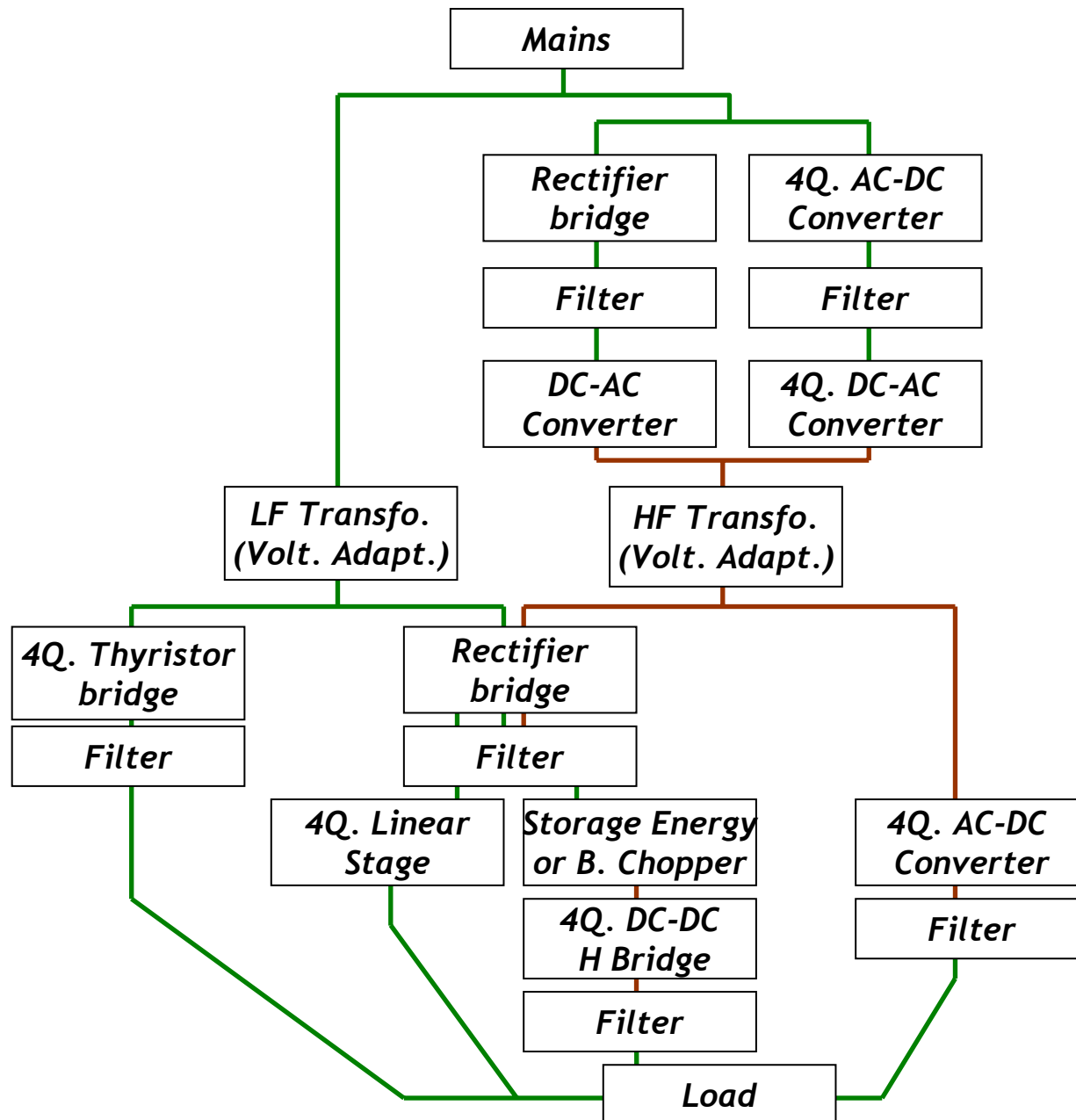NUMBER OF CPTS, DESIGN
COMPLEXITY, MTBF, USE OF
COMMERCIAL PART




Topologies: Thyristor (Principle)

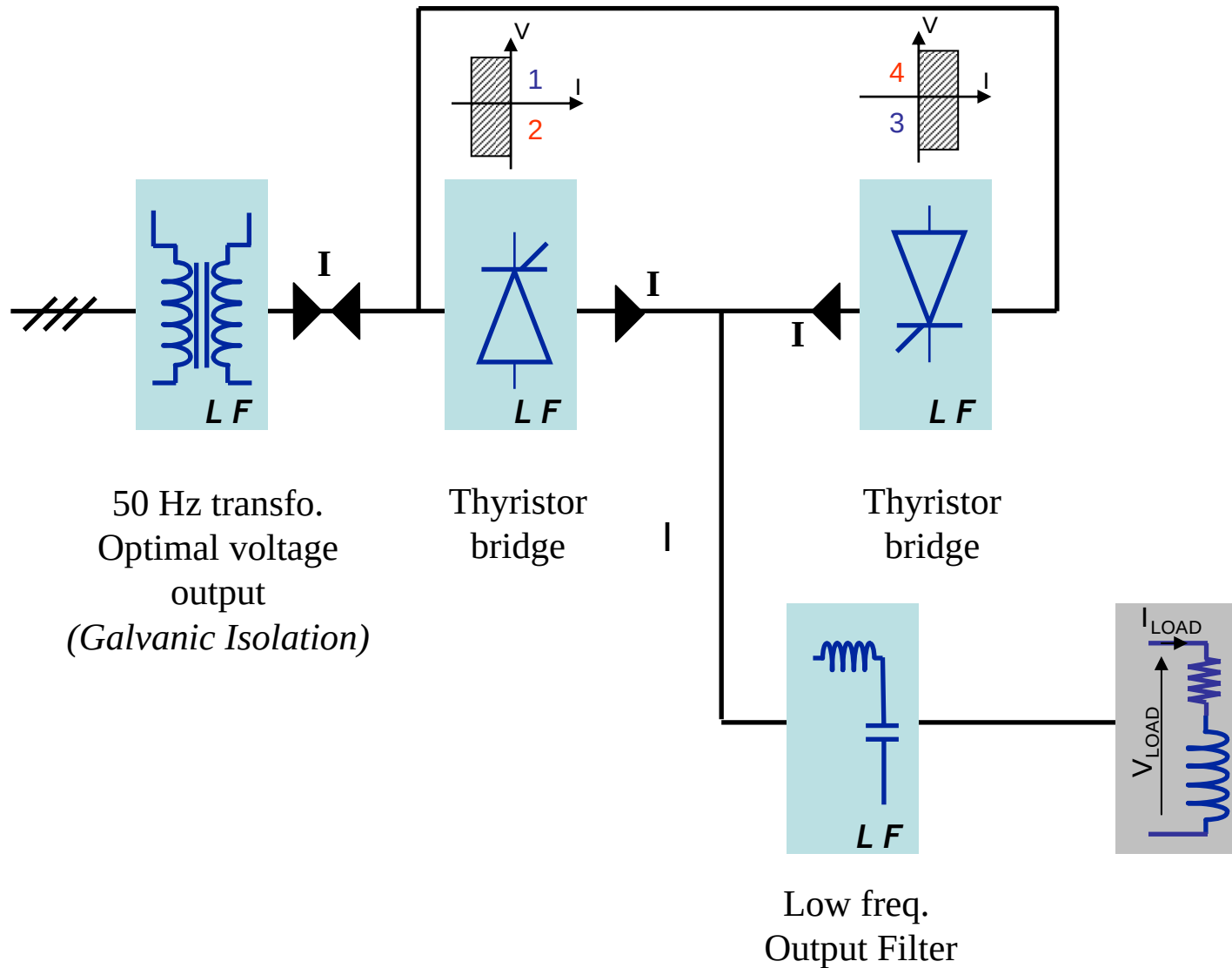

Topologies: Thyristor (schematics Example)

Basic schematic

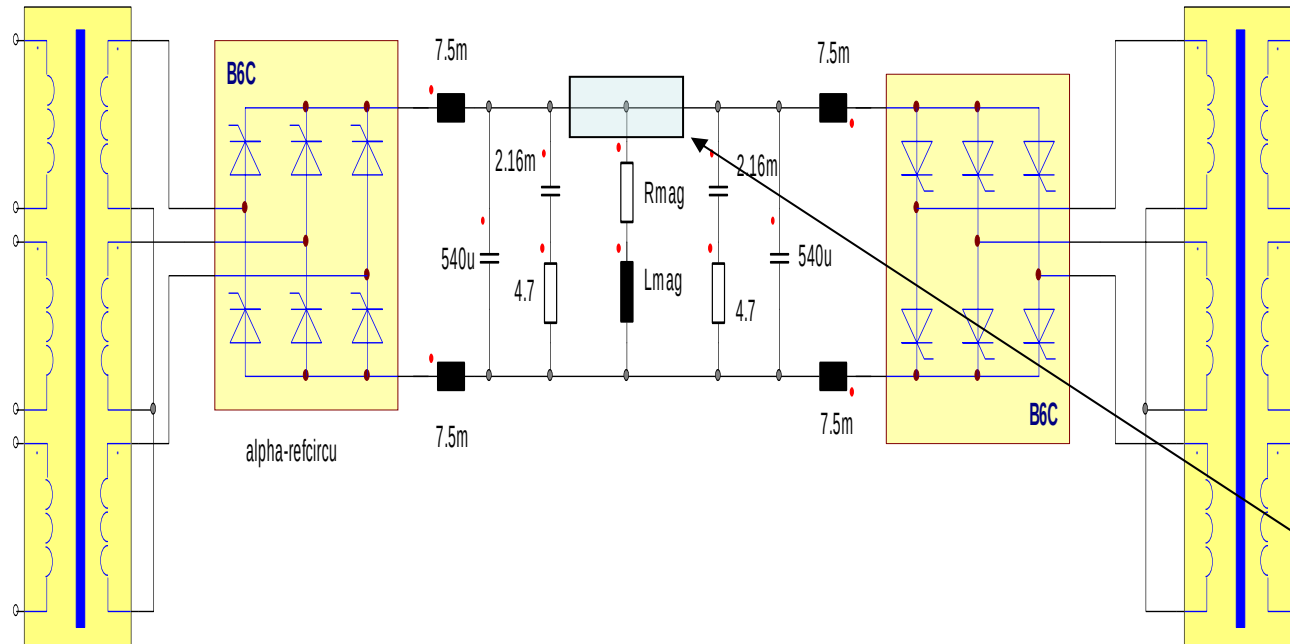- $[0,0]$ & $[V]$ axis required circulating current between the 2 bridges



- Active Filter increase dynamic performance (low amplitude bandwidth, low frequency ripple, perturbation...)



Adding a circulating current between the 2 thyristor bridges helps!!!


Topologies: Thyristor (Discussion)

Advantages


- Huge power possible
- Not Dissipative: power returned to mains
- High Efficiency
- Very well known topology
- Rather simple design
- No High frequency signal (low frequency operation): EMC easy to handle

Drawbacks

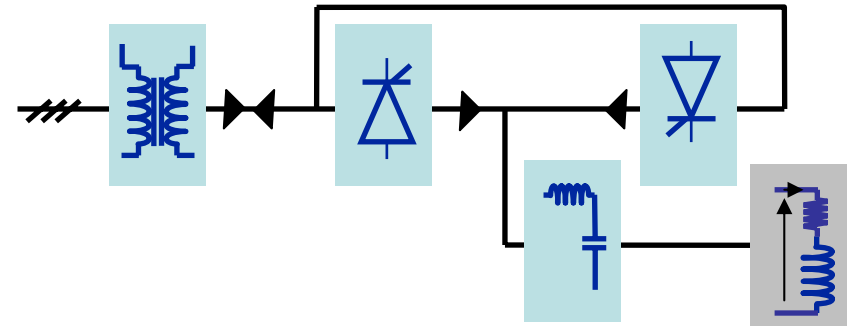- Low Bandwidth (addition of active filter can help a bit in small signal)
- Poor AC mains perturbation rejection (speed loop limited by L-C filter)
- Distortion (crossing axes, and point $[0,0]$) requires some additional circuit for high precision converter: Circulating current
- Size, weight of transformer and filtering elements



Topologies: 50Hz + Linear (Principle)

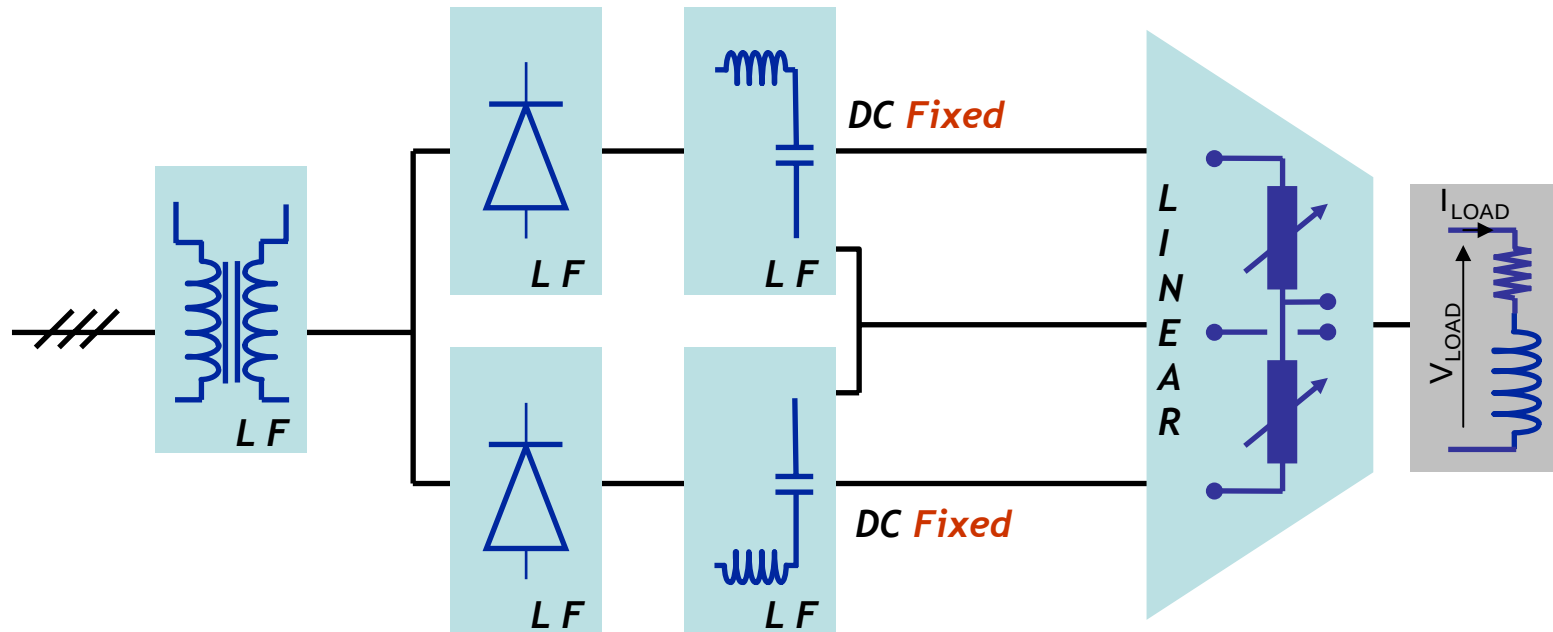


50 Hz transfo.
Optimal voltage
output
(Galvanic Isolation)

Rectifier +
Double Output
High Freq.
Filter

Linear Stage
(Dissipate Magnet
Energy)

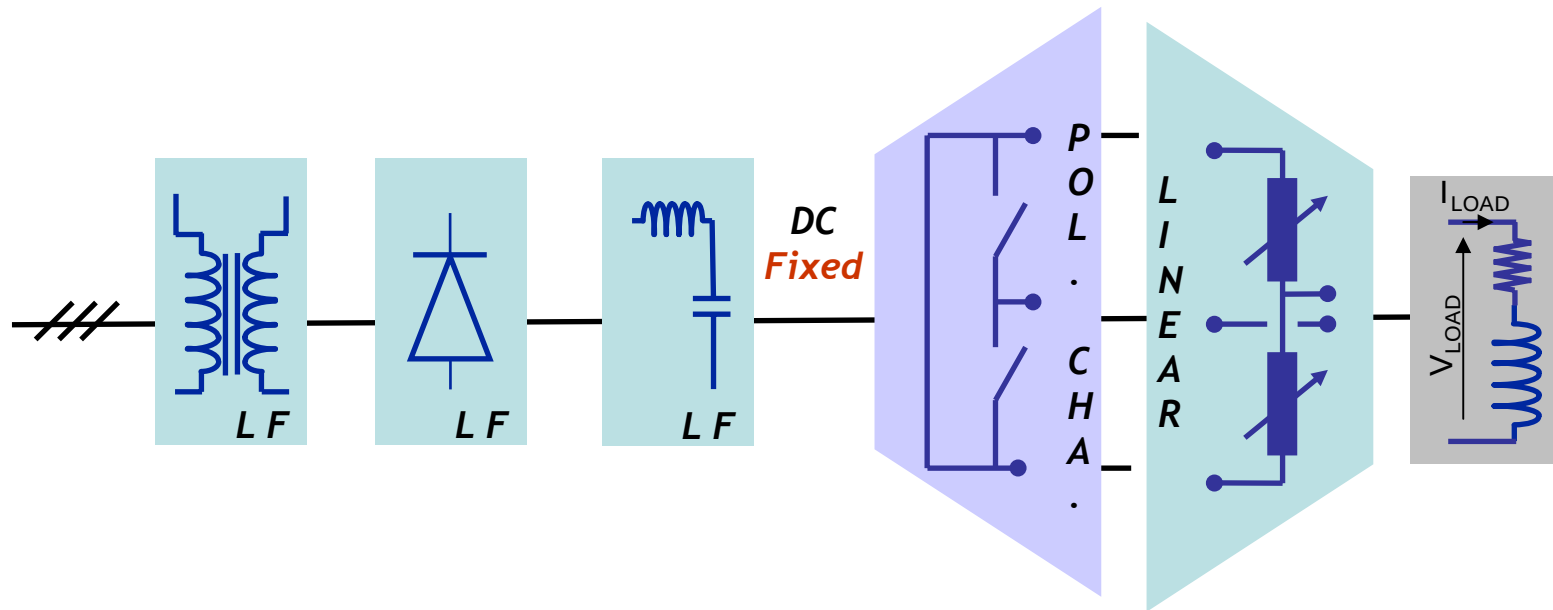Topologies: 50Hz + Linear (Principle *variation*)



50 Hz transfo.
Optimal voltage
output
(*Galvanic Isolation*)

Diode
bridge

Low freq.
Output Filter

H Bridge
Linear Stage
(*Polarity Changer*
/
*Dissipate Magnet
Energy*)

Topologies: 50Hz + Linear (Discussion)


Advantages

- Schematics and topologies are very well known
- Simple schematics
- Adding circulation current helps
- Bandwidth (10 kHz)

Drawbacks

- Dissipative
- Efficiency very low in generator mode
- Size, weight of transformer and filtering elements
- Often realized with several transistors in // (MTBF and avalanche failure)

Topologies: 50Hz + Switching (Principle)

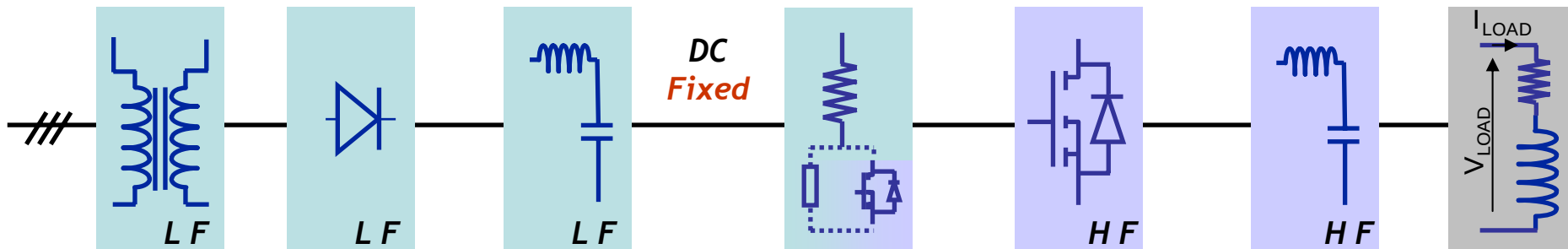

50 Hz transfo.
Optimal voltage
output
(Galvanic Isolation)

Diode
bridge

Low freq.
Output Filter
(Magnet Energy
 $\rightarrow 1/2.C.V^2$)


Add.
Brake Chopper
(Optional)
(Dissipate Magnet
Energy)

PWM
Converter
Hard
Commutation

High freq.
Output Filter

Topologies: 50Hz + Switching (Schematics Example)

Basic schematic

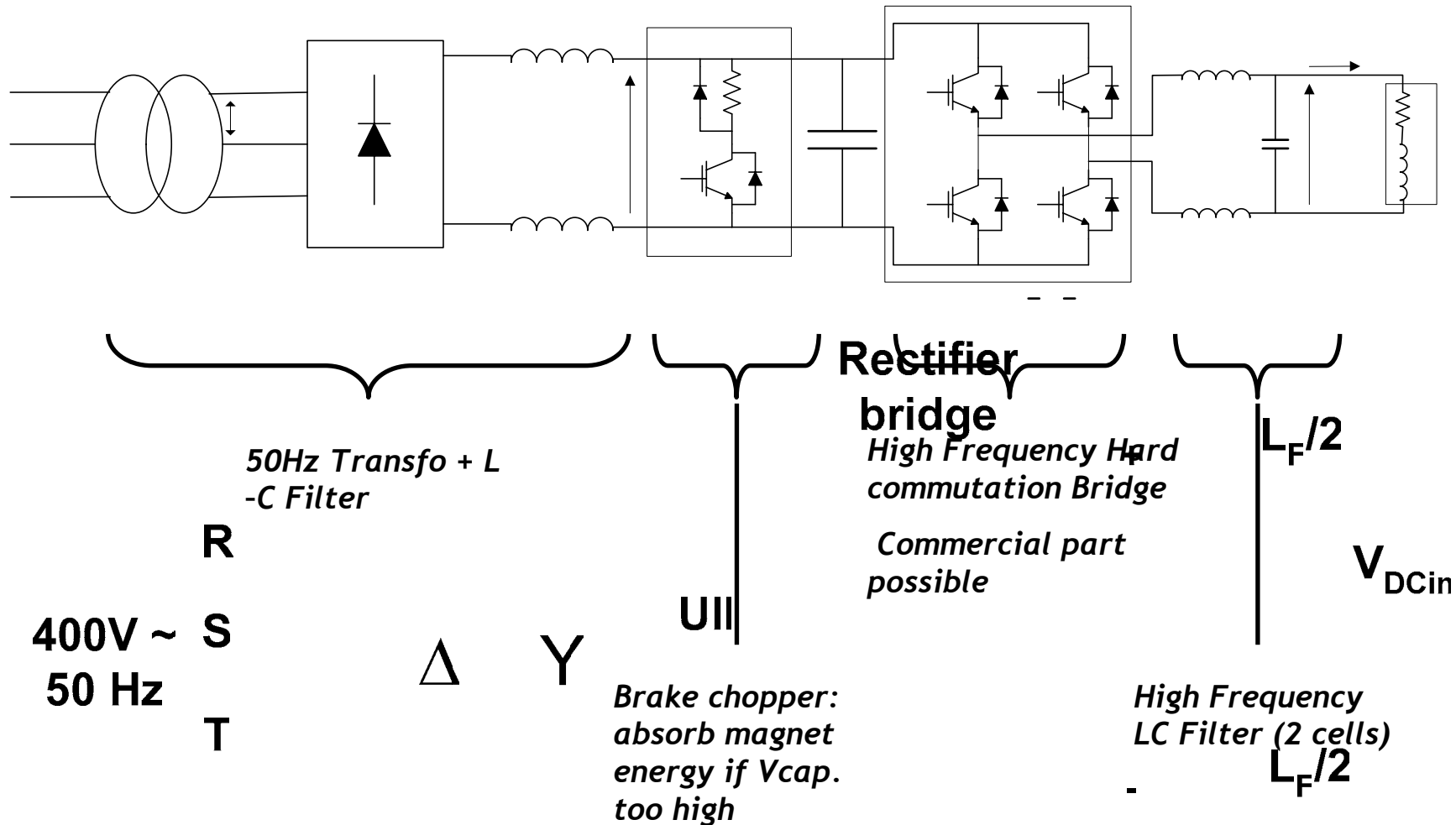

Topologies: 50Hz + Switching (Discussion)


Advantages

- Huge power possible
- Part of magnet energy re-used
- Very well known topology– possible to use commercial standard elements
- High bandwidth (10 kHz)
- Good AC mains perturbation rejection
- No distortion of the signal (if H bridge not changing mode)


Drawbacks

- H bridge hard commutation @ high current
- 50Hz LC-Filter can be un-damped by H bridge negative equivalent resistor
- Size, weight of transformer and filtering elements
- Hard commutation EMC to cope with
- Low voltage high current not ideal (loss of the switching H bridge, $f_{\text{switching}}$ limited)
- HF filtering Ripple difficult (if buck mode not used), at “only $f_{\text{switching}}$ ”


$\pm 150A$
 $\pm 200V$

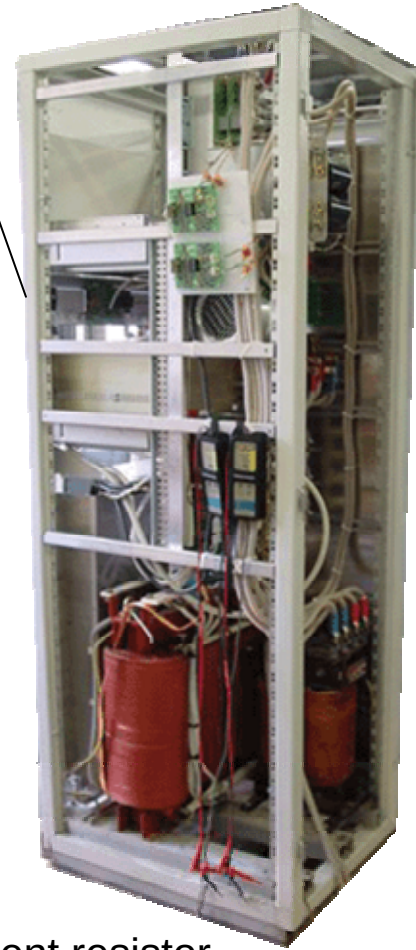

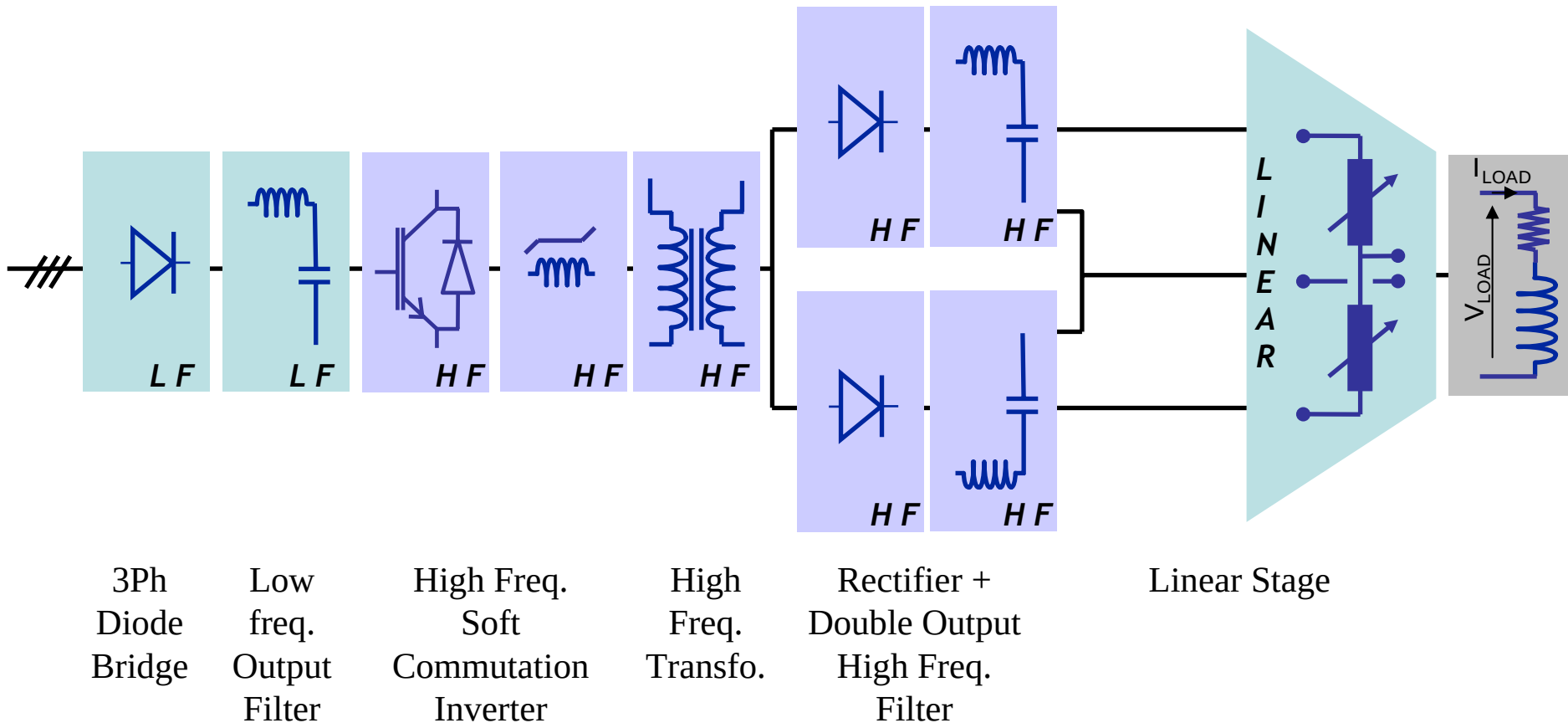Topologies: Switching + Linear (Principle)





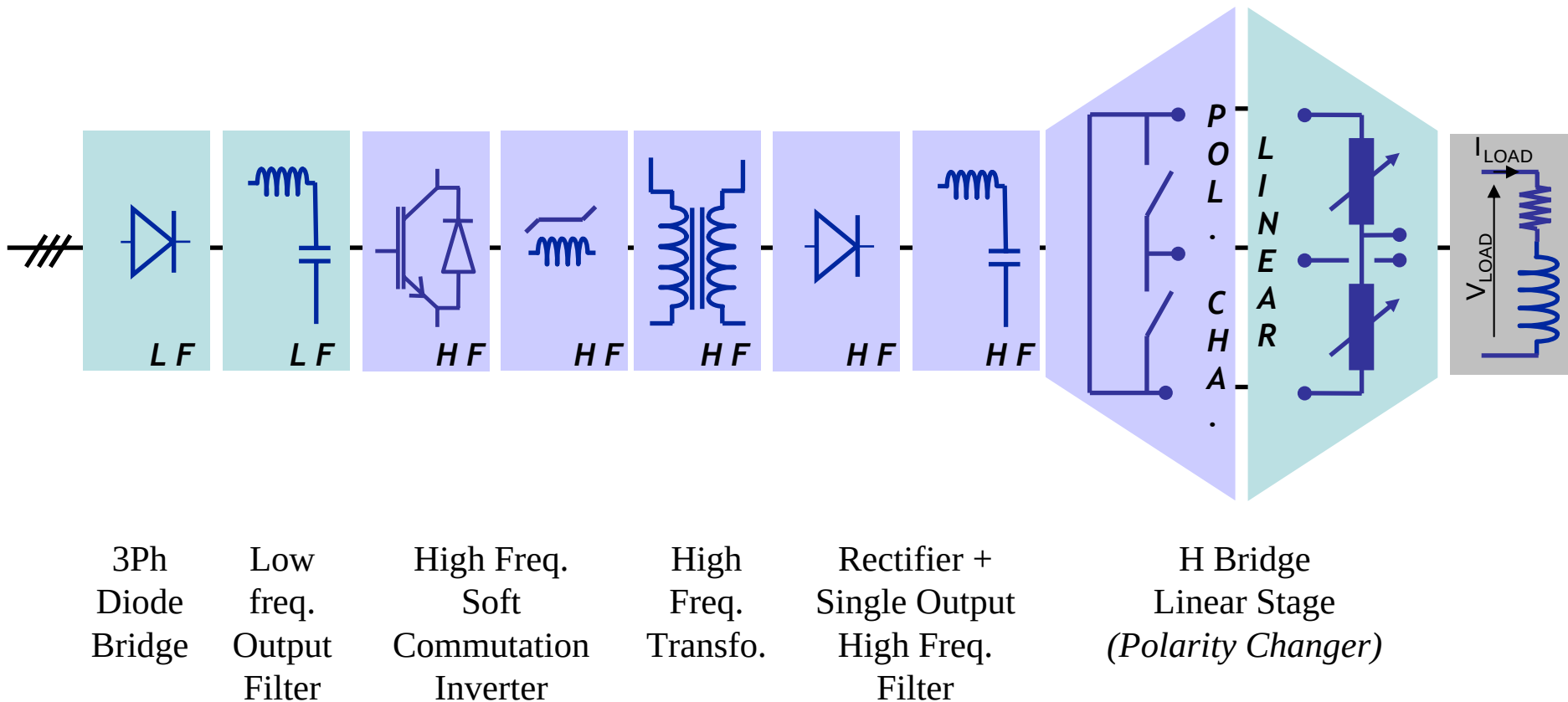Topologies: Switching + Linear (Principle *variation*)



Topologies: Switching + Linear (Schematics Example)

Basic schematic

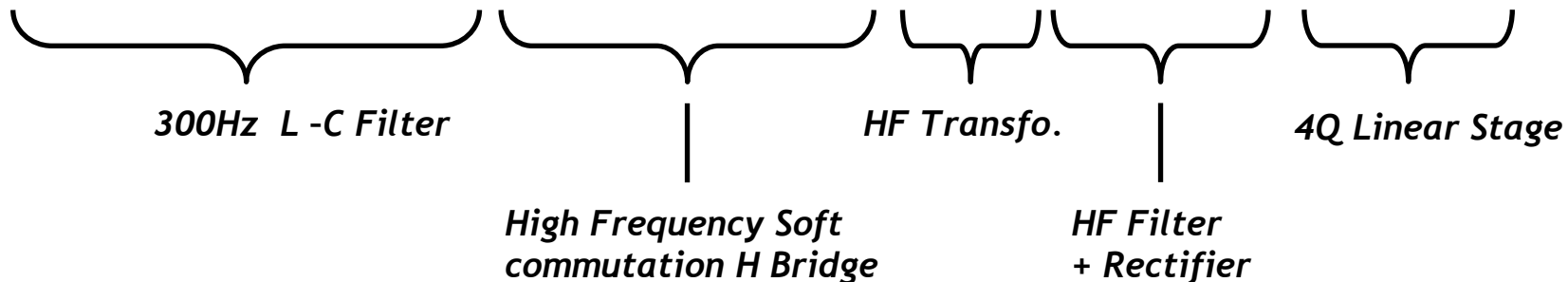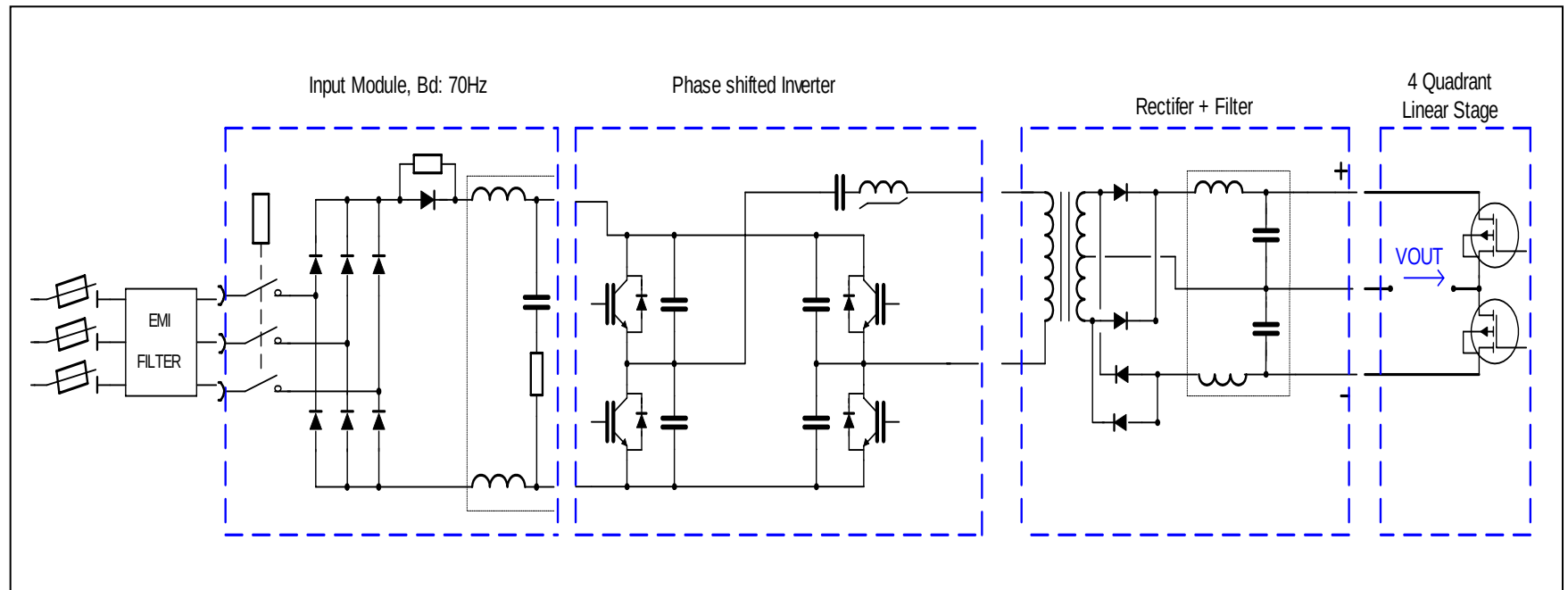

Topologies: Switching + Linear (Discussion)


Advantages

- Medium power possible
- Addition of 2 distinct well known topologies
- High bandwidth
- Good AC mains perturbation rejection
- No distortion of the signal (if circulating current used)
- HF filtering Ripple at $2 \times f_{\text{switching}}$ possible
- Efficiency OK, (no switching Loss at secondary side)
- EMC OK, since Soft commutation possible

Drawbacks

- Dealing with Inverter Loop & Circulation current Loop can lead to some complexity
- Double output voltage requires additional power components (L-C Filtering + Rectifiers)
- Dissipative (No energy back to anywhere, except Output transistors!!!)

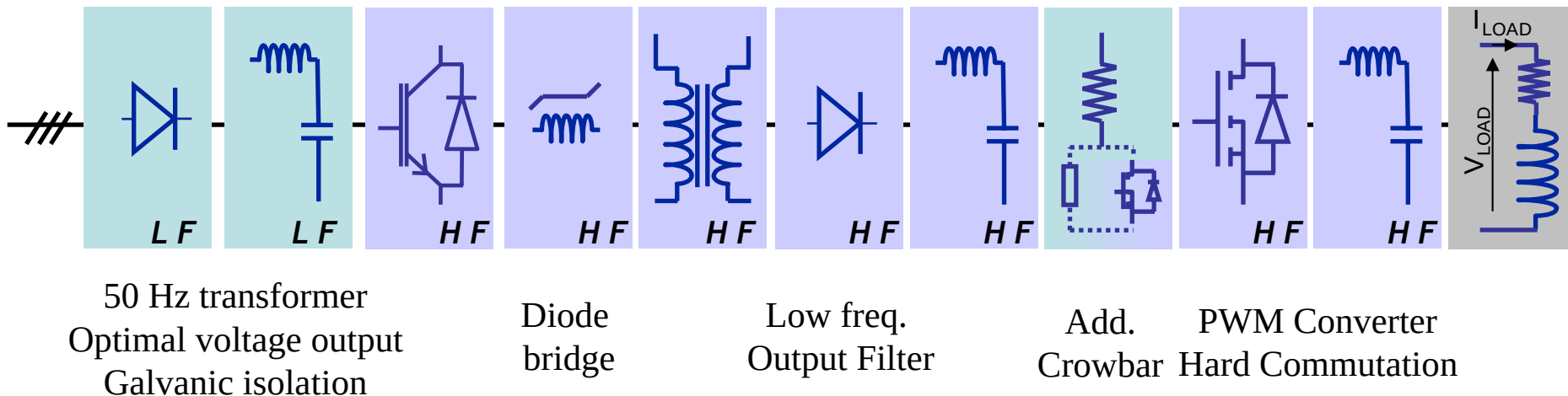Topologies: Switching + Switching Type 1 (Principle)



Topologies: Switching + Switching Type 1 (Discussion)


Advantages

- High power possible
- Part of magnet energy re-used
- Very well known topology
- High bandwidth
- Good AC mains perturbation rejection
- No distortion of the signal (if H bridge not changing mode)


Drawbacks

- Secondary H bridge hard commutation @ high current (Losses EMC to cope with)
- Low voltage high current not ideal (loss of the switching H bridge, $f_{\text{switching}}$ limited)
- 2 HF filtering levels
- Complexity (2 inverters, Gate drives) & Cost
- Efficiency low
- HF filtering Ripple difficult (if buck mode not used), at “only $f_{\text{switching}}$ ”

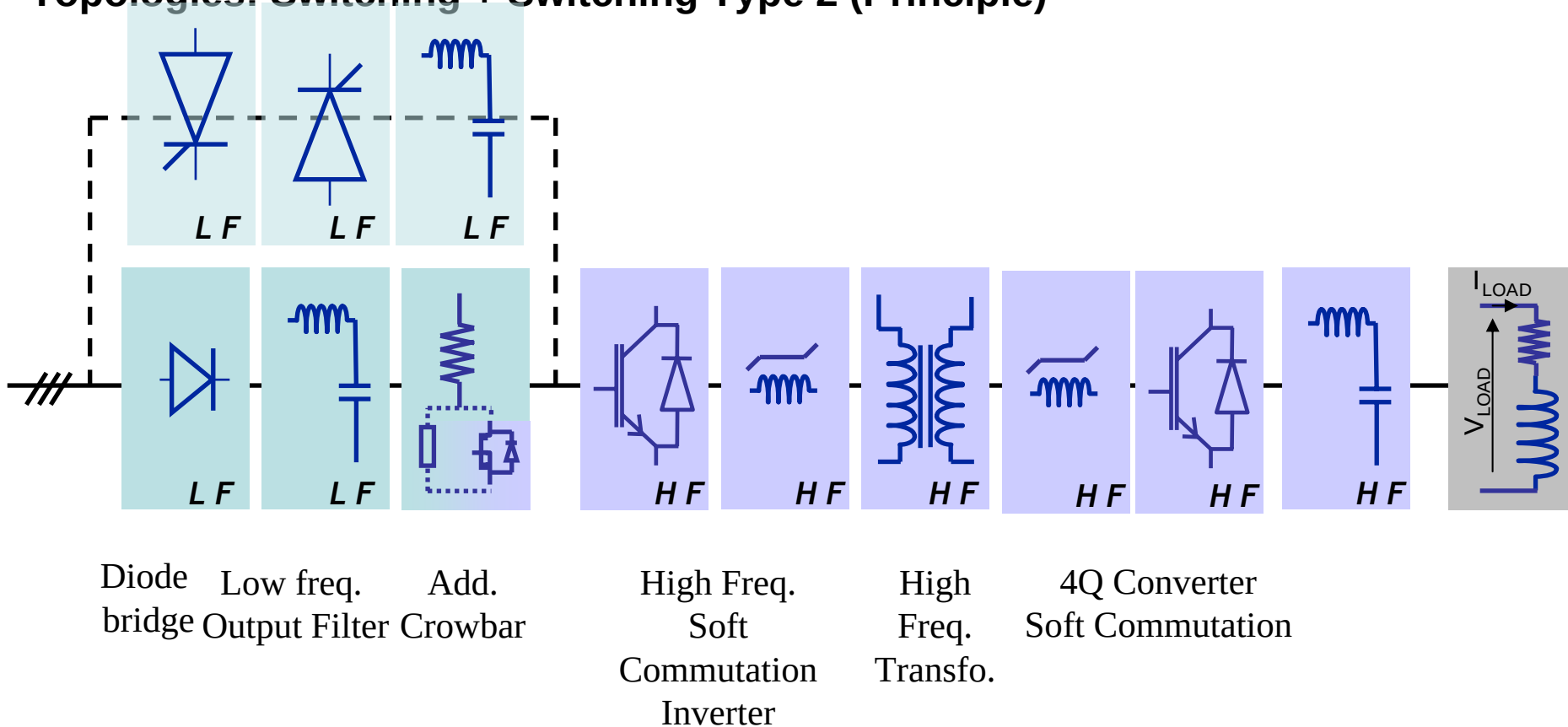Topologies: Switching + Switching Type 2 (Principle)



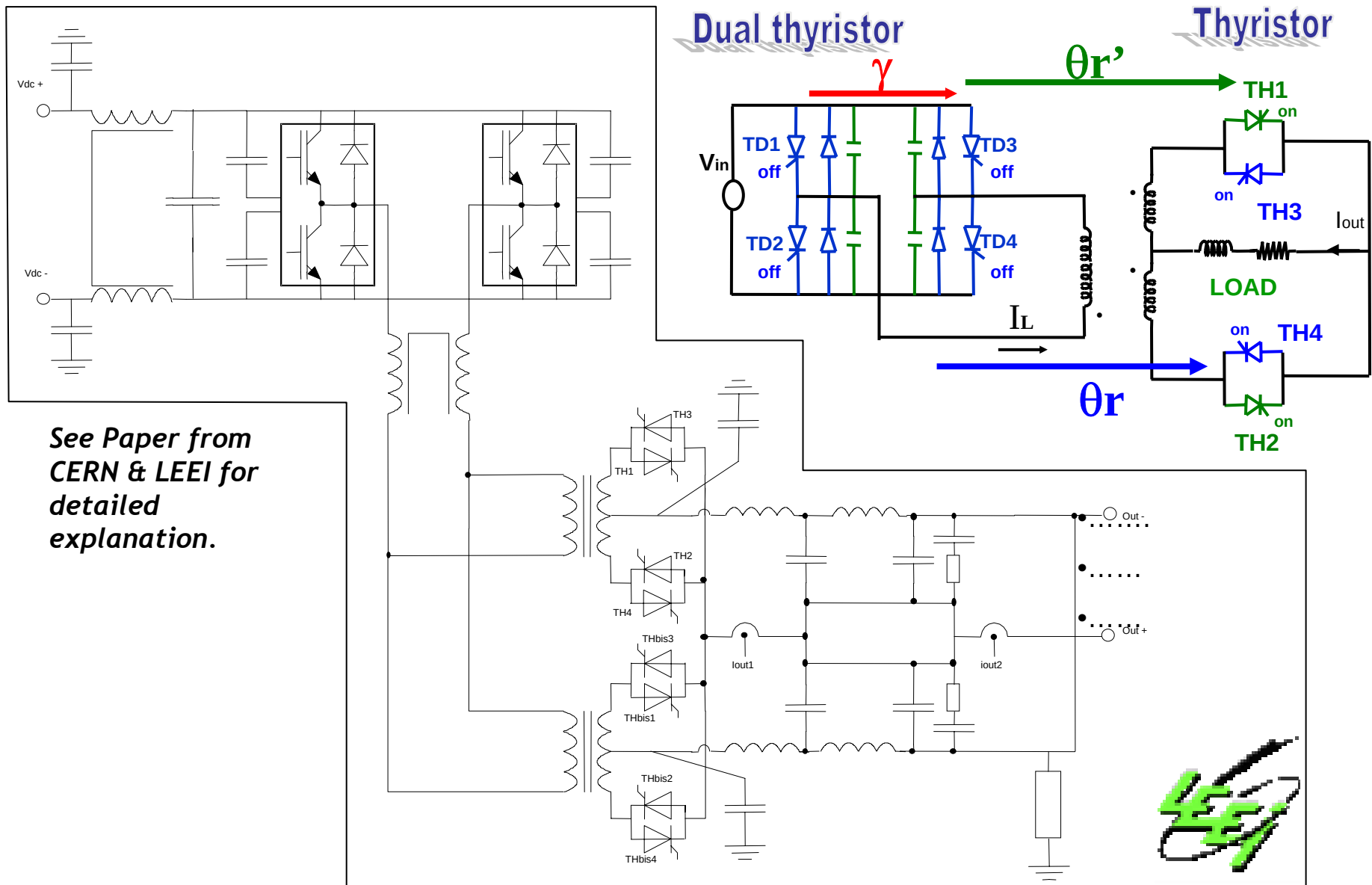Topologies: Switching + Switching Type 2 (Schematic Example)



Topologies: Switching + Switching Type 2 (Discussion)

Advantages

- Fully reversible with energy sent back to mains (thyristor bridge to be added)
- High frequency power converter (low volume and high dynamic performance)
- High bandwidth
- Good AC mains perturbation rejection
- No distortion of the signal (if H bridge not changing mode)
- Soft commutation possible on the 2 H-Bridges
- High efficiency

Drawbacks

- Complex control

$\pm 600A$
 $\pm 12V$



4 Quadrant basic background

- 4Q. Conventions

- 4Q. Working area / loads

- 4Q. Basic schematics

4 Quadrant topologies Review

- Principle schematics (main ones presented)

- Advantages / Drawbacks

- Some realizations

4 Quadrant practical realization & example

- LHC Specifications

- LHC Topology choice explained

- LHC Converter principles

- Technical points highlighted (loops, circulating current,...)

- Realizations

LHC: Specifications

- Electrical Characteristics
 - Low Output Voltage / High Output Current
 - High Efficiency (Losses in Tunnel must be as low as possible)
 - High bandwidth
 - No need for returning power to mains (slow machine)
 - Operation close to [0V-0A]
 - Low BF ripple (magnet current precision) & Low HF Ripple (EMC)
- Mechanical Characteristics
 - To be installed in LHC tunnel
 - Must be possible to change it as a plug-in module
 - Low volume and low weight
- Electrical Environment
 - Good immunity to mains perturbation (phase loss of 100ms)
 - Very low level of distortion tolerated (high precision)
 - EMC behavior must be very good (IN & OUT)
 - To be integrated in a few ppm current loop regulation
- Other key points
 - 15 years of operation (MTBF)
 - Principle as simple as possible (operation)

LHC Power Converters Family

=====

LHC $\pm 600A \pm 40V$

Transtechnik

Germany

50 Units

LHC $\pm 600A \pm 10V$

Cirtem

France

440 Units

LHC $\pm 120A \pm 10V$

CERN & EFACEC

Portugal

330 Units

LHC $\pm 60A \pm 08V$


CERN & CEL

France



800 Units

LHC $\pm 120\text{A}$ $\pm 10\text{V}$: EMC Highlighted

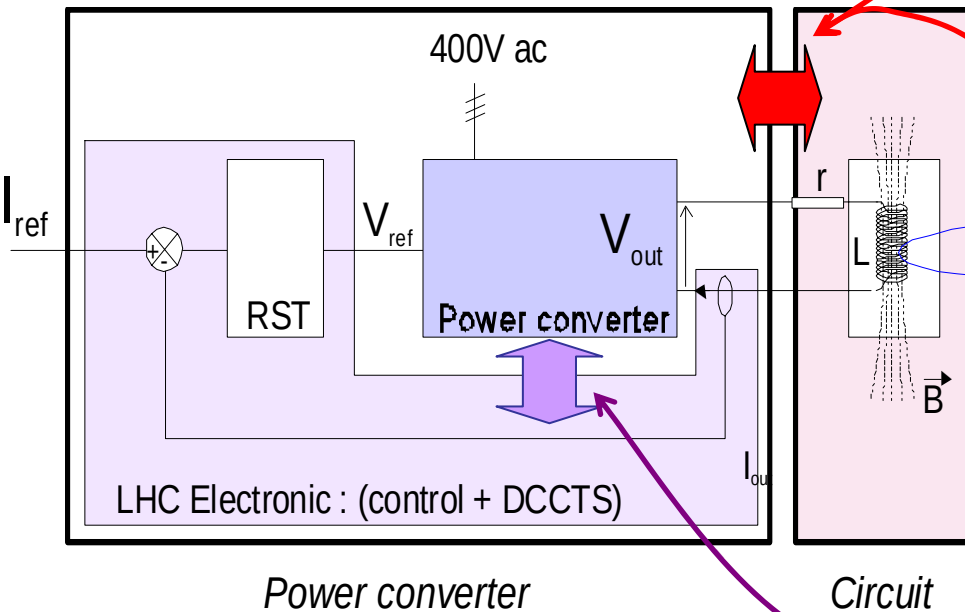*Magnet loads are several magnets in series
(hundreds of meters “load”)
IEC478.3 C applied INPUT and OUTPUT side*






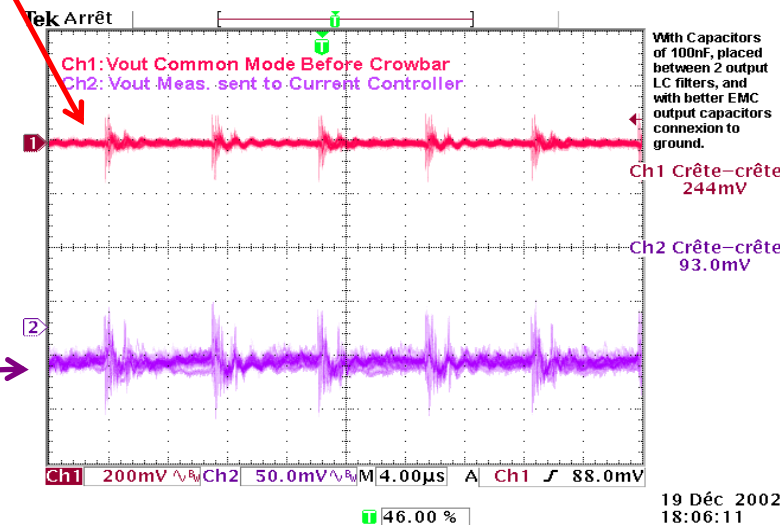
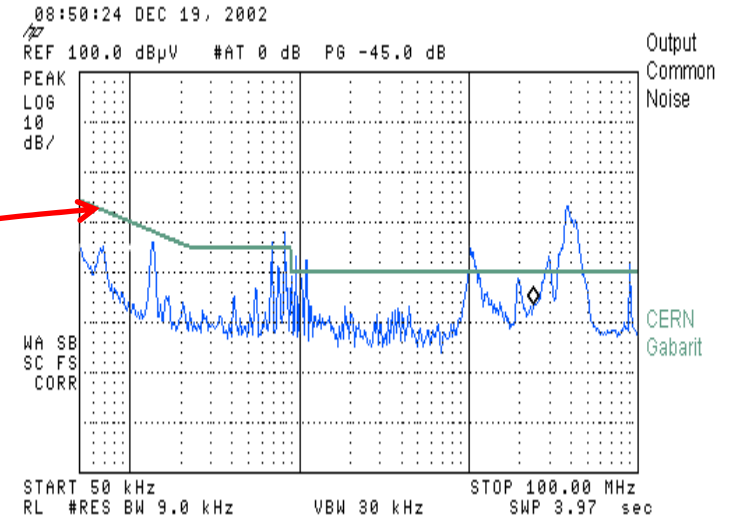
*Digital & Analog signals exchanged between
Power converter
& High Precision Current Controller*



LHC $\pm 120\text{A}$ $\pm 10\text{V}$ Topology Choice

Minimum 50Hz Components for size & weight reduction

(tunnel installation)

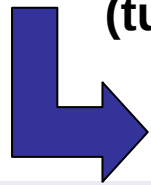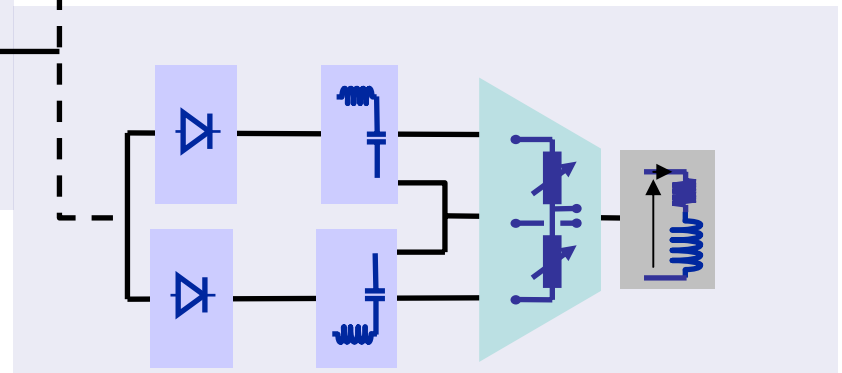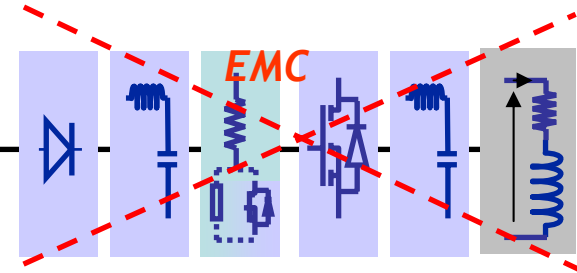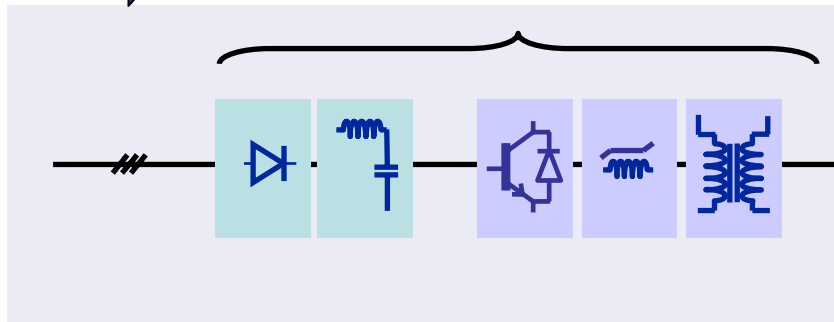
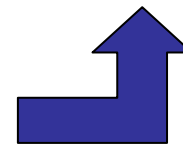
*Switching based topology**Linear base topology*

High precision environment:

EMC must be as good as possible

No distortion / operation [0V-0A]

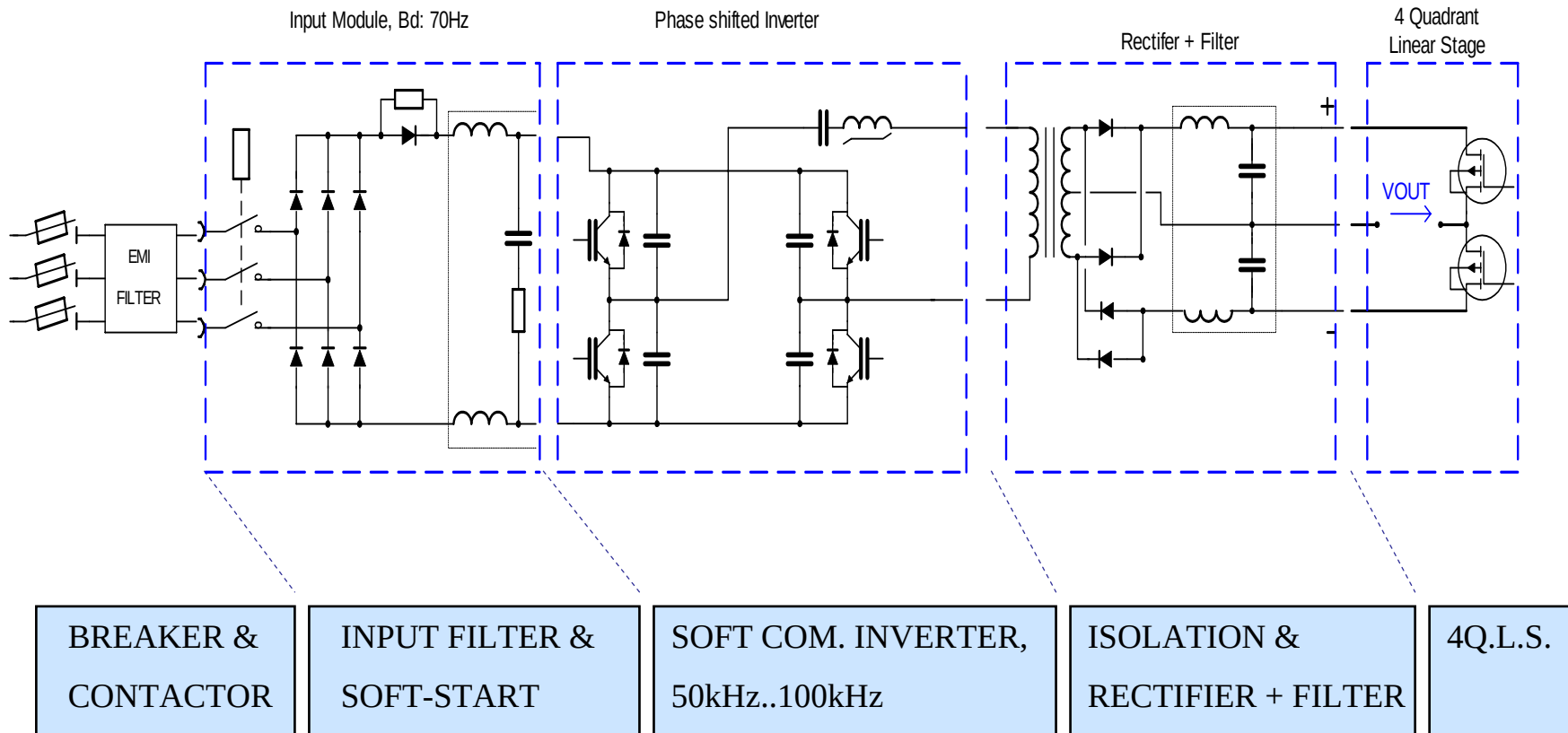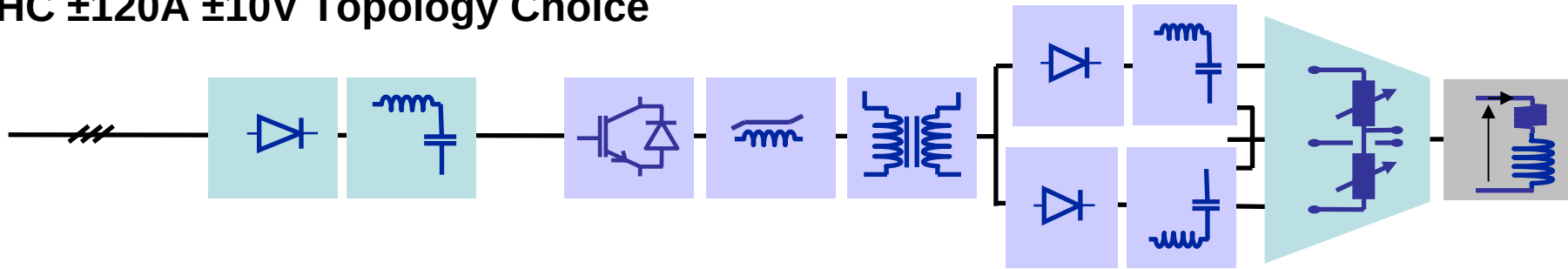LHC $\pm 120\text{A}$ $\pm 10\text{V}$ Topology Choice





LHC $\pm 120\text{A}$ $\pm 10\text{V}$ Topology Choice

AC-DC

- 3 phases + Neutral (used for auxiliary power supply)
- 1400V Rectifiers
- 70Hz Input filter (damped with C-4C) to give a flat 540V DC (around -20dB on 300Hz)
- Soft start based on “R + switch”.

High Frequency Soft commutation Inverter

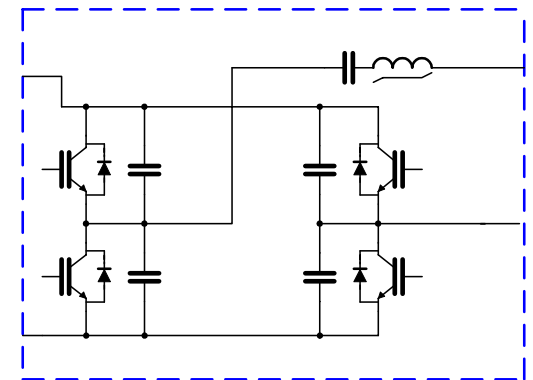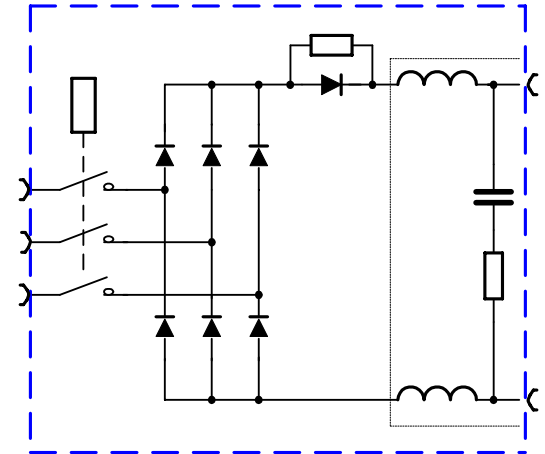- Fixed switching frequency (50..100kHz).
- ZVS operation with Phase Shifted command.
- ZCS for lagging leg
- IGBT Bridge
- “Voltage” or “current” mode possible





LHC $\pm 120\text{A}$ $\pm 10\text{V}$ Topology Choice

Rectifier + DC Filter

- HF Ripple at $2 \times$ inverter $F_{\text{switching}}$
- Schottky rectifiers.
- Double LC cell at 5..10 kHz.

4 Quadrant Linear Stage

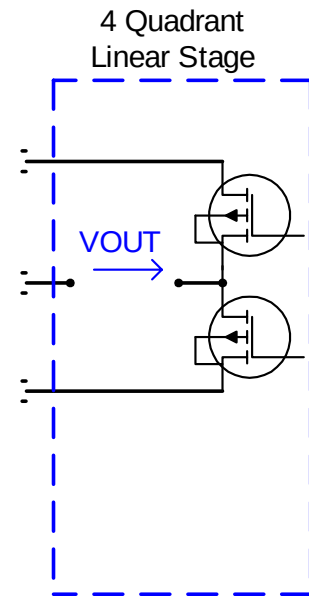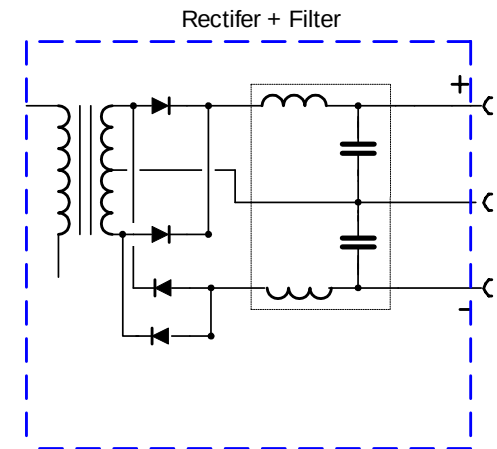- Linear Regulation based on Mosfets.
- Mosfet used as
 - polarity switch in generator mode
 - programmable resistor to dissipate Magnet energy.
- Use of 4QLS as an active filter
- Use of 4QLS to pre-load inverter (continuous mode)
- Circulating current always present but value depending from load current (no mode change transition, both DCDC outputs always minimum loaded)




LHC $\pm 120\text{A}$ $\pm 10\text{V}$ Topology ChoiceHighlights on 4QLS

- A double power source programmable via inverter (V_E)
- 2 MOSFETS, Q1 & Q2, used as switch and programmable **resistor**. (high level of power possible)
- A command which works according to :

$$V_{\text{OUT}} = +(V_E - R_{\text{HIGH}} \cdot I_{\text{HIGH}})$$

$$V_{\text{OUT}} = -(V_E - R_{\text{LOW}} \cdot I_{\text{LOW}})$$

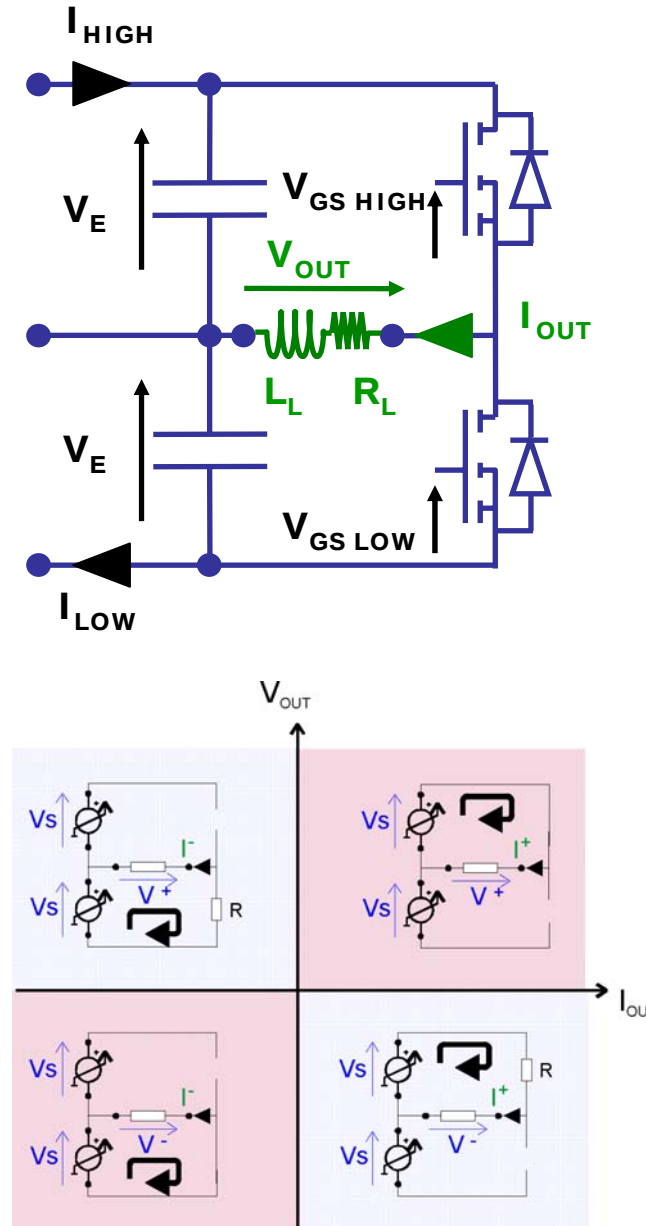R_{HIGH} & R_{LOW} are equivalent MOSFET resistance





LHC: 4QLS without circulation current

- Remember a limitation of the linear stage...




- Main Loop (VOUT linear regulation loop) cannot provide needed step for biasing MOSFET (-3V to + 3V)

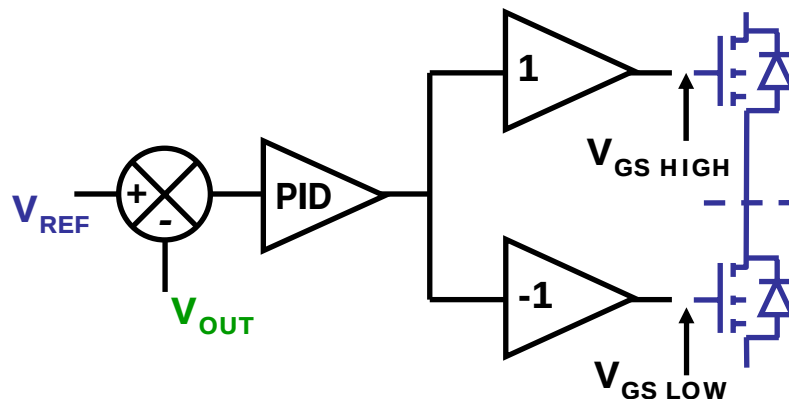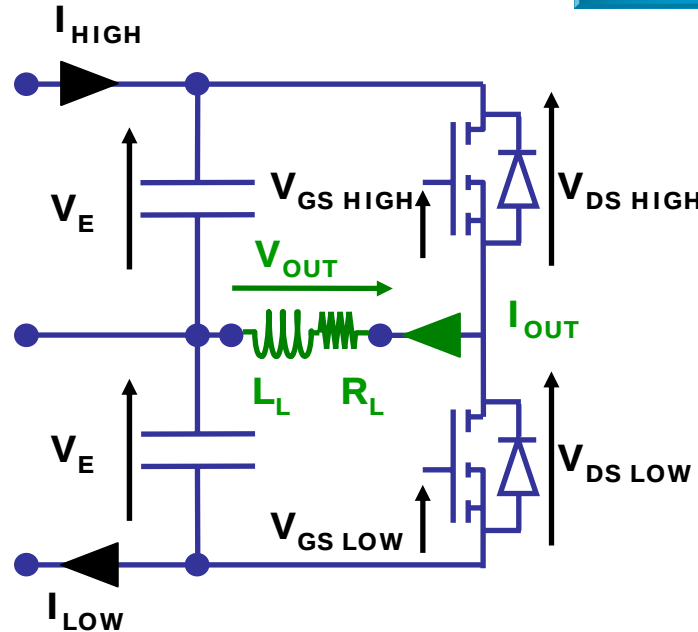
- Playing with fixed bias is a bad idea!!!
- Discrepancies on $V_{GS\ ON} \pm 1V$!!!



LHC $\pm 120A \pm 10V$ Measurements

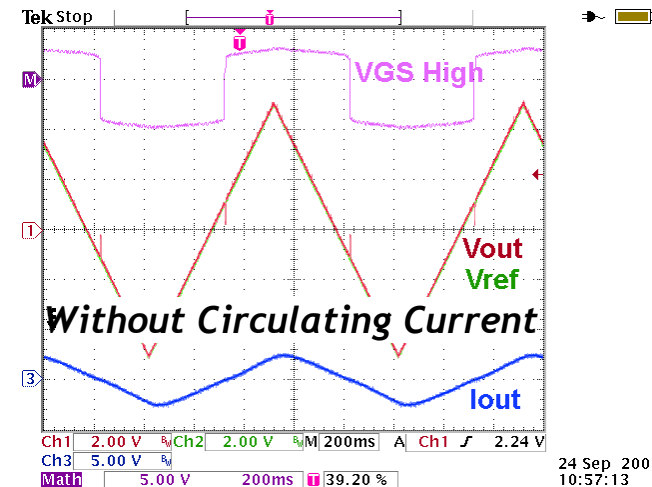

24 Sep 2001
10:57:13

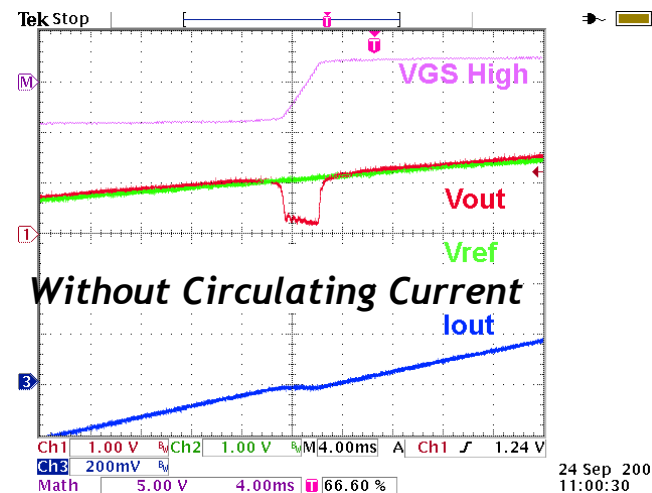

24 Sep 2001
11:00:30


LHC: 4QLS with circulation current

- Adding 2x circulation current loop


- To avoid 0A distortion crossing, a circulating can help, biasing MOSFET gates.

- These additional loops (one per MOSFET) must not perturb main loop. (must be slower)


- $I_{\text{Circulation}}$ can vary

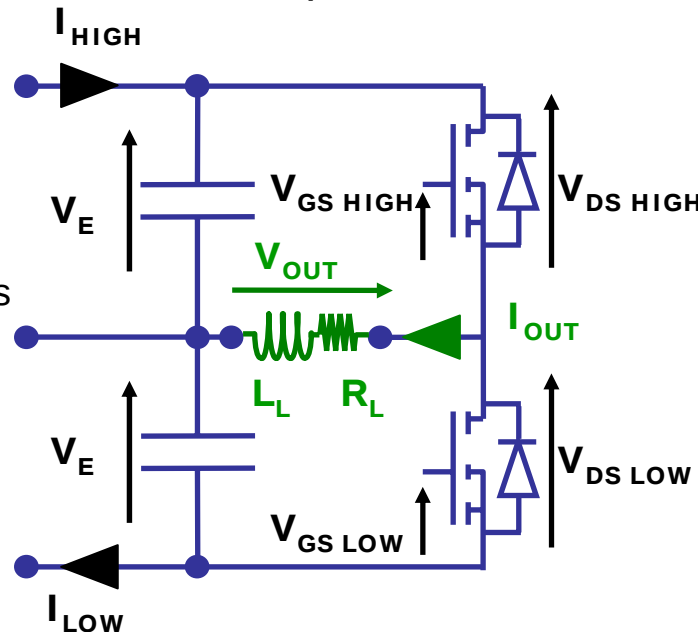


LHC $\pm 120A \pm 10V$ Measurements

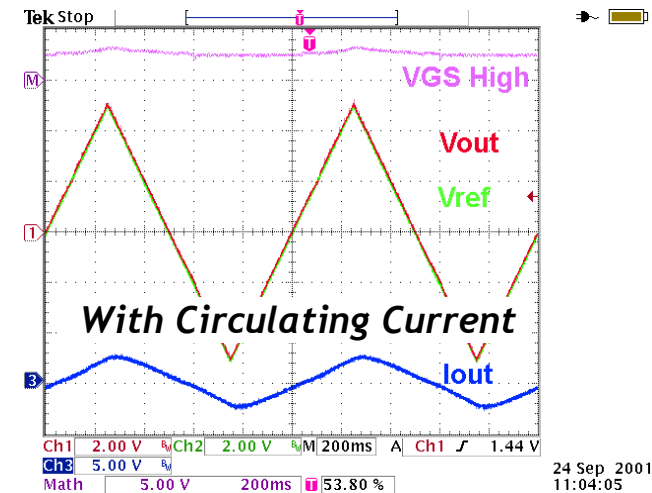

24 Sep 2001
11:04:05

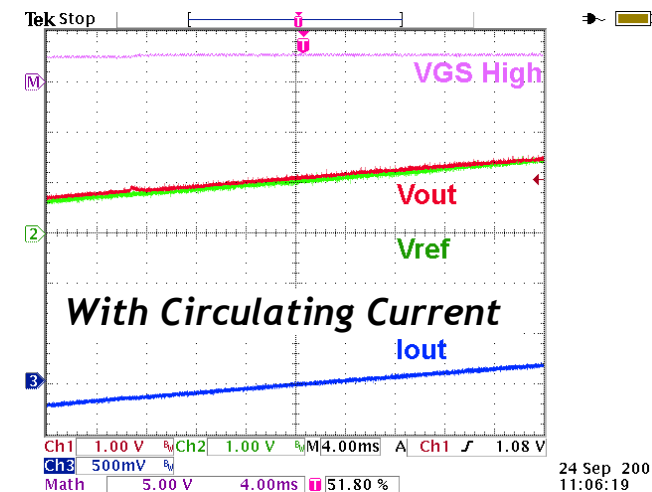

24 Sep 2001
11:06:19

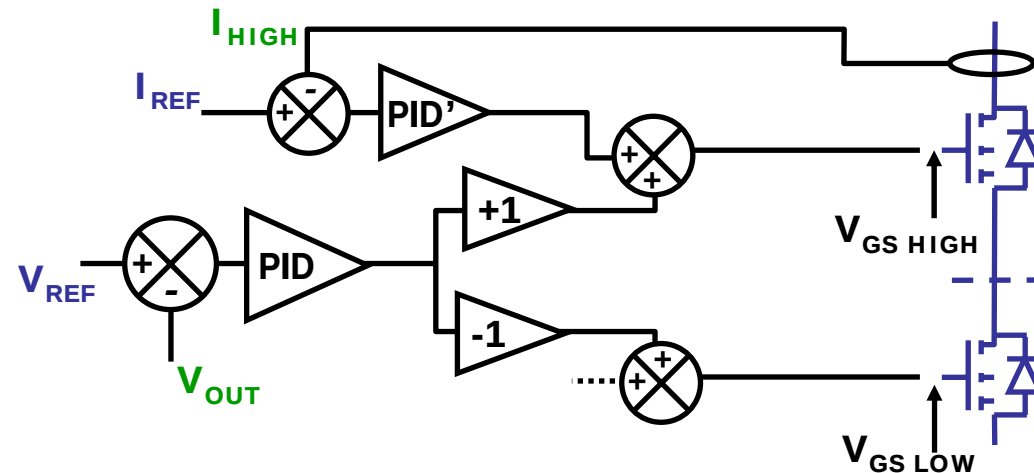

LHC: 4QLS with circulation current

different approaches:


- Circulating current always present, changing its value depending on output current

- Its control is easy (reference is only smoothly changing with I_{OUT})
- Inverter reference must always be set so that this circulating current is possible leading to higher losses in receptor mode.
- No changing mode (Gate of each side MOSFET always biased)




- Circulating current only present when close to a potential transition

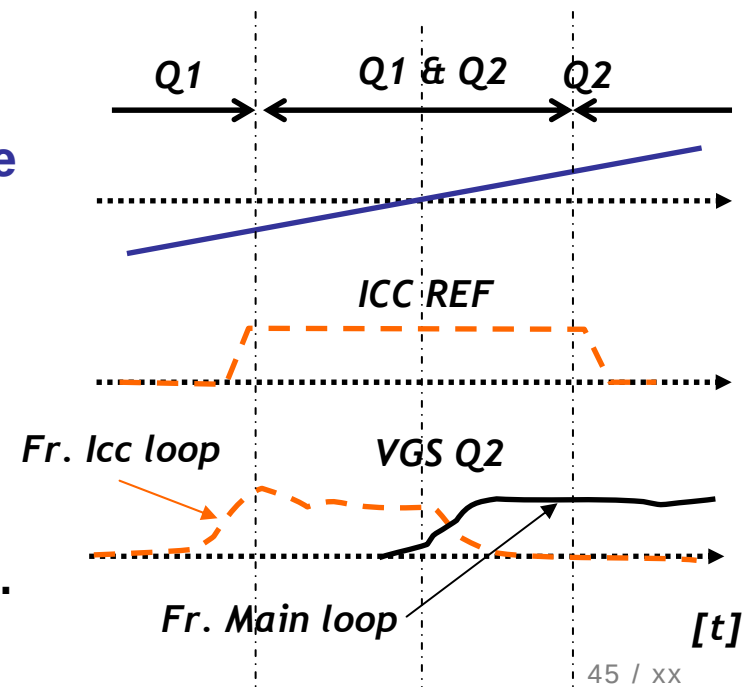- This solution saves a lot of energy when recovering, since inverter doesn't inject power in MOSFET when absorbing power.
- di/dt Limitation exists, since if too fast, circulating current doesn't have time to appear and MOSFET Gate are not well biased.




LHC: 4QLS / Inverter Reference

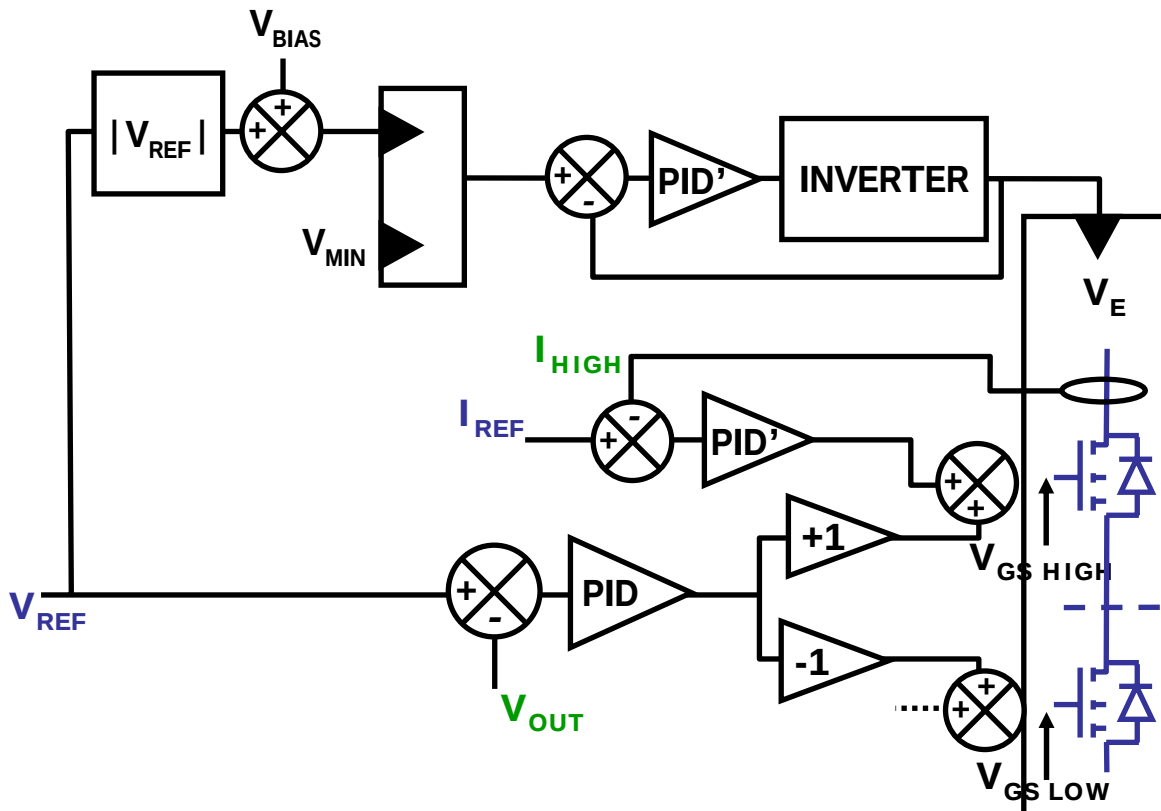
- Inverter REF is built according to
 - VBIAS MIN. not to saturate MOSFET (i.e saturate Loop)
 - VBIAS OPT. For 4Q Linear stage acting as active filter (better rejection of mains disturbances and 300 Hz)
 - VMIN coupled to I circulation MIN to always minimum load inverter (Conduction mode un-changed)
 - Inverter Loop must be faster / transparent than 4Q stage loop



LHC $\pm 120A \pm 10V$ Measurements

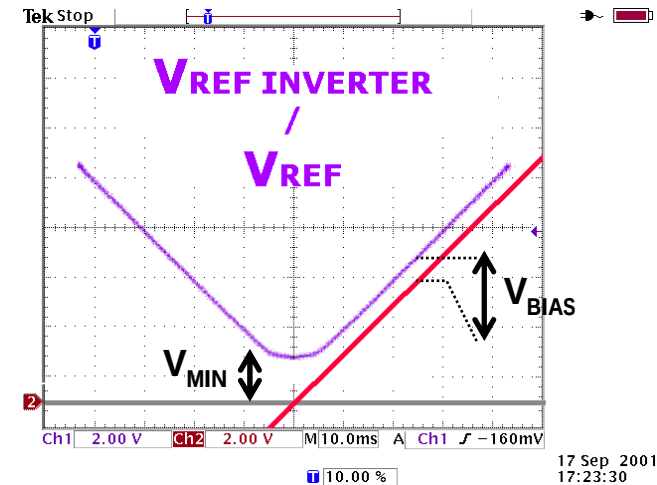

17 Sep 2001
17:23:30

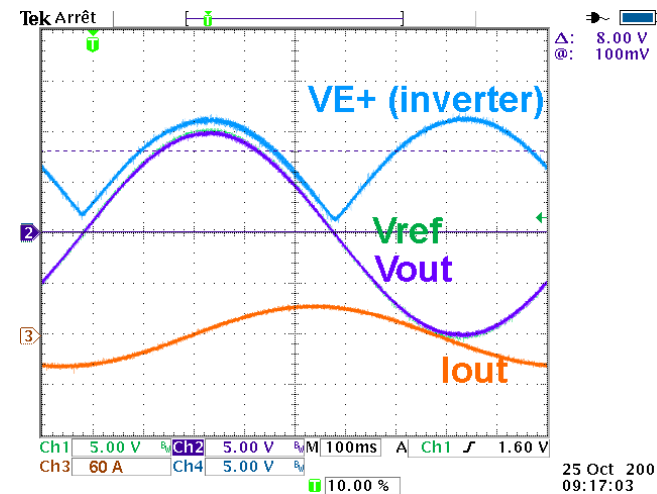

25 Oct 2001
09:17:03

LHC: 4QLS MOS working Area (Example)


Practical case of Circulation current always ON, at the same value: 5A.

RDSON variations limited by circulating current.

Dissipate Power is:

- $21\text{V} \times 120\text{A}$ in recovering MOSFET instead of $10\text{V} \times 120\text{A}$ required by the load.

- Only valid if not often the case.

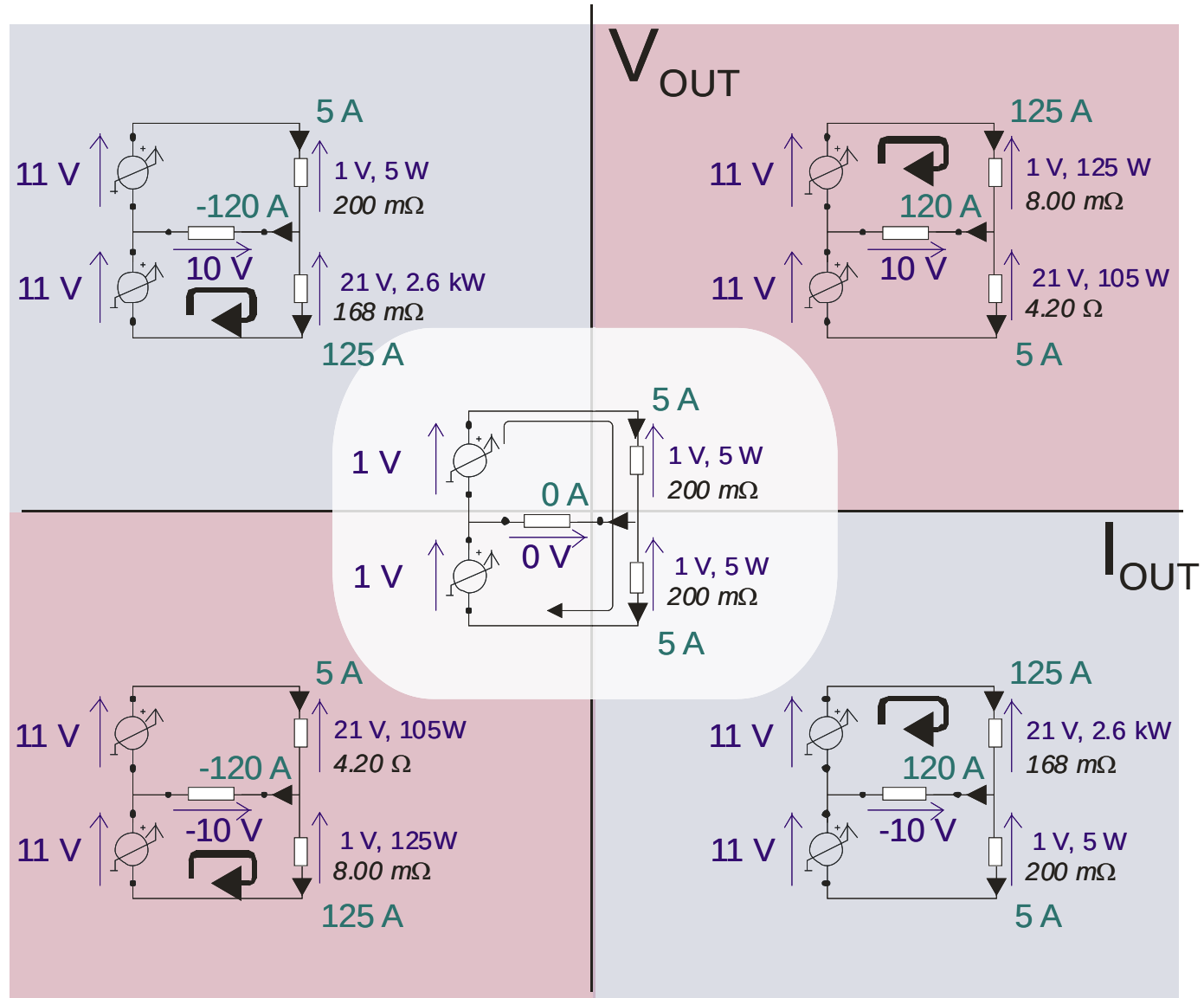


LHC: 4QLS MOS Model (FB180SA10 I.R.)


MOSFET is difficult to control directly from the main loop to the gate. Indeed gain is from virtually 0 if saturated to thousands when almost OFF.

Settings like:

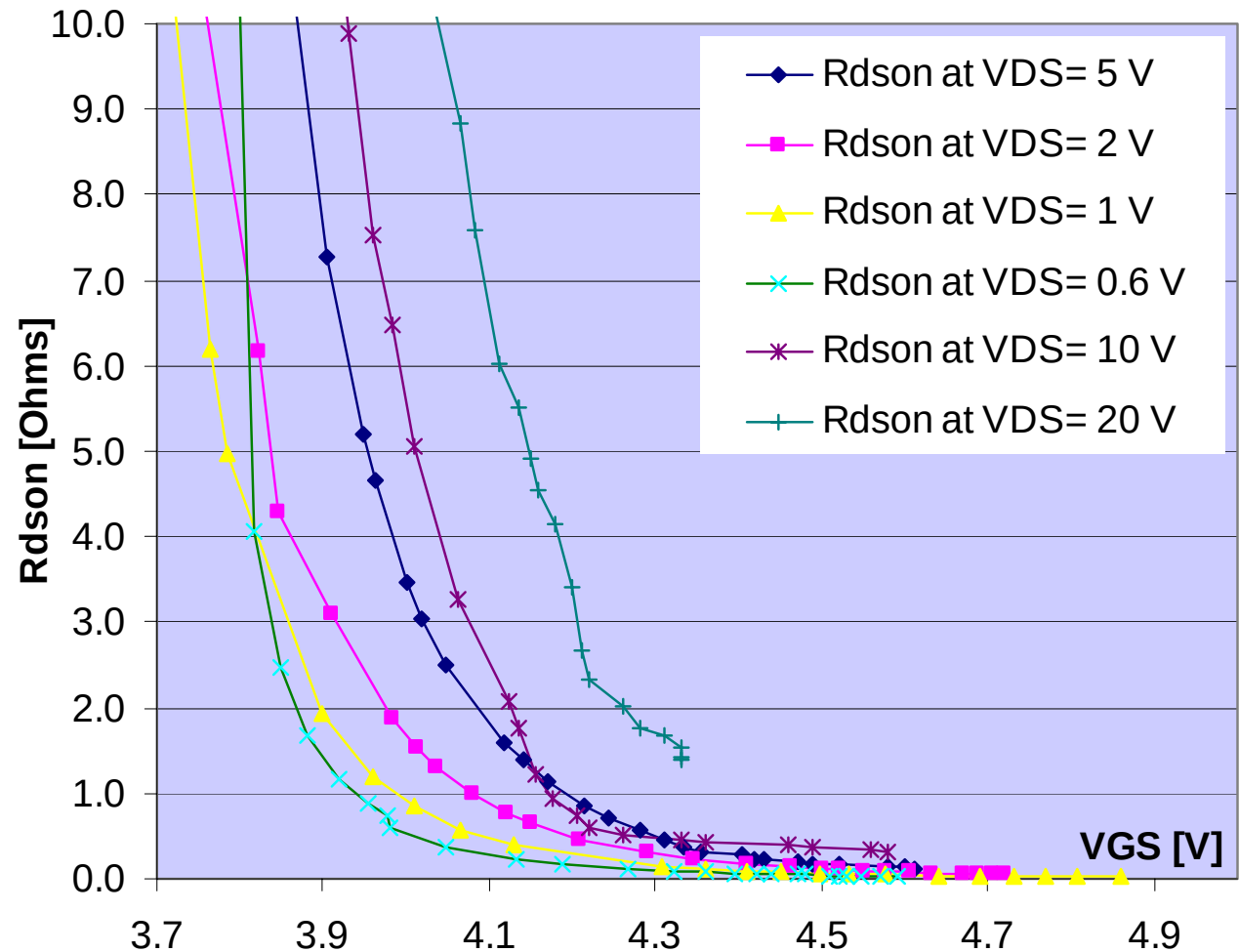- *Circulating current value*
 - *Difference voltage issued from the inverter output voltage*
 - *Number of MOSFET in //*
- are the key to maintain a stable efficient analog loop.*



LHC: Practical Results

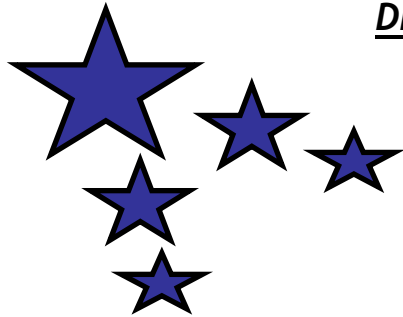




DISTORTION ?:

Crossing axis is OK. No distortion, achieved thanks to circulating current.

CONTROL:

*Bandwidth in generator & receptor quadrant
Crossing 0A is OK, being unchanged.*

LHC $\pm 120A$ $\pm 10V$ Measurements

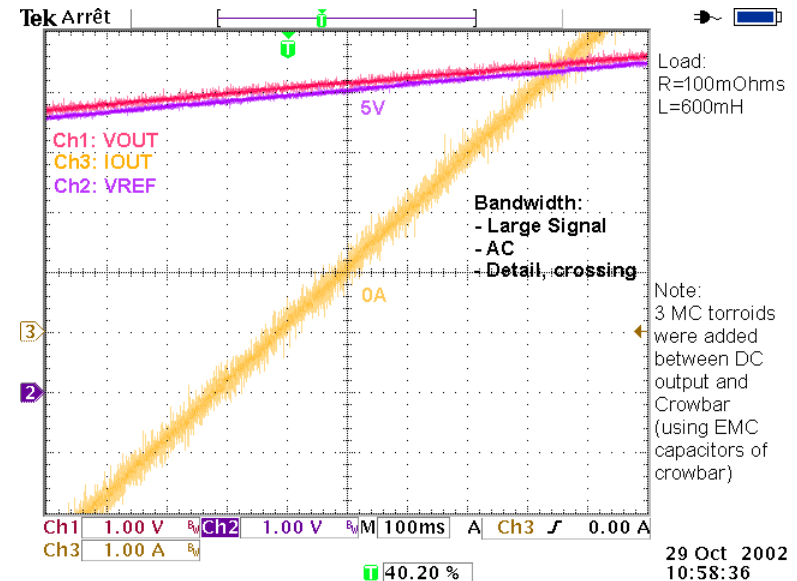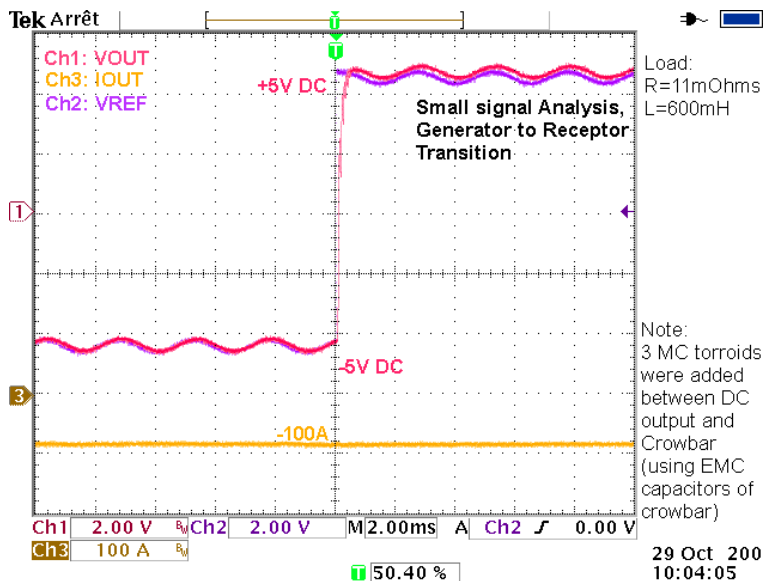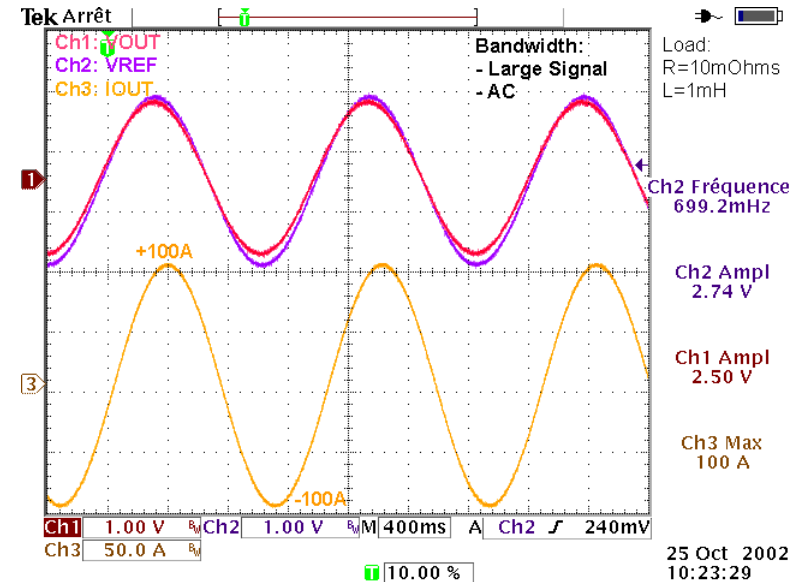

LHC: Realizations




LHC $\pm 120A \pm 10V$

- 330 Converters
- Correctors
- CERN Internal Design

CERN / EFACEC / CEL

LHC $\pm 60A \pm 8V$

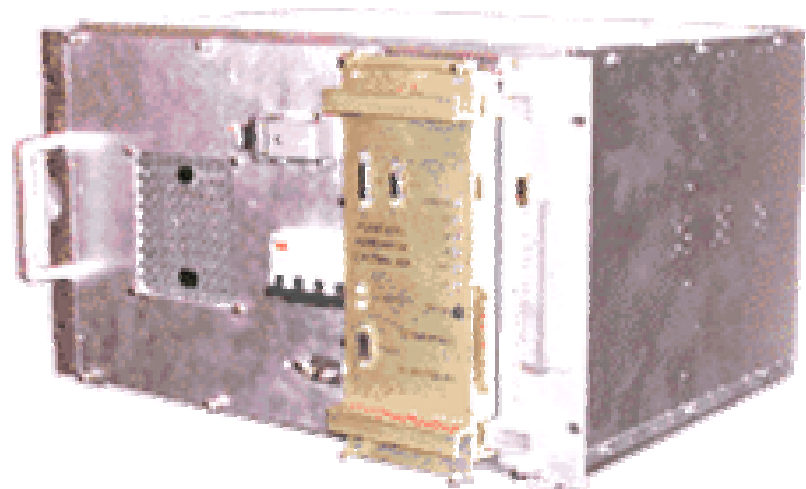- 800 Converters
- Orbit Correctors
- Below Dipoles, in a radiation zone
- CERN Internal Design





CIRTEM

LHC $\pm 600\text{A}$ $\pm 10\text{V}$

- 440 Converters
- 1x 6U Module

TRANSTECHNIK

LHC $\pm 600\text{A}$ $\pm 40\text{V}$



- 50 Converters
- 2x 6U module





Thank you for your attention.

AND?...END.

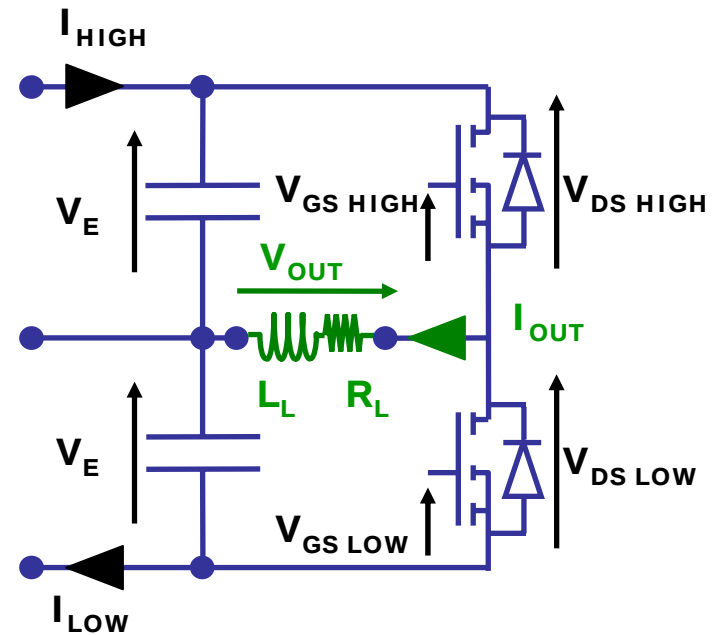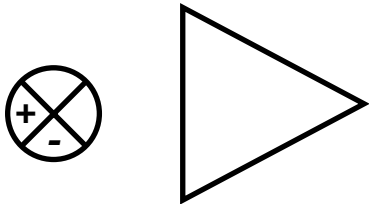

Reference

Care with test invisible so that alignment is ok

